

④ Active filters

→ combination of both active and passive components (OPAMP).

→ (generation energy)

⇒ A filter is a frequency selective circuit, which allows

signals of certain range of frequencies to pass through it & rejecting other frequencies.

→ Active filters





① Low pass filter

② High pass filter

③ Band pass filter


④ Band reject filter / Band stop filter.

frequency responses

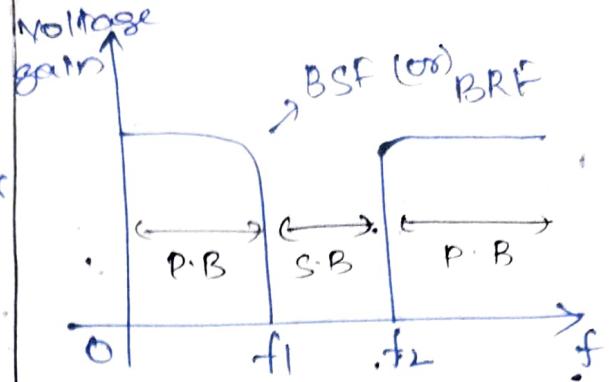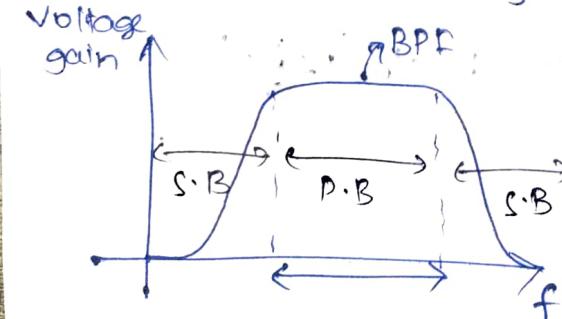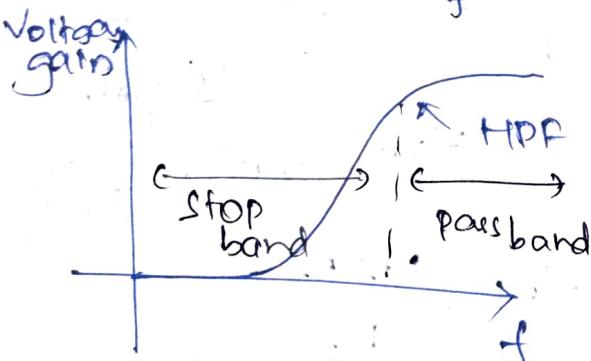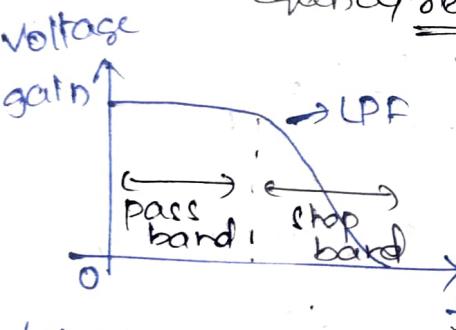

* Low Pass filter

first order LPF

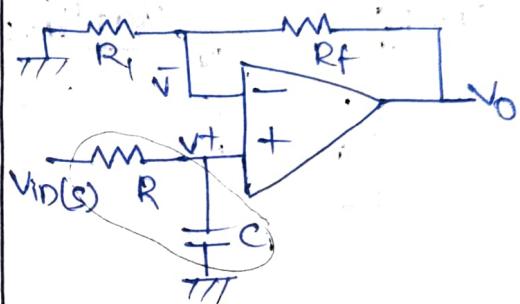

$$V^+ = \frac{V_{in}(s)}{R + \frac{1}{sC}} \times sC$$

$$V^+(s) = \frac{V_{in}(s)}{RSC + 1}$$

$$V_o(s) = \left(1 + \frac{R_f}{R}\right)V^+(s) = \left(1 + \frac{R_f}{R}\right)\frac{V_{in}(s)}{1 + RSC}$$

$$Av_f(s) = \frac{V_o(s)}{V_{in}(s)} = \left(1 + \frac{R_f}{R}\right) \frac{1}{1 + RSC}$$

$$\text{let } s = j\omega$$

$$Av_f(j\omega) = \left(1 + \frac{R_f}{R}\right) \frac{1}{1 + j\omega RC}$$

$$|Av_f(j\omega)| = \sqrt{\left(1 + \frac{R_f}{R}\right)^2 + \omega^2 R^2 C^2}$$

$$X = \frac{a+ib}{c+id}; |X| = \sqrt{a^2+b^2} / \sqrt{c^2+d^2}$$

$$|A_{Vf}| = \left(1 + \frac{R_f}{R_1}\right)$$

max

$\omega = 0$

$$\Rightarrow |A_{Vf}(j\omega)| = \frac{A_{Vf\max}}{\sqrt{1 + \omega^2 R^2 C^2}}$$

cutoff frequency = f_0

corresponding angular frequency = ω_0

At this frequency, the voltage gain is $\frac{1}{\sqrt{2}}$ times the maximum gain.

At $\omega = \omega_0$ or $f = f_0$

$$\frac{|A_{Vf}|_{\max}}{\sqrt{2}} = \frac{A_{Vf\max}}{\sqrt{1 + \omega_0^2 R^2 C^2}}$$

$$\omega_0 = 1/RC \Rightarrow f_0 = \frac{1}{2\pi RC}$$

when ' ω ' is very large,

$$|A_{Vf}(j\omega)| \approx 0$$

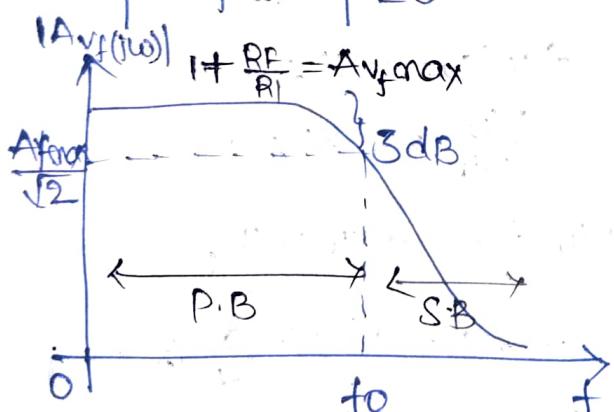



Fig: Frequency response of LPF

$$A_{Vf}(s) = \frac{1 + \frac{R_f}{R_1}}{1 + \frac{s}{RC}}$$

1st order filter

only one RC section

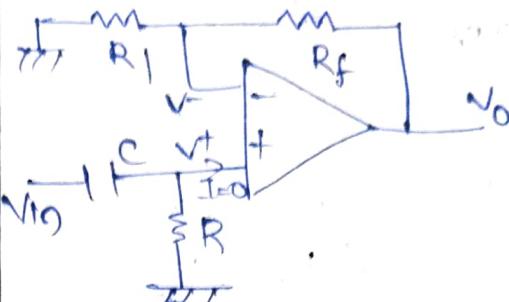* 1st Order High Pass Filter
(Butterworth)



$$V_t(s) = \frac{V_{in}(s) \times (R)}{\frac{1}{sC} + R}$$

$$V_t(s) = \frac{V_{in}(s) \cdot SRC}{1 + SRC}$$

for non-inverting opamp,

$$V_o(s) = V_t(s) \left[1 + \frac{R_f}{R_1} \right]$$


$$= \frac{V_{in}(s)SRC}{1 + SRC} \left[1 + \frac{R_f}{R_1} \right]$$

$$A_{Vf}(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{SRC \left[1 + \frac{R_f}{R_1} \right]}{1 + SRC}$$

$$A_{Vf}(j\omega) = \frac{j\omega RC \left[1 + \frac{R_f}{R_1} \right]}{1 + j\omega RC}$$

$$|A_{Vf}(j\omega)| = \frac{RC \left[1 + \frac{R_f}{R_1} \right]}{\sqrt{1 + (\omega RC)^2}}$$

$$|A_{Vf}(j\omega)| = \frac{(1 + R_f/R_1)}{1 + \frac{1}{(\omega RC)^2}}$$

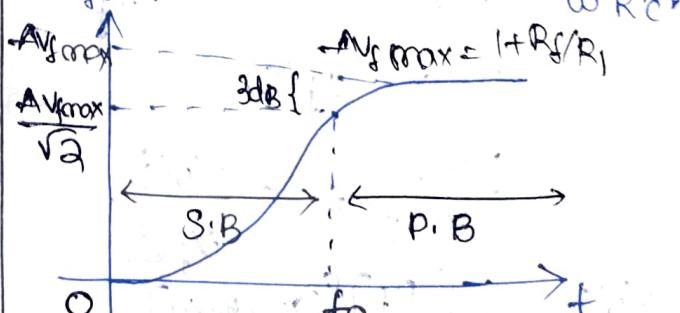

$$A_{Vf\max} = 1 + \frac{R_f}{R_1} \quad \text{when } \omega_0 = 0 \quad \text{gain} = 0$$


At $f = f_0$,

$$|AV_f(s)| = \frac{AV_{f\max}}{\sqrt{2}}$$

$$\frac{AV_{f\max}}{\sqrt{2}} = \frac{AV_{f\max}}{\sqrt{1 + \frac{1}{\omega_0 R C'}}$$

$$\Rightarrow f_0 = \frac{1}{2\pi R C}$$

Practical Differentiator using OPAMP

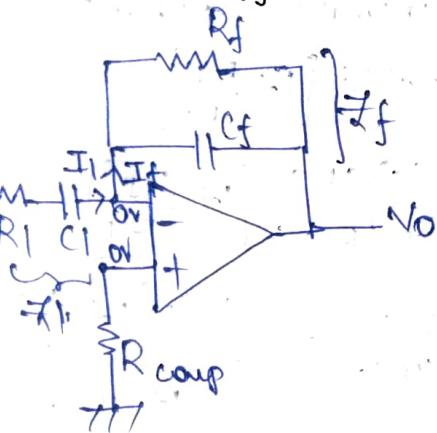

$$Z_I(s) = R_1 + \frac{1}{sC_1} = \frac{sR_1C_1 + 1}{sC_1}$$

$$Z_f(s) = \frac{R_f \times \frac{1}{sC_f}}{R_f + \frac{1}{sC_f}} = \frac{R_f}{sC_f R_f + 1}$$

$$I_I(s) = \frac{V_{in}(s) - 0}{Z_I(s)} ; I_f(s) = \frac{0 - V_o(s)}{Z_f}$$

$$I_I(s) = I_f(s)$$


$$\frac{V_{in}(s)}{Z_I(s)} = - \frac{V_o(s)}{Z_f(s)}$$

$$\frac{V_o(s)}{V_{in}(s)} = - \frac{[R_f][sC_f R_f + 1]}{[sC_f R_f + 1][sC_f R_f + 1]}$$

$$|AV(s)| = \frac{SR_f C_f}{(1 + sC_f R_f)(1 + sR_I C_f)}$$

$$\text{If } R_I C_f = C_f R_f$$

$$|AV(s)| = \frac{SR_f C_f}{(1 + sR_I C_f)^2} = \frac{SR_f C_f}{1 + (2\pi f C_f)^2}$$

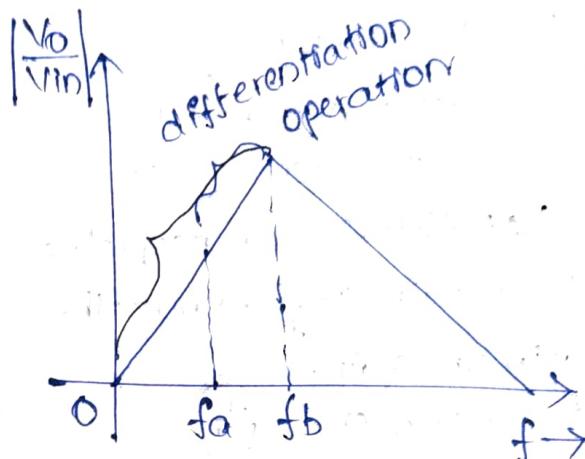

$$f_a = \text{frequency at which gain} = 1$$

$$f_a = \frac{1}{2\pi R_f C_f} ; f_b = \frac{1}{2\pi R_I C_f}$$

for proper differentiation;

$$R_f C_f \gg R_I C_f$$

$$R_f C_f \gg R_I C_f ; \text{ then}$$

$$AV(s) = -SR_f C_f$$

$$\frac{V_o}{V_{in}} = -SR_f C_f$$

$$V_o(s) = -sV_{in}(s)R_f C_f$$

$$\therefore V_o(s) = +R_f C_f \frac{d}{dt} V_{in}(t)$$

Now;

$$|AV(s)| = \frac{\omega R_f C_f}{1 + (\omega C_f R_f)^2}$$

$$|AV(s)| = \frac{2\pi f R_f C_f}{1 + (2\pi f C_f R_f)^2}$$

where,

$$f_a = \frac{1}{2\pi R_f C_1} ; f_b = \frac{1}{2\pi R_f C_1}$$

$$|A_{V(S)}| = 1$$

$$1 = \frac{f/f_b}{1 + (f/f_b)^2}$$

$$1 + (f/f_b)^2 = f/f_a$$

$$\frac{f_a}{f_b} < 1$$

The above eqn satisfies

$$\text{If } \left(\frac{f_a}{f_b}\right)^2 < 1$$

for, at $f = f_a$; Both LHS & RHS equals to 1

$$\left(\frac{f_a}{f_b}\right)^2 < 1 \quad (\text{or})$$

$$\frac{f_a}{f_b} < 1 \quad \begin{array}{l} \text{from} \\ \text{graph} \end{array}$$

$$\Rightarrow (f = f_a)$$

$$f_b > f_a$$

$$\frac{f_a}{f_b} < 1$$

Q) Design a differentiator using OPAMP to differentiate an I/P signal with $f_{\text{max}} = 200\text{Hz}$. Draw the output waveform for sine wave with N peak at 200Hz .

$$\boxed{\begin{aligned} f_{\min} &= f_a \\ f_{\max} &= f_b \end{aligned}}$$

$$f_{\min} = f_a = 200\text{Hz}$$

$$\frac{1}{2\pi R_f C_1} = 200$$

$$\text{Let, } [C_1 = 0.12\mu\text{F}]$$

$$R_f = \frac{200\text{Hz}}{2\pi \times 200 \times 0.12 \times 10^6}$$

$$[R_f = 7.996\text{k}\Omega]$$

$$\text{Let, } [f_b = 10f_a] \quad (\text{for designing purpose})$$

$$\frac{1}{2\pi R_f C_1} = 10 \times 200$$

$$C_1 = 0.1\mu\text{F}$$

$$\Rightarrow [R_1 = 0.796\text{k}\Omega]$$

work



$$\Rightarrow R_1 C_1 = R_f C_f$$

$$\frac{(0.796 \times 10^3)(0.1 \times 10^{-6})}{(7.996 \times 10^3)} = C_f$$

$$\therefore C_f = 0.01\mu\text{F}$$

O/p waveform

Practical Integrator:

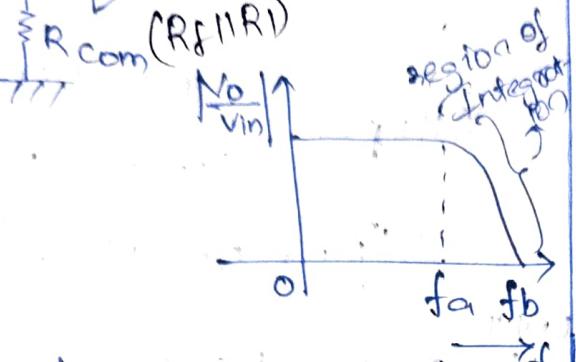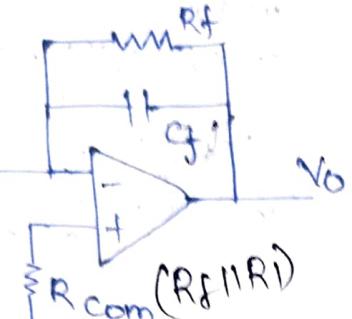

$$fa = \frac{1}{2\pi R_f C_f} ; fb = \frac{1}{2\pi R_1 C_f}$$

$$fb = 10fa \quad (\text{Calculus})$$

Q1 Design an practical Integrator with lower limit of frequency is 160Hz.

$$fa = 160 \text{ Hz} \Rightarrow fb = 1600 \text{ Hz}$$

$$\frac{1}{2\pi R_f C_f} = 160$$

$$\text{let } C_f = 0.01 \text{ nF}$$

$$\Rightarrow R_f =$$


$$fb = 1600 \text{ Hz}$$

$$\frac{1}{2\pi R_1 C_f} = 1600$$

$$\Rightarrow R_1 =$$

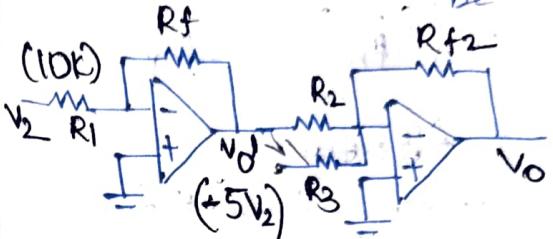Q1 Design a circuit using OPAMP which gives output $V_0 = 5V_2 - 8V_1$, where V_2 and V_1 are inputs.

O/P $V_0 = 5V_2 - 8V_1$ \rightarrow astrodit
i/p: V_2 and V_1 \rightarrow 2 OPAMP's should be used



$$\frac{V_d}{V_2} = -5 \Rightarrow \frac{-R_f}{R_1} = -5 \\ \Rightarrow R_f = 5R_1$$

$$\text{let } R_1 = 10 \text{ k}$$

$$\Rightarrow R_f = 50 \text{ k}$$

$$V_0 = \frac{-R_{f2}}{R_2} (V_d) - \frac{R_{f2}}{R_3} (V_1)$$

$$= \frac{-R_{f2}}{R_2} (-5V_2) - \frac{R_{f2}}{R_3} (V_1)$$

$$\Rightarrow R_{f2} = R_2 = 10 \text{ k} \quad (\text{Assumption})$$

$$\Rightarrow R_{f2} = 8R_3$$


$$\Rightarrow R_3 = \frac{10 \text{ k}}{8} = 125 \text{ }\Omega$$

Q) Design an OPAMP circuit which performs the following operation

$$V_O = -V_1 - 2V_2 - 3V_3$$

as all have same sign

∴ 1 OPAMP is enough

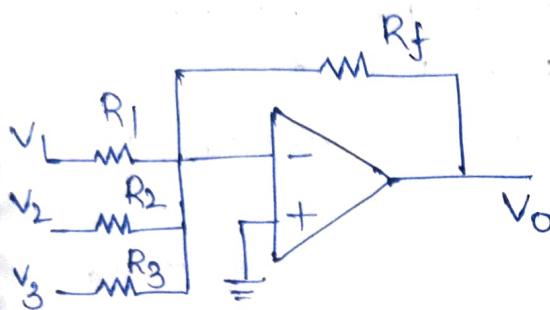

$$V_O = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

$$\frac{R_f}{R_1} = 1; \frac{R_f}{R_2} = 2; \frac{R_f}{R_3} = 3$$


$$\text{let, } R_f = 100K$$

$$\Rightarrow R_1 = 100K\Omega$$

$$R_2 = 50 K\Omega$$

$$R_3 = 33.3 K\Omega$$

Q) find the output.

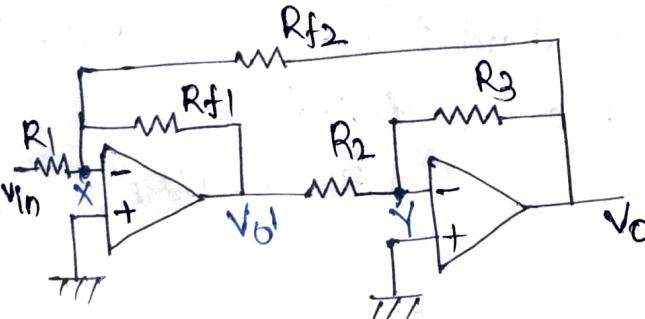

KCL at node X

$$\frac{V_{in}-0}{R_1} = \frac{0-V_d}{R_{f1}} + \frac{0-V_0}{R_{f2}}$$

(1)

KCL at node Y

$$\frac{V_d-0}{R_2} = \frac{0-V_0}{R_3}$$

$$V_0' = -V_0 \left[\frac{R_2}{R_3} \right] \quad (2)$$

(1) & (2)

$$\frac{V_{in}}{R_1} = + \frac{1}{R_{f1}} \left[\frac{V_0 R_2}{R_3} \right] - \frac{V_0}{R_{f2}}$$


$$\frac{V_{in}}{R_1} = V_0 \left[\frac{R_2}{R_3 R_{f1}} - \frac{1}{R_{f2}} \right]$$

$$\frac{V_{in}}{R_1} = V_0 \left[\frac{R_2 R_{f2} - R_3 R_{f1}}{R_2 R_3 R_{f1}} \right]$$

$$\therefore V_0 = V_{in} \left[\frac{R_2 R_3 R_{f1}}{R_1 (R_2 R_{f2} - R_3 R_{f1})} \right]$$

→ Problem on Analog Computer

Butterworth LPF (W)

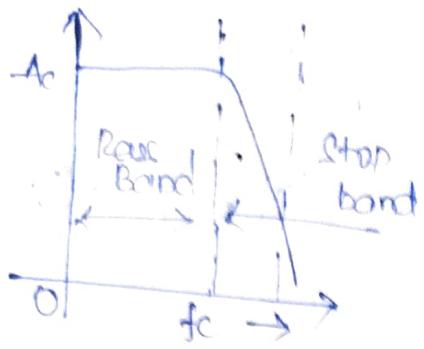


flat - flat filter

- As both PB and SB are flat
- Require high order filter to have fast transition from PB to SB.


Flat = flat filter

Chebychev filter

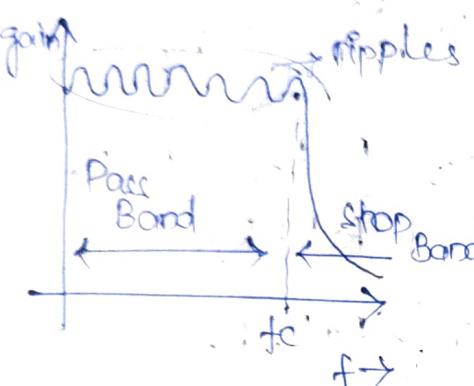

- Ripples are present in PB and SB
- Stop Band is flat
- Have a sharp transition PB to SB
- Require low order filter to have fast transition from PB to SB.

Butterworth second order LPF

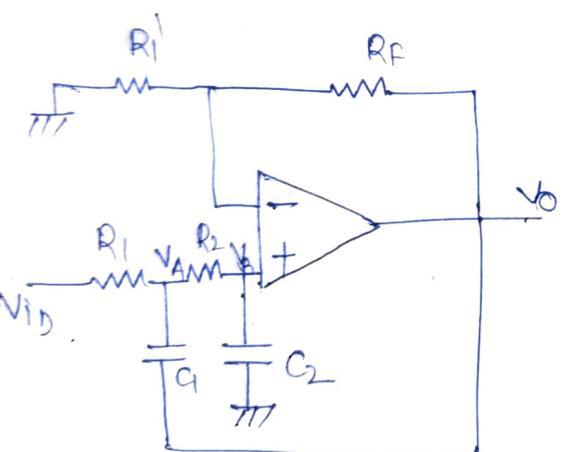

Apply KCL at node A:

$$\frac{V_{in}(s) - V_A(s)}{R_1} = \frac{V_A(s) - V_B(s)}{R_2} + \frac{V_A(s) - V_{out}(s)}{1/sC_1}$$

$$V_B(s) = \frac{V_A(s)}{R_2 + 1/sC_2} \times \frac{1}{sC_2} \quad \text{--- (1)}$$

$$\therefore V_B(s) = \frac{V_A(s)}{1 + sR_2C_2} \quad \text{--- (2)}$$

and, as non-inverting amp.

$$V_o = \left[1 + \frac{R_f}{R_1} \right] V_B(s) \quad \text{--- (3)}$$

(2) & (3) in (1)

$$\frac{V_{in}(s)}{V_{out}(s)} = \frac{\frac{A_o}{R_1 R_2 C_1 C_2}}{s^2 + s(C_2(R_1 + R_2) + (1 - A_o)R_1G) + \frac{R_1 R_2 C_1 C_2}{A_o}}$$

standard 2nd ODE

$$H(s) = \frac{A_o s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \text{--- (4)}$$

$$\zeta = \frac{1}{2\sqrt{\omega_n}}$$

Comparing (2) & (4)

$$2\pi f_D = \omega_D = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\Omega = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 R_2 + R_2 C_2 + R_1 C_1 (1 - A_0)}$$

$$-A_0 = 1 + \frac{R_F}{R_1}$$


when $R_1 = R_2 = R$ & $C_1 = C_2 = C$

then

$$f_C = f_D = \frac{1}{2\pi R C}$$

$$\Omega = \frac{1}{3 - A_0}$$

for Butterworth response

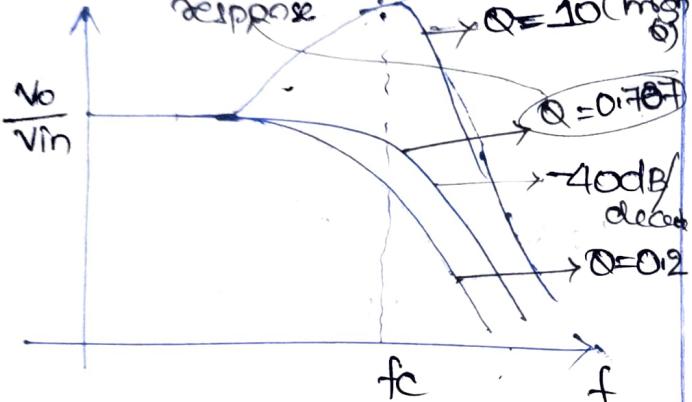


\rightarrow 20dB/decade \rightarrow LPF

B.W.F

$$0.707 = \frac{1}{3 - A_0}$$

$$\therefore A_0 = 1.586$$

Butterworth second order HPF:

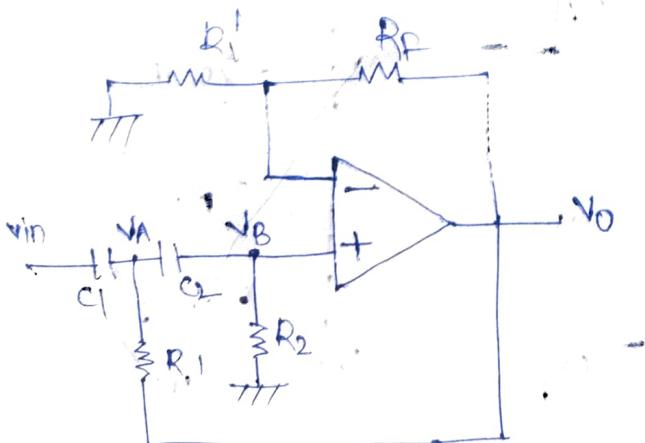

KCL at node A:

$$\frac{V_{in}(s) - V_A(s)}{1/C_1} = \frac{V_A(s) - V_B(s)}{1/C_2} + \frac{V_A(s) - V_o(s)}{R_1}$$
(1)

$$V_B(s) = \frac{V_A(s) \times R_2}{1/C_2 + R_2}$$
(2)

$$V_{o(s)} = \left[1 + \frac{R_F}{R_1} \right] V_B(s)$$
(3)

(1) & (2) & (3):

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 s^2}{s^2 + s(R_1 C_1 + R_2 C_2(1 - A_0)) + \frac{A_0 s^2}{R_1 R_2 C_1 C_2}}$$
R_1, R_2, C_1, C_2
(4)

$$-A_0 = 1 + \frac{R_F}{R_1}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 s^2}{s^2 + \alpha_{dB} s + \omega_0^2}$$
(5)

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$


$$\frac{d}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{R_1 C_1 + R_2 C_2 + R_2 C_2(1 - A_0)}{R_1 R_2 C_1 C_2}$$

If $R_1 = R_2 = R$ & $C_1 = C_2 = C$

$$f_C = f_D = \frac{1}{2\pi R C} \quad i.d = 3 - A_0$$

for Butterworth response

$$\frac{1}{\alpha} = 0.707$$

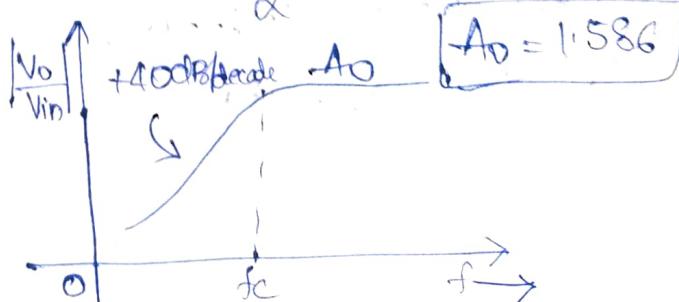

Q] Design a Butterworth second order LPF with cut-off frequency = 1 kHz.

Anc: ① Select value of capacitor $C \leq 1\mu F$

② Assume $R_1 = R_2 = R$ and $C_1 = C_2 = C$; using $f_c = \frac{1}{2\pi RC}$ ^{find} R .

③ Passband gain = 1.586 ; $1 + \frac{R_F}{R_1} = 1.586$

$$\Rightarrow 1. C = 0.1\mu F, f_c = 1\text{kHz}$$

$$R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi(10^3)(0.1 \times 10^{-6})} \approx 1.6\text{ k}\Omega$$


$$2. 1 + \frac{R_F}{R_1} = 1.586$$

$$\frac{R_F}{R_1} = 0.586$$

$$\text{Assume } R_1 = 50\text{ k} \Rightarrow R_F = 0.586 \times R_1$$

$$\therefore R_F = 29.3\text{ k}$$

Ckt diagram:

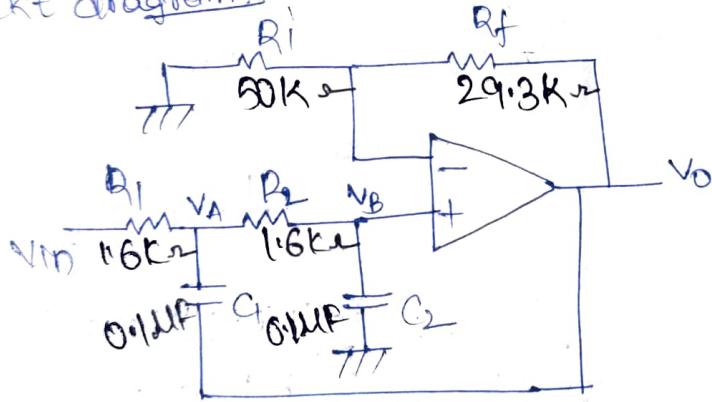


Butterworth filter (LPF)

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}}$$

ω_c is the filter cutoff freq.

'n' - order of filter

Butterworth filters

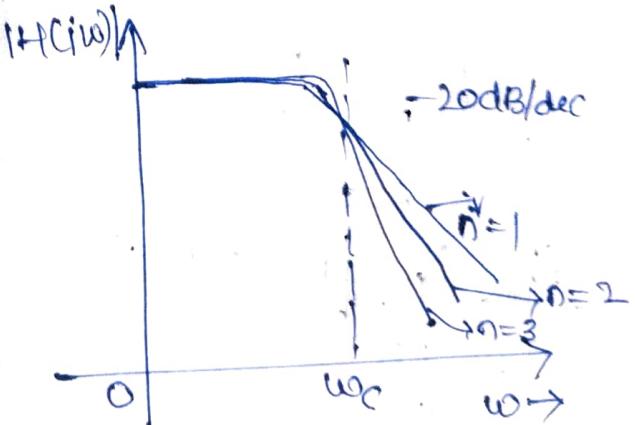

Normalised Butterworth LPF

$$|H_n(j\omega)| = \frac{1}{\sqrt{1+\omega^2 n}} ; \omega_c = 1 \text{ rad/sec}$$

$$|H_n(j\omega)|^2 = H_n(j\omega) H_n(-j\omega) = \frac{1}{1+\omega^{2n}}$$

$$\text{Let } \omega = \frac{s}{j}$$

$$|H_n(j\omega)|^2 = H_n(j\omega) H_n(-j\omega) \\ = H_n(s) H_n(-s)$$

$$|H_n(j\omega)|^2 = \frac{1}{1 + \left(\frac{s}{j}\right)^{2n}}$$

The $2n$ poles of $H_n(s) H_n(-s)$
occur when $\left(\frac{s}{j}\right)^{2n} = -1$

$$s^{2n} = -1$$

$$\text{since, } -1 = e^{j\pi(2k-1)}$$

for k integer & $j \in$

$$\text{we have, } s^{2n} = e^{j(2\pi)(2k-1+n)}$$

$$s_k = e^{j\pi n(2k+n-1)}$$

$$s_k = \cos\left(\frac{\pi}{n}(2k+n-1)\right) + j\sin\left(\frac{\pi}{n}(2k+n-1)\right)$$

$$\text{for } k = 1, 2, \dots, 2n$$

Plot



n poles in LHP correspond to $H_n(s)$

n poles in RHP " " $H_n(-s)$

For obtaining stable & causal

filter
we set

$$H_n(s) = \frac{1}{(s-s_1)(s-s_2) \dots (s-s_n)}$$

$$= \frac{1}{s^n + a_{n-1}s^{n-1} + \dots + a_1s + 1}$$

$$= \frac{1}{P_m(s)}$$

order n	factors of polynomial $B_n(s)$
1	$s+1$
2	$s^2 + 1 \cdot 414s + 1$
3	$(s+1)(s^2 + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.8478s + 1)$
5	$(s+1)(s^2 + 0.6180s + 1)(s^2 + 1.6180s + 1)$
6	$(s^2 + 0.5176s + 1)(s^2 + 1.4142s + 1)$ $(s^2 + 1.9319s + 1)$

scaling for normalized filter

① Replace ' ω ' with $\frac{\omega}{\omega_c}$ in $H_n(\omega)$

② Replace ' s ' with $\frac{s}{\omega_c}$ in $H_n(s)$


Q7 Design a 5th order butterworth LPF with cutoff freq 1KHz.

$$H_n(s) = \frac{1}{(s+1)(s^2+s+1)}$$

$$H_n(s) = \left(\frac{1}{s^2+s+1}\right) \left(\frac{1}{s+1}\right)$$

let cutoff angular frequency = ω_0
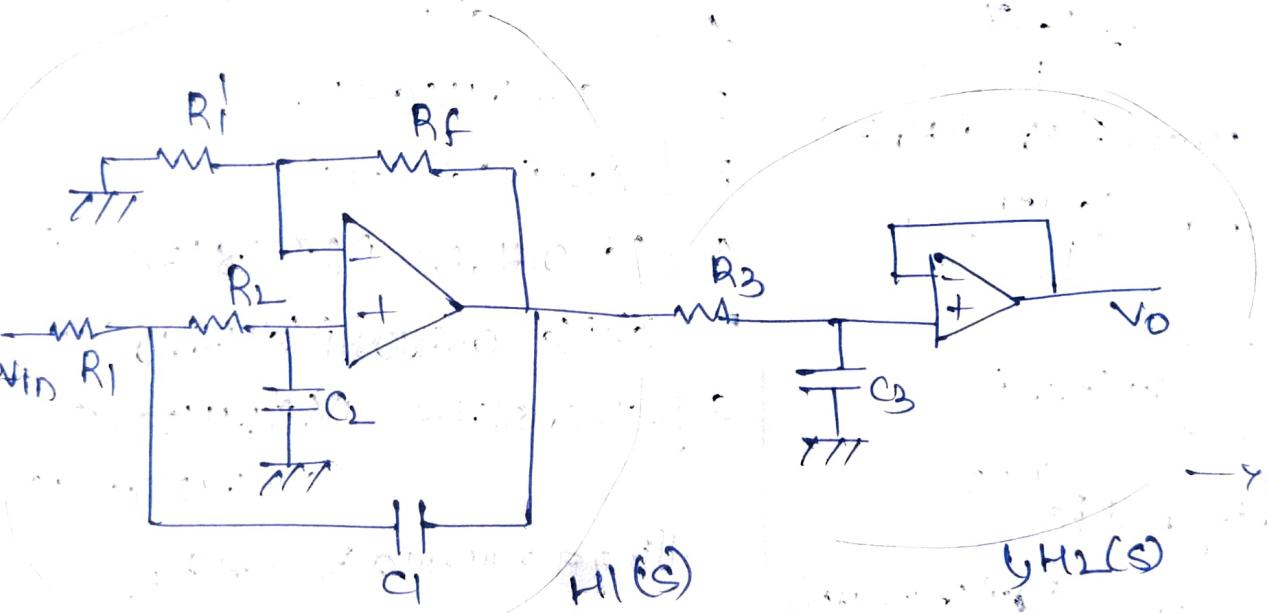
$$H(s) = \frac{1}{\left[\left(\frac{s}{\omega_0}\right)^2 + \left(\frac{s}{\omega_0}\right) + 1\right]} \times \frac{1}{\left(\frac{s}{\omega_0} + 1\right)} = \left(\frac{\omega_0^2}{s^2 + \omega_0 s + \omega_0^2}\right) \left(\frac{\omega_0}{s + \omega_0}\right)$$



$$\omega_{c0} = \frac{1}{2\pi R_3 C_3}$$

Booth have same cutoff frequencies.

when $R_1 = R_2 = R$ & $C_1 = C_2 = C$

$$f_0 = \frac{1}{2\pi RC} = 1 \times 10^3 \text{ Hz}$$

$$C = 0.01 \mu\text{F}$$

$$\Rightarrow R = \frac{1}{2\pi f_0} \Rightarrow R \approx 16 \text{ k}\Omega$$

$$H_1(s) = \frac{A_0 / R_1 C_1 R_2 C_2}{s^2 + s \left[\frac{R_1 C_2 + R_2 C_1 + R_1 C_1 (1 - A_0)}{R_1 R_2 C_1 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

when $R_1 = R_2 = R$ & $C_1 = C_2 = C$

\Downarrow

$$H_1(s) = \frac{A_0 / R^2 C^2}{s^2 + s \left(\frac{3 - A_0}{RC} \right) + \frac{1}{R^2 C^2}}$$

By comparing \Rightarrow

$$\boxed{\omega_0 = \frac{1}{RC} \text{ and } 3 - A_0 = 4 \Rightarrow A_0 = 2}$$

$$H_1(s) = \frac{A_0 \omega_0^2}{s^2 + \omega_0 s + \omega_0^2}$$

$$A_0 = 1 + \frac{R_F}{R_1} \Rightarrow \boxed{R_F = R_1} = \underline{10 k\Omega}$$


$$\left[1 + \frac{1}{1 + \epsilon^2} = A_{max} \right]$$

chebyshev filter (LPF)

$$H(j\omega) = \frac{1}{\left(1 + \epsilon^{2n} \left(\frac{\omega}{\omega_p} \right)^2 \right)^{1/2}}$$

$$H_n(j\omega) = \frac{1}{\left(1 + \epsilon^{2n} (\omega) \right)^{1/2}}$$
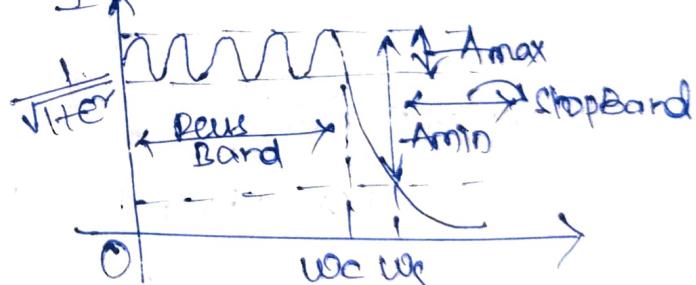
$$\text{where } \epsilon = \left(10^{\frac{A_{max}}{10}} - 1 \right)^{1/2}$$



A_{max} & A_{min} are in dB

$w_C = w_p = \text{pass band edge}$

$w_S = \text{stop band edge}$

$$20 \log 1 - 20 \log \frac{1}{\sqrt{1 + \epsilon^2}} = A_{max}$$

$$\boxed{20 \log (1 + \epsilon^2) = A_{max}} \Rightarrow \log (1 + \epsilon^2) = \frac{A_{max}}{20} = \log_{10} \frac{A_{max}}{10}$$

$$1 + \epsilon^2 = \frac{A_{max}}{10} \Rightarrow \epsilon = \left(10 \frac{A_{max}}{10 - 1} \right)^{1/2}$$

$$f(\omega) = e^{\gamma} c_n(\omega)$$

= chebyshev polynomial

$$c_n(\omega) = \cosh(n \coth(\omega)) \text{ for } \omega \leq 1$$

$$= \cosh(n \coth(\omega)) \text{ for } \omega > 1$$

$$n=0 ; c_0(\omega) = 1$$

$$n=1 ; c_1(\omega) = \omega$$

$$c_{n+1}(\omega) = 2\omega c_n(\omega) - c_{n-1}(\omega)$$

n	$c_n(\omega)$
0	1
1	ω
2	$2\omega^2 - 1$
3	$4\omega^3 - 3\omega$
4	$8\omega^4 - 8\omega^2 + 1$

$$\text{ripple width} = 1 - \frac{1}{(1+e^{\gamma})^2}$$

order of chebyshev filter (LPF)

Given A_{min} , A_{max} , w_s , w_p :

find 'D'

$$-A_{min} = 10 \log_{10} (1 + e^{\gamma} \cosh(c_n(\omega)))$$

for $\omega = \frac{w_s}{w_c}$; normalized

$$e^{\gamma} c_n(\omega) = e^{\gamma} (\cosh(c_n(\coth(\omega))))$$

$$= 10^{-A_{min}/10} - 1$$

$$|A_{min}| = 10 \log_{10} (1 + e^{\gamma} (\cosh(c_n(\coth(\omega))))^2)$$

$$e^{\gamma} = 10^{-\frac{A_{max}}{10}} - 1$$

$$\cosh(c_n(\coth(\omega))) = \left[\frac{10^{-\frac{A_{min}}{10}} - 1}{10^{-\frac{A_{max}}{10}} - 1} \right]^{1/2}$$

$$n \geq \cosh^{-1} \left[\frac{(10^{-\frac{A_{min}}{10}} - 1)}{(10^{-\frac{A_{max}}{10}} - 1)} \right] / \left[\frac{(\cosh^{-1})^2}{10} \right]$$

$$\cosh^{-1} \left(\frac{w_s}{w_c} \right)$$

Poles:

$$1 + e^{\gamma} c_n(\omega) = 0$$

$$s_K = \sigma_K + j\omega_K$$

$$K = 0, 1, 2, \dots, 2n-1$$

$$\sigma_K = \sinh^{-1} \sin((2K+1)\pi/2n)$$

$$\omega_K = \cosh^{-1} \cos((2K+1)\pi/2n)$$

$$\theta_K = (2K+1)\pi/2n$$

$$\text{for } K = 0, 1, 2, \dots, 2n-1$$

$$\$ a = \frac{1}{n} \sinh^{-1}(\frac{1}{e})$$

$$\frac{\sigma_K}{\sinh a} = \sin((2K+1)\pi/2n)$$

$$\frac{\omega_K}{\cosh a} = \cos((2K+1)\pi/2n)$$

$$\left(\frac{\sigma_K}{\sinh a} \right)^2 + \left(\frac{\omega_K}{\cosh a} \right)^2 = 1$$

The specification for chebyshev filter is given by $A_{min} = 20 \text{ dB}$

$$A_{max} = 3 \text{ dB}, \left(\frac{w_s}{w_c} \right) = 1.5$$

determine order of filter \$

confirm stop band requirement
is fulfilled.

$$n = \frac{\cosh^{-1} \left[\left(10^6 - 1 \right) / \left(10^{0.3} - 1 \right) \right]^{1/2}}{\cosh^{-1}(1.5)} \Rightarrow n = 3.11$$

choose $n=4$, $\epsilon = (10^{0.3} - 1)^{1/2} = 1$

$$A_{\min} = 10 \log_{10} \left(1 + \frac{1}{\epsilon} \left[\cosh(4 \cosh^{-1}(1.5)) \right]^2 \right) = 27.4 \text{ dB}$$

> 20 dB
satisfied.

Q] A chebychev filter is required to provide the following specification:-

→ passband maximum ripple width 0.5dB upto 3KHz

→ stopband maximum to be 60dB at 30KHz

$$A_{\max} = 0.5 \text{ dB} \quad | \quad f_c - f_p = 3 \text{ KHz}$$

$$A_{\min} = 60 \text{ dB} \quad | \quad f_s = 30 \text{ KHz}$$

$$n = \frac{\cosh^{-1} \left[\left(10^6 - 1 \right) / \left(10^{0.05} - 1 \right) \right]^{1/2}}{\cosh^{-1} \left(\frac{30}{3} \right)} = 2.88 \Rightarrow \boxed{n=3}$$

$$\epsilon = (10^{A_{\max}/10} - 1)^{1/2} = 0.135$$

$$a = \frac{1}{3} \sinh^{-1} \left(\frac{1}{0.135} \right) = 0.159$$

$$\theta_K = (2k+1) \frac{\pi}{2n} \Rightarrow \theta_0 = \frac{\pi}{6} = 30^\circ$$

$$\theta_1 = 90^\circ$$

$$\theta_1 = -\sinh^{-1} a = -\sinh(0.159) = -0.1625$$

$$s_2 = -0.685 \sin 30^\circ \pm j 1.18 \cos 30^\circ \Rightarrow s_2 = -0.313 \pm j 1.022$$

$$s_3 = -0.685 \sin 90^\circ \pm j 1.18 \cos 90^\circ = -0.685 \quad (\text{repeated root})$$

$$H(s) = \frac{K}{(s+0.685)(s+0.313+j1.022)(s+0.313-j1.022)}$$

$$\therefore H(s) = \frac{K}{(s+0.685)(s+0.6268+1.142j)}$$

as n is odd

where 'K' value occurs when $H(0)=1$

$$\Rightarrow K = (0.685)(1.142)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + e^{2N} c_n^2(\omega)}}$$

when $\omega = 0$


$$c_n(\omega=0) = \cos(N \cos(0))$$

$$c_n(\omega=0) = \cos(N \times \pi/2)$$


when $N \rightarrow \text{even} \Rightarrow c_n(\omega=0) = \pm 1 \rightarrow |H(j\omega)| = \frac{1}{\sqrt{1+e^2}}$

when $N \rightarrow \text{odd} \Rightarrow c_n(\omega=0) = 0 \rightarrow |H(j\omega)| = 1$

$$|H(j\omega)|$$

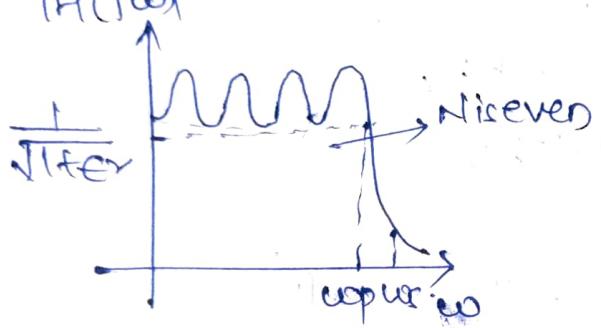

$$|H(j\omega)|$$

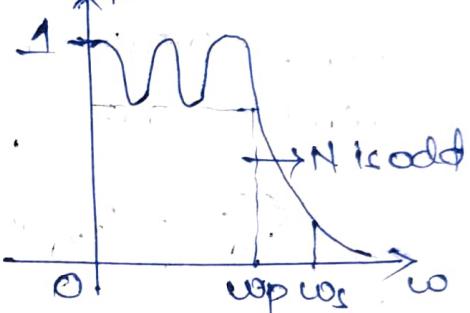

Q] Design a LPF with maximum gain of 5dB with passband ripple of 0.5dB & cutoff frequency = 2500 rad/sec. stopband frequency of filter is 12,500 rad/sec with stop band attenuation of 30dB or more.

$$A_{\max} = 0.5 \text{ dB}, \omega_p = 2500 \text{ rad/sec}, \omega_s = 12500 \text{ rad/sec}$$

$$A_{\min} = 30 \text{ dB}$$

$$\epsilon = 0.1549$$

$$n = 3$$

$$P_1 = -0.312 + j1.029$$

$$P_2 =$$

$$P_3 =$$

$$[K \times \text{gain}]$$

$$H(s) = \frac{0.715 \times \text{gain}}{(s^2 + 0.6264s + 1.424)(s + 0.6264)}$$

Since, $N \text{ is odd}$, $H(s=0) = 1$


$$1 = \frac{K}{1.424 \times 0.6264}$$

$$\Rightarrow K = 0.715$$

$$20 \log(\text{gain}) = 5$$

$$\Rightarrow \text{gain} = 10^{0.25} = 1.7783$$

second order filter

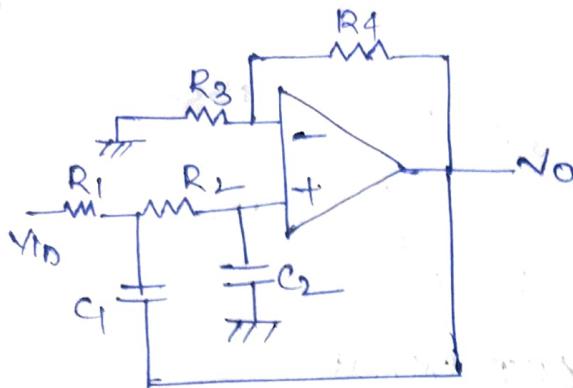

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 / R_1 C_1 R_2 C_2}{s^2 + s \left[\frac{R_1 G_a + R_2 G_2 + R_1 A_0 (1 - A_0)}{R_1 R_2 C_1 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2)$$

when $R_1 = R_2 = R, C_1 = C_2 = C$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 / R^2 C^2}{s^2 + \frac{1}{RC} s (3 - A_0) + \left(\frac{1}{RC} \right)^2}$$

On comparing (1) & (2) eqns.

$$\left(\frac{1}{RC} \right)^2 = 1.1424 \Rightarrow RC = \sqrt{\frac{1}{1.1424}}$$

$$\frac{3 - A_0}{RC} = 0.6264 \Rightarrow (3 - A_0) \sqrt{1.1424} = 0.6264 \\ \Rightarrow A_0 = 2.41$$

Set $A_0 = 1$, (unity gain of filter)

Then, $\frac{V_o(s)}{V_{in}(s)} = \frac{1 / R_1 R_2 C_1 C_2}{s^2 + \left[\frac{R_1 G_a + R_2 G_2}{R_1 R_2 C_1 C_2} \right] s + \frac{1}{R_1 R_2 C_1 C_2}}$

Since $\omega_p = 2500 \text{ rad/sec}$

$$s \rightarrow s/\omega_p$$

$$\Rightarrow H(s) = \frac{0.415 \times 1.1783}{\left(\left(\frac{s}{\omega_p} \right)^2 + 0.6264 \left(\frac{s}{\omega_p} \right) + 1.1424 \right) \left(\frac{s}{\omega_p} + 0.6264 \right)}$$

$$H(s) = \frac{0.415 \times 1.1783 \times \omega_p^3}{(s^2 + 0.6264 s \omega_p + 1.1424 \omega_p^2)(s + 0.6264 \omega_p)} \quad (3)$$

Compare (3) and (2)

$$\frac{1}{R_1 R_2 C_1 C_2} = 1.1414 \times (2500)^2$$

$$\frac{R_1 C_1 + R_2 C_2}{R_1 R_2 C_1 C_2} = 0.6264 \times 2500$$

Let, $R_1 = R_2 = R = 10k\Omega$

$$R_1 = R_2$$

$$\frac{1}{C_1} \text{ assumes } C_1 = C_2 = 1000 \text{ pF}$$



$$\hookrightarrow R_1 \text{ & } R_2$$

$$\frac{1}{R_1 R_2} = 1.1414 \times (2500)^2 (1 \times 10^{-6})^2$$

$$\frac{R_1 + R_2}{R_1 R_2} = 1.1414 \times (2500)^2 (1 \times 10^{-6})^2 \times 0.6264 \times 2500$$

$$\Rightarrow R_1 =$$

$$R_2 =$$

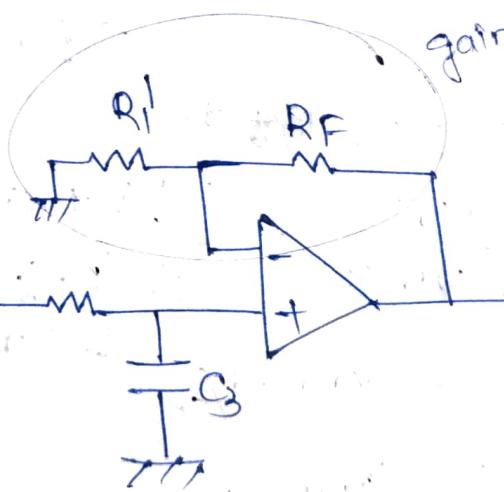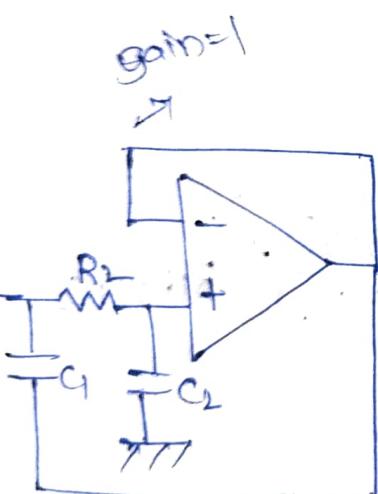

gain = 5dB

$$1 + \frac{RF}{R1} = 1.77$$

$$R1 = 10k\Omega$$


$$\Rightarrow RF = 0.77 \times 10k\Omega$$

$$\Rightarrow \frac{1}{R_3 C_3} = 0.6264 \times 2500$$

$$C_3 = 1 \mu F$$

$$R_3 = ?$$

Butterworth approximation:

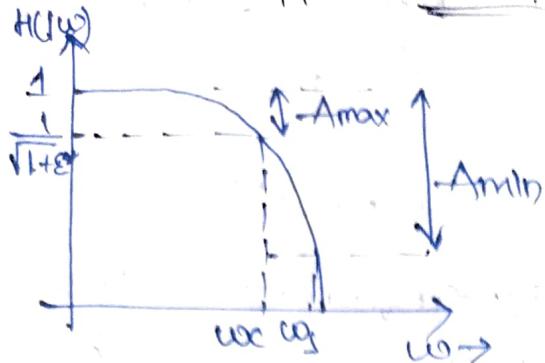

w_c = pass band edge

w_s = stop band edge

A_{\max} = Maximum pass band attenuation

(A_{\min} = Minimum stop band attenuation)
in dB

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 \omega^{2n}}}$$

$$|A_{\max}| = 10 \log_{10} (1 + \epsilon^2)$$

$$\epsilon = \left(10^{\frac{A_{\max}/10}{2}} - 1 \right)^{1/2} \quad \text{--- (1)}$$

$$\text{At } \omega = \frac{w_s}{w_c}$$

$$|A_{\min}| = 10 \log_{10} (1 + \epsilon^2 \omega^{2n}) \quad \text{--- (2)}$$

sub. (1) in (2)

$$A_{\min} = 10 \log_{10} \left(1 + \left\{ 10^{\frac{A_{\max}}{10}} - 1 \right\} (\omega^{2n}) \right)$$

$$\omega^{2n} = \left\{ \frac{10^{\frac{A_{\min}}{10}} - 1}{10^{\frac{A_{\max}}{10}} - 1} \right\}$$

$$\omega = \frac{w_c}{w_c}$$

Taking log on both sides

$$n = \frac{1}{2 \log_{10}(\omega_s/\omega_c)} \times \log_{10} \left\{ \frac{10^{\frac{A_{\min}/10}{2}} - 1}{10^{\frac{A_{\max}/10}{2}} - 1} \right\}$$

- Q) A butterworth LPF is required to provide the following specification passband upto 10KHz with 3dB of loss, stop band to be atleast 100dB down at 100KHz calculate the order of the filter & roots of butterworth polynomials.

$$A_{\max} = 3 \text{ dB}$$

$$A_{\min} = 100 \text{ dB}$$

$$f_s = 100 \text{ KHz}$$

$$f_c = 10 \text{ KHz}$$


$$\Rightarrow n = 5$$

$$H(s) = \frac{1}{(s+1)(s^2 + 1.618s + 1)(s^2 + 0.618s + 1)}$$


Bandpass filter

wide bandpass ($Q < 10$) narrow bandpass ($Q > 10$)


$$Q = \frac{f_c}{BW}$$

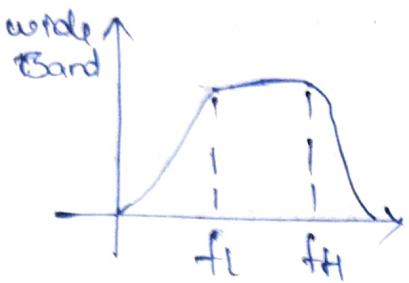

wide band pass filter

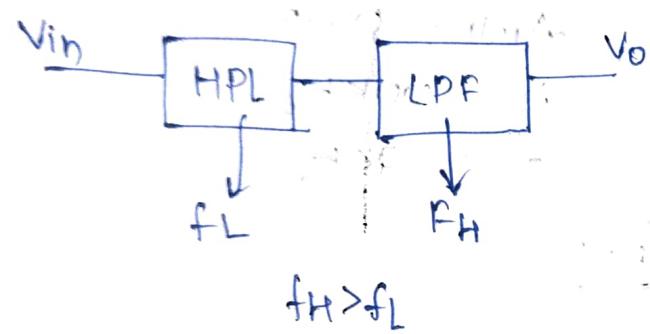


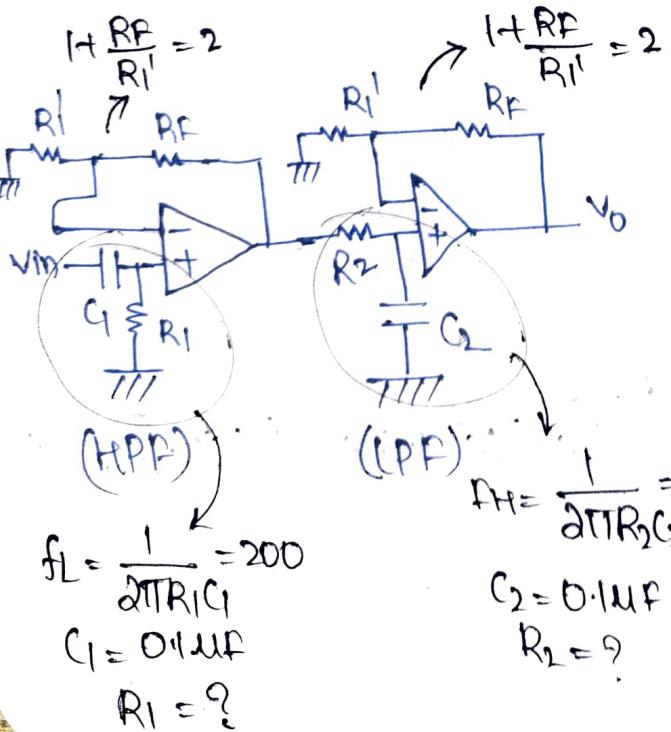
Q Design a wide bandpass filter so that $f_L = 200\text{Hz}$, $f_H = 1\text{kHz}$, & a pass band gain = 4.



$$Q = \frac{f_c}{BW} = \frac{\sqrt{f_L f_H}}{(f_H - f_L)} = 0.56$$

Narrow bandpass filter

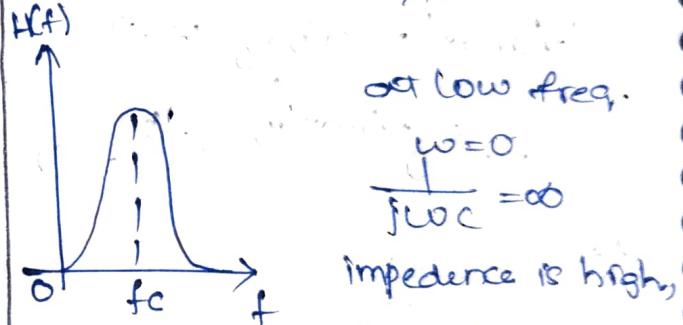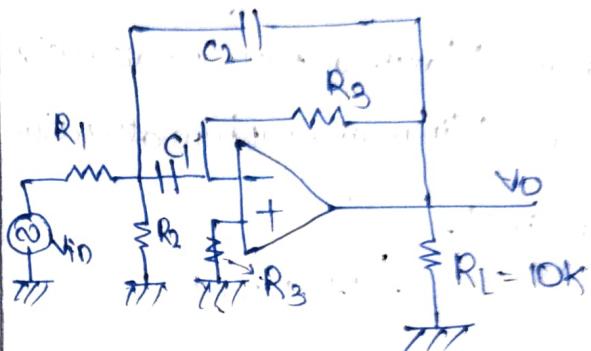High frequencies and low frequencies are rejected by the filter and only narrow frequencies are allowed.



Given f_c , Q , BW , Design Equations are,

Assume,

$$C_1 = C_2 = C$$

$$R_1 = \frac{Q}{2\pi f_c C A_F}$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_F)}$$

$$R_3 = \frac{Q}{\pi f_c C}$$

$$\text{Pass Band gain} = A_p = \frac{R_3}{2R_1}$$

$[A_F < 2Q^2]$ → condition must be satisfied.

→ centre frequency (f_c) can be changed to new centre frequency (f_c'), keep gain & BW constant by changing R_2 to R_2' . $R_2' = R_2 \left(\frac{f_c}{f_c'} \right)^2$

Q. a) Design a narrow bandpass filter with $f_c = 1\text{ kHz}$, $Q = 3$, $A_F = 10$.

b) Change the center freq. to 1.5 kHz , keeping AF and BW constant.

$$C_1 = C_2 = C = 0.01\text{ uF}$$

$$R_1 = 4.72\text{ k}\Omega$$

$$R_2 = 5.97\text{ k}\Omega$$

$$R_3 = 95.5\text{ k}\Omega$$

$$R_2' = 5.97 \times \left(\frac{1\text{ k}}{1.5\text{ k}} \right)^2 = 2.65\text{ k}\Omega$$



Band Reject filters (Band Stop)




$$Q = \frac{f_c}{BW} \quad | \quad Q < 10$$

$$Q > 10$$

wideband reject filter:

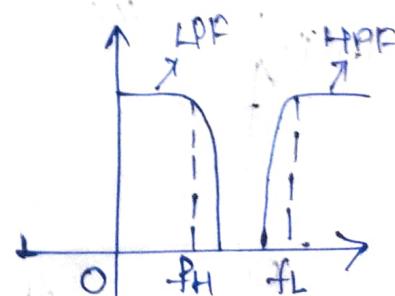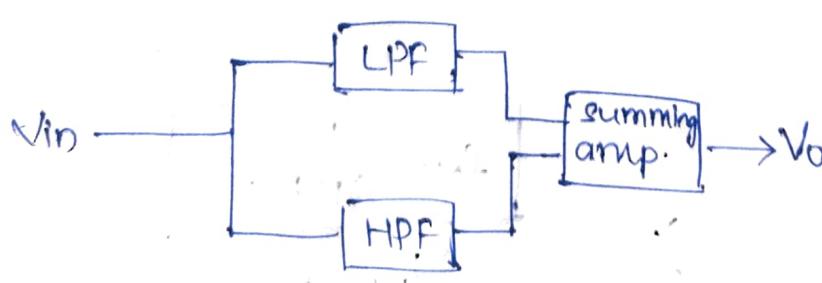

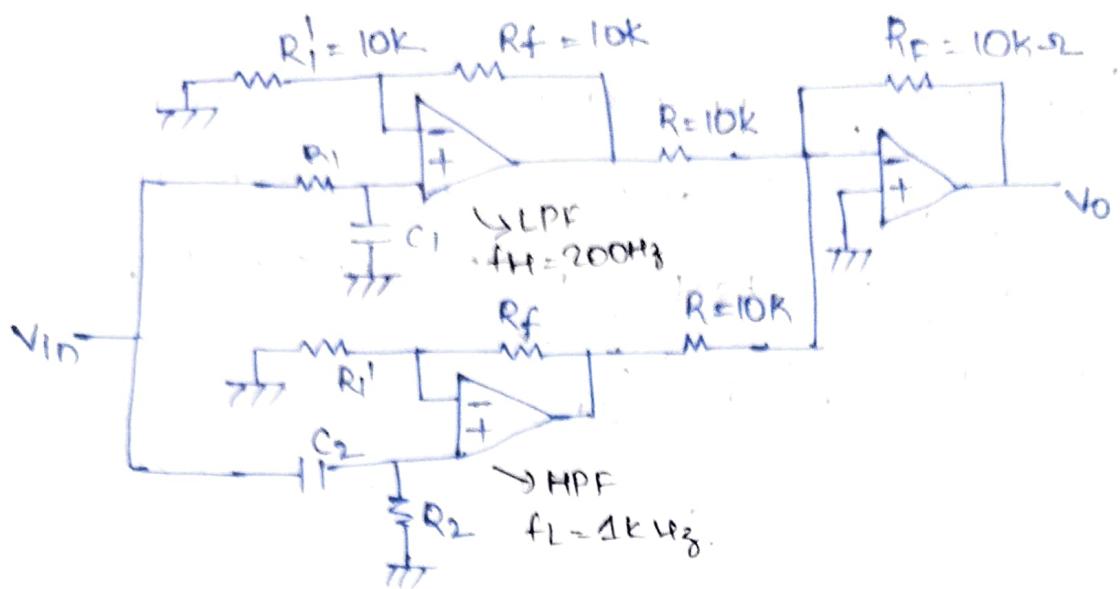Q1 Design a wide band reject filter with $f_H = 200\text{Hz}$ & $f_L = 1\text{kHz}$



Assume $C_1 = C_2 = 0.01\mu\text{F}$

LPF

$$\frac{1}{2\pi R_1 C} = 200$$

$$R_1 = \frac{1}{2\pi \times 200 \times 0.01 \times 10^{-6}}$$

$$\therefore R_1 = \underline{79.5\text{ k}\Omega}$$



HPF

$$\frac{1}{2\pi R_2 C} = 1000$$

$$R_2 = \underline{15.9\text{ k}\Omega}$$

Narrow band reject filter (notch filter):- \rightarrow Twin-T network

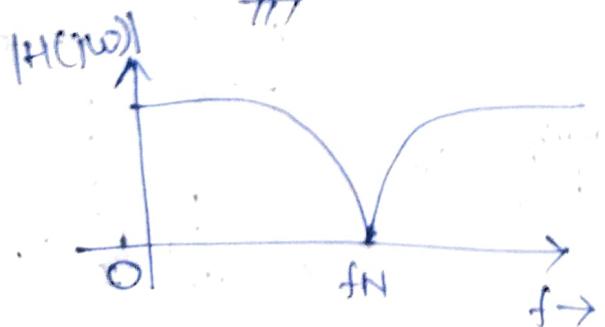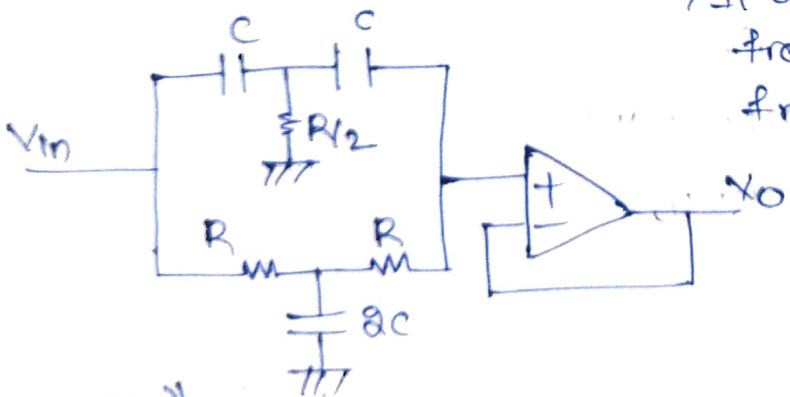\hookrightarrow It will pass both high and low frequencies and reject medium freq.



$$X_C = \frac{1}{j\omega C}$$

$\rho_{\text{low}} \rightarrow X_C \approx 0$
O.C

$\rho_{\text{high}} \rightarrow X_C \approx \infty$
S.C

$$f_N = \frac{1}{2\pi R C}$$

notch frequency

Q. Design a 60Hz active notch filter.

$$f_{notch} = 60\text{Hz}$$

$$\text{let } C = 0.068\mu\text{F}$$

$$R = \frac{1}{2\pi f_{notch} C} = 39.01\text{ k}\Omega$$

Frequency Transformations

① Normalised LPF to LPF;

$$s \rightarrow \frac{s}{\omega_c}$$

$H(s) \rightarrow$ Normalised LPF

$$(\text{LPF} \leftarrow H'(s) = H\left(\frac{s}{\omega_c}\right))$$

② Normalised LPF to HPF

$$s \rightarrow \frac{s}{\omega_c} \quad s \rightarrow \frac{\omega_c}{s}; \quad H(s) \rightarrow \text{normalised LPF}$$

$$H'(s) = H\left(\frac{\omega_c}{s}\right) \rightarrow \text{HPF}$$

③ Normalised LPF to BPF

$$s \rightarrow \frac{s^2 + \omega_L \omega_H}{s(\omega_H - \omega_L)}$$


$$H'(s) = H\left[\frac{s^2 + \omega_L \omega_H}{s(\omega_H - \omega_L)}\right] \rightarrow \text{Band Pass filter}$$

④ Normalised LPF to BSF

$$s \rightarrow \frac{s(\omega_H - \omega_L)}{s^2 + \omega_L + \omega_H}$$

$$H'(s) = H\left[\frac{s(\omega_H - \omega_L)}{s^2 + \omega_L \omega_H}\right] \rightarrow \text{Band-stop filter.}$$

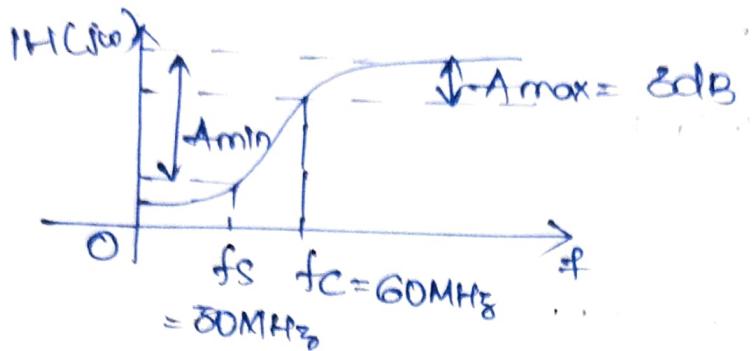Q) A butterworth HPF has $f_c = 60 \text{ MHz}$, $A_{\min} = 40 \text{ dB}$
 $f_s = 30 \text{ MHz}$, $A_{\max} = 3 \text{ dB}$. Find order of filter.



$$n = \frac{1}{2 \log\left(\frac{\omega_c}{\omega_s}\right)} \times \log_{10} \left(\frac{\frac{A_{\min}}{10^{10}} - 1}{\frac{A_{\max}}{10^{10}} - 1} \right) \rightarrow \text{normalised LPF}$$

$$\text{normalised HPF} \rightarrow n = \frac{1}{2 \log\left(\frac{\omega_c}{\omega_s}\right)} \log_{10} \left(\frac{\frac{A_{\min}}{10^{10}} + 1}{\frac{A_{\max}}{10^{10}} - 1} \right)$$

$$n = 6.64 \Rightarrow n = 7$$


Poles: $\rightarrow ?$

Transfer
 $H(s) \rightarrow ?$

Q. A chebyshev HPF has,

$f_c = 60 \text{ MHz}$, $A_{\min} = 40 \text{ dB}$, $f_s = 30 \text{ MHz}$, $A_{\max} = 0.15 \text{ dB}$

find order of filter.

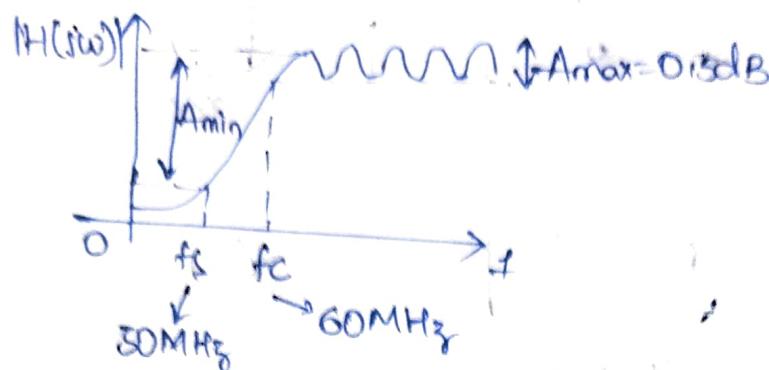

norm HPF $\Rightarrow n = \cosh^{-1} \left(\frac{(10^{\frac{A_{\min}}{10}} - 1)}{(10^{\frac{A_{\max}}{10}} - 1)} \right)^{\frac{1}{2}}$


$\cosh^{-1} \left(\frac{\omega_s}{\omega_c} \right)$

$n \rightarrow ?$

pole $\rightarrow ?$

T.F $\rightarrow ?$

IC555:

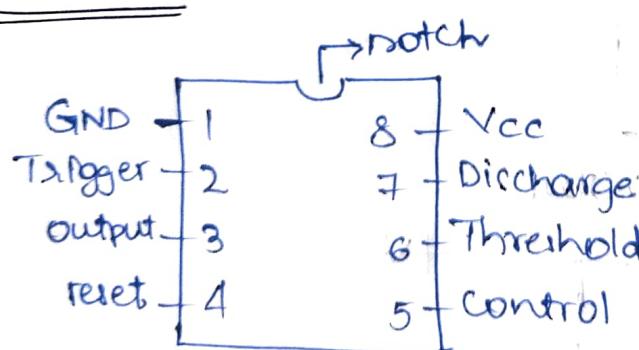

pin diagram