
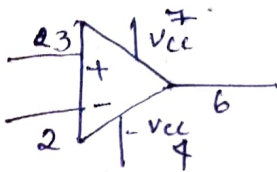


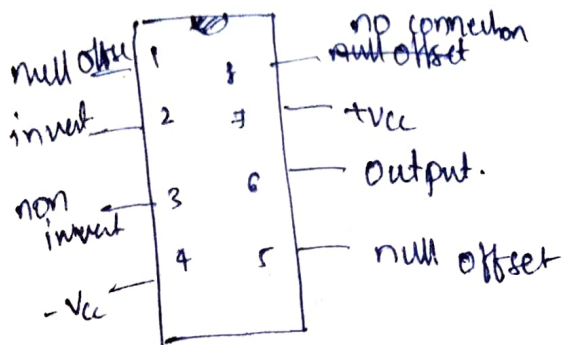
1) Amplifiers which performs operations like addition, subtraction, division, multiplication, integration, differentiation ^{many more} on applied input voltage are known as Operational amplifiers.



Ideal conditions:

- $A_d = \infty$ (differential gain)
- $CMRR = \infty$, $\text{slew rate} = \infty$
- $R_{\text{input}} = \infty$, $\text{Bandwidth} = \infty$
- $R_o = 0$. → Output voltage will be zero if offset voltage is zero.

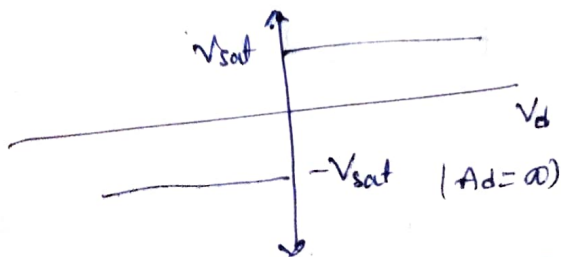
2) Ideal Transfer characteristic of OPAMP



Here (ideally) whenever there is $-ve V_d$, V_o will be $-V_{\text{sat}}$ and when there is $+ve V_d$, V_o will



change $+V_{\text{sat}}$.

Practical OPAMP:

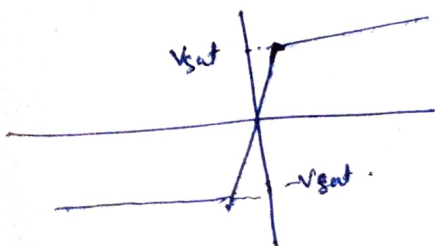

But in practical there will not be any sudden change to $-V_{\text{sat}}$ to $+V_{\text{sat}}$. it will take some time to change.

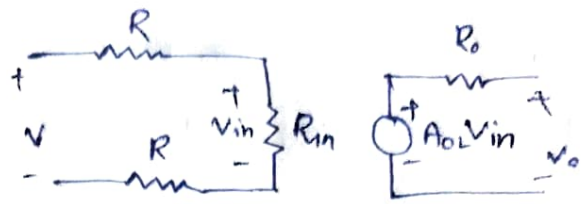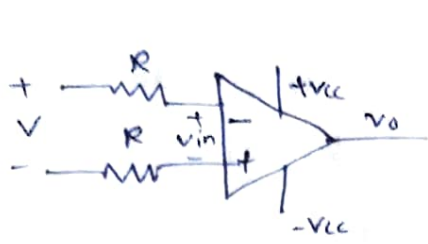3) measurement of input Resistance of OPAMP.



(Equivalent circuit)

Case 1: $R=0 \Rightarrow V=v_{in}$

$$V_o = A_{OL} V \Rightarrow A_{OL} = \frac{V_o}{V}$$

Case 2: $R \neq 0$



$$v_{in} = \frac{V}{R_{in} + 2R} \times R_{in} \quad \left(\because \text{I in loop} = \frac{V}{R_{in} + 2R} \right)$$

$$V_o' = \frac{A_{OL} \times V \times R_{in}}{R_{in} + 2R} \quad \left(\because V_o' = A_{OL} v_{in} \right)$$

$$\Rightarrow V_o' R_{in} + 2R V_o' = A_{OL} V R_{in}$$

$$\boxed{R_{in} = \frac{2R V_o'}{A_{OL} V - V_o'}} \quad \text{input resistance of OPAMP.}$$

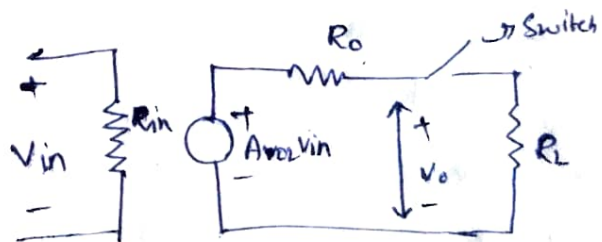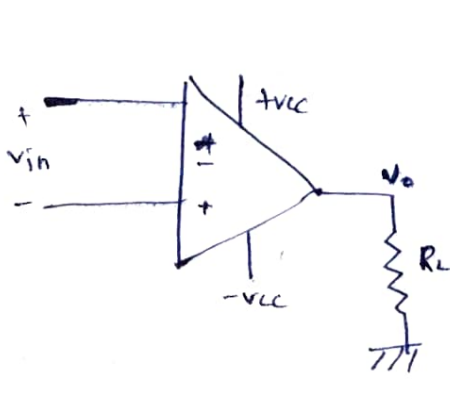Measurement of output resistance of OPAMP:



(Equivalent ckt)

Case 1: (Switch is Open)

$$V_o = A_{OL} V_{in} \Rightarrow A_{OL} = \frac{V_o}{V_{in}}$$

case 2 (switch is closed)


$$\frac{A_{ol} V_{in}}{R_o + R_L} \times R_L = V_o'$$

$$\Rightarrow A_{ol} V_{in} R_L = V_o' R_o + V_o' R_L$$

$$R_L = \frac{V_o' R_o}{A_{ol} V_{in} - V_o'}$$

output Resistance of OPAMP.

4) measurement of slew rate:

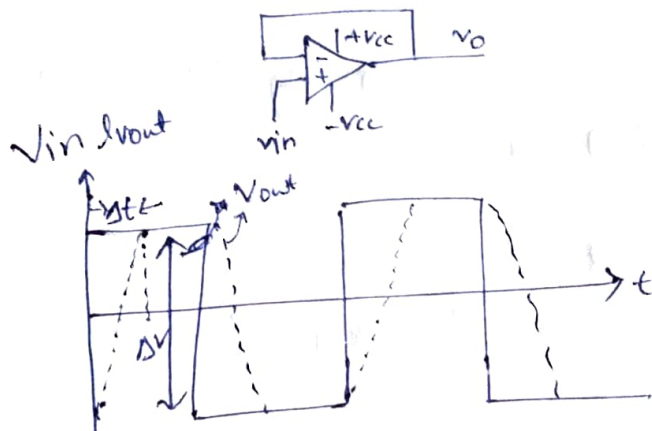

$$S.R. = \frac{dv_o}{dt} = \frac{\Delta V}{\Delta t}$$

→ measurement of CMRR:

case-1




(differential input)

$$CMRR = \frac{A_d}{A_c}$$

(common mode input = 0, $\frac{V_1 + V_2}{2} = 0$)

case-2

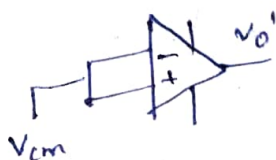

(common mode input)

(Same op. as in case 1)

(differential i/p = 0)

$$\therefore CMRR = \frac{A_d}{A_c} = \frac{V_o' / V_d}{V_o' / V_{cm}} = \frac{V_{cm}}{V_d}$$

(V_o' is a constant).

w.r.t $V_o = A_d V_d + A_c V_c$

in case ① $\rightarrow V_o' = A_d V_d$ ($\because V_c = 0$)


case ② $\rightarrow V_o' = A_c V_{cm}$ ($\because V_d = 0$)

$$CMRR = \frac{A_d}{A_c} = \frac{V_{cm}}{V_d}$$

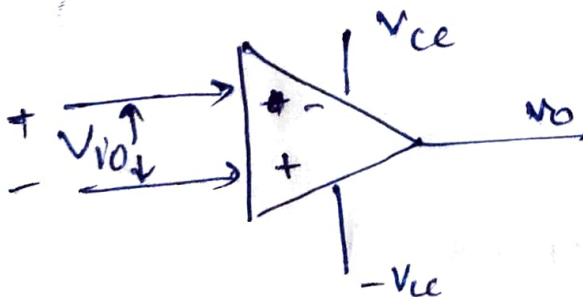
5) \rightarrow let us take V_{cc1} corresponding to input offset voltage V_{io1}

\rightarrow let us take V_{cc2} corresponding to input offset voltage V_{io2}

now $PSRR = \frac{dV_{io}}{dV_{cc}} = \frac{V_{io2} - V_{io1}}{V_{cc2} - V_{cc1}} //$



6). $V_o' = -2V_1 + 3V_2 - 4V_3$

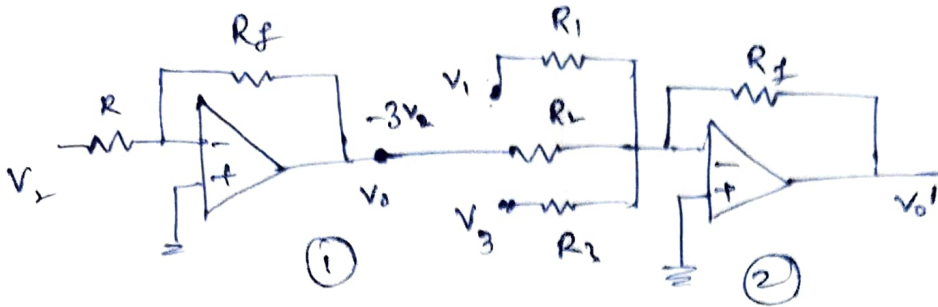

$$\frac{R_f}{R} = 3$$

$$R_f = 3R$$

$$R = 10k$$

$$R_f = 30k$$

$$V_o' = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_o - \frac{V_3 R_f}{R_3}$$

$$-2V_1 + 3V_2 - 4V_3 = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} 3V_2 - \frac{V_3 R_f}{R_3}$$

$$\frac{R_f}{R_1} = 2$$

$$R_1 = 15k$$


$$\frac{R_f}{R_2} = 1$$

$$R_2 = 30k$$

$$\frac{R_f}{R_3} = 4$$

$$R_3 = 7.5k$$

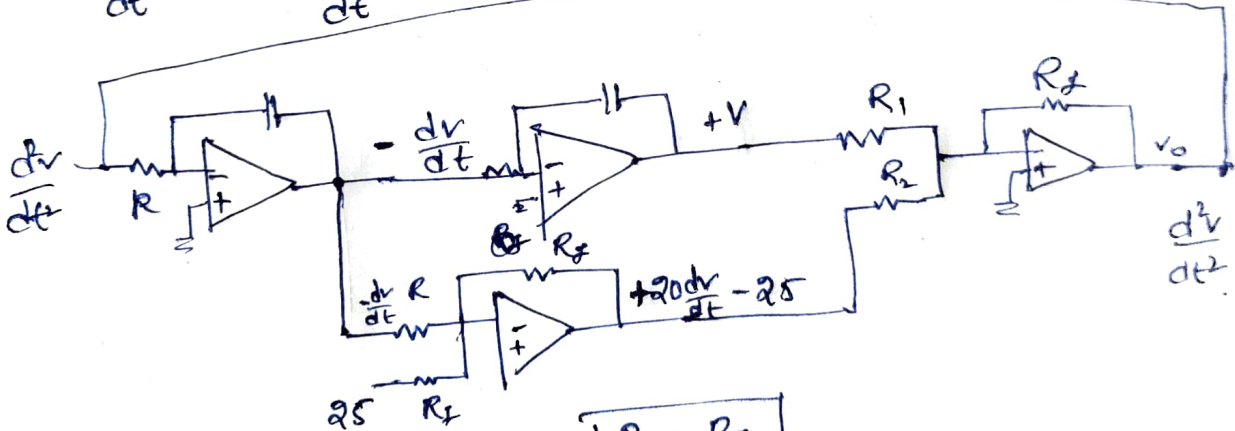7) $\frac{d^2v}{dt^2} = -20\frac{dv}{dt} - 100v + 25$



$$R_2 = R_f$$

$$\frac{R_f}{R} = 20$$

$$R_f = 100k\Omega$$

$$R = 5k\Omega$$

$$\frac{R_f}{R_1} = 100$$

$$R_1 = 100\Omega$$