
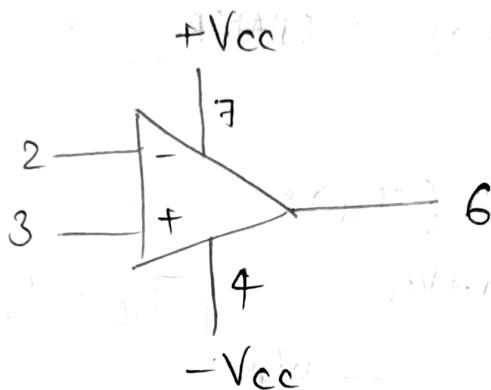


24/08/22


## Operational Amplifier:

→ performs mathematical operations

e.g: IC741

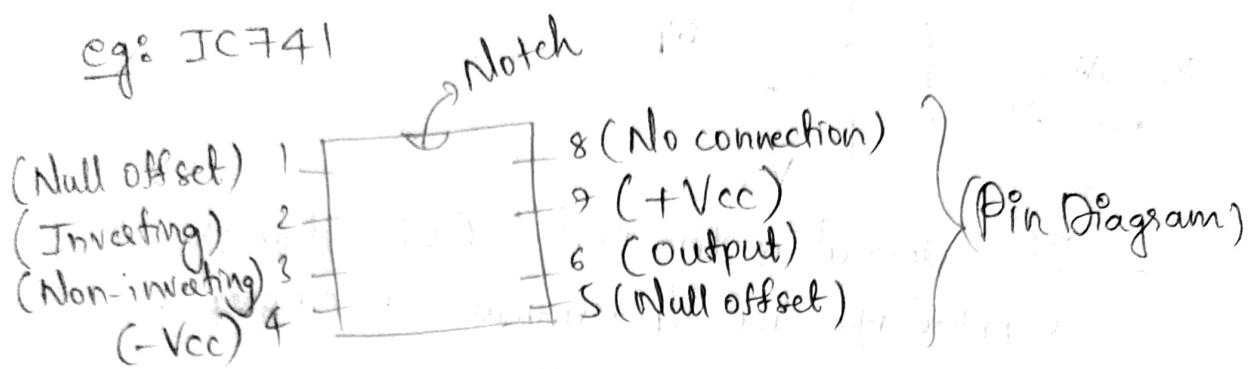


## Block diagram of OPAMP:

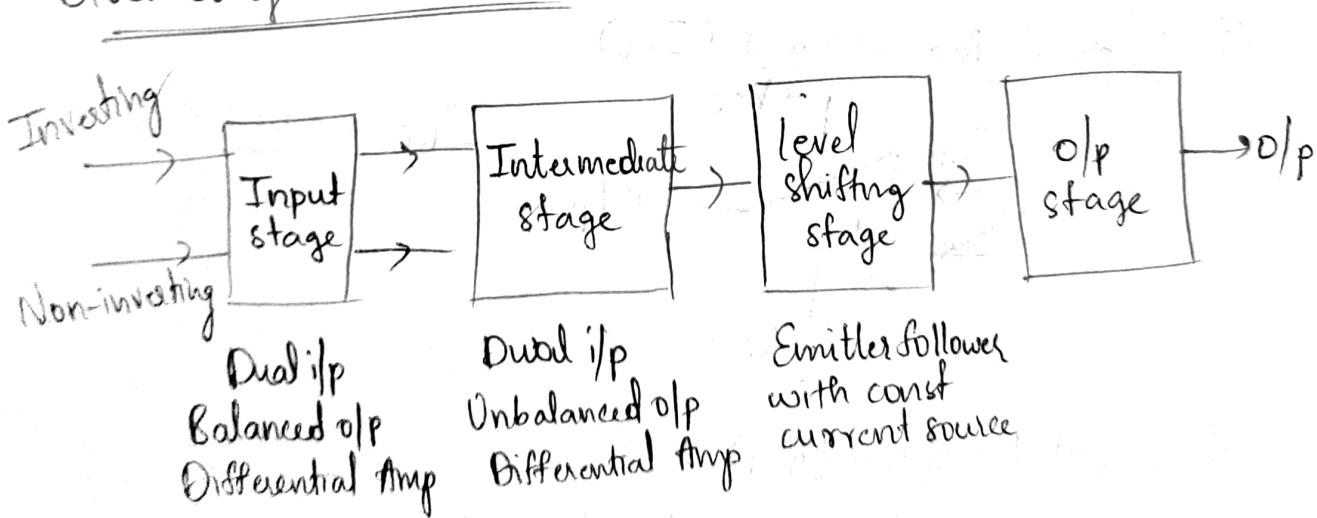


## • Parameters of OPAMP:

### ① Input offset Voltage ( $V_{IO}$ ):

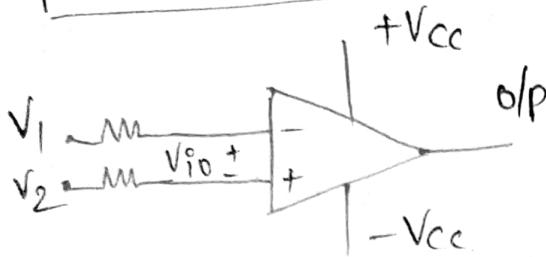


→ It is defined as the voltage ( $V_{IO}$ ) that should be supplied b/w two i/p terminals of OPAMP to make the o/p voltage of OPAMP zero.

### ② Input offset current ( $I_{IO}$ ):

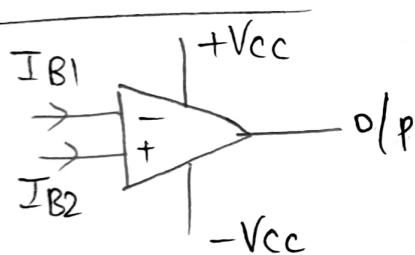

$$I_{IO} = I_{B2} - I_{B1}$$

### ③ Output Bias Current: ( $I_{BO}$ )

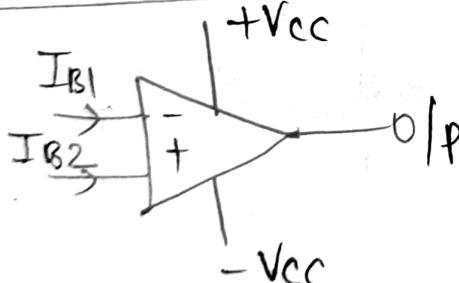

$$I_{BO} = \frac{I_{B1} + I_{B2}}{2}$$

### ④ Input Resistance ( $R_{IN}$ ):

→ It is defined as input resistance seen by one of the i/p terminal with other i/p terminal grounded.

## ⑤ Input capacitance ( $C_{in}$ ):

→ It is defined as capacitance as seen by the one of i/p terminal with other i/p terminal grounded.

## ⑥ Common mode rejection ration (CMRR):

$$CMRR = \frac{A_d}{A_c} = \frac{\text{Differential gain of OPAMP}}{\text{Common mode gain of OPAMP}}$$

$$V_d = V_1 - V_2$$

$$V_c = \frac{V_1 + V_2}{2}$$

$$V_o = A_d V_d + A_c V_c$$

$$A_d \gg A_c$$

## ⑦ Power supply rejection ratio (PSRR):

→ It is defined as ratio of change in i/p offset voltage & change in  $\downarrow$  one of the biasing voltages with other biasing voltages remaining constant.

$$PSRR = \frac{dV_{io}}{dV_{cc}}$$

## ⑧ Slew rate: If is the maximum change in o/p voltage wrt time

$$\text{Slew rate} = \frac{dV_o}{dt}$$

## ⑨ Input offset Voltage diff:

$$\frac{dV_{io}}{dT}$$

Temperature.

## ⑯ Input offset Current drift:

$$\frac{dI_{io}}{dT} \rightarrow \text{Temperature.}$$

## • Ideal OPAMP characteristics :

$$① A_d = \infty$$

$$② R_{in} = \infty$$

③ Zero o/p voltage when difference input ( $V_1 - V_2$ ) = 0


④ Infinite Bandwidth

$$⑤ CMRR = \infty$$


$$⑥ \text{Slew rate} = \infty$$

$$⑦ R_{out} = 0$$

## • Equivalent circuit of OPAMP:

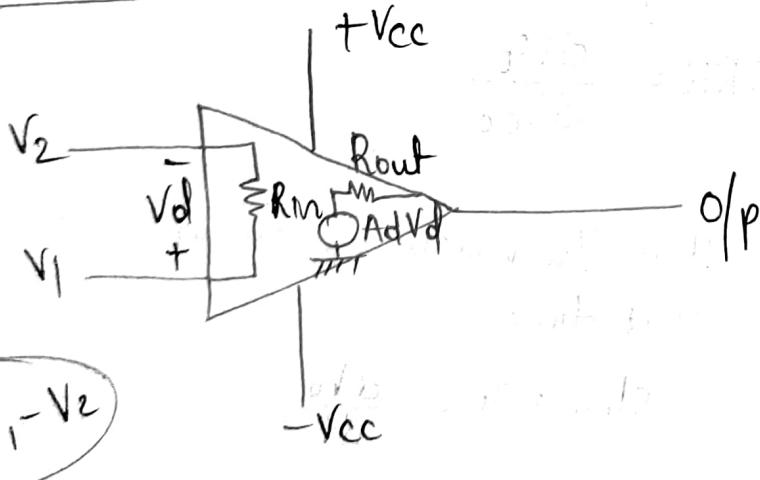
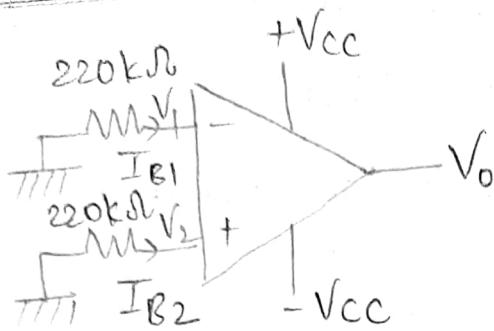
## Measurement of Input bias current and Input offset current.



Observation table:


$V_1, V_2 \rightarrow$  given

$$I_{B1} = \frac{V_1}{220k}; I_{B2} = \frac{V_2}{220k}$$

$$\text{Input bias current} = \frac{I_{B1} + I_{B2}}{2}$$

$$\text{Input offset current} = |I_{B1} - I_{B2}|$$

## Measurement of Input offset voltage:

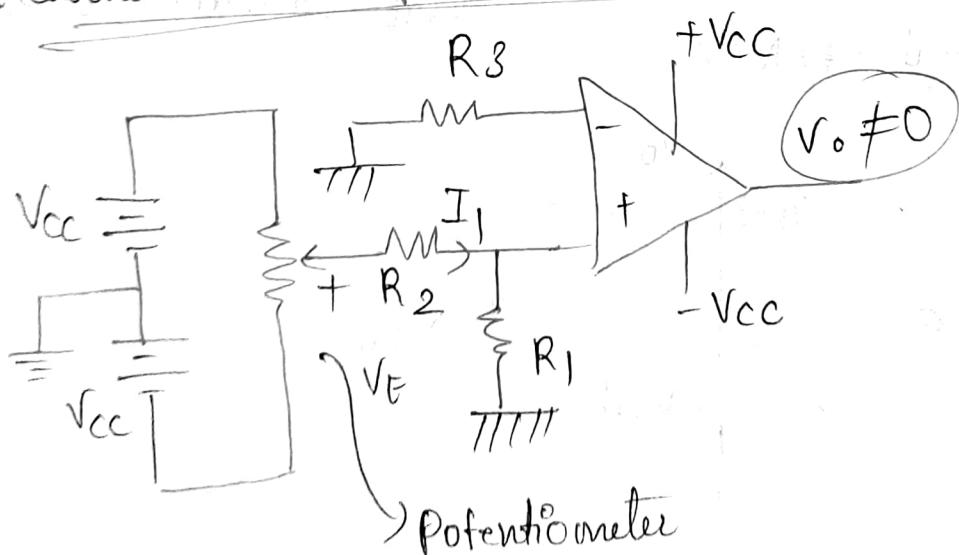

$$I_1 = \frac{V_E}{R_1 + R_2} \quad \left\{ \begin{array}{l} V_I = R_1 \times I_1 = \frac{V_E R_1}{R_1 + R_2} \\ \text{Input offset Voltage} \end{array} \right.$$


## Measurement of PSRR on SVRR:

① Set  $V_{cc} = 13V$  & measure the corresponding input offset voltage ( $V_{io1}$ ).

② set  $V_{cc} = 17V$  & measure the corresponding input offset voltage ( $V_{io2}$ )


$$\boxed{PSRR = \frac{dV_{io}}{dV_{cc}}}$$
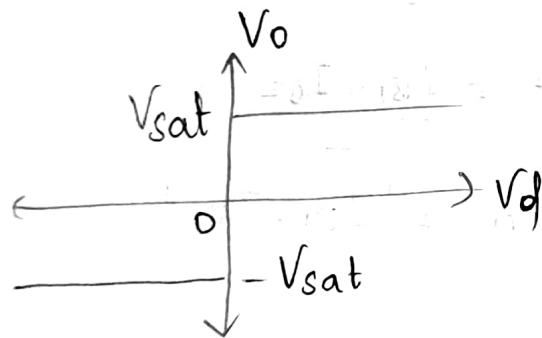
## \* Ideal transfer characteristics of OPAMP:




$V_{sat}$  - Saturation voltage.

## \* Practical OPAMP:

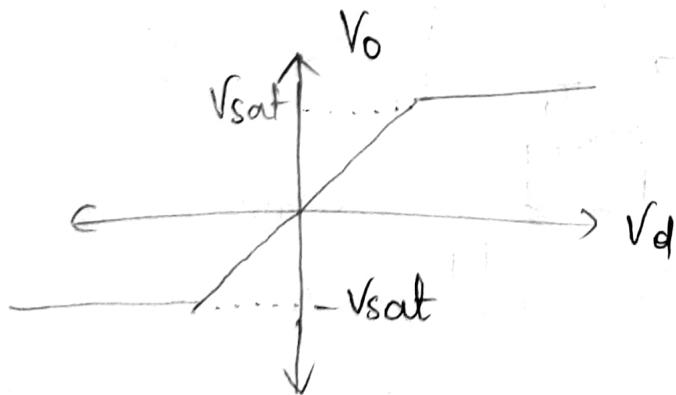

## • Virtual Ground Concepts

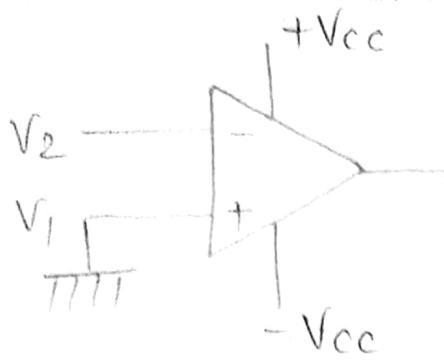


$$V_d = V_1 - V_2 \Rightarrow V_1 \approx V_2$$

$$V_{out} = (V_1 - V_2) A_d$$

↳ differential gain.

$$V_1 - V_2 = \frac{V_o}{A_d} \approx 0 \text{ (since } A_d \text{ is very large)}$$

## • Non-inverting Amplifier:

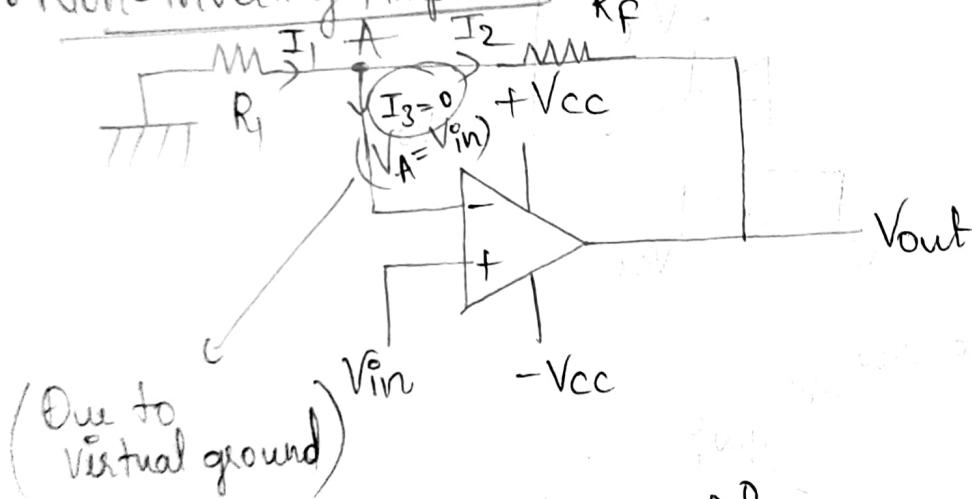

$$I_1 = I_2 + I_3$$

$$\boxed{I_1 = I_2}$$

$$0 - \frac{V_{in}}{R_1} = \frac{V_{in} - V_o}{R_F}$$


$$V_{in} - V_o = \frac{R_F}{R_1} (-V_{in})$$

$$V_{in} + \frac{R_F}{R_1} V_{in} = V_o$$

$$\boxed{\frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_1}}$$

Gain of  
Non-inverting  
amplifier.


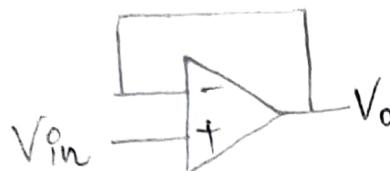
→ If  $R_f = \infty$  and  $R_i = 0$  then the circuit is called Voltage follower circuit.



Voltage follower circuit

$$\frac{V_0}{V_{in}} = 1 \rightarrow V_0 = V_{in}$$


• Measurement of slew rate:

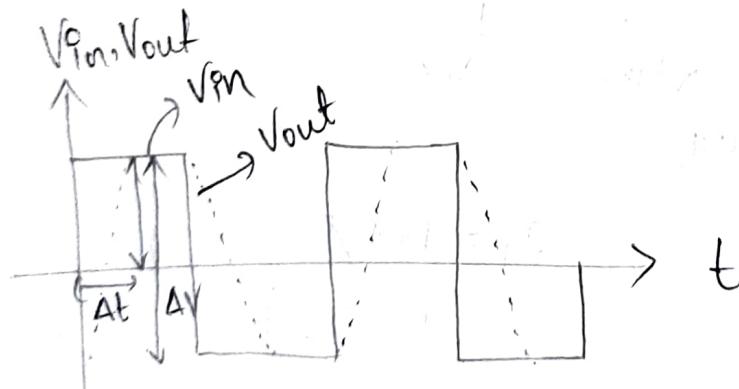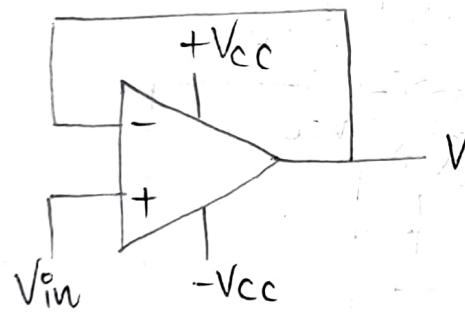


$$\text{Slew rate} = \frac{dV_0}{dt} = \frac{\Delta V}{\Delta t}$$

## Measurement of CMRR:

Case-I:


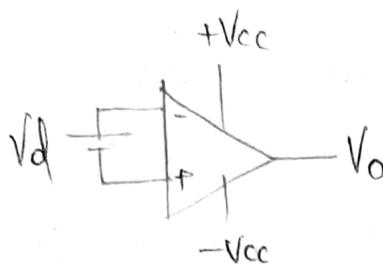


Case-II:

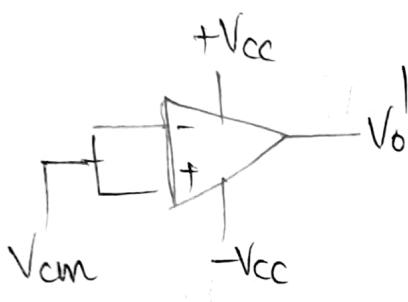

$$CMRR = \frac{A_d}{A_c} = \frac{\frac{V_o}{V_d}}{\frac{V_o}{V_{cm}}} = \frac{V_{cm}}{V_d}$$
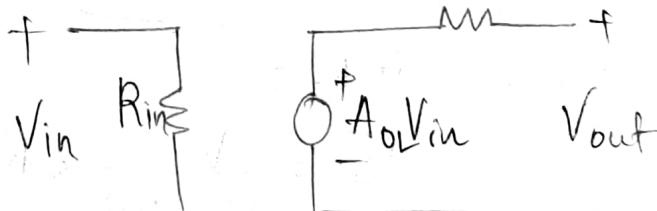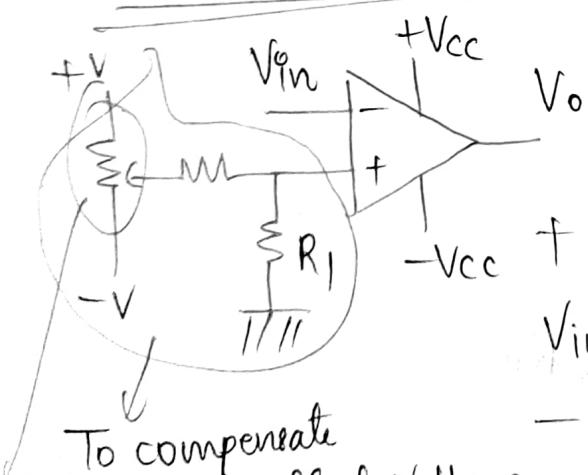
## Measurement of Open loop gain of Amplifier:



To compensate  
input offset Voltage



Equivalent Circuit

Potentiometer

$$V_o = A_{OL} V_{in}$$

$$A_{OL} = \text{open loop gain} = \frac{V_o}{V_{in}}$$
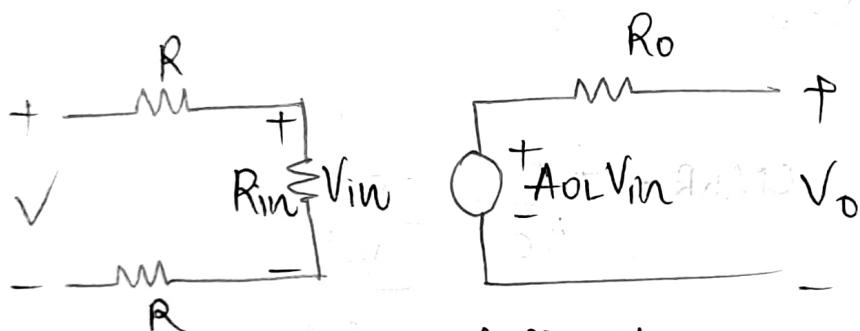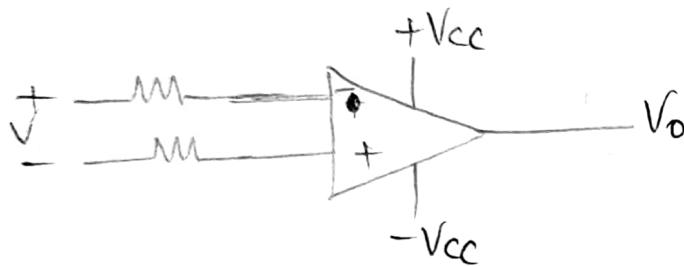
## Measurement of Input Resistance of OPAMP:



Equivalent Circuit

Case-1: if  $R = 0$

$$V_o = A_{OL} V$$



$$A_{OL} = \frac{V_o}{V}$$

Case-2: if  $R \neq 0$

$$V_{in} = \frac{V}{R_{in} + 2R} \times R_{in}$$

$$V_o = \frac{A_{OL} \times V R_{in}}{R_{in} + 2R}$$
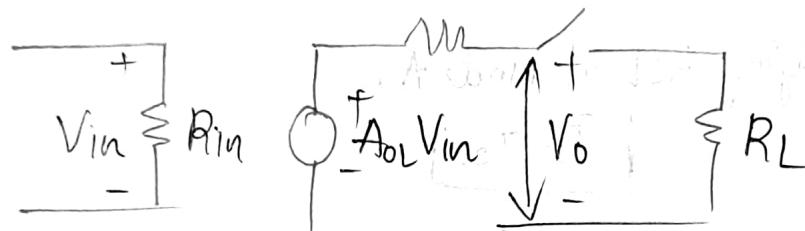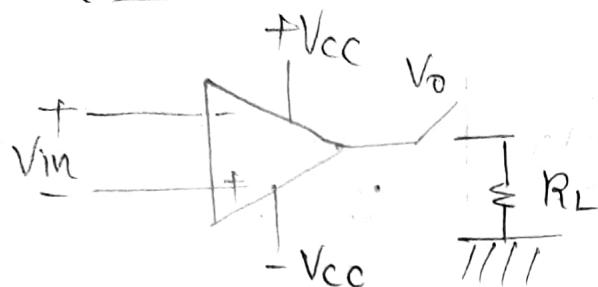
## Measurement of Output resistance of OPAMP




case-1: (switch is open)

$$V_o = A_{OL} V_{in}, \quad A_{OL} = \frac{V_o}{V_{in}}$$

case-2: (switch is closed)

$$\frac{A_{OL} V_{in}}{R_o + R_L} \times R_L = -V_o$$

• Integrator using OPAMPs

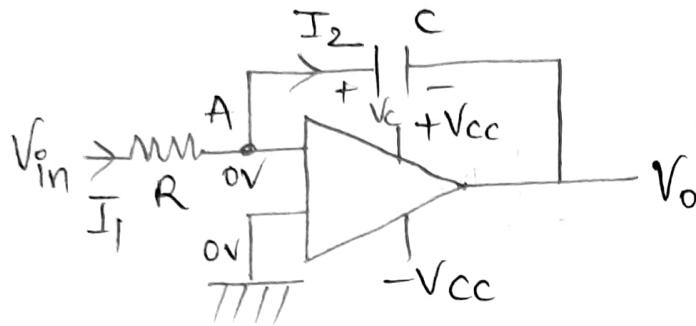

Applying KCL at Node A,

$$I_1 = I_2$$

$$\frac{V_{in} - 0}{R} = I_2 = \frac{CdV_c}{dt} = \frac{Cd}{dt}(0 - V_o)$$

$$\frac{V_{in}}{R} = -\frac{CdV_o}{dt}$$

$$\frac{dV_o}{dt} = -\frac{1}{RC} V_{in}$$

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{Z_f}{Z_i} = \frac{\frac{1}{SC}}{R} = \frac{1}{SCR}$$

$$A_V \xrightarrow{\frac{V_o(s)}{V_{in}(s)}} = \frac{1}{SCR}$$

$$S = j\omega$$


Voltage gain in Laplace domain.

$$A_V = \frac{V_o(j\omega)}{V_{in}(j\omega)} = \frac{1}{j\omega CR}$$


$$|A_v| = \frac{1}{wCR} = \frac{1}{2\pi f RC}$$

$f_a \rightarrow$  the frequency at which voltage gain is '1'.
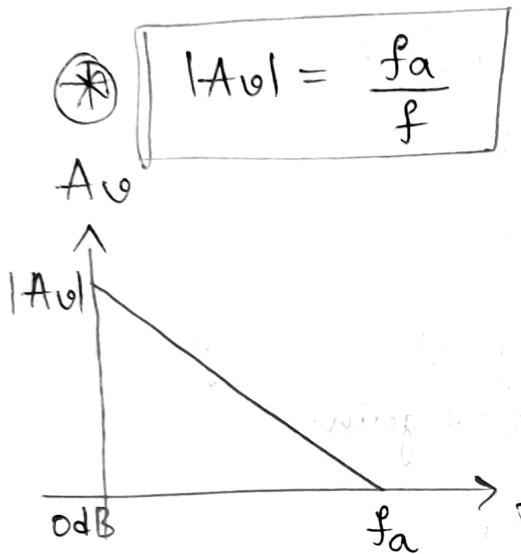
$$1 = \frac{1}{2\pi f_a RC} \rightarrow f_a = \frac{1}{2\pi RC}$$



### • Practical Integrator circuit :

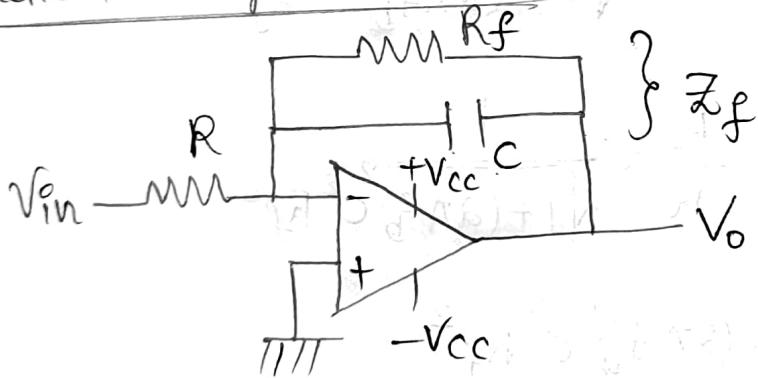

$$Z_f = R_f \parallel \frac{1}{SC}$$

$$Z_I = R$$

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{Z_f}{Z_I} = -\frac{R_f \parallel \frac{1}{SC}}{R} = -\left[ \frac{\frac{R_f}{SC}}{R + \frac{1}{SC}} \right]$$

$$|A_v(s)| = \frac{-R_f}{(1+SCR_f)R}$$

R

$$S = j\omega$$

$$A_V(j\omega) = -\frac{R_f}{R} \left( \frac{1}{1 + j\omega C R_f} \right)$$

$$|A_V| = \frac{R_f}{R} \times \frac{1}{\sqrt{1 + \omega^2 C^2 R_f^2}}$$

$$|A_V|_{\max} = \frac{R_f}{R}$$

$f_b \Rightarrow$  It is the frequency at which gain is  $\frac{1}{\sqrt{2}}$  times the max. gain.


$$|A_V| = \frac{R_f}{R} \times \frac{1}{\sqrt{1 + (2\pi f_b)^2 C^2 R_f^2}}$$

$$\frac{1}{\sqrt{2}} \times \frac{R_f}{R} = \frac{R_f}{R} \times \frac{1}{\sqrt{1 + (2\pi f_b)^2 C^2 R_f^2}}$$


$$2 = 1 + (2\pi f_b)^2 C^2 R_f^2$$

$$(2\pi f_b)^2 C^2 R_f^2 = 1$$

$$f_b = \frac{1}{2\pi R_f C}$$

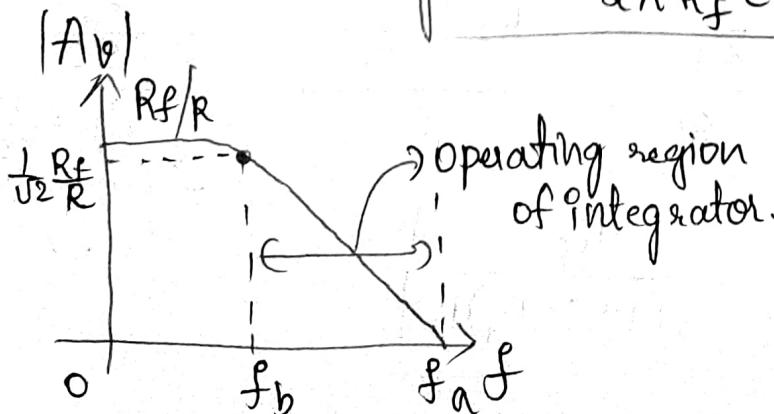

## Subtractor or Difference Amplifier:

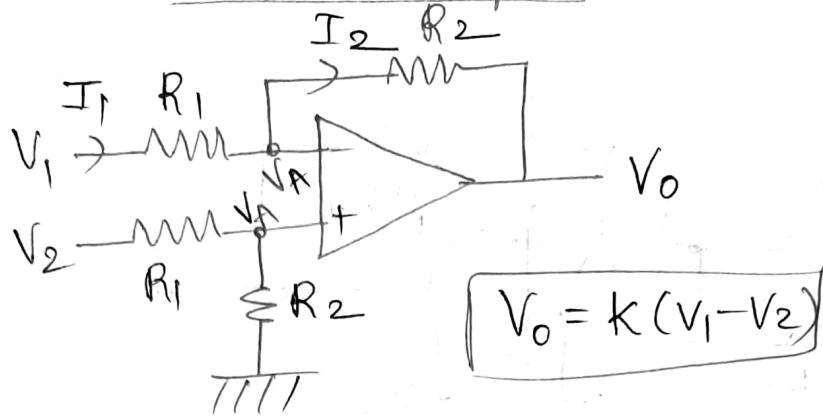

$$V_A = \frac{V_2}{R_1 + R_2} \times R_2 \quad \text{--- (1)}$$

Applying KCL,


$$\boxed{I_1 = I_2}$$

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_2}$$

$$\frac{V_1}{R_1} - \frac{1}{R_1} \left( \frac{V_2 R_2}{R_1 + R_2} \right) = \frac{\cancel{V_2 R_2}}{(R_1 + R_2) \cancel{R_2}} - \frac{V_0}{R_2}$$

$$\boxed{V_0 = -\frac{R_2}{R_1}(V_1 - V_2)}$$

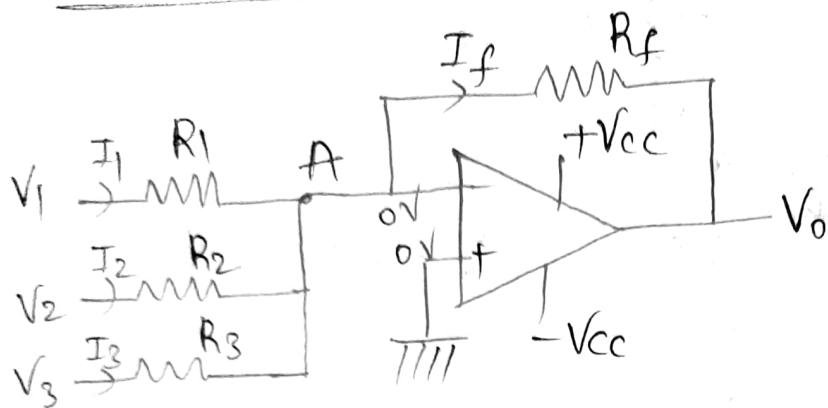• Summer circuit using Inverting OPAMP amplifier:



At Node A,

$$I_1 + I_2 + I_3 = I_f$$


$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{0 - V_o}{R_f}$$

$$V_o = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

If  $R_f = R_1 = R_2 = R_3$ , then

$$V_o = -(V_1 + V_2 + V_3)$$
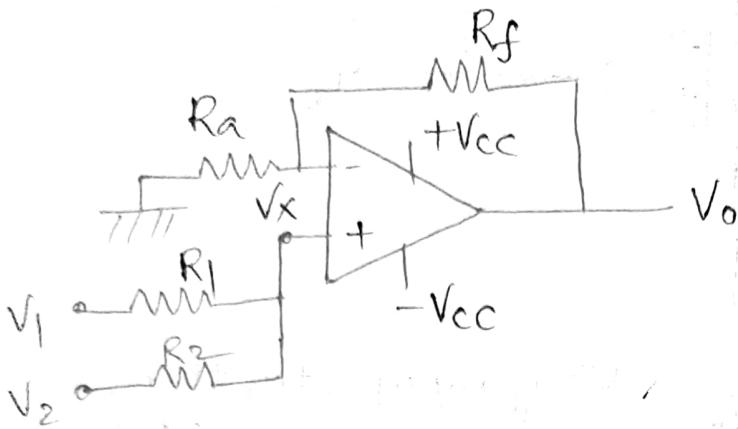
# Summing circuit using Non-inverting OP-AMP amplifier



Using superposition theorem,

case-①: Apply only  $V_1$ , deactivating  $V_2$ .

$$V_{X1} = \frac{V_1}{R_1 + R_2} \times R_2$$

case-②: Apply only  $V_2$ , deactivating  $V_1$ .

$$V_{X2} = \frac{V_2}{R_1 + R_2} \times R_1$$

$$\begin{aligned} V_X &= V_{X1} + V_{X2} \\ &= \frac{V_1 R_2}{R_1 + R_2} + \frac{V_2 R_1}{R_1 + R_2} \end{aligned}$$

$$V_X = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$

if  $R_1 = R_2 = R$

then,

$$V_O = \left(1 + \frac{R_f}{R_a}\right) \left(\frac{V_1 + V_2}{2}\right)$$

$$V_O = \left(1 + \frac{R_f}{R_a}\right) \left(\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}\right)$$


gain of  
non-inverting  
amplifier

input  
Voltage

→ if  $R_f = R_a$  &  $R_1 = R_2 = R$

then,

$$V_O = V_1 + V_2$$

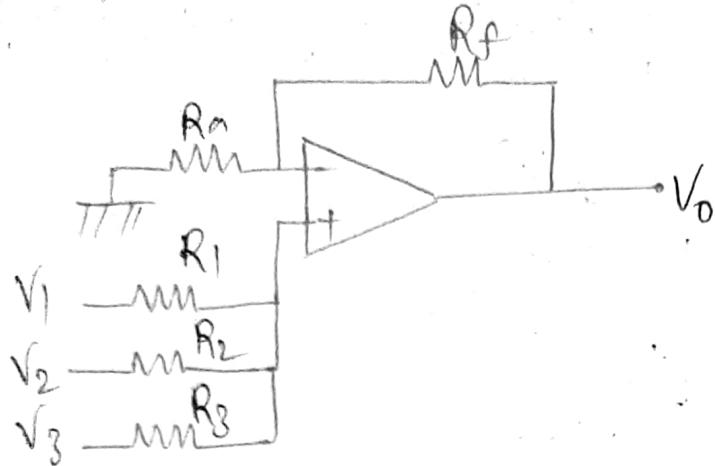

Using superposition theorem,

$$V_{X_1} = \frac{V_1 \times \left( \frac{R_2 R_3}{R_2 + R_3} \right)}{R_1 + \left( \frac{R_2 R_3}{R_2 + R_3} \right)}$$

$$V_{X_2} = \frac{V_2 \times \left( \frac{R_1 R_3}{R_1 + R_3} \right)}{R_2 + \left( \frac{R_1 R_3}{R_1 + R_3} \right)}$$

$$V_{X_3} = \frac{V_3 \times \left( \frac{R_1 R_2}{R_1 + R_2} \right)}{R_3 + \left( \frac{R_1 R_2}{R_1 + R_2} \right)}$$

$$V_x = V_{X_1} + V_{X_2} + V_{X_3}$$


$$V_x = \frac{V_1 R_2 R_3 + V_2 R_1 R_3 + V_3 R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

if  $R_1 = R_2 = R_3 = R$

$$V_x = \frac{V_1 + V_2 + V_3}{3}$$

$$V_0 = \left( 1 + \frac{R_f}{R_a} \right) V_x \Rightarrow V_0 = \left( 1 + \frac{R_f}{R_a} \right) \left( \frac{V_1 + V_2 + V_3}{3} \right)$$
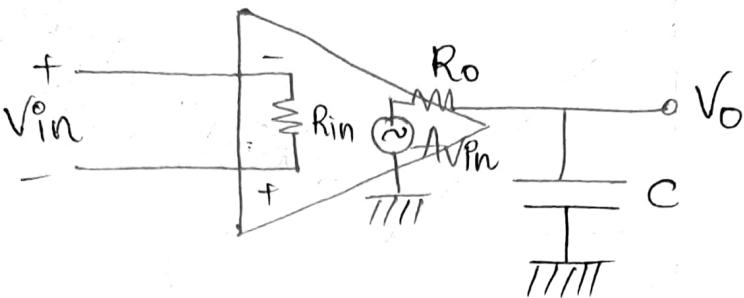
## High frequency OPA/NP equivalent Circuit:



A - voltage gain at zero frequency.

$$V_o(s) = \frac{AV_{in}(s) \times \frac{1}{SC}}{R_o + \frac{1}{SC}}$$

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{A}{1 + SCR_o}$$

(Gain in dB  
=  $20 \log |A_{OL}(f)|$ )

$$s = j\omega$$

$$A_{OL}(f) = \frac{A}{1 + j\omega CR_o} = \frac{A}{1 + j(2\pi f)CR_o}$$

Open loop voltage gain.


$$|A_{OL}(f)| = \frac{A}{\sqrt{1 + (2\pi f CR_o)^2}}$$

→ if  $f = 0$  then  $|A_{OL}(f)|_{max} = A$

→ at  $f = f_1$  (frequency at which gain is  $\frac{f_2}{f_1}$  times the max gain)

$$f_1 = \frac{1}{2\pi CR_o}$$

Cut-off frequency | Break frequency.

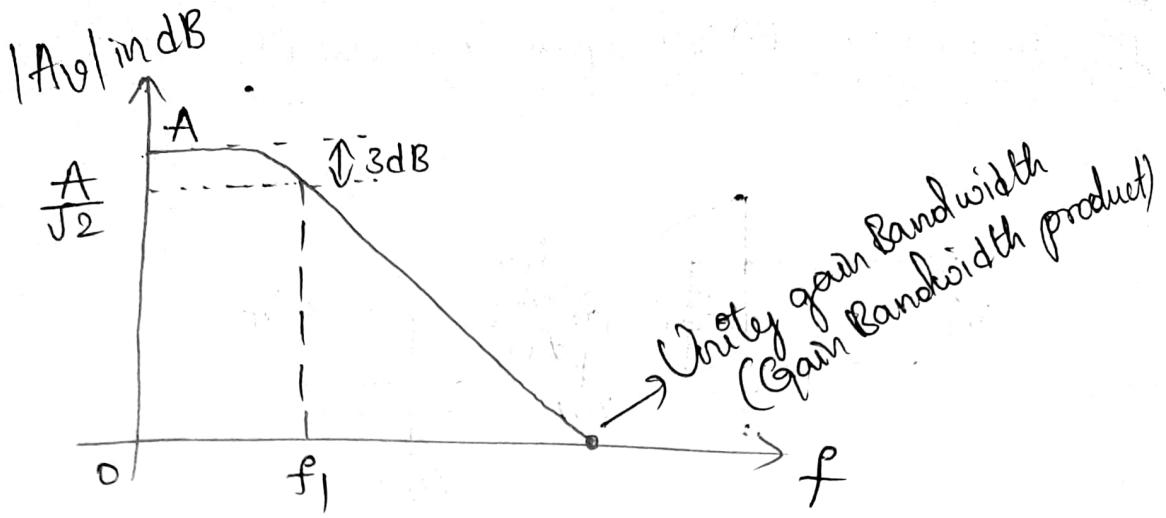

for IC741 OPAMP

→ Break frequency for IC741 OPAMP is 5Hz.

→ At unity gain Bandwidth (UGB)


$$|A_{OL}(f)| = 1$$

$$1 = \frac{A}{\sqrt{1 + \left(\frac{UGB}{f_1}\right)^2}}$$

$$1 = \frac{A}{\left(\frac{UGB}{f_1}\right)} \quad (\text{since } UGB \gg 1)$$

$$f_1 = \frac{UGB}{A} \quad \rightarrow \text{Break frequency.}$$

## Differentiator using OPAMP:

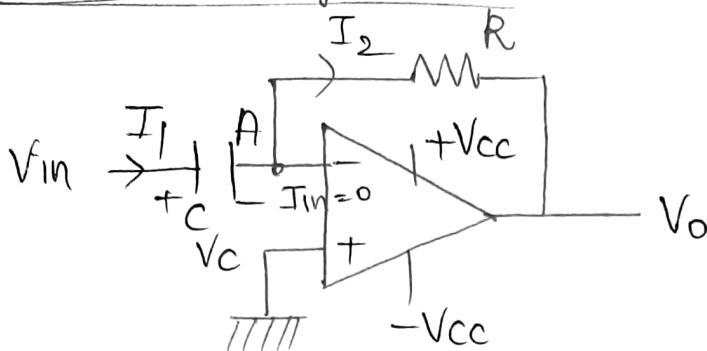

at Node A,

$$\boxed{I_1 = I_2}$$

$$Cd\frac{V_c}{dt} = \frac{0 - V_o}{R}$$

$$Cd\frac{(V_{in} - 0)}{dt} = -\frac{V_o}{R}$$

$$\boxed{V_o = -RC \frac{dV_{in}}{dt}}$$

Apply laplace transform,


$$V_o(s) = -RCs V_{in}(s)$$

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = -RCs = -j\omega RC$$


$$A_v(s) = -j(2\pi f) RC$$

$$\boxed{|A_v(s)| = 2\pi f RC}$$

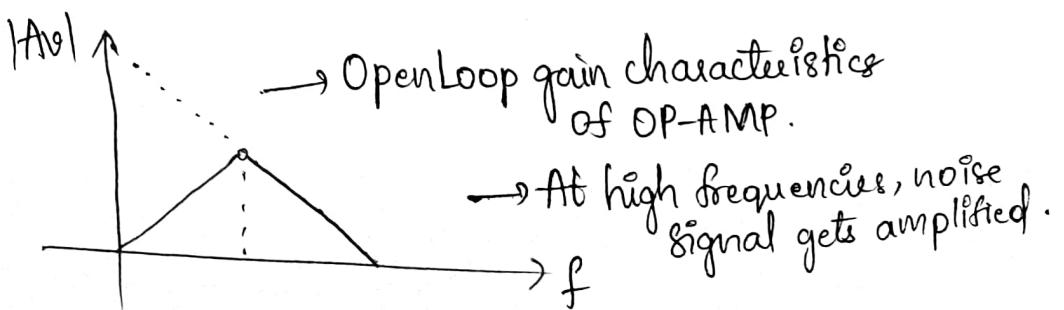→ This circuit cannot be used at low frequencies.



## Practical Differentiator using OPAMP

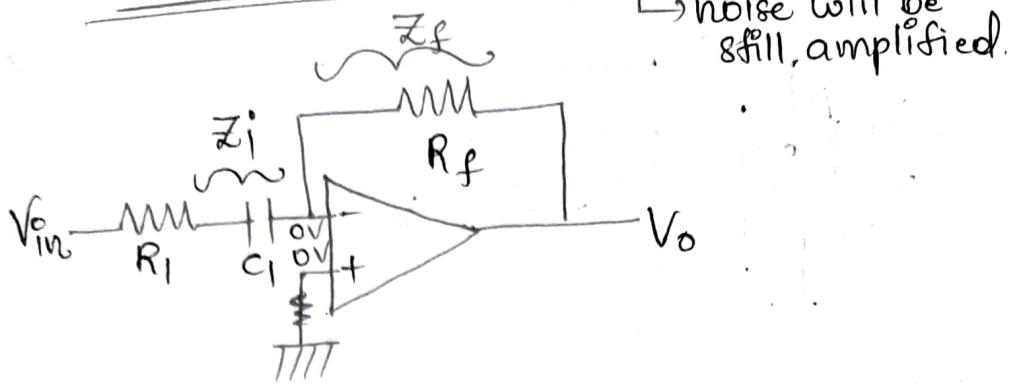

$$\frac{V_o(s)}{V_{in}(s)} = -\frac{Z_f}{Z_i} = \frac{-R_f}{R_1 + \frac{1}{SC_1}}$$

$$V_o(s) = -\frac{V_{in}(s) \times R_f}{R_1 + \frac{1}{SC_1}}$$

$$V_o(s) = \frac{-V_{in}(s)}{\frac{R_1}{R_f} + \frac{1}{SC_1 R_f}}$$

if  $R_1 \ll R_f$ ,  $\frac{R_1}{R_f} \ll 1$ , so,  $\rightarrow V_o(s) = -\frac{V_{in}(s)}{\frac{1}{SC_1 R_f}}$

$$V_o(s) = -SC_1 R_f V_{in}(s)$$


$$V_o(t) \approx -R_f C_1 \frac{dV_{in}}{dt}$$

frequency response,

$$A_{v(s)} = \frac{V_o(s)}{V_{in}(s)} = \frac{-R_f}{R_1 + \frac{1}{SC_1}} = \frac{-R_f SC_1}{1 + j\omega R_1 C_1} = \frac{-R_f j\omega C_1}{1 + j\omega R_1 C_1}$$

$$|A_v| = \frac{R_f 2\pi f C_1}{\sqrt{1 + \omega^2 R_1^2 C_1^2}}$$

$f_1 \rightarrow$  cut-off frequency.

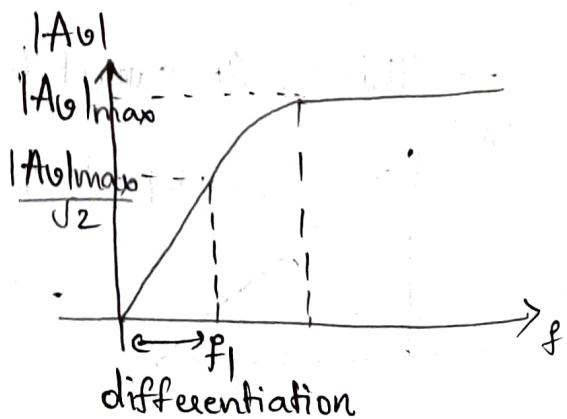

$$\frac{R_f}{R_1} \times \frac{1}{\sqrt{2}} = \frac{R_f(2\pi f_1)C_1}{\sqrt{1 + (2\pi f_1)^2 R_1^2 C_1^2}}$$


$$1 + 4\pi^2 f_1^2 R_1^2 C_1^2 = 4\pi^2 f_1^2 R_1^2 C_1^2 \times 2$$

$$1 = 4\pi^2 f_1^2 R_1^2 C_1^2$$

$$f_1 = \frac{1}{2\pi f_1 C_1 R_1}$$

frequency at which gain is  $\frac{1}{\sqrt{2}}$  times max gain.
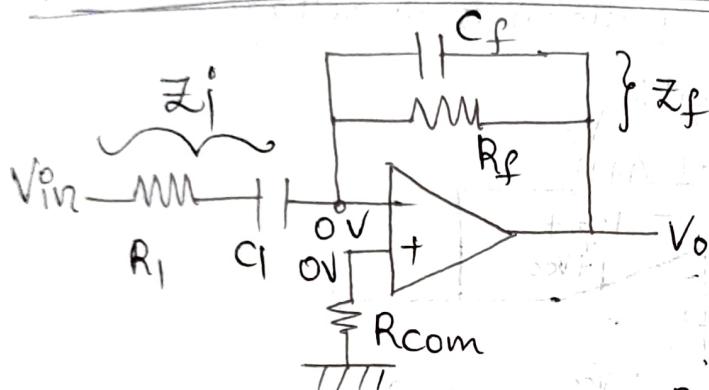
### Improved practical Differentiator using OPAMP:




$$\frac{V_o(s)}{V_{in}(s)} = -\frac{Z_f}{Z_i} = \frac{\frac{1}{SC_f} || R_f}{R_1 + \frac{1}{SC_1}} = \frac{\frac{R_f \times 1}{SC_f}}{R_1 + \frac{1}{SC_1}}$$

$$A_{10}(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{\frac{R_f}{SC_f} \times \frac{SC_f}{1 + R_f C_f s}}{1 + R_1 C_1 s}$$

$$A_{10}(s) = \frac{SR_f C_1}{(1 + SC_f R_f)(1 + SC_1 R_1)}$$

having two poles,
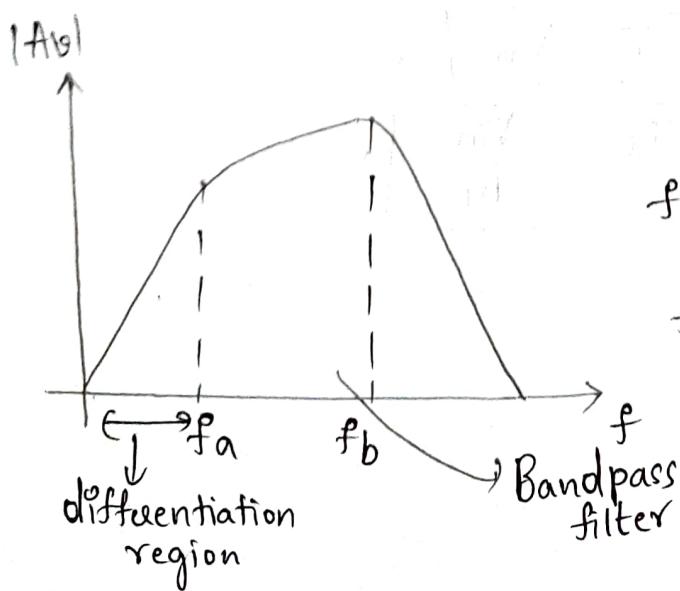
$$\left\{ \begin{array}{l} s_1 = -\frac{1}{C_f R_f} \\ s_2 = -\frac{1}{C_1 R_1} \end{array} \right\}$$



$$f_a = \frac{1}{2\pi R_1 C_1}$$

$$f_b = \frac{1}{2\pi R_f C_f}$$

when  $P_a = f_b$ ,


$$\frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi R_f C_f} \Rightarrow R_1 C_1 = R_f C_f$$

$$|A_{v(j\omega)}| = \frac{\omega R_1 C_1}{\sqrt{(1 + (\omega C_f R_f)^2) \times (1 + (\omega C_1 R_1)^2)}}$$

### Voltage to current converter:

L, produces o/p current which is proportional to i/p voltage.

#### ① With floating load :

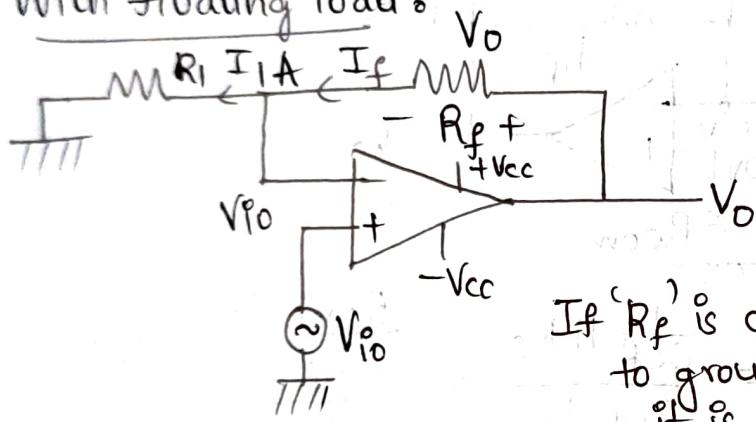

If  $R_f$  is connected to ground then it is non-floating load.

#### At node A, (KCL) :

$$I_1 = I_f$$


$$\frac{V_{in}^o - 0}{R_i} = \frac{V_o - V_{in}^o}{R_f} = I_f$$

$$I_f \propto V_{in}^o$$

$$I_f = \frac{V_{in}^o}{R_i}$$

## Voltage to current converter:

### ② With grounded load

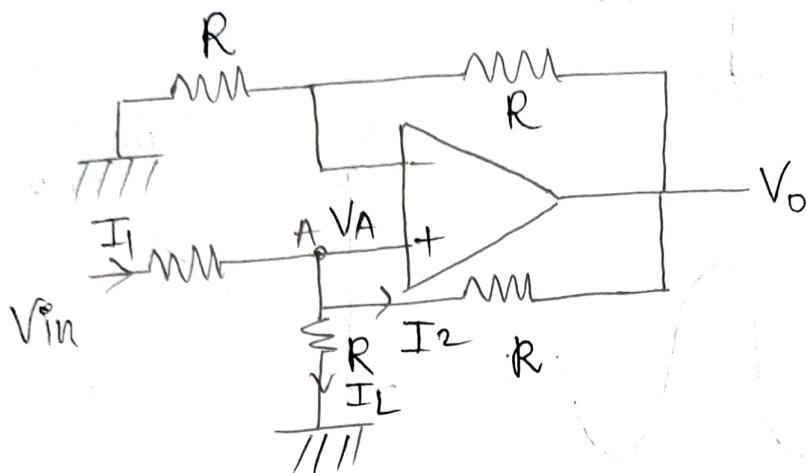

Apply KCL at node A,

$$I_1 = I_2 + I_L$$

$$\frac{V_{in} - V_A}{R} = \frac{V_A - V_0}{R} + I_L$$

$$I_L = \frac{V_{in} - 2V_A + V_0}{R} \quad \text{--- (1)}$$

Since, it is non-inverting amplifier, Gain is  $1 + \frac{R_f}{R_a}$






$$\frac{V_0}{V_A} = 1 + \frac{R_f}{R_a} = 2$$

$$V_0 = 2V_A \quad \text{--- (2)}$$




from (1) & (2),

$$I_L = \frac{V_{in}}{R}$$

## • Half-wave rectifier:

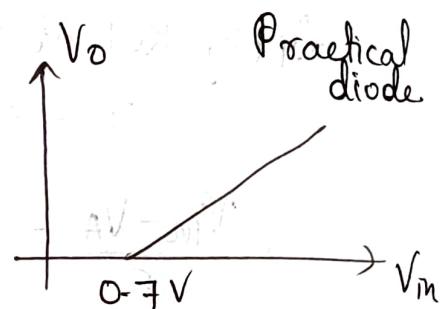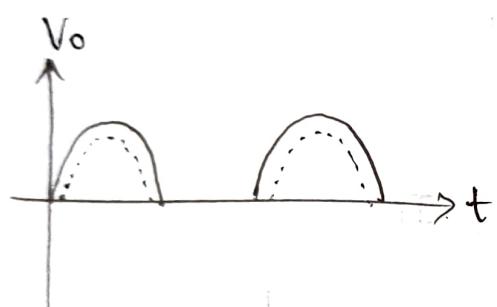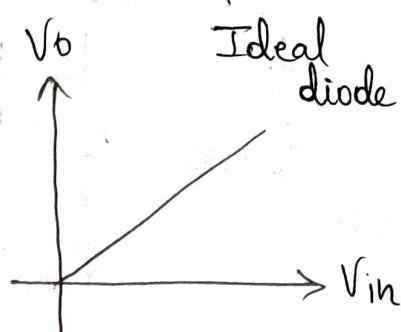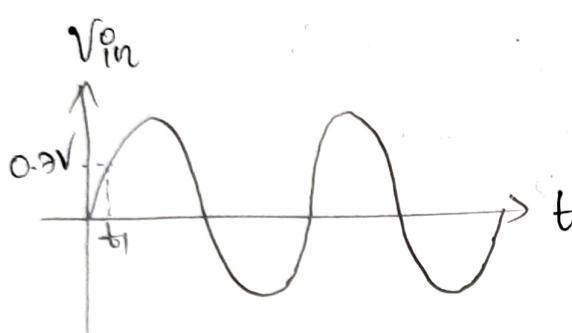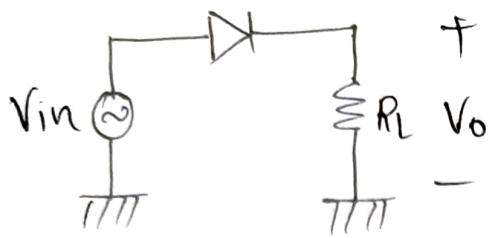


## • Half-wave precision rectifier:

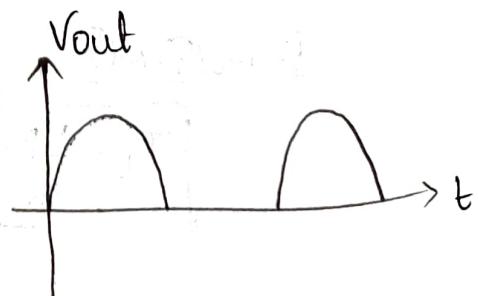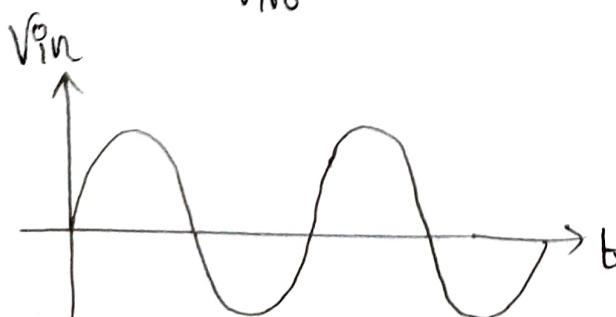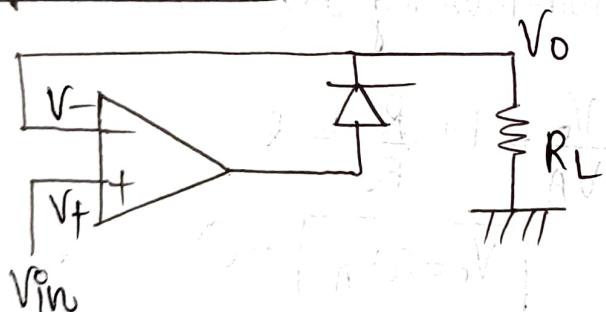

Whenever  $V_{in}$  is '+ve' and  $V_o > 0.7V$  then diode conducts and is forward biased.

Whenever  $V_{in}$  is '-ve' then diode is Reverse Biased.

## • Full wave precision Rectifier:

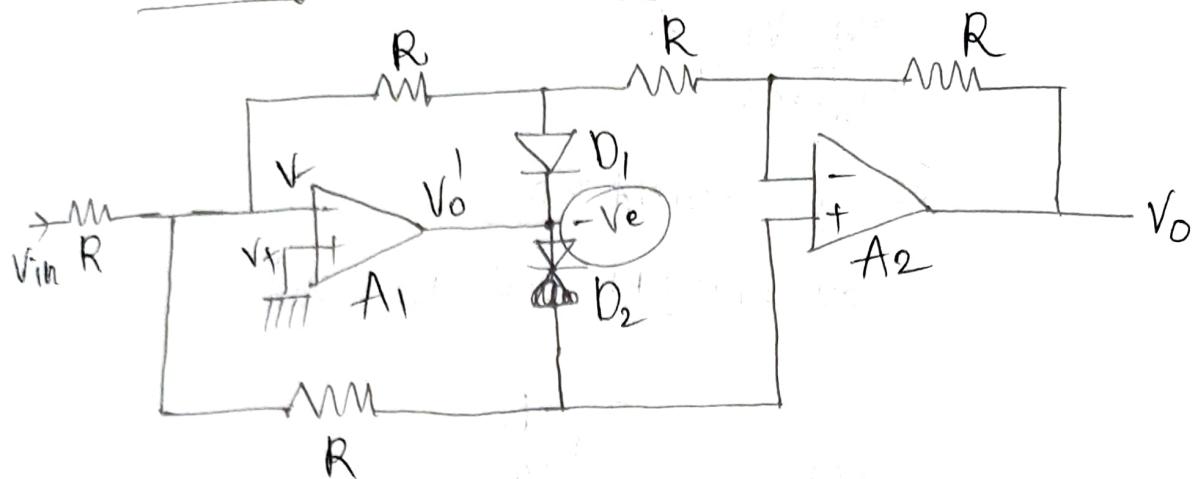


Whenever  $V_{in}$  is '+ve'

$$V_d = V_+ - V_-$$

$$V_d < 0$$

$$V_0' = A_d V_d < 0$$

So,  $D_1$  is ON and  $D_2$  is OFF

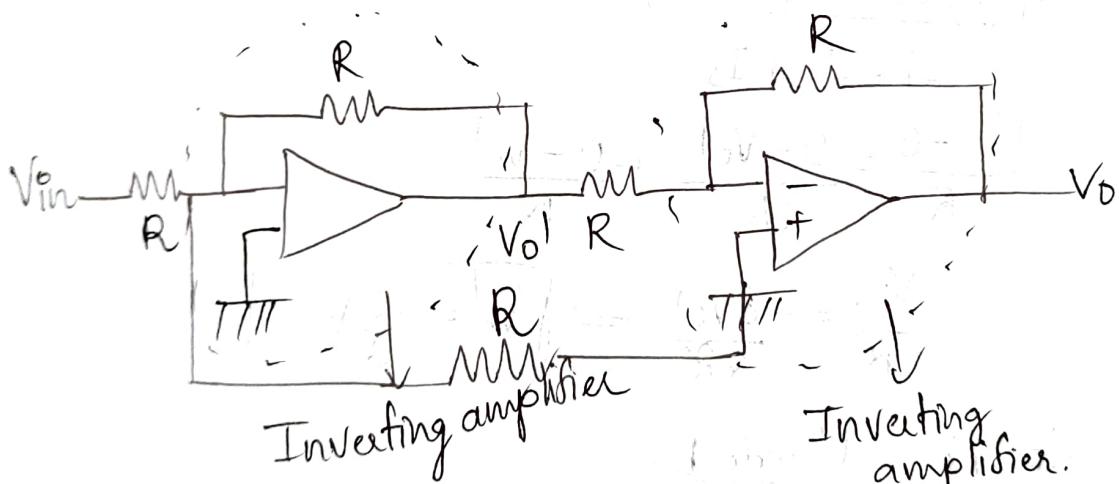

Inverting amplifier

Inverting amplifier.

$$\frac{V_0'}{V_{in}} = -\frac{R_f}{R_i} = -\frac{R}{R} = -1$$

$$V_0' = -V_{in}$$

$$\frac{V_0}{V_0'} = -\frac{R}{R} = -1$$

$$V_0 = -V_0' = V_{in}$$


Whenever,  $V_{in}$  is '-ve',

$$V_d = V_+ - V_-$$

$$\boxed{V_d \geq 0V}$$

$$\text{So, } V_o^1 = A_d V_d > 0$$

So,  $D_1$  is OFF and  $D_2$  is ON

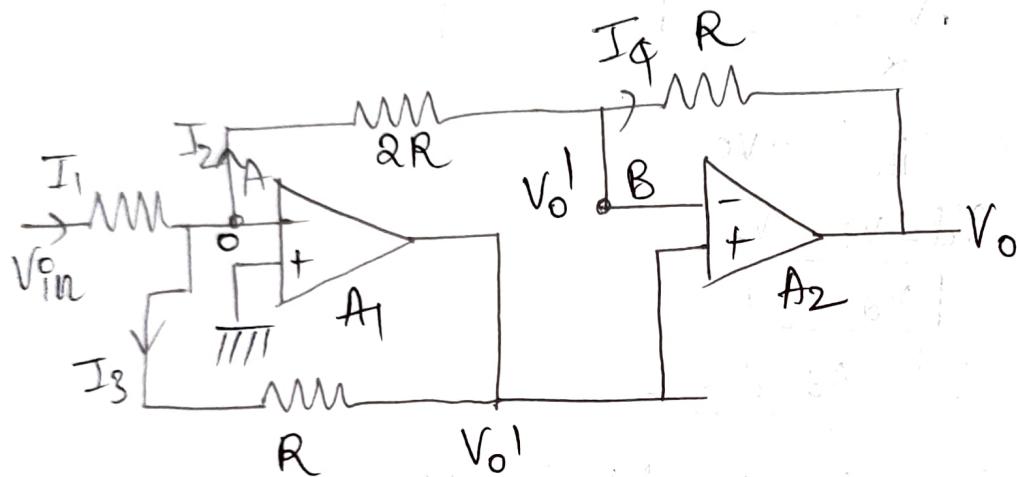

Apply KCL at Node A,

$$I_1 = I_2 + I_3$$

$$\frac{V_{in} - 0}{R} = \frac{0 - V_o^1}{2R} + \frac{0 - V_o}{R}$$

$$\frac{V_{in}}{R} = -\frac{3V_o}{2R} \Rightarrow \boxed{V_o^1 = -\frac{2}{3}V_{in}}$$

Apply KCL at node B,


$$I_2 = I_q$$

$$\frac{0 - V_o^1}{2R} = \frac{V_o^1 - V_o}{R}$$


$$3V_o^1 = 2V_o$$

$$V_o = \frac{3V_o^1}{2} \rightarrow V_o = \frac{3}{2} \left( -\frac{2}{3} V_{in} \right)$$

$$\boxed{V_o = -V_{in}}$$

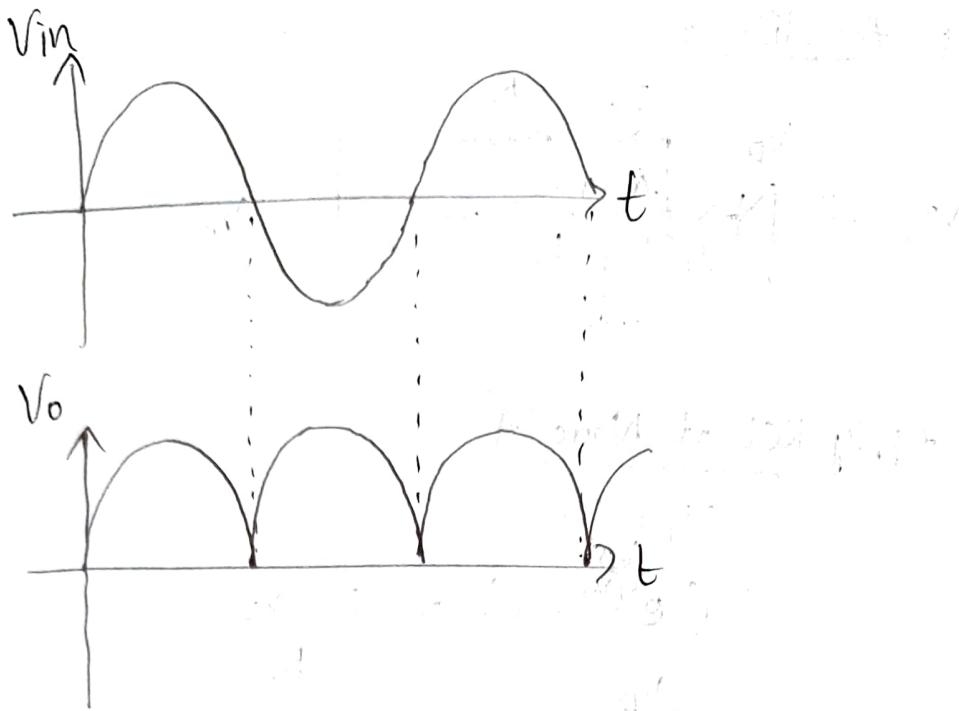

### • Logarithmic Amplifier using OPAMP:

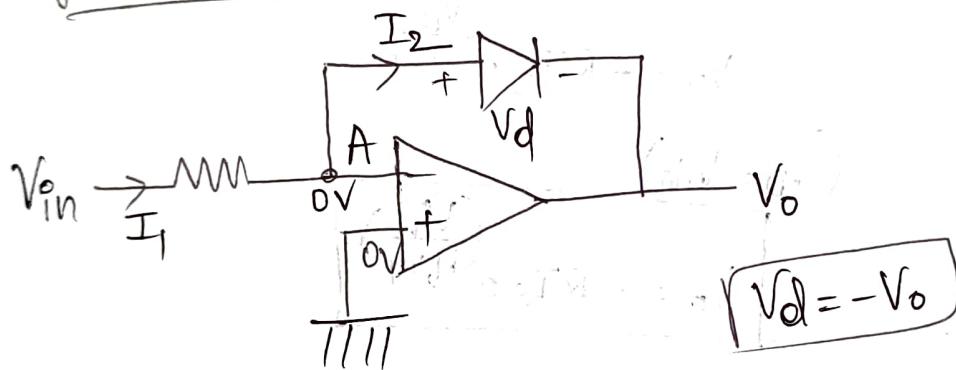

Apply KCL at node A,


$$\frac{V_{in} - 0}{R} = I_2 = I_s \left( e^{\frac{V_d}{nV_T}} - 1 \right)$$

$$\frac{V_{in}}{R} \approx I_s \cdot e^{\frac{V_o}{nV_T}}$$

$$\ln\left(\frac{V_{in}}{I_s R}\right) = -\frac{V_o}{nV_T}$$

$$V_o = -nV_T \ln\left(\frac{V_{in}}{I_s R}\right)$$

## • Antilog Amplifier:

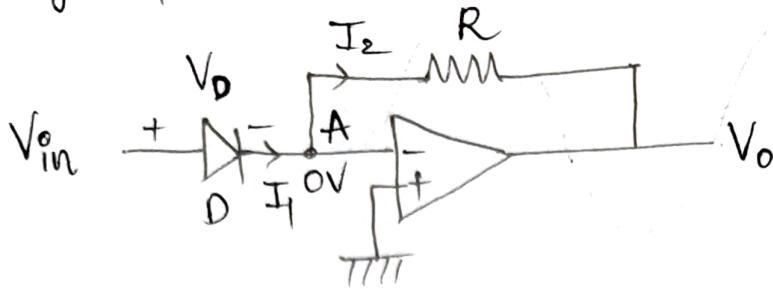


Apply KCL at Node 'A'.

$$\begin{aligned} I_1 &= I_2 \\ I_s(e^{\frac{V_D}{nV_T}} - 1) &= \frac{0 - V_o}{R} \\ I_s e^{\frac{V_D}{nV_T}} &\approx -\frac{V_o}{R} \\ V_o &= -R I_s e^{\frac{V_D}{nV_T}} \end{aligned}$$

$(V_D = V_{in})$

$$V_o = -R I_s e^{\left(\frac{V_{in}}{nV_T}\right)}$$

## • Logarithmic Amplifier using BJT:

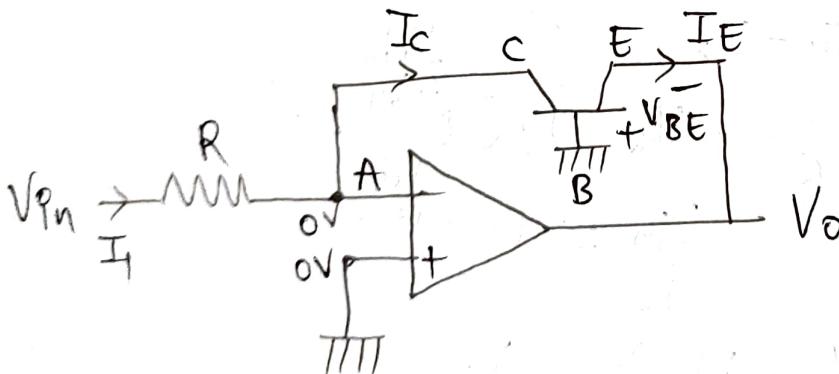

$$-V_{BE} \approx V_o$$

$$I_c \approx I_E$$

$$I_E \approx I_s(e^{\frac{V_{BE}}{V_T}})$$

Apply KCL at node A

$$I_I = I_E$$

$$\frac{V_{in} - 0}{R} = I_S e^{\frac{V_{BE}}{V_T}}$$


$$\frac{V_{in}}{R} = I_S e^{\frac{-V_O}{V_T}}$$

$$\frac{V_{in}}{I_S R} = e^{\frac{-V_O}{V_T}}$$

$$V_O = -V_T \ln \left( \frac{V_{in}}{I_S R} \right)$$

~~Use open loop~~

### Anti-log Amplifier using BJT

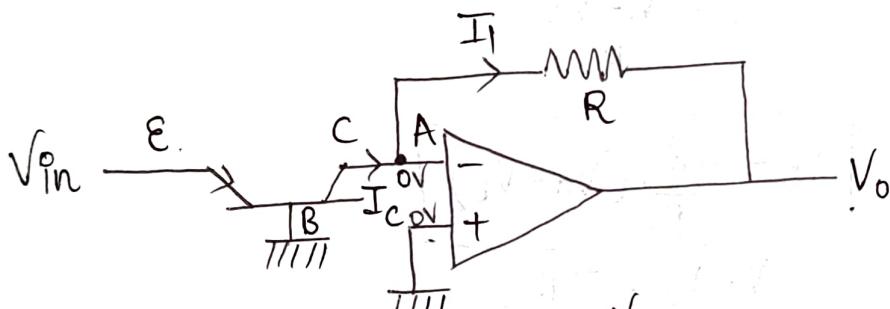

$$I_C \approx I_E \approx I_S e^{\frac{V_{EB}}{V_T}}$$


$$I_C \approx I_S e^{\frac{V_{in}}{V_T}}$$

Apply KCL at Node A,

$$I_C = I_I$$

$$I_S e^{\frac{V_{in}}{V_T}} = 0 - V_O$$

$$V_O = -R I_S e^{\frac{V_{in}}{V_T}}$$

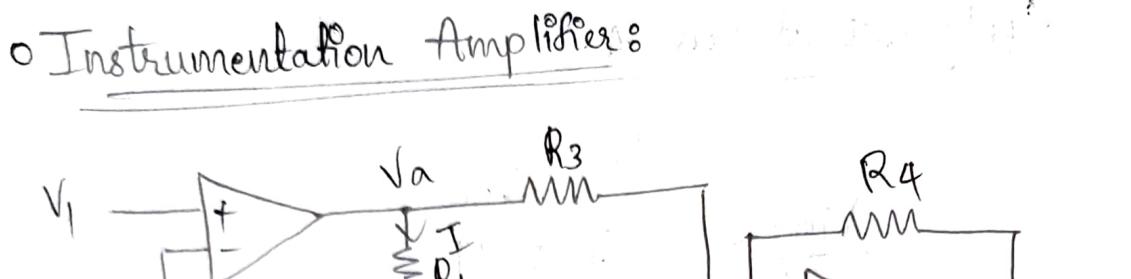

$$I = \frac{V_a - V_b}{2R_1 + R_2}$$

$$I = \frac{V_1 - V_2}{R_2}$$

$$V_0 = -\frac{R_4}{R_3}(V_a - V_b)$$

$$V_1 - V_2 = IR_2$$


$$V_1 - V_2 = \frac{(V_a - V_b)R_2}{2R_1 + R_2}$$

$$V_a - V_b = \frac{(V_1 - V_2)(2R_1 + R_2)}{R_2}$$

$$V_0 = \frac{(2R_1 + R_2)R_4}{R_2 R_3} (V_2 - V_1)$$

$$V_0 = \frac{R_4}{R_3} \left( 1 + \frac{2R_1}{R_2} \right) (V_2 - V_1)$$
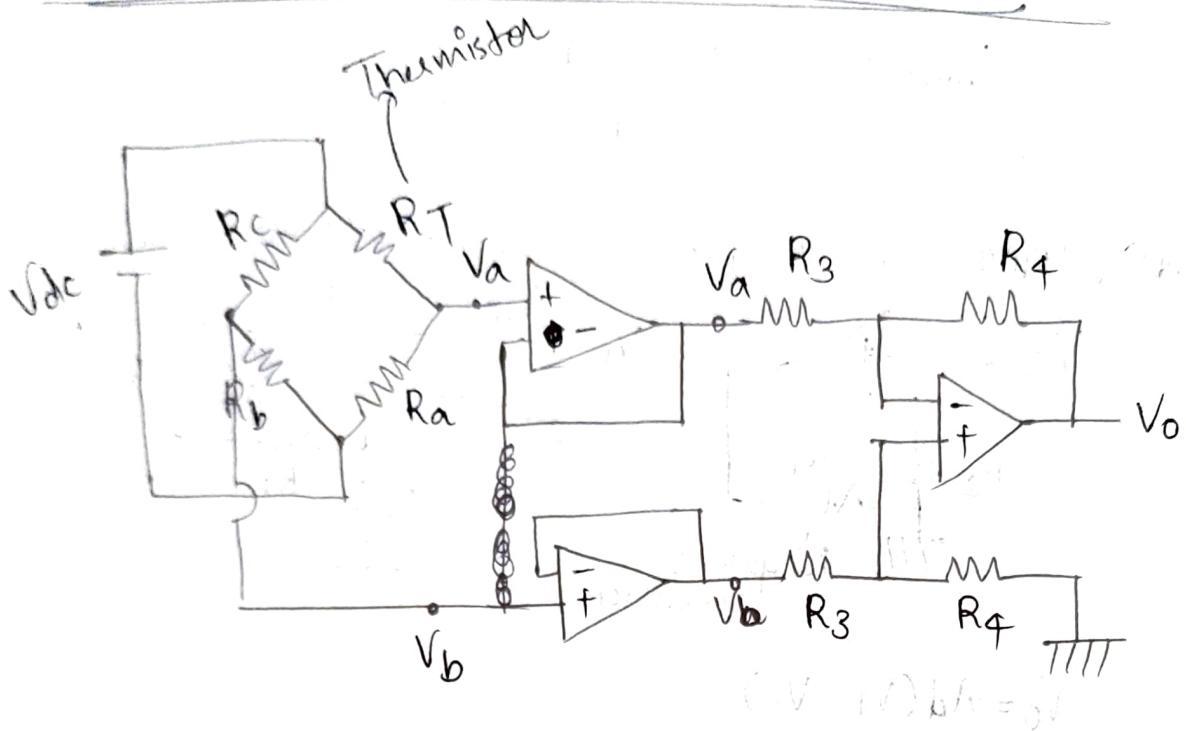
# • Instrumentation Amplifier with Resistive Transducer bridge :



① Initially bridge is balanced for some value of  $R_T$

$$V_a = V_b$$

$$V_a = \frac{V_{dc}}{R_T + R_a} \times R_a$$

$$V_b = \frac{V_{dc}}{R_b + R_c} \times R_b$$

$$\text{since } V_a = V_b \quad (V_o = V_a - V_b = 0V)$$

② If bridge is not balanced,

$$V_a = \frac{V_{dc} \times R_a}{R_T \pm \Delta R + R_a}$$

Assuming

$$V_b = \frac{V_{dc} \times R_b}{R_c + R_b}$$

$$\Rightarrow R_a = R_b = R_c = R_T = R$$


$$V_o = V_a - V_b = \frac{V_{dc} \times R}{2R} - \frac{V_{dc} \times R}{2R \pm \Delta R} = \frac{\pm V_{dc} \Delta R}{4R \pm 2\Delta R}$$

$$(4R \gg \Delta R) \quad \boxed{V_o = \frac{\pm V_{dc} \Delta R}{4R}}$$

$$V_{out} = \frac{R_4}{R_3} (V_b - V_a)$$

$$\boxed{V_{out} = \frac{R_4}{R_3} \left[ \frac{\pm V_{dc} \Delta R}{4R} \right]}$$

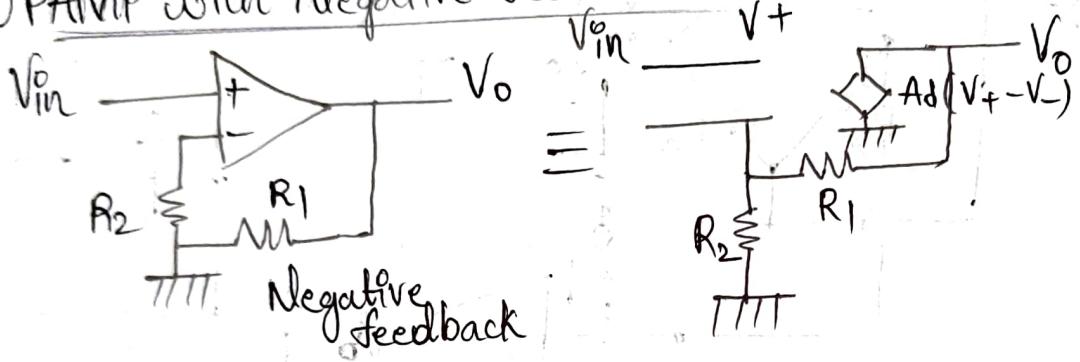\* O PAMP with Negative feedback: (stable circuit)



$$V_o = Ad(V_+ - V_-)$$

$$V_+ = V_{in}$$

$$V_- = \frac{V_o \times R_2}{R_1 + R_2}$$

$$V_o = Ad \left( V_{in} - \frac{V_o R_2}{R_1 + R_2} \right)$$

$$V_o \left[ 1 + \frac{R_2 Ad}{R_1 + R_2} \right] = Ad \times V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{Ad}{1 + R_2 Ad} \underset{R_1 + R_2}{\approx} \frac{Ad}{R_2 Ad} = \frac{1}{1 + \frac{R_1}{R_2}}$$


$$\boxed{\frac{V_o}{V_{in}} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}}$$

$$\rightarrow V_+ = V_- - \text{Virtual short circuit}$$


This concept is applicable only when,

(i) OPAMP is connected in negative feedback.

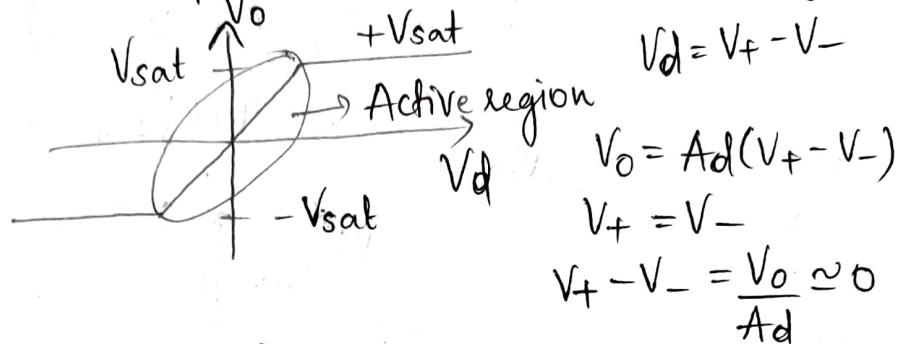(ii) OPAMP is operated in Active or linear region.



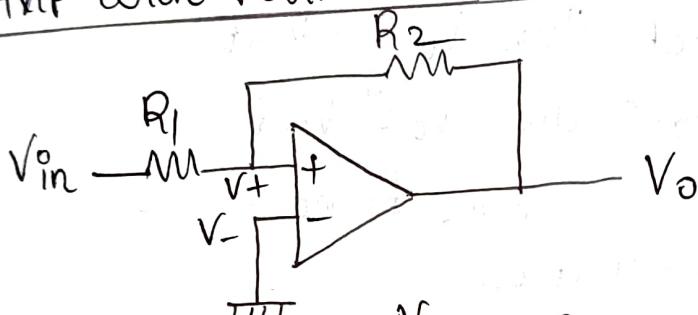
## OPAMP with Positive feedback: (Unstable circuit)



$$\frac{V_o}{V_{in}} = -\frac{R_2}{R_1}$$


→ Output ( $V_o$ ) is not stable, it gradually attains a large negative value.

## \* Inverting Comparator circuit:

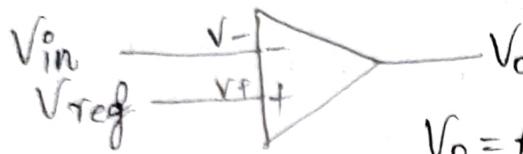

$$V_0 = A_d (V_+ - V_-)$$

$$V_0 = A_d (V_{ref} - V_{in})$$

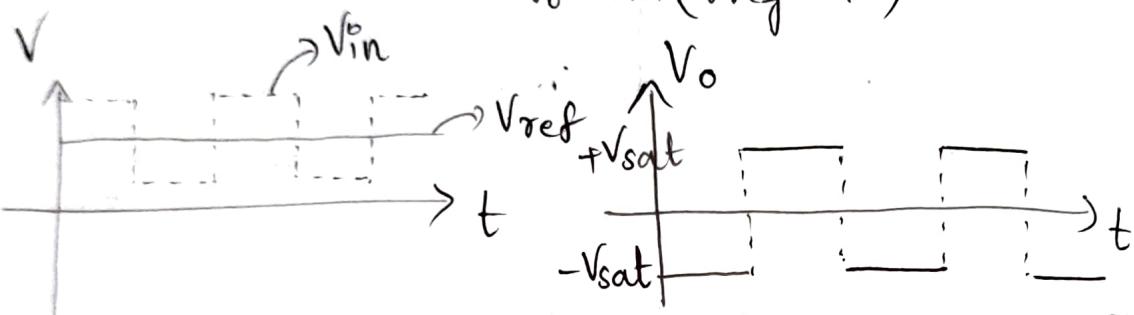


→ if  $V_{in} > V_{ref}$  then  $V_o \approx +V_{sat}$ .

→ if  $V_{in} < V_{ref}$  then  $V_o \approx -V_{sat}$ .

→ This circuit is immune to noise because output is not stable.

## \* Inverting Schmitt Trigger circuit:

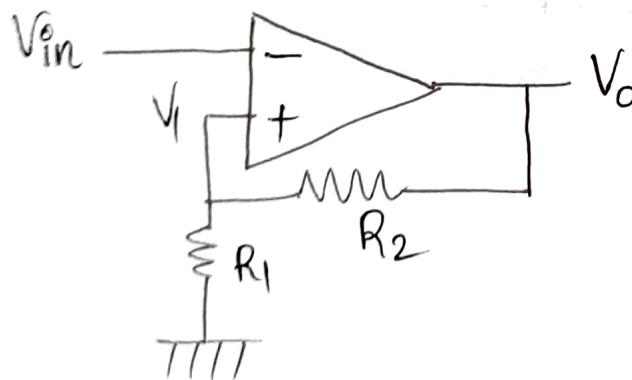

Assume that  $V_o = +V_{sat}$

$$V_d = V_+ - V_- = V_i - V_{in}$$

$$V_i = +\frac{V_{sat} \times R_1}{R_1 + R_2} = V_{UT} \rightarrow \text{Upper threshold Voltage.}$$


- ① If  $V_{in} > \text{Upper threshold Voltage } (V_{UT})$       Initial Voltage  
     then  $V_o = -V_{sat}$
- ② If  $V_{in} < V_{UT}$  then  $V_o = +V_{sat}$ .      + $V_{sat}$

Assume  $V_o = -V_{sat}$


$$V_1 = \frac{-V_{sat} \times R_1}{R_1 + R_2} = V_{LT} - \text{lower threshold Voltage.}$$

$$V_d = V_+ - V_- = V_{LT} - V_{in}$$

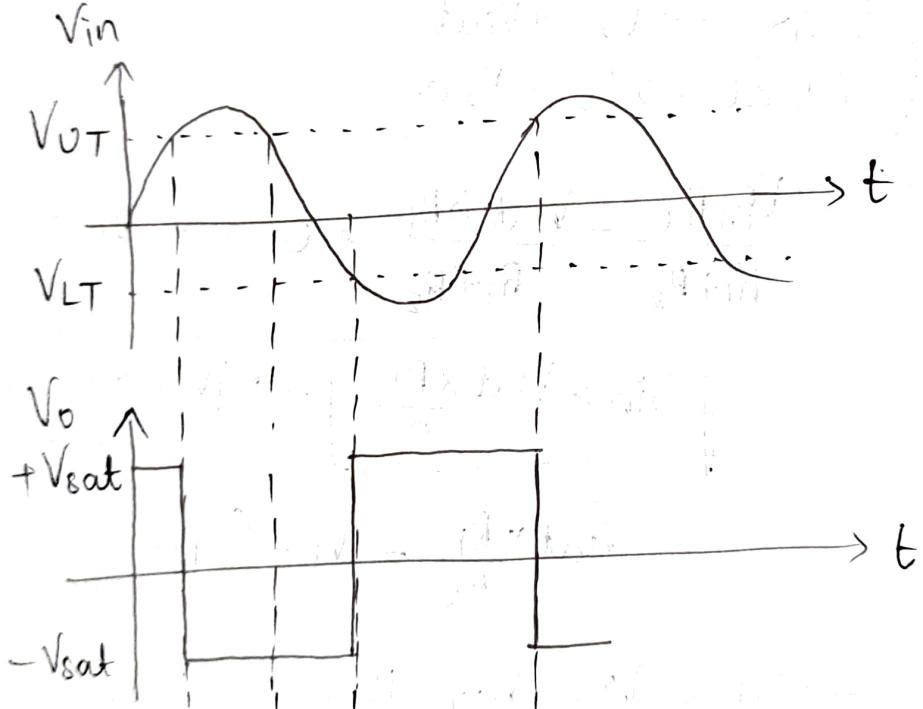
- ① If  $V_{in} > V_{LT}$ ,  $V_o = -V_{sat}$ .      Initial off voltage  
        - $V_{sat}$
- ② If  $V_{in} < V_{LT}$ ,  $V_o = +V_{sat}$ .


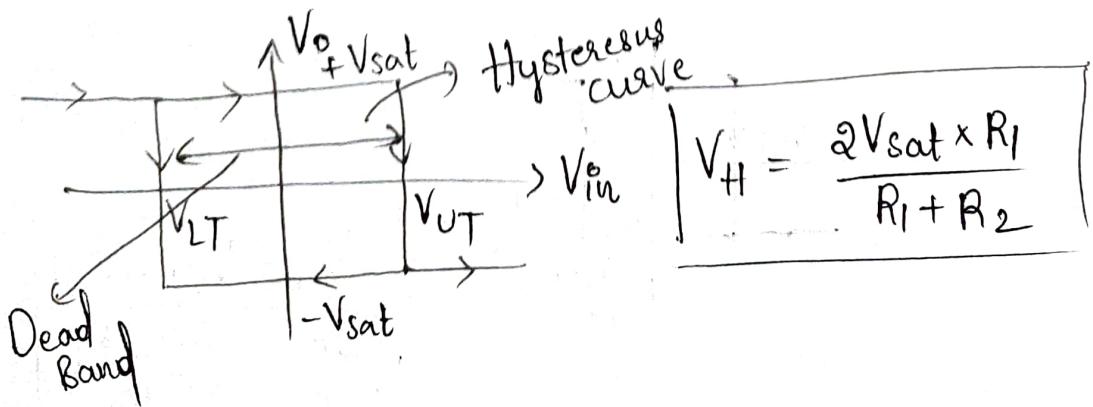
$$V_{UT} - V_{LT} = V_H \text{ (Hysteresis Voltage)}$$



# \* Non-inverting Schmitt Trigger :

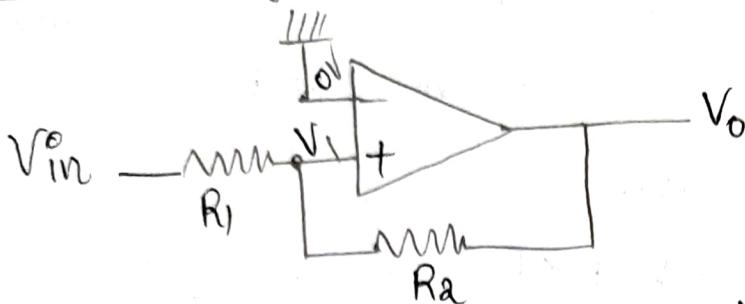

positive feedback → initial o/p voltage

① when,  $V_o = -V_{sat}$

$$V_1 = \frac{V_{in} \times R_2}{R_1 + R_2} + \frac{V_o \times R_1}{R_1 + R_2}$$

if  $V_1 > 0 \rightarrow V_o = +V_{sat}$

if  $V_1 < 0 \rightarrow V_o = -V_{sat}$


$$\frac{V_{in} R_2}{R_1 + R_2} - \frac{V_{sat} \times R_1}{R_1 + R_2} > 0 \rightarrow V_o = +V_{sat}$$

$$V_{in} > V_{sat} \times \frac{R_1}{R_2} \rightarrow V_{in} > V_{UT}$$

$$V_{sat} \times \frac{R_1}{R_2} = V_{UT} \text{ (Upper threshold voltage)}$$

→ When  $V_{in} > V_{UT}$  then  $V_o = +V_{sat}$

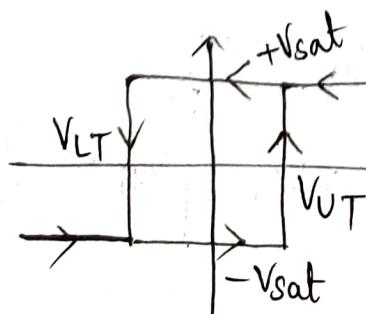→ When  $V_{in} < V_{UT}$  then  $V_o = -V_{sat}$



} Hysteresis curve  
(Transfer characteristic)

$$V_H = V_{UT} - V_{LT}$$

$$V_H = \frac{2V_{sat}R_1}{R_2}$$

② when,  $V_o = +V_{sat}$   $\rightarrow$  initial o/p voltage.

$$V_i = \frac{V_{in} R_2}{R_1 + R_2} + \frac{V_{sat} R_1}{R_1 + R_2}$$

If  $V_i > 0 \rightarrow V_o = +V_{sat}$

If  $V_i < 0 \rightarrow V_o = -V_{sat}$

$$\frac{V_{in} R_2}{R_1 + R_2} + \frac{V_{sat} R_1}{R_1 + R_2} > 0 \rightarrow V_o = +V_{sat}$$


$$V_{in} > -V_{sat} \times \frac{R_1}{R_2} \rightarrow V_o = +V_{sat}$$


$$\boxed{V_{in} > V_{LT}}$$

$$V_{LT} = -V_{sat} \times \frac{R_1}{R_2} \text{ (lower threshold voltage)}$$

$\rightarrow$  When,  $V_{in} > V_{LT} \rightarrow V_o = +V_{sat}$

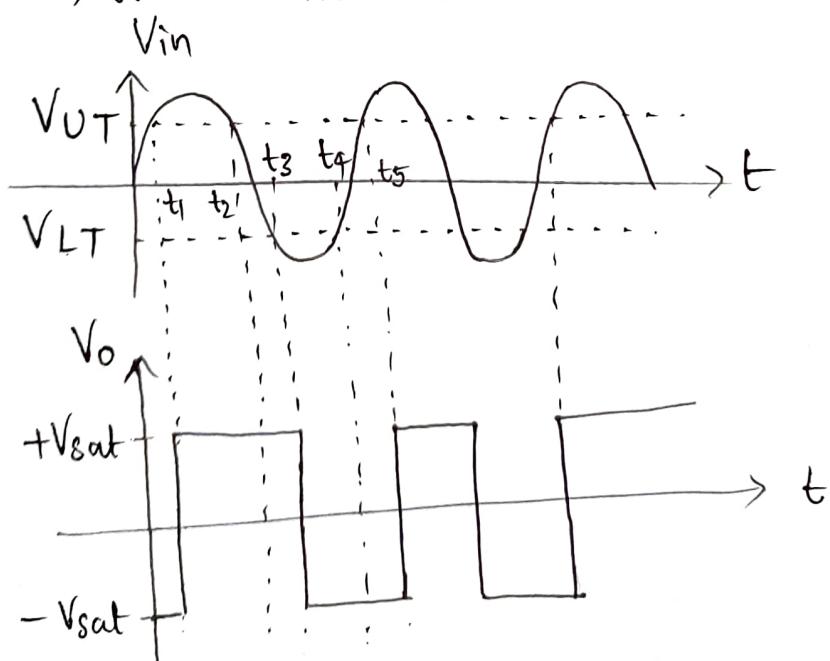$\rightarrow$  When  $V_{in} < V_{LT} \rightarrow V_o = -V_{sat}$



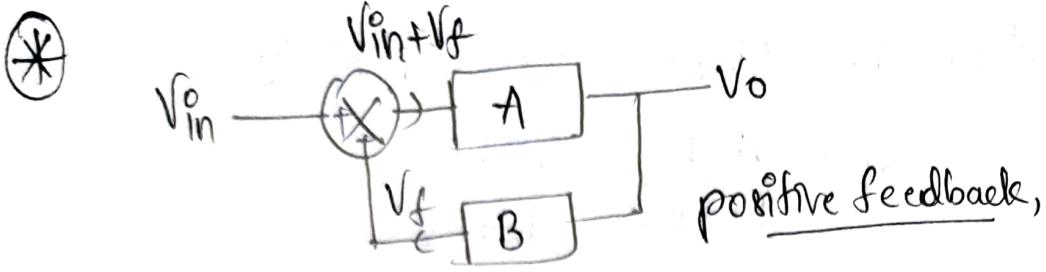

$$\frac{V_o}{V_{in}} = \frac{A}{1-AB}$$


AB-loop gain

$AB \rightarrow$  open loop gain


$$\rightarrow \text{If } AB=1 \text{ then } \frac{V_o}{V_{in}} = \frac{A}{0} = \infty$$

- Barkhausen criteria,

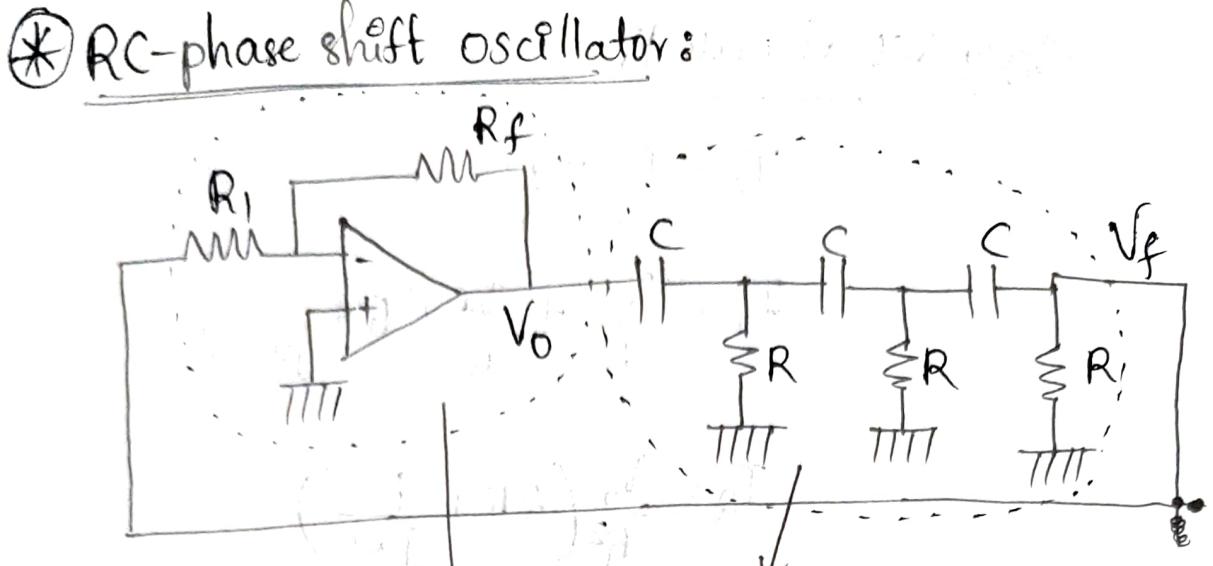- ① Circuit will produce sustained oscillations when two conditions are satisfied,
  - (i) loop gain  $AB=1$
  - (ii) Total phase shift around closed loop is  $0^\circ$  or integral multiples of  $2\pi$ .



Since it is inverting amplifier,

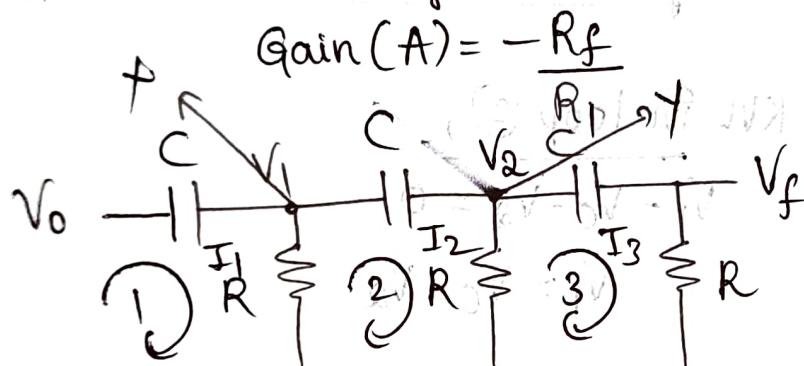

Apply KVL in loop ③,

$$V_2 - V_C - V_f = 0$$

$$V_2 = V_C + V_f$$

$$\text{But, } I_3 = \frac{V_f}{R}$$

$$V_2 = \frac{1}{j\omega C} \times \frac{V_f}{R} + V_f$$

$$V_2 = \frac{V_f}{R} \left( R + \frac{1}{j\omega C} \right)$$

Apply KCL at node Y,

$$I_2 = I_3 + \frac{V_2}{R}$$

$$I_2 = \frac{V_f}{R} + \frac{V_f}{R^2} \left( R + \frac{1}{j\omega C} \right)$$

$$I_2 = \frac{V_f}{R^2} \left( 2R + \frac{1}{j\omega C} \right)$$

$$\boxed{I_2 = \frac{V_f}{R} \left( 2 + \frac{1}{j\omega CR} \right)}$$

Apply KVL in loop ②,

$$V_i - V_C - V_2 = 0$$

$$V_i = V_C + V_2$$

$$V_i = V_f \left( 1 + \frac{1}{j\omega RC} \right) + I_2 \times \frac{1}{j\omega C}$$

$$V_i = V_f \left( 1 + \frac{1}{j\omega RC} \right) + \frac{V_f}{R} \left( 2 + \frac{1}{j\omega RC} \right) + \frac{1}{j\omega C}$$

$$V_i = V_f + \frac{3V_f}{j\omega RC} + \frac{V_f}{(j\omega RC)^2}$$

$$V_i = V_f + \frac{3V_f}{j\omega RC} - \frac{V_f}{\omega^2 R^2 C^2}$$

$$\boxed{V_i = V_f \left( 1 + \frac{3}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right)}$$

Apply KCL at node X

$$I_1 = I_2 + \frac{V_f}{R}$$

$$I_1 = \frac{V_f}{R} \left( 2 + \frac{1}{j\omega RC} \right) + \frac{V_f}{R} \left( 1 + \frac{3}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right)$$

$$I_1 = \frac{V_f}{R} \left( 3 + \frac{4}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right)$$

Apply KVL in loop ①

$$V_o - V_c - V_1 = 0$$

$$V_o = V_1 + V_c = V_1 + \frac{I_1}{j\omega C}$$

$$V_o = V_f \left( 1 + \frac{3}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right) + \frac{V_f}{j\omega RC} \left( 3 + \frac{4}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right)$$

$$V_o = V_f \left( 1 + \frac{6}{j\omega RC} - \frac{5}{\omega^2 R^2 C^2} - \frac{1}{j\omega^3 R^3 C^3} \right)$$

$$\frac{1}{B} = \frac{V_o}{V_f} = 1 + \frac{6}{j\omega RC} - \frac{5}{\omega^2 R^2 C^2} - \frac{1}{j\omega^3 R^3 C^3}$$

for 'B' to be real,

$$\frac{6}{j\omega RC} - \frac{1}{j(\omega RC)^3} = 0$$

$$\frac{6}{\omega RC} = \frac{1}{(\omega RC)^3}$$

$$f_0 = \frac{1}{2\pi RC \sqrt{6}}$$

$$\omega_0 = \frac{1}{\sqrt{6} RC}$$

$$\frac{1}{B} = 1 - \frac{5}{\omega_0^2 R^2 C^2}$$

$$\frac{1}{B} = 1 - \frac{5}{\cancel{6R^2C^2}} \times \cancel{R^2C^2}$$

$$\frac{1}{B} = 1 - 30 \rightarrow B = -\frac{1}{29}$$

$$AB = 1$$


$$A \times \left(-\frac{1}{29}\right) = 1$$

$$A = -29$$

$$+\frac{R_f}{R_1} = +29$$

$$R_f = 29R_1$$

# Wien-Bridge Oscillator:

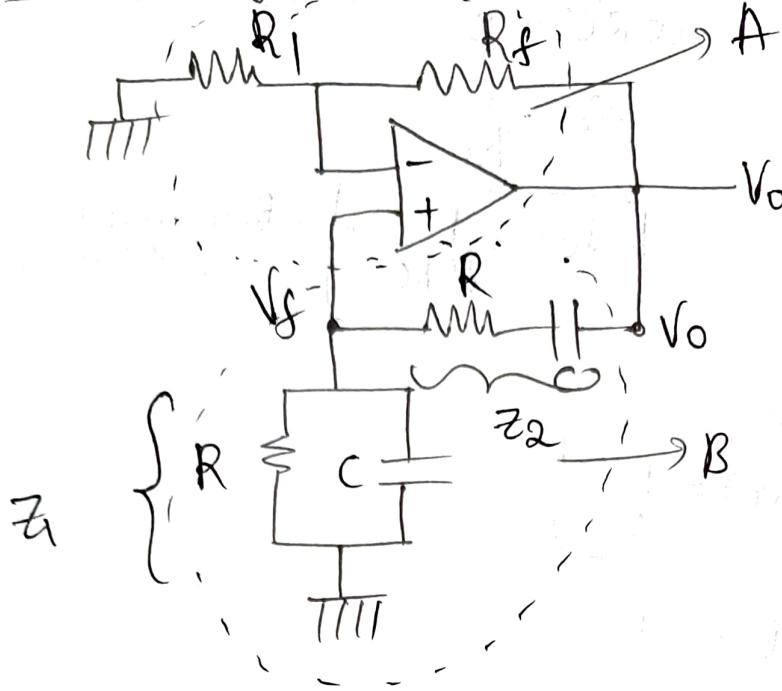

$$A = 1 + \frac{R_f}{R_1}$$

$$B = \frac{V_f}{V_0}$$

$$V_f(s) = \frac{V_0(s) \times Z_1(s)}{Z_1(s) + Z_2(s)}$$

$$Z_1(s) = R \parallel \frac{1}{sC} = \frac{R}{1+sCR}$$

$$Z_2(s) = R + \frac{1}{sC} = \frac{1+sCR}{sC}$$

$$B(s) = \frac{V_f(s)}{V_0(s)} = \frac{Z_1(s)}{Z_1(s) + Z_2(s)} = \frac{\frac{R}{1+sCR}}{\frac{R}{1+sCR} + \frac{1+sCR}{sC}}$$

$$= \frac{sCR}{sCR + 1 + 2sCR + s^2C^2R^2}$$

$$B(s) = \frac{V_f(s)}{V_0(s)} = \frac{sCR}{1 + 3sCR + s^2C^2R^2}$$

Put  $s = j\omega$ ,

$$B(j\omega) = \frac{j\omega RC}{1 + 3j\omega RC + (j\omega)^2 C^2 R^2}$$

$$B(j\omega) = \frac{j\omega RC}{1 + 3j\omega RC - \omega^2 C^2 R^2}$$

for  $B(j\omega)$  to be real,

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega_0 = \frac{1}{RC}$$

$$f_0 = \frac{1}{2\pi RC}$$

frequency of oscillation

At  $\omega = \omega_0$

$$B(j\omega_0) = \frac{1}{3}$$

$$AB = 1$$

$$A \times \frac{1}{3} = 1$$

$$A = 3$$


$$1 + \frac{R_f}{R_i} = 8$$

$$R_f = 2R_i$$

# \* Astable Multivibrator (or) Square wave Generator :


- It has zero stable states.
- It has 2 Quasi stable states.

↓  
temporary stable state.

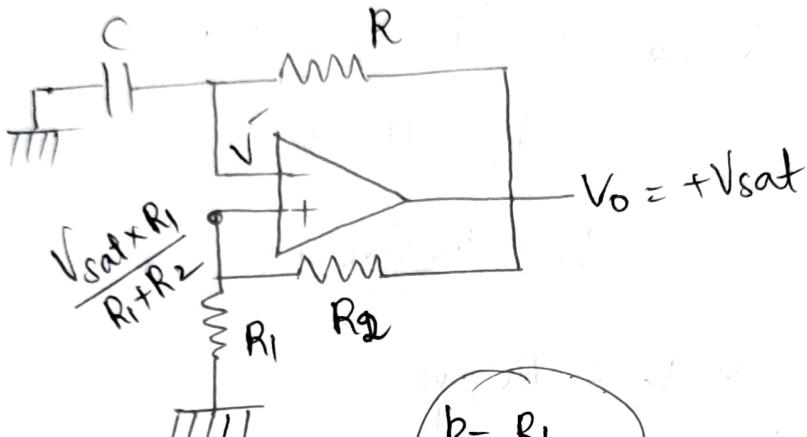


$$\beta = \frac{R_1}{R_1 + R_2}$$

Capacitor is  
charging

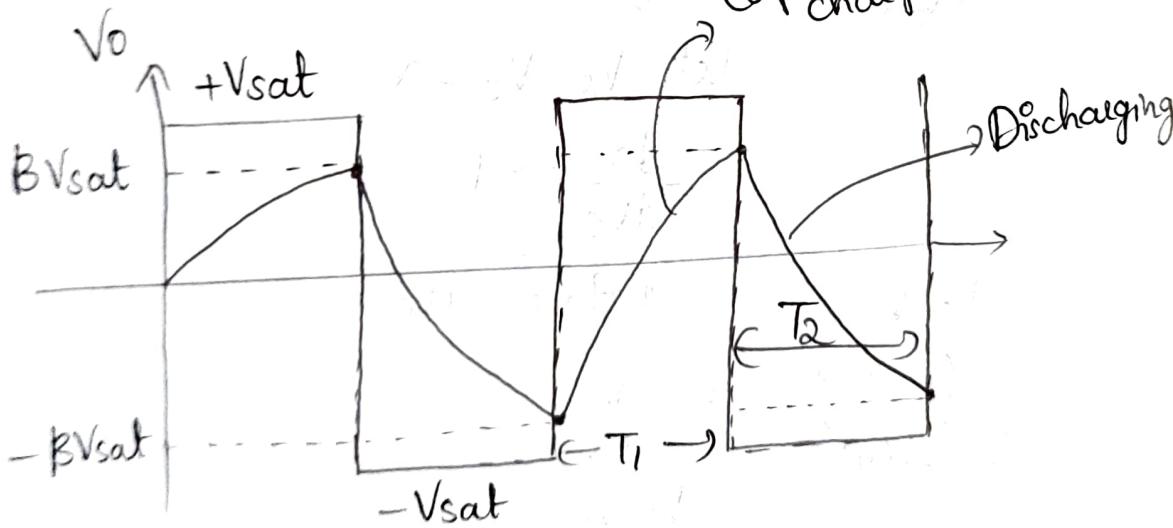
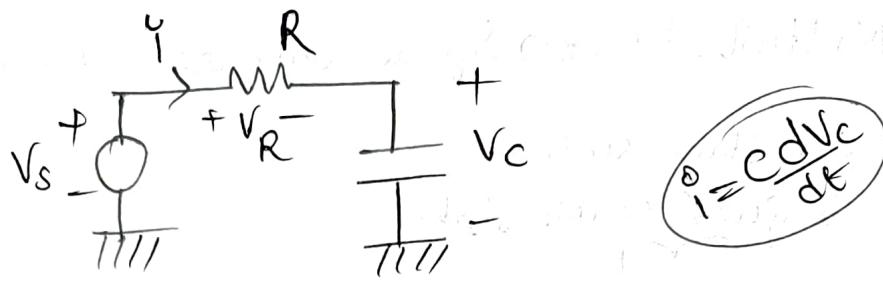
$$V_0 = \begin{cases} +Vsat \\ -Vsat \end{cases} \quad \left. \begin{array}{l} \text{Two Quasi stable states.} \\ \text{= -Vsat} \end{array} \right\}$$



RC-series circuit

$$V_s - iR - V_c = 0$$

$$V_s = iR + V_c$$

$$V_s = RC \frac{dV_c}{dt} + V_c$$

$$V_s - V_c = RC \frac{dV_c}{dt}$$

$$\int_{V_c(0)}^{V_c} \frac{dV_c}{V_s - V_c} = \int_0^t \frac{dt}{RC}$$

$$\text{let } V_s - V_c = x$$

$$\frac{dx}{dV_c} = -1$$

$$\boxed{dx = -dV_c}$$

$$-\int_{V_s - V_c(0)}^{V_s - V_c} \frac{dx}{x} = \frac{t}{RC}$$

$$-\ln|x| \Big|_{V_s - V_c(0)}^{V_s - V_c} = \frac{t}{RC}$$

$$-\left[ \ln(V_s - V_c) - \ln|V_s - V_c(0)| \right] = \frac{t}{RC}$$

$$\ln \left| \frac{V_s - V_c(0)}{V_s - V_c} \right| = \frac{t}{RC}$$

$$\boxed{t = RC \ln \left| \frac{V_s - V_c(0)}{V_s - V_c} \right|}$$

(i)  $V_S = +V_{sat}$ ,

$$V_C(0) = \pm \beta V_{sat}$$

$$V_C = \pm \beta V_{sat}$$

$$T_1 = RC \ln \left| \frac{V_{sat} + \beta V_{sat}}{V_{sat} - \beta V_{sat}} \right|$$

$$T_1 = RC \ln \left| \frac{1 + \beta}{1 - \beta} \right| \quad (\beta = \frac{R_1}{R_1 + R_2})$$

$$T_1 = RC \ln \left| \frac{2R_1 + R_2}{R_2} \right|$$

$T_1 = RC \ln \left| 1 + \frac{2R_1}{R_2} \right|$

Capacitor is charging.

(ii)  $V_S = -V_{sat}$

$$V_C(0) = \pm \beta V_{sat}$$

$$V_C = -\beta V_{sat}$$

$$T_2 = RC \ln \left| \frac{-V_{sat} - \beta V_{sat}}{-V_{sat} + \beta V_{sat}} \right|$$

$$T_2 = RC \ln \left| \frac{1 + \beta}{1 - \beta} \right|$$

$T_2 = RC \ln \left| 1 + \frac{2R_1}{R_2} \right|$

Capacitor is discharging.

$$T_0 = \text{Time period} = T_1 + T_2$$

$T_0 = 2RC \ln \left( 1 + \frac{2R_1}{R_2} \right)$

# Solving Differential Equations using OPAMP : (Analog Computer)


$$\frac{d^2 V_o}{dt^2} + k_1 \frac{dV_o}{dt} + k_2 V_o - V_i = 0$$

$V_i \rightarrow$  input voltage


$k_1, k_2 \rightarrow$  real constants.

Summing circuit

Integrator,

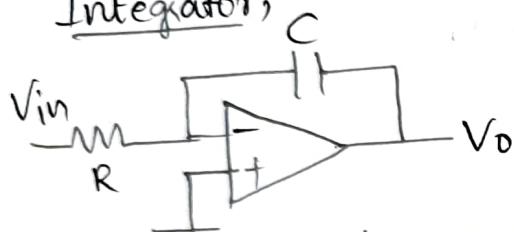


$$V_o = -\frac{1}{RC} \int V_{in} dt$$

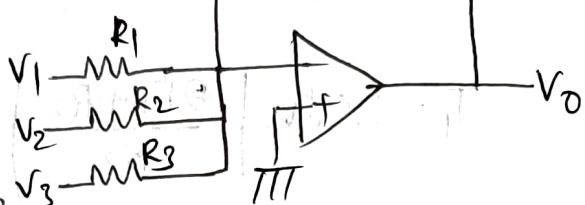

$$V_o = -\frac{R_f V_1}{R_1} - \frac{R_f V_2}{R_2} - \frac{R_f V_3}{R_3}$$

$$RC = 1$$

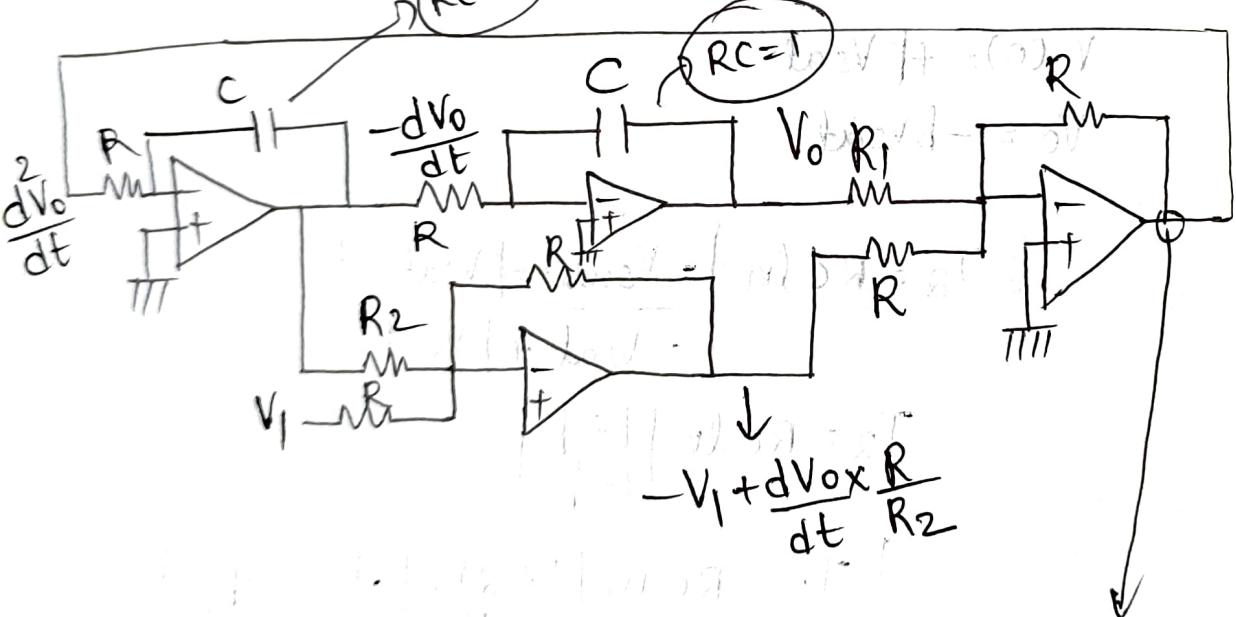


$$\frac{d^2 V_o}{dt^2} = -V_o \frac{R}{R_1} - \frac{R}{R_2} \frac{dV_o}{dt} + V_i + V_1$$

$$-V_o \frac{R}{R_1} - \frac{R}{R_2} \frac{dV_o}{dt} + V_1$$


$$k_1 = \frac{R}{R_2}$$

$$k_2 = \frac{R}{R_1}$$
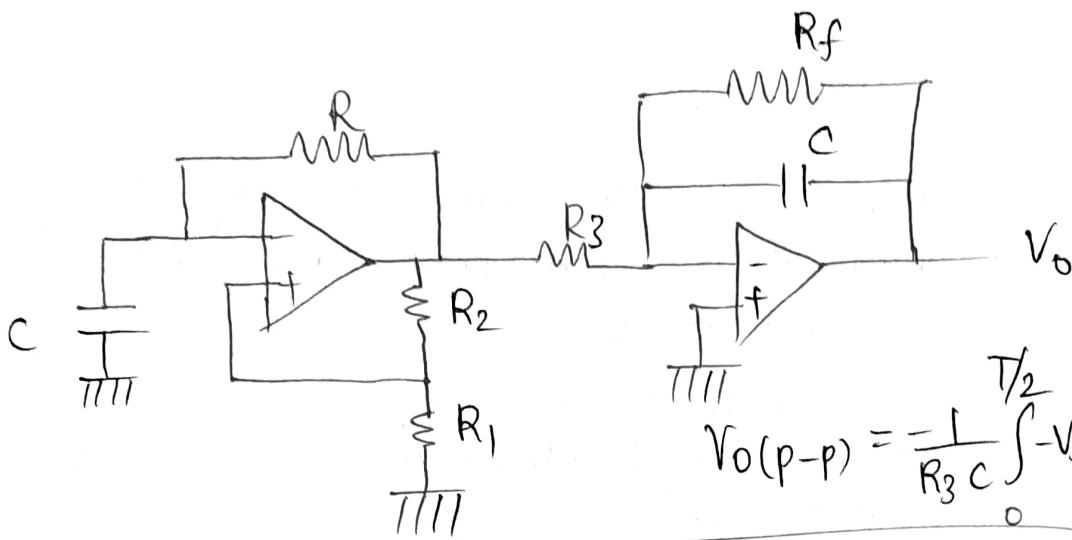
## • Triangular wave generator using OPAMP:


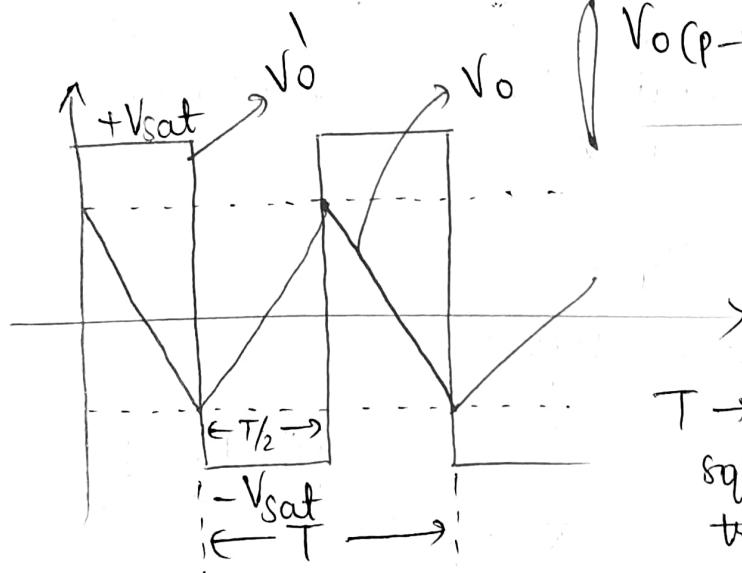
$$V_o(p-p) = \frac{1}{R_3 C} \int_{0}^{T/2} -V_{sat} dt$$



$T \rightarrow$  time period of square wave and triangular wave.


$$V_o = -\frac{1}{R_3 C} \int v_o^l dt$$

$$\frac{V_o(p-p)}{2} = \frac{V_{sat} T}{4 R_3 C}$$

Amplitude of triangular wave.


$$T = 2 R C \ln \left( \frac{1+\beta}{1-\beta} \right) \quad \beta = \frac{R_1}{R_1+R_2}$$


## • Analog Multiplier:

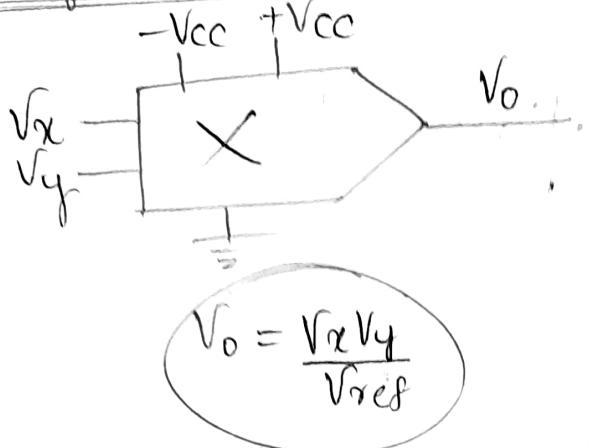

- Analog multiplier IC which works only when both inputs  $V_x$  &  $V_y$  are positive and are called first Quadrant IC's.
- In Second Quadrant Analog multiplier will produce correct output only when any of the input is '+ve'.
- In Fourth Quadrant Analog multiplier will produce correct output only when  $V_x$  &  $V_y$  are either positive or negative.


## • Simple Analog Multiplier:

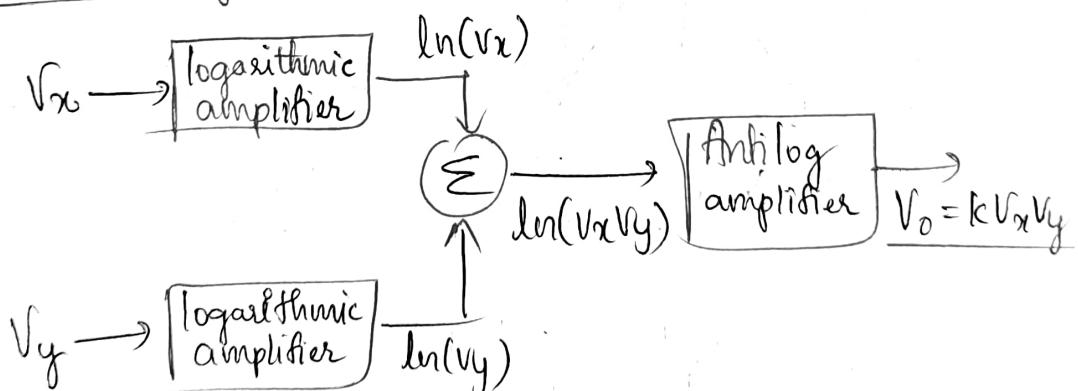

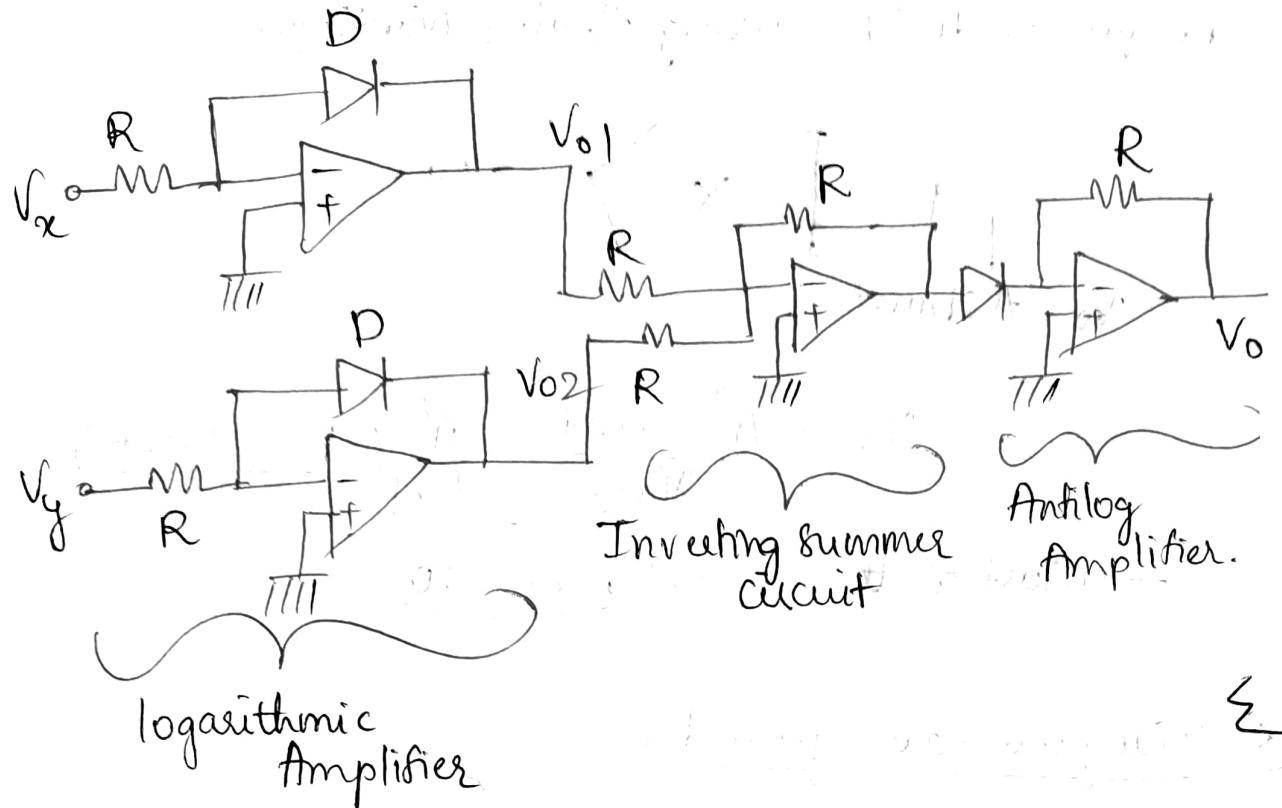

## \*Applications of Analog Multiplier:

### ① Divider circuit:

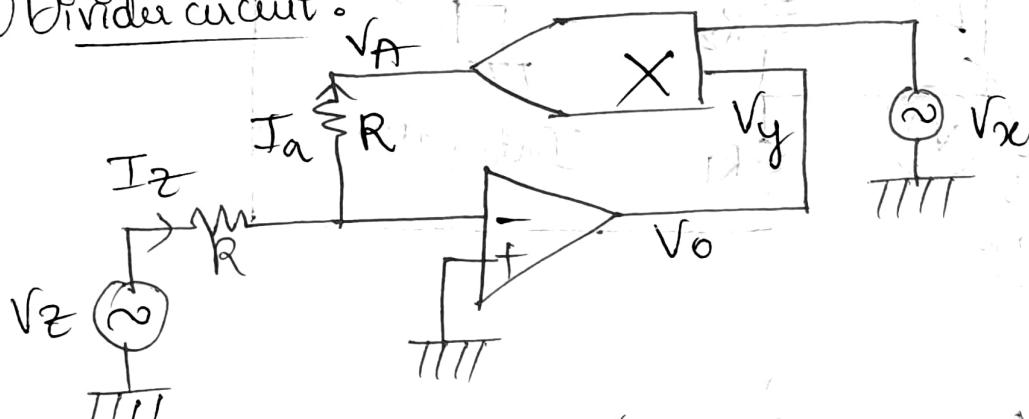

$$I_Z = \frac{V_Z}{R}, \quad I_a = -\frac{V_A}{R} \rightarrow I_Z = I_a$$

$$V_A = \frac{V_X V_Y}{V_{ref}} = \frac{V_X V_0}{V_{ref}}$$

$$V_Z = -V_A$$


$$-V_Z = \frac{V_X V_0}{V_{ref}}$$

$$V_0 = -V_{ref} \cdot \frac{V_Z}{V_X}$$

dividend

divisor.
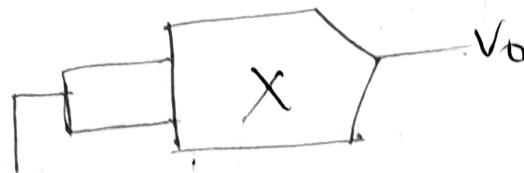
## ② Frequency doubler using Analog Multiplier:





$$V_o = A \sin \omega t$$

$$V_o = \frac{A^2 \sin^2 \omega t}{V_{ref}} = \frac{A^2}{V_{ref}} \left( 1 - \cos 2\omega t \right)$$

→ Most of the cases,  $V_{ref} = 10$

## \* Triangular wave generator:

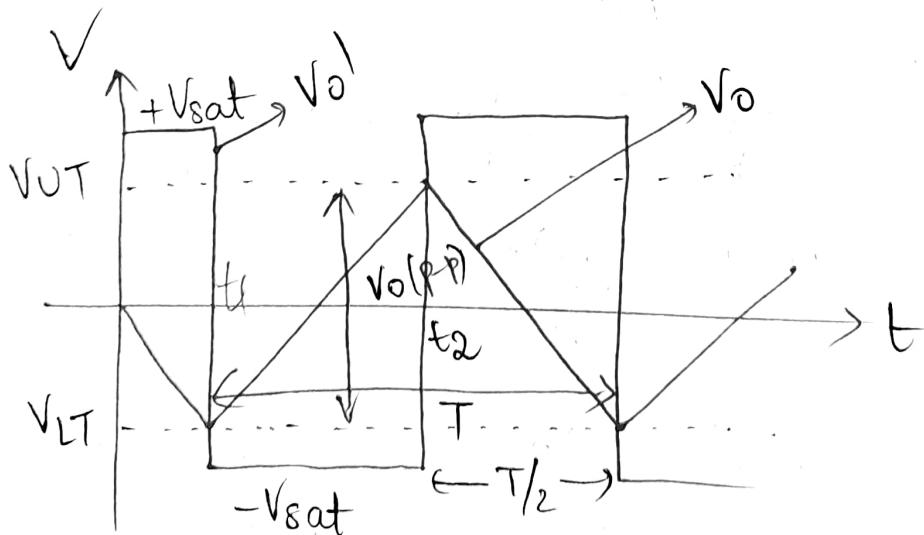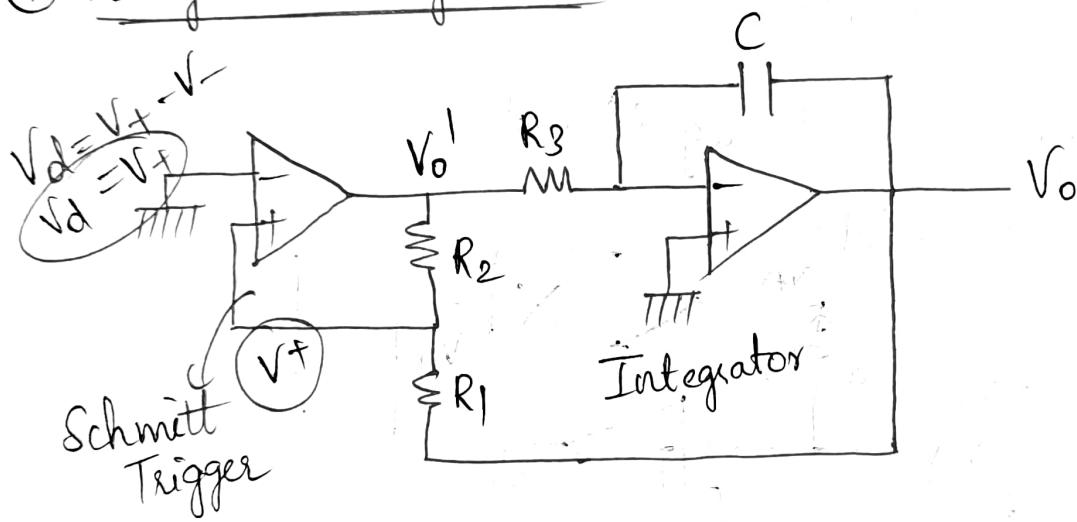

$$V_T = \frac{V_0' R_1}{R_1 + R_2} + \frac{V_0 R_2}{R_1 + R_2}$$

$$V_o = -\frac{1}{R_3 C} \int_0^t V_{sat} dt$$

$$\boxed{V_o = -\frac{V_{sat} \times t}{R_3 C}}$$

→ When  $V_o = +V_{sat}$ ,

$$V_T = \frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

→ At instant  $t_1$ ,  $\boxed{V_T = 0}$

$$0 = \frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

$$\boxed{V_o = -\frac{V_{sat} \times R_1}{R_2} = V_{LT}}$$

→ When  $V_o = -V_{sat}$

$$V_T = -\frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

At time instant,  $t = t_2$ :

$$\boxed{V_T = 0}$$

$$-\frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2} \rightarrow$$

$$\boxed{V_o = \frac{V_{sat} \times R_1}{R_2} = V_{UT}}$$

$$V_{o(p-p)} = V_{UT} - V_{LT}$$

$$\boxed{V_{o(p-p)} = 2 \frac{V_{sat} \times R_1}{R_2}}$$

$$V_{o(p-p)} = \frac{-1}{R_3 C} \int_0^{T/2} -V_{sat} dt$$

$$2 \frac{V_{sat} \times R_1}{R_2} = \frac{1}{R_3 C} V_{sat} \times \frac{T}{2} \rightarrow \boxed{T = \frac{4 R_3 C R_1}{R_2}}$$

Q: Design a triangular wave generator using OPAMP, with  $f = 1 \text{ kHz}$  &  $V_{o(\text{P-P})} = 2V$ .

Sol:

$$V_{o(\text{P-P})} = 2 \frac{V_{\text{sat}} \times R_1}{R_2} \quad \text{if } V_{\text{cc}} = \pm 15V$$

$$\cancel{A} = \cancel{\frac{V_{\text{sat}} \times R_1}{R_2}} \quad \text{then assume } V_{\text{sat}} \approx 14V$$

$$\boxed{R_2 = 14R_1}$$

$$\cancel{R_1} \quad \cancel{R_2} \quad \text{if } R_1 = 10k\Omega$$

$$\text{then } R_2 = 140k\Omega$$

$$f = \frac{R_2}{4R_3 C R_1} \quad \cancel{140k\Omega}$$

$$1 \times 10^8 = \frac{140 \times 10^8}{4 \times R_3 \times C \times 10 \times 10^3}$$


$$R_3 C = 3.5 \times 10^{-3}$$

$$\rightarrow \text{Assume } C = 1 \mu F$$

$$R_3 \times 10^6 = 3.5 \times 10^3$$

$$\boxed{R_3 = 3.5 \times 10^3 \Omega}$$

# \* Monostable Vibrator using OPAMP:

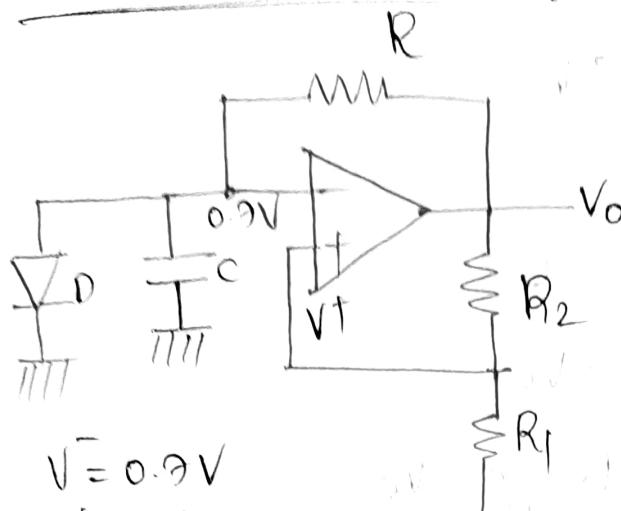

If  $V_0 = +V_{sat}$   
then it is stable.


$$V^- = 0.3V$$


$$V^+ = \frac{V_{sat} \times R_1}{R_2} \quad V_T = 0V$$

(if  $V_0 = +V_{sat}$ )

$$V_d = V^+ - V^-$$

$$V_d = V^+ - 0.3$$

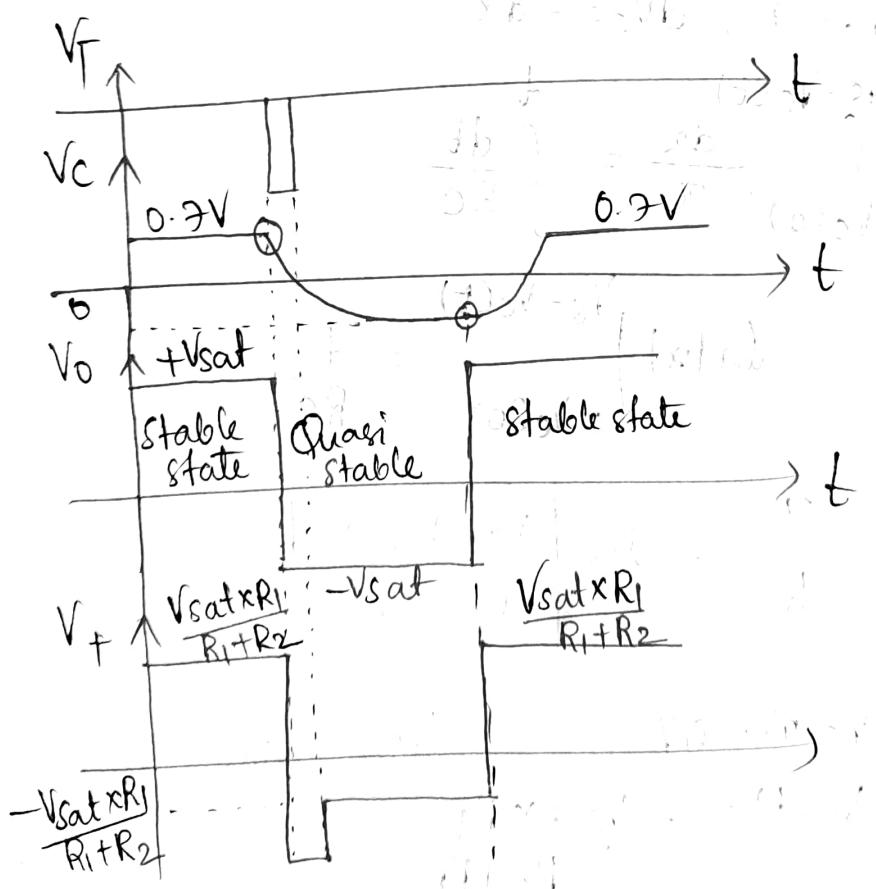

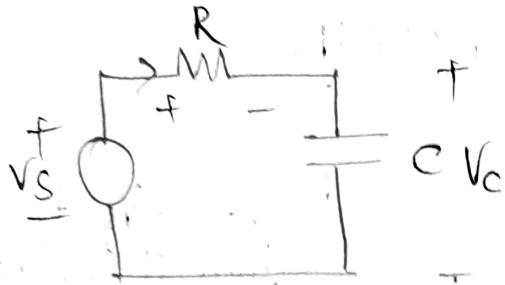

$$V_s - iR - V_c = 0$$

$$V_s = iR + V_c$$

$$V_s = RC \frac{dV_c}{dt} + V_c$$

$$\int_{V_c(0)}^{V_c(t)} \frac{dV_c}{V_s - V_c} = \int_0^t \frac{dt}{RC}$$

$$V_s - V_c = x, \quad dV_c = -dx$$

$$\int_{-V_c(0)}^{V_s - V_c(t)} \frac{dx}{x} = \int_0^t \frac{dt}{RC}$$

$$\ln|x| \Big|_{-V_c(0)}^{V_s - V_c(t)} = \frac{t}{RC}$$

$$\frac{t}{RC} = \ln \left| \frac{V_s - V_c(0)}{V_s - V_c(t)} \right|$$


$$V_c(0) = 0V$$

$$V_s = -V_{sat}$$

$$V_c(t) = -\frac{V_{sat} \times R_1}{R_2 + R_1}$$

$$T = RC \ln \left( 1 + \frac{R_1}{R_2} \right)$$

## Practical Differentiator using OPAMP:

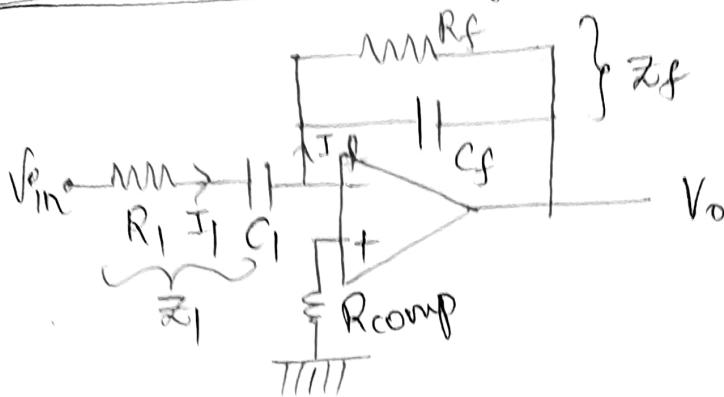

$$Z_1(s) = R_1 + \frac{1}{sC_1} = \frac{sC_1 R_1 + 1}{sC_1}$$

$$Z_f(s) = R_f \parallel C_f = \frac{R_f \times \frac{1}{sC_f}}{R_f + \frac{1}{sC_f}} = \frac{R_f}{1 + sC_f R_f}$$

$$I_1(s) = \frac{V_{in}(s) - 0}{Z_1(s)} \quad I_2(s) = \frac{0 - V_o(s)}{Z_2(s)}$$


$$I_1(s) = I_2(s) \quad (\text{Virtual ground})$$

$$\frac{V_{in}(s)}{Z_1(s)} = \frac{-V_o(s)}{Z_2(s)}$$

$$\frac{V_{in}(s)}{\frac{1 + sC_1 R_1}{sC_1}} = \frac{-V_o(s)}{\frac{R_f}{1 + sC_f R_f}}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-R_f}{(1 + sC_f R_f)} \times \frac{sC_1}{(1 + sC_1 R_1)}$$

$$|A_v(s)| = \frac{sR_f C_1}{(1 + sC_f R_f)(1 + sR_1 C_1)}$$

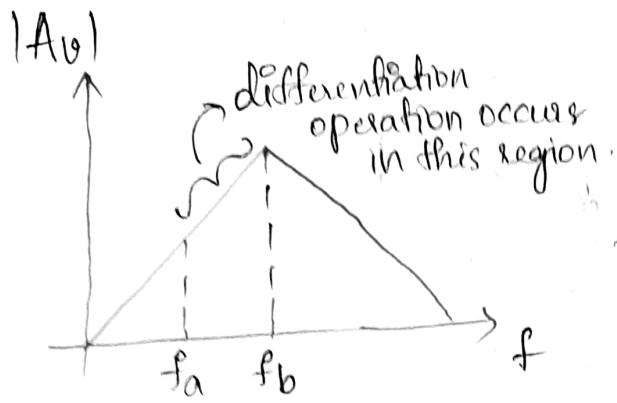

$f_a \rightarrow$  frequency at which  $|Av| = 1$

For proper differentiation,

$$\text{If } R_f C_1 > R_f C_f \\ R_f C_1 > R_1 C_1 \text{ then}$$

$$A_v(s) = -s R_f C_1$$

$$\frac{V_o(s)}{V_{in}(s)} = -s R_f C_1$$

$$V_o(s) = -s V_{in}(s) R_f C_1$$

$$V_o(t) = -R_f C_1 \frac{d}{dt} V_{in}(t)$$

$$\text{If } R_1 C_1 = R_f C_f$$

$$|A_v(s)| = \frac{s R_f C_1}{(1+s R_f C_1)^2}$$

$$|A_v(s)| = \frac{j \omega R_f C_1}{(1 + j \omega C_1 R_1)^2}$$

$$|A_v(s)| = \frac{f/f_a}{1 + (f/f_b)^2}$$

Q: Design a differentiator using op-amp to differentiate an input signal with  $f_{max} = 200\text{Hz}$ . Draw output waveform for sine wave with 1V peak at 200Hz.

Sol:  $f_{max} = f_a = 200\text{Hz}$

$$\frac{1}{2\pi R_f C_1} = 200$$

(let  $C_1 = 0.1\mu\text{F}$ )

$$R_f = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 200} = 7.962\text{k}\Omega$$


$$f_b = 10f_a$$

$$\frac{1}{2\pi R_1 C_1} = 10 \times 200$$

$$R_1 = \frac{1}{2\pi \times 2000 \times 0.1 \times 10^{-6}} = 0.796\text{k}\Omega$$

$$R_1 C_1 = R_f C_f$$

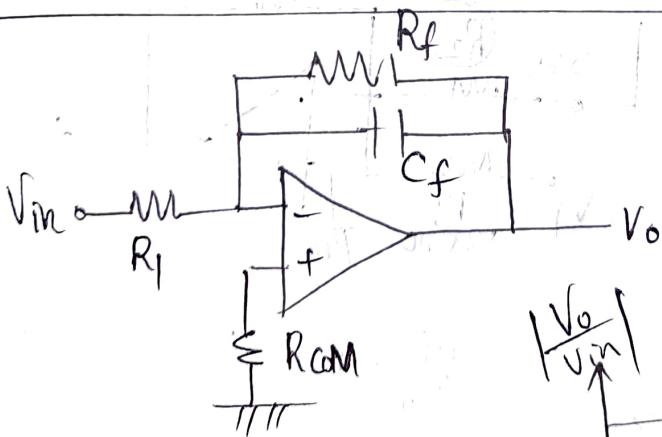
$$C_f = \frac{R_1 C_1}{R_f} = 0.01\mu\text{F}$$



$$f_b = 10f_a$$

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$f_b = \frac{1}{2\pi R_1 C_f}$$

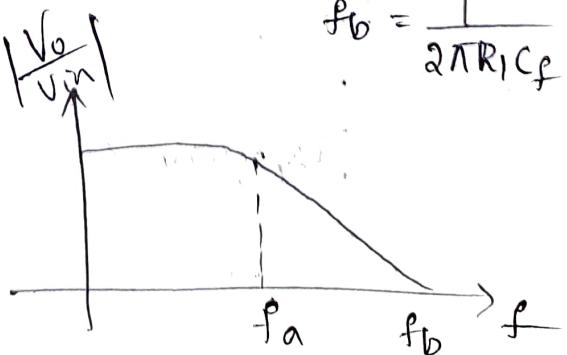

Q: Design a practical integrator with lower limit of frequency is 160 Hz.

Solt:  $f_a = 160 \text{ Hz}$

$$\frac{1}{2\pi R_f C_f} = 160 \quad \text{Assume, } C_f = 0.01 \text{ nF}$$


$$R_f = \frac{1}{2\pi \times 160 \times 0.01 \times 10^{-9}}$$

$$f_b = 10 f_a = 1600 \text{ Hz}$$

$$\frac{1}{2\pi R_i C_f} = 1600 \rightarrow R_i = \frac{1}{2\pi \times 1600 \times 0.01 \times 10^{-9}}$$

Q: Design a circuit using OPAMP, which gives output  $V_o = 5V_2 - 8V_1$ , where  $V_2$  &  $V_1$  are inputs.

Solt:

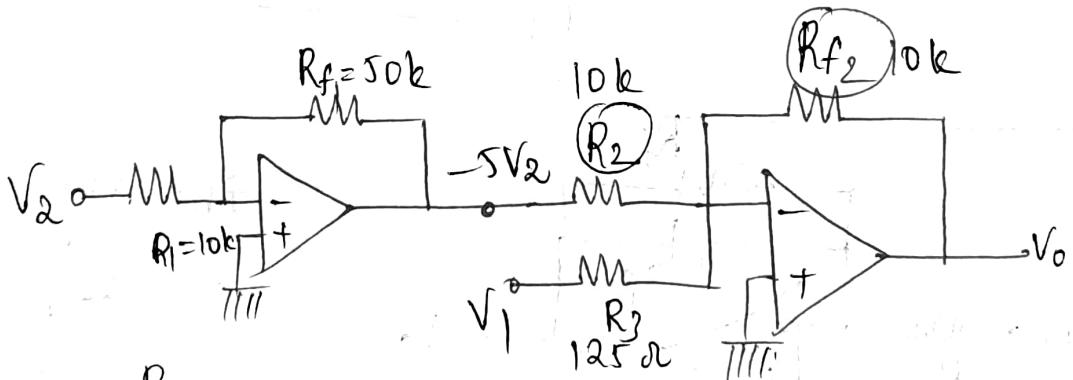

$$\frac{R_{f1}}{R_1} = 5$$

$$\boxed{R_{f1} = 50k}$$


$$\frac{R_{f2}}{R_2} = 1 \rightarrow R_{f2} = R_2 = 10k$$

$$\frac{R_{f2}}{R_3} = 8 \rightarrow R_3 = \frac{10k}{8} = 125\Omega$$

Q: Design an OPAMP circuit which performs following operation

$$V_o = -V_1 - 2V_2 - 3V_3$$

Solt:

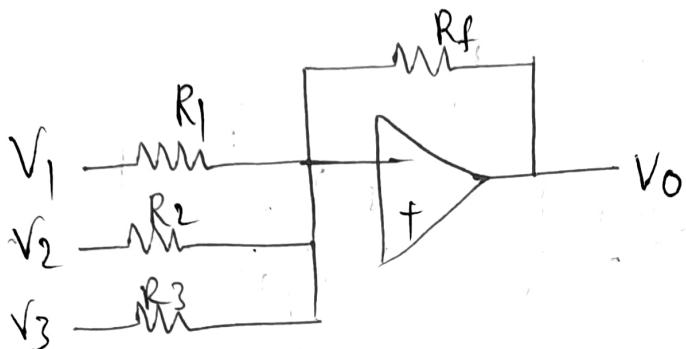

$$-\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 - \frac{R_f}{R_3} \times V_3 = V_o$$


$$\frac{R_f}{R_1} = 1 \quad \frac{R_f}{R_2} = 2 \quad \frac{R_f}{R_3} = 3$$

Let  $R_f = 100\text{k}$ ,

$$\boxed{\begin{aligned} R_1 &= 100\text{k} \\ R_2 &= 50\text{k} \\ R_3 &= \frac{100\text{k}}{3} \end{aligned}}$$

Q: Design a practical integrator which differentiates a signal having max freq 800MHz.

Q: Find the output

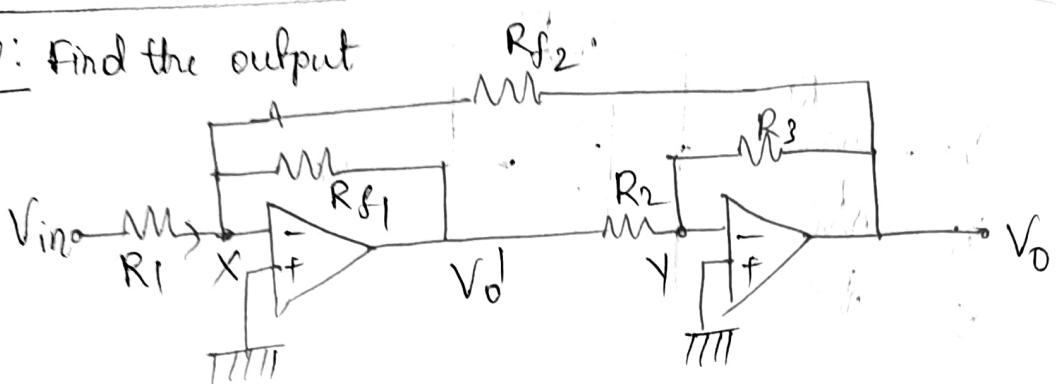

Sol:-

Apply KCL at Node X,

$$\frac{V_{in}}{R_1} = -\frac{V_0'}{R_{f1}} - \frac{V_0}{R_{f2}}$$

Apply KCL at Node Y,

$$\frac{V_0'}{R_2} = -\frac{V_0}{R_3}$$

$$V_0' = -\frac{R_2}{R_3} V_0$$

$$\frac{V_{in}}{R_1} = +\frac{R_2}{R_3 R_{f1}} V_0 - \frac{V_0}{R_{f2}}$$



$$= -V_0 \left( \frac{-R_2 R_{f2} + R_3 R_{f1}}{R_3 R_{f1} R_{f2}} \right)$$

$$\frac{V_0}{V_{in}} = \frac{-R_3 R_{f1} R_{f2}}{R_1 (-R_2 R_{f2} + R_3 R_{f1})}$$


# ACTIVE FILTERS

- A filter is a frequency selective circuit, which allows signals of certain range of frequencies to pass through it and rejecting other frequencies.
- There are two kinds of filters
  - ① Active filters - {made of passive + active elements}
  - ② Passive filters - {made of only passive elements}
- Types of Active filters
  - ① Low pass filters
  - ② High pass filters
  - ③ Band pass filters
  - ④ Band reject filter (or) Band stop filter.

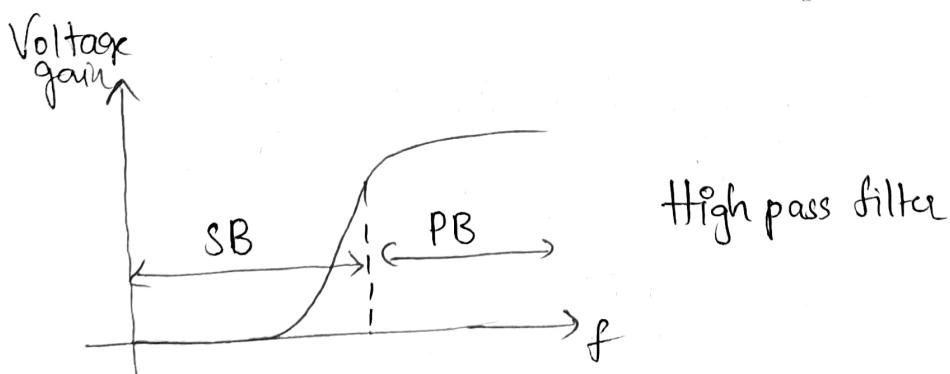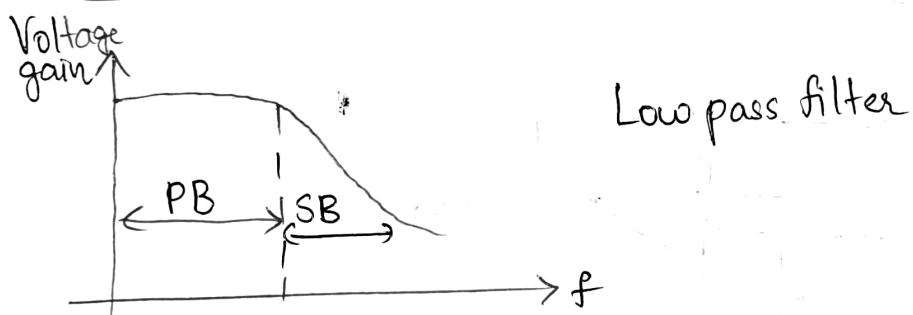
## frequency responses of active filters:



SB - Stop Band  
PB - Pass Band

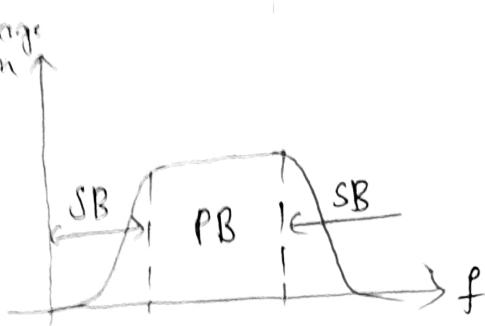


Band Pass filter

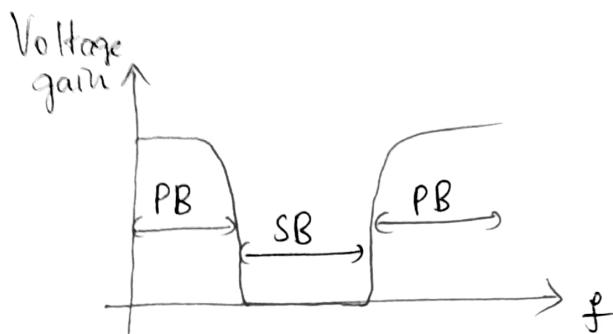

Band Reject filter

## D) Low pass filter:

### (i) first order low pass filter:

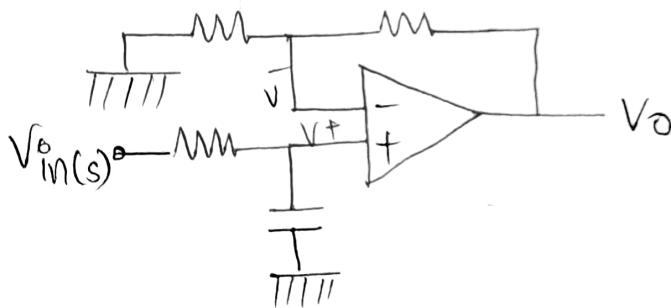

→ If it is first order because  $A_V(s) = \frac{1 + \frac{R_f}{R_1}}{1 + SRC}$   
 ↳  $s$  has only 1 degree.

$$V^+(s) = \frac{V_{in}(s)}{R + \frac{1}{SC}} \times \frac{1}{SC}$$

$$V^+(s) = \frac{V_{in}(s)}{1 + SRC}$$

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) V_{in}(s)$$

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) \frac{V_{in}(s)}{1 + SRC}$$

$$A_{vf}(s) = \frac{V_o(s)}{V_{in}(s)} = \left(1 + \frac{R_f}{R_i}\right) \times \frac{1}{1 + SRC}$$

$$s = j\omega$$

$$A_{vf}(j\omega) = \left(1 + \frac{R_f}{R_i}\right) \times \frac{1}{1 + j\omega R C}$$

$$|A_{vf}(j\omega)| = \frac{\left(1 + \frac{R_f}{R_i}\right)}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$|A_{vf}(j\omega)|_{max}$  when  $\omega = 0$

$$|A_{vf}(j\omega)|_{max} = 1 + \frac{R_f}{R_i}$$

$$|A_{vf}(j\omega)| = \frac{|A_{vf}(j\omega)|_{max}}{\sqrt{1 + \omega^2 R^2 C^2}}$$


$\omega_0$   $f_0 \rightarrow$  frequency at which gain is  $\frac{1}{\sqrt{2}}$  times maximum gain.

$$\frac{|A_{vf}|_{max}}{\sqrt{2}} = \frac{|A_{vf}|_{max}}{\sqrt{1 + \omega^2 R^2 C^2}}$$

cutoff frequency


$$\omega_0 = \frac{1}{RC} \rightarrow f_0 = \frac{1}{2\pi RC}$$

→ When  $\omega_0$  is very large, then  $|A_{\text{Avf}}|_{\text{max}} = 0$

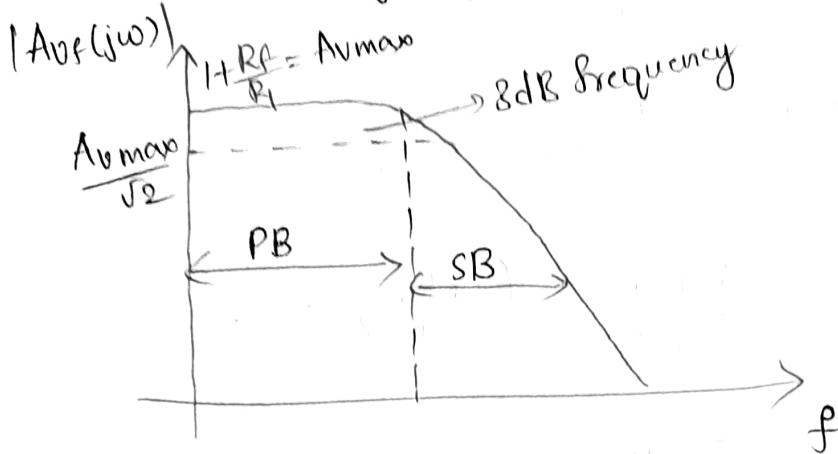

→ This is also called as Butterworth 1st order LPF.

## ② High pass filter:

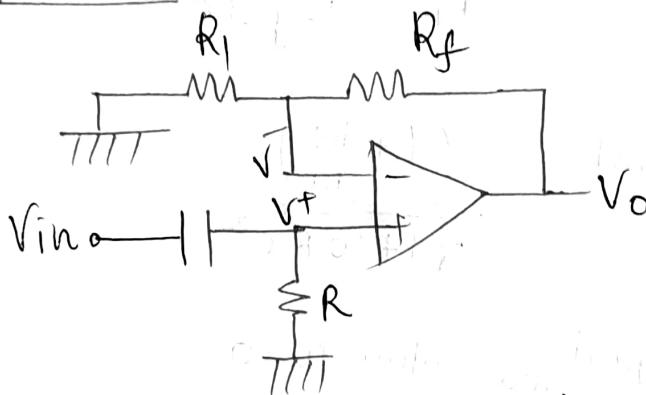

→ This is first order HPF, also called as Butterworth 1st order HPF.

$$V^+(s) = \frac{V_{\text{in}}(s) \times R}{\frac{1}{sC} + R}$$

$$V^+(s) = \frac{V_{\text{in}}(s) \times SCR}{1 + SCR}$$

for non-inverting OP-AMP,

$$V_o(s) = V^+(s) \left( 1 + \frac{R_f}{R_1} \right)$$

$$\boxed{V_o(s) = \frac{V_{\text{in}}(s) \times SCR}{1 + SCR} \left( 1 + \frac{R_f}{R_1} \right)}$$

$$A_{Vf}(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{SRC \left(1 + \frac{R_f}{R_L}\right)}{1 + SRC}$$

$s = j\omega$

$$A_{Vf}(j\omega) = \frac{j\omega R C \left(1 + \frac{R_f}{R_L}\right)}{1 + j\omega R C}$$

$$|A_{Vf}(j\omega)| = \frac{\omega R C \left(1 + \frac{R_f}{R_L}\right)}{\sqrt{1 + \omega^2 R^2 C^2}}$$


$$|A_{Vf}(j\omega)| = \frac{\left(1 + \frac{R_f}{R_L}\right)}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}}$$

→ Maximum voltage gain occurs at  $\omega = \infty$

$$|A_{Vf}|_{\max} = \left(1 + \frac{R_f}{R_L}\right)$$

→ Minimum voltage gain occurs at  $\omega = 0$

$$|A_{Vf}|_{\min} = 0$$

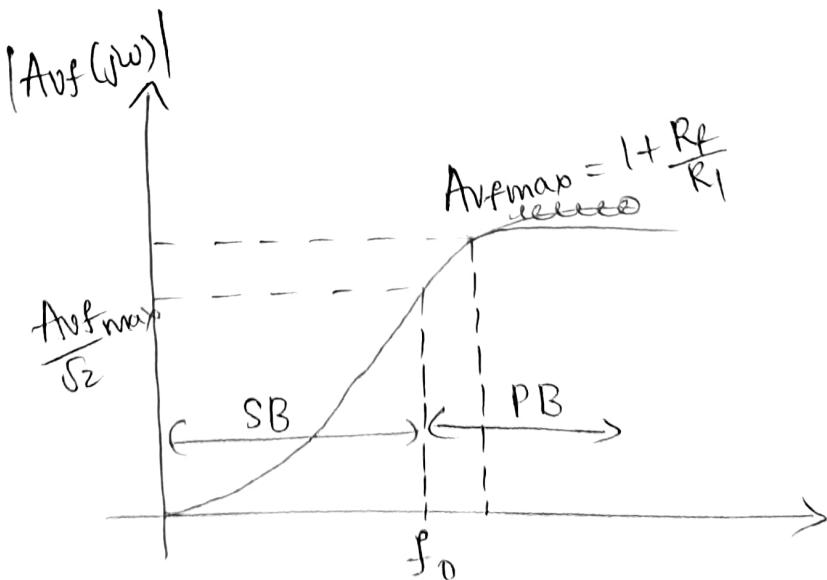

At  $f = f_0$  (cut off frequency),  
gain is  $\frac{1}{\sqrt{2}}$  times the maximum gain.

$$|A_{vf}(2\pi f_0)| = \frac{A_{vf \max}}{\sqrt{2}}$$


$$\frac{A_{vf \max}}{\sqrt{2}} = \frac{A_{vf \max}}{\sqrt{1 + \frac{1}{\omega_0^2 R^2 C^2}}}$$

$$\frac{1}{\omega_0^2 R^2 C^2} = 2 - 1$$

$$\omega_0^2 R^2 C^2 = 1$$


$$\boxed{\omega_0 = \frac{1}{RC}}$$

$$\boxed{f_0 = \frac{1}{2\pi RC}}$$

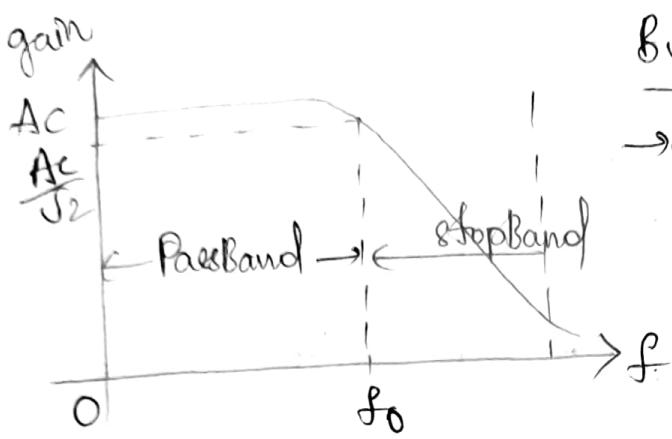
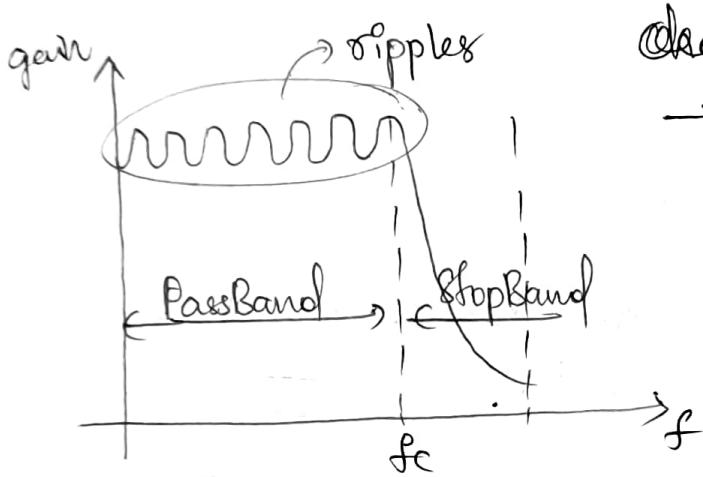
### Butterworth LPF


→ for faster transition from Passband to stopband  
Higher order filter is used


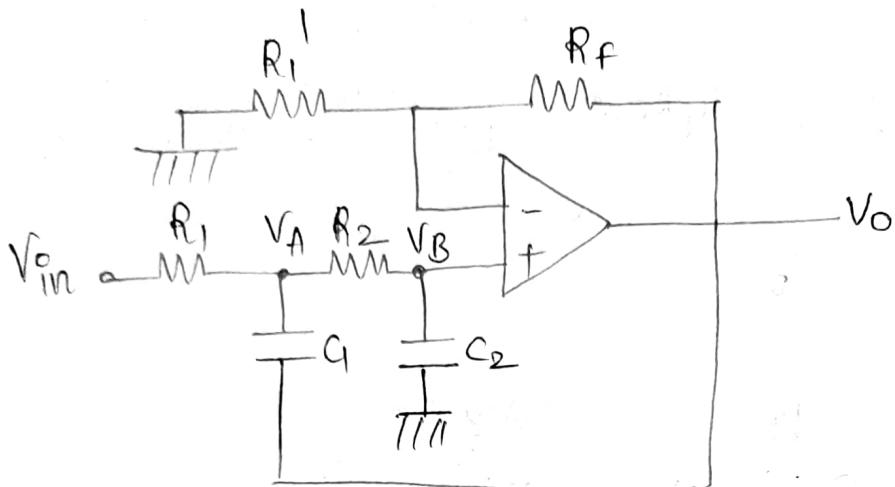
### Chebyshov filter

→ for faster transition from passband to stopband  
Low order filter is used.

• Butterworth Secondorder Low pass filter:



Apply KCL at node A,

$$\frac{V_{in}(s) - V_A(s)}{R_1} = \frac{V_A(s) - V_B(s)}{R_2} + \frac{V_A(s) - V_o(s)}{\frac{1}{sC_1}} \quad \text{--- (1)}$$

$$V_B(s) = \frac{V_A(s) \times \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{V_A(s)}{1 + sC_2 R_2} \quad \text{--- (2)}$$

$$V_o(s) = \left(1 + \frac{R_f}{R_1}\right) V_B(s) \quad \text{--- (3)}$$

Substituting eq(2) & (3) in eq(1),

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 / R_1 R_2 C_1 C_2}{s^2 + s(C_2(R_1 + R_2) + (1 - A_0)R_1 C_1) + \frac{1}{R_1 R_2 C_1 C_2}}$$

Generally,

$$H(s) = \frac{A_0 \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2} \quad \text{--- (5)}$$

where,  $\zeta = \frac{1}{2\zeta}$

Comparing eq(4) & eq(5),

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} ; 2\zeta = \frac{C_2(R_1 + R_2) + (1 - A_0)R_1 C_1}{\sqrt{R_1 R_2 C_1 C_2}}$$


$$\frac{1}{2\zeta} = Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 + R_2 C_2 + R_1 C_1 (1 - A_0)}$$

$$A_0 = 1 + \frac{R_F}{R_1}$$

when  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$  then,

$$f_C = f_n = \frac{1}{2\pi R C}$$


$$Q = \frac{1}{3 - A_0}$$

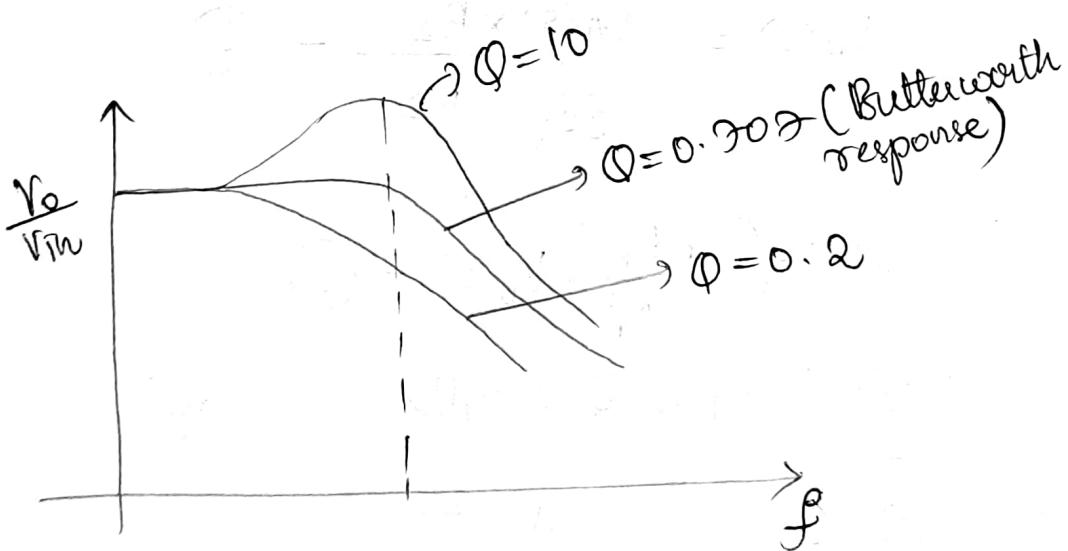

$$0.707 = \frac{1}{3 - A_0} \quad (\text{for Butterworth response})$$

$$A_0 = 1.586 \quad (\text{when } Q = 0.707)$$

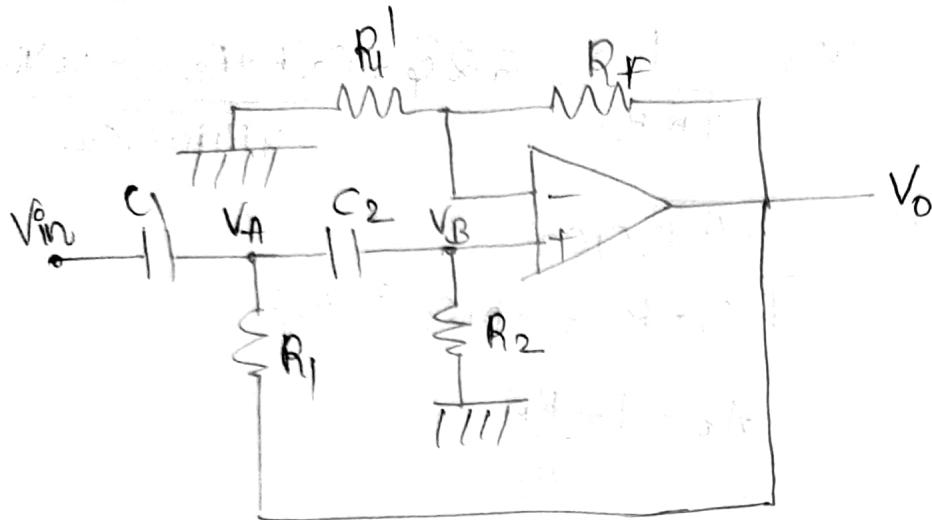• Butterworth Highpass Filter (Second order) :



Apply KCL at node A,

$$\frac{V_{in}(s) - V_A(s)}{\frac{1}{sC_1}} = \frac{V_A(s) - V_B(s)}{\frac{1}{sC_2}} + \frac{V_A(s) - V_o(s)}{R_1} \quad \text{--- (1)}$$

$$V_B(s) = \frac{V_A(s) \times R_2}{\frac{1}{sC_2} + R_2} \quad \text{--- (2)}$$

$$V_o(s) = \left(1 + \frac{R_F}{R_1}\right) V_B(s) \quad \text{--- (3)}$$

Substitute eq(2) & (3) in eq(1),

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 s^2}{s^2 + s(R_1 C_1 + R_1 C_2 + R_2 C_2 (1 - A_0)) + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$A_0 = 1 + \frac{R_F}{R_1}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_0 s^2}{s^2 + \alpha \omega_0 s + \omega_0^2} \quad \textcircled{5}$$

Comparing ④ & ⑤,

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{\alpha}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{R_1 C_1 + R_1 C_2 + R_2 C_2 (1 - A_0)}{R_1 R_2 C_1 C_2}$$


If  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$ ,

$$\text{then, } f_c = f_0 = \frac{1}{2\pi R C}$$

$$\underline{\alpha = 3 - A_0}$$

for Butterworth response,  $\frac{1}{\alpha} = 0.307$

$$A_0 = 1.586$$

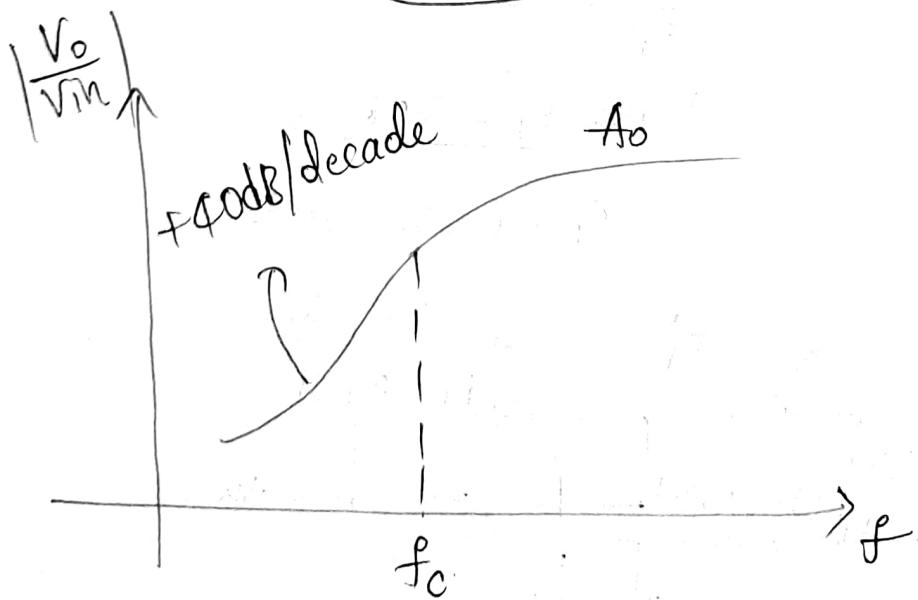

Q: Design a Butterworth Second order LPF with cutoff frequency of 1KHz.

- Sol:
- ① Select a value of capacitor  $C_C \leq 1\text{ uF}$ .
  - ② Assume  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$ .  
using eq,  $f_c = \frac{1}{2\pi RC}$ , find 'R'.
  - ③ passband gain = 1.586

$$1 + \frac{R_F}{R_1} = 1.586$$

$$C = 0.1\text{ uF}$$

$$f_c = \frac{1}{2\pi RC} \rightarrow 10^8 = \frac{1}{2\pi \times R \times 0.1 \times 10^{-6}}$$

$$R = \frac{10^4}{2\pi}$$

$$R \approx 1.6\text{ k}\Omega$$

$$1 + \frac{R_F}{R_1} = 1.586$$

$$\frac{R_F}{R_1} = 0.586$$


$$\text{Assume } R_1 = 50\text{ k},$$

$$R_F = 0.586 \times 50\text{ k}$$

$$50\text{ k} = R_1$$

$$R_F = 29.3\text{ k}$$


$$R_F = 29.8\text{ k}$$

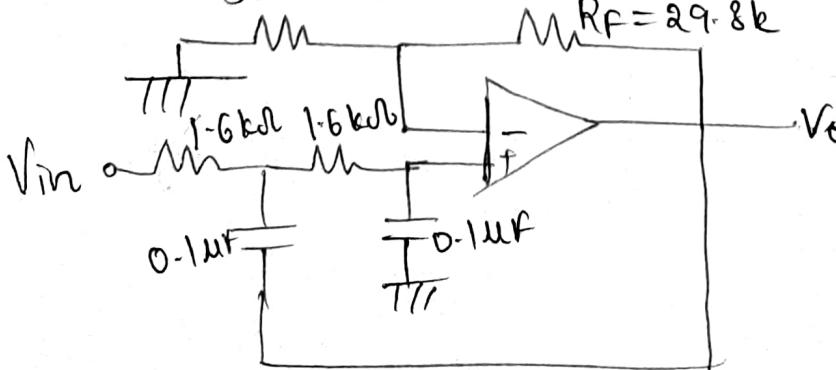

\* Butterworth filter (LPF):

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}}$$

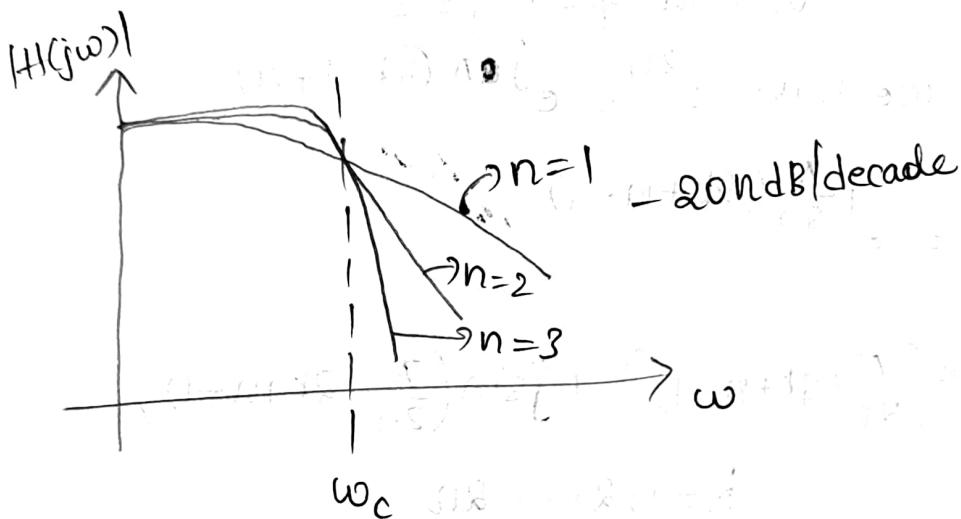$\omega_c \rightarrow$  cut-off frequency of the filter.  
 $n \rightarrow$  order of the filter.



\* Normalised Butterworth LPF:

$$|H_n(j\omega)| = \frac{1}{\sqrt{1 + \omega^{2n}}} \quad \text{where } \omega_c = 1 \text{ rad/s.}$$

$$|H_n(j\omega)|^2 = H_n(j\omega) \cdot H_n(-j\omega) = \frac{1}{1 + \omega^{2n}}$$

$$\text{Let } \omega = \frac{s}{j}$$

$$|H_n(j\omega)|^2 = H_n(j\omega) \cdot H_n(-j\omega) \\ = H_n(s) H_n(-s)$$

$$|H_n(j\omega)|^2 = \frac{1}{1 + \left(\frac{s}{j}\right)^{2n}}$$

→ The  $2n$  poles of  $H_n(s)H_n^*(s)$  occur,

when  $\left(\frac{s}{j}\right)^{2n} = -1$

$$s^{2n} = -(j)^{2n}$$

Since,  $-1 = e^{j\pi(2k-1)}$

for  $k$  integer &  $j = e^{j\pi/2}$


we have  $s^{2n} = e^{j\pi(2k-1+n)}$

$$s_k = e^{j\frac{\pi}{2n}(2k+n-1)}$$

$$s_k = \cos\left(\frac{\pi}{2n}(2k+n-1)\right) + j\sin\left(\frac{\pi}{2n}(2k+n-1)\right)$$

$$k=1, 2, \dots, 2n$$

Imaginary

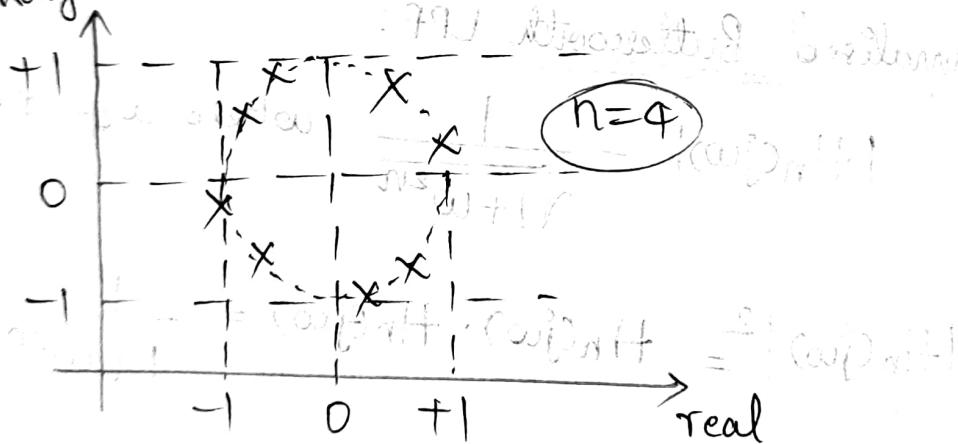

$n$  poles in LHP correspond to  $H_n(s)$

$n$  poles in RHP correspond to  $H_n(-s)$

For obtaining stable & causal filter

we set,

$$H_n(s) = \frac{1}{(s-s_1)(s-s_2)\dots(s-s_n)}$$

$$H_n(s) = \frac{1}{s^n + a_{n-1}s^{n-1} + \dots + a_1s + 1} = \frac{1}{B_n(s)}$$

Order(n)	factors of polynomial $B_n(s)$
1	$s + 1$
2	$s^2 + 1 \cdot 414s + 1$
3	$(s+1)(s^2+s+1)$
4	$(s^2+0.765s+1)(s^2+1.8478s+1)$
5	$(s+1)(s^2+0.6180s+1)(s^2+1.6180s+1)$
6	$(s^2+0.5176s+1)(s^2+1.4142s+1)$ $(s^2+1.9319s+1)$

### \* Scaling of Normalized filter:

① Replace ' $\omega$ ' with  $\frac{\omega}{\omega_c}$  in  $H_n(\omega)$

② Replace ' $s$ ' with  $\frac{s}{\omega_c}$  in  $H_n(s)$

$\omega_c \rightarrow$  cut-off frequency

Q: Design a 3rd order Butterworth LPF with cut-off frequency 1 kHz.

Sol:-


$$H_n(s) = \frac{1}{(s+1)(s^2+s+1)}$$

$$H_n(s) = \left( \frac{1}{s^2+s+1} \right) \left( \frac{1}{s+1} \right)$$

Let cut off angular frequency =  $\omega_0$

$$H_n(s) = \left[ \frac{1}{\left( \frac{s}{\omega_0} \right)^2 + \left( \frac{s}{\omega_0} \right) + 1} \right] \times \left[ \frac{1}{\left( \frac{s}{\omega_0} \right) + 1} \right]$$
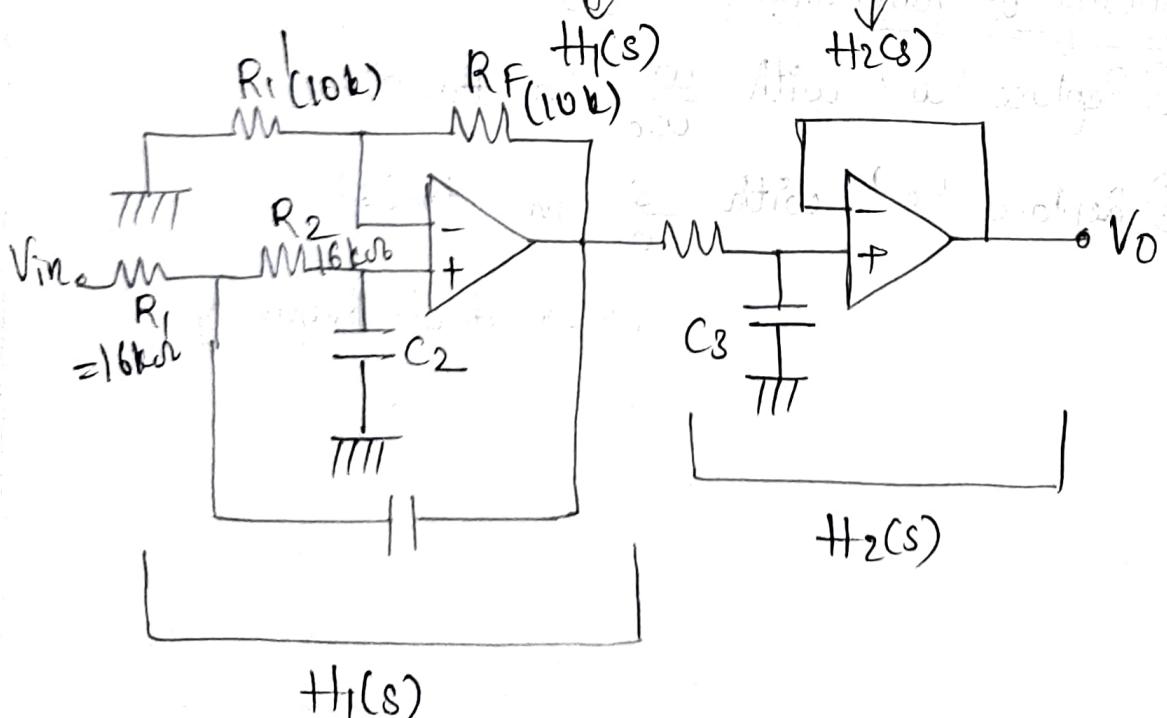
$$H_n(s) = \left( \frac{\omega_0^2}{s^2 + \omega_0 s + \omega_0^2} \right) \left( \frac{\omega_0}{s + \omega_0} \right)$$



when  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$

$$\omega_0 = \frac{1}{2\pi RC} = 1 \text{ kHz}$$

Assume,  $C = 0.01 \mu F$

$$R = \frac{1}{2\pi f_0 C} = 1000 \Omega$$

$$R \approx 16 k\Omega$$

$$H_1(s) = \frac{A_0 / R_1 R_2 C_1 C_2}{s^2 + s \left( \frac{R_1 C_2 + R_2 C_1 + R_1 A_0 (1 - A_0)}{R_1 R_2 C_1 C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

when  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$

$$H_1(s) = \frac{A_0 / R^2 C^2}{s^2 + s \left( \frac{3 - A_0}{R C} \right) + \frac{1}{R^2 C^2}}$$

Comparing  $H_1(s)$ ,  $\omega_0 = \frac{1}{RC}$

$$3 - A_0 = 1$$

$$A_0 = 2$$

$$1 + \frac{R_F}{R_1} = 2$$


$$\frac{R_F}{R_1} = 1 \rightarrow R_F = R_1 = 10 k$$

## \* Chebyshev filter (LPF):

$$H(j\omega) = \frac{1}{(1 + \epsilon^2 C_n^2 \left(\frac{\omega}{\omega_p}\right)^2)^{1/2}}$$

where  $\epsilon = (10^{\frac{A_{max}}{10}} - 1)^{1/2}$
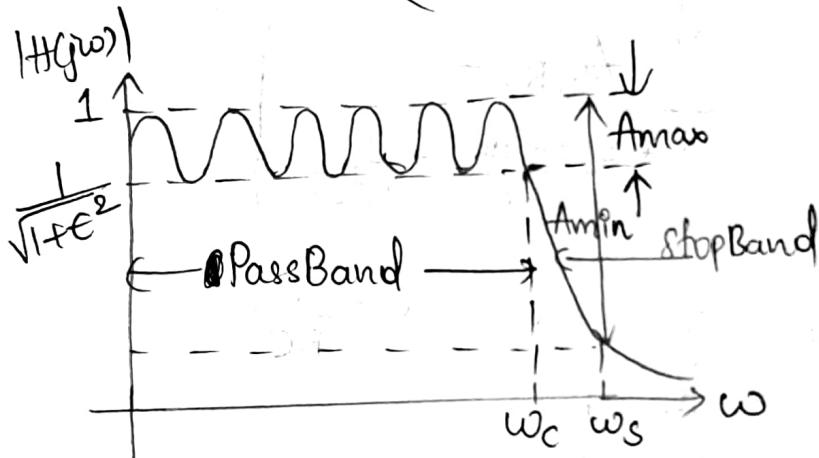
$$H_n(j\omega) = \frac{1}{(1 + \epsilon^2 C_n^2(\omega))^1}$$



$A_{max}$  &  $A_{min}$  are in dB.

$\omega_c = \omega_p =$  pass band edge

$\omega_s =$  stop band edge

$A_{max}$  — maximum passband attenuation

$A_{min}$  — minimum stopband attenuation

From the graph,

$$20 \log 1 - 20 \log \frac{1}{\sqrt{1+\epsilon^2}} = A_{max}$$

$$10 \log (1 + \epsilon^2) = A_{max}$$

$$1 + \epsilon^2 = 10^{A_{max}/10}$$

$$\epsilon = (10^{\frac{A_{max}/10}{10}} - 1)^{1/2}$$

$f(\omega^2) = \epsilon^2 C_n^2(\omega) \rightarrow$  chebyshev polynomial.

$$\begin{cases} c_n(\omega) = \cos(n \cosh^{-1}\omega) & \text{for } \omega \leq 1 \\ c_n(\omega) = \cosh(n \cosh^{-1}\omega) & \text{for } \omega > 1 \end{cases}$$

if  $n=0 \rightarrow c_0(\omega) = 1$

if  $n=1 \rightarrow c_1(\omega) = \omega$

$$C_{n+1}(\omega) = 2\omega C_n(\omega) - C_{n-1}(\omega)$$

$n$	$C_n(\omega)$
0	1
1	$\omega$
2	$2\omega^2 - 1$
3	$4\omega^3 - 8\omega$
4	$8\omega^4 - 8\omega^2 + 1$

$$\text{ripple width} = 1 - \frac{1}{(1+\epsilon^2)^{1/2}} = 10\%$$

### Order of Chebyshev filter (LPF):

Given  $A_{min}$ ,  $A_{max}$ ,  $\omega_s$ ,  $\omega_p$ , find  $c_n$ .

$$A_{min} = 10 \log (1 + \epsilon^2 C_n^2(\omega))$$

for  $\omega = \frac{\omega_s}{\omega_c} \rightarrow$  normalized

$$\epsilon^2 C_n^2(\omega) = \epsilon^2 (\cosh(n \cosh^{-1}\omega))^2$$

$$= 10 \log_{10} \frac{A_{min}/10}{1}$$

$$|A_{min}| = 10 \log_{10} (1 + \epsilon^2 (\cosh(n \cosh^{-1}\omega))^2)$$

Substitute  $\epsilon^2 = 10^{\frac{A_{max}/10}{10}} - 1$  in above eq,

$$\cosh(n \cosh^{-1} \omega) = \left[ \frac{10^{\frac{A_{\min}}{10} - 1}}{10^{\frac{A_{\max}}{10} - 1}} \right]^{\frac{1}{2}}$$

$$n > \cosh^{-1} \left[ \frac{(10^{\frac{A_{\min}}{10} - 1}) / (10^{\frac{A_{\max}}{10} - 1})}{\cosh^{-1} \left( \frac{\omega_s}{\omega_c} \right)} \right]^{\frac{1}{2}}$$

→ Poles,

$$1 + e^{\frac{2}{C_n^2(\omega)}} = 0$$

$$\sigma_k = (\tau_k) \pm j\omega_k$$

where  $k = 0, 1, 2, \dots, 2n-1$

$$\tau_k = \sinh a \sin \left( \frac{(2k+1)\pi}{2n} \right)$$

$$\omega_k = \cosh a \cos \left( \frac{(2k+1)\pi}{2n} \right)$$

$$\theta_k = \frac{(2k+1)\pi}{2n}$$

for  $k = 0, 1, 2, \dots, 2n-1$  &  $a = \frac{1}{n} \sinh^{-1} \left( \frac{1}{e} \right)$

$$\frac{\tau_k}{\sinh a} = \sin \left( \frac{(2k+1)\pi}{2n} \right)$$

$$\frac{\omega_k}{\cosh a} = \cos \left( \frac{(2k+1)\pi}{2n} \right)$$

$$\left( \frac{\tau_k}{\sinh a} \right)^2 + \left( \frac{\omega_k}{\cosh a} \right)^2 = 1$$

Q: The specification for chebyshev filter is given by,

$$A_{\min} = 20 \text{ dB},$$

$$A_{\max} = 3 \text{ dB}$$

$\frac{w_s}{w_c} = 1.5$ , determine order of the filter & confirm stopband requirement is fulfilled?

Solt

$$n > \cosh^{-1} \left[ \frac{(10^2 - 1)}{(10^0 - 1)} \right]^{1/2}$$

$$\cosh^{-1}(1.5)$$

$$n > \frac{\cosh^{-1}(9.97)}{\cosh^{-1}(1.5)}$$

$$n > 3.11$$

$$\text{choose } n=4, \epsilon = (10^{0.3} - 1)^{1/2} = 0.99 //$$

$$A_{\min} = 10 \log_{10} \left( 1 + 1^2 \{ \cosh(4 \cosh^{-1}(1.5)) \}^2 \right)$$

$$= 27.4 \text{ dB} \quad \text{Requirement is satisfied.}$$

Q: A chebyshev filter is required to provide the following specifications,

→ Passband max ripple width 0.5 dB up to 3 kHz

→ Stopband minimum to be 60 dB at 80 kHz

Solt Given  $A_{\max} = 0.5 \text{ dB}$   $w_c = 8 \text{ kHz} \times 2\pi$

$$A_{\min} = 60 \text{ dB} \quad w_s = 2\pi \times 30 \text{ kHz}$$

$$n > \cosh^{-1} \left[ \frac{(10^6 - 1)}{(10^{0.05} - 1)} \right]^{1/2}$$

$$\cosh^{-1}(10)$$

$$n > 2.89$$

$n=3$

$$\epsilon = \left(10 \frac{A_{max}}{10} - 1\right)^{1/2}$$

$$\boxed{\epsilon = 0.35}$$

$$a = \frac{1}{8} \sinh^{-1}\left(\frac{1}{0.35}\right) = 0.59$$

$$\theta_k = (2k+1) \frac{\pi}{8n}$$

$$\theta_0 = \frac{\pi}{6} = 80^\circ$$

$$\theta_1 = 90^\circ$$

$$s_1 = -8 \sinh a = -\sinh(0.59)$$

$$\boxed{s_1 = -0.625}$$

$$s_2 = -0.625 \sin 80^\circ \pm j 1.18 \cos 80^\circ$$

$$\boxed{s_2 = -0.313 \pm j(1.022)}$$

$$s_3 = +0.625 \sin 90^\circ \pm j(1.18) \cos 90^\circ$$

$$\boxed{s_3 = -0.625} \rightarrow \text{repeated root}$$

$$H(s) = \frac{K}{(s-s_1)(s-s_2)(s-s_3)}$$

$$H(s) = \frac{K}{(s+0.625)(s+0.313+j(1.022))(s+0.313-j(1.022))}$$

$$\boxed{H(s) = \frac{K}{(s+0.625)(s^2+0.625s+1.142)}}$$

where K value occurs when  $H(s) = 1$

$$\boxed{H(s) = \frac{0.625 \times 1.142}{(s+0.625)(s^2+0.625s+1.142)}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_N^2(\omega)}}$$

when  $\omega = 0$

$$C_N(\omega=0) = \cos(N \cos(0))$$


$$\boxed{C_N(\omega=0) = \cos(N \times \pi/2)}$$

when  $N \rightarrow \text{even}$

$$C_N(\omega=0) = \pm 1 \rightarrow |H(j\omega)| = \frac{1}{\sqrt{1+\epsilon^2}}$$

when  $N \rightarrow \text{odd}$

$$C_N(\omega=0) = 0 \rightarrow |H(j\omega)| = 1$$

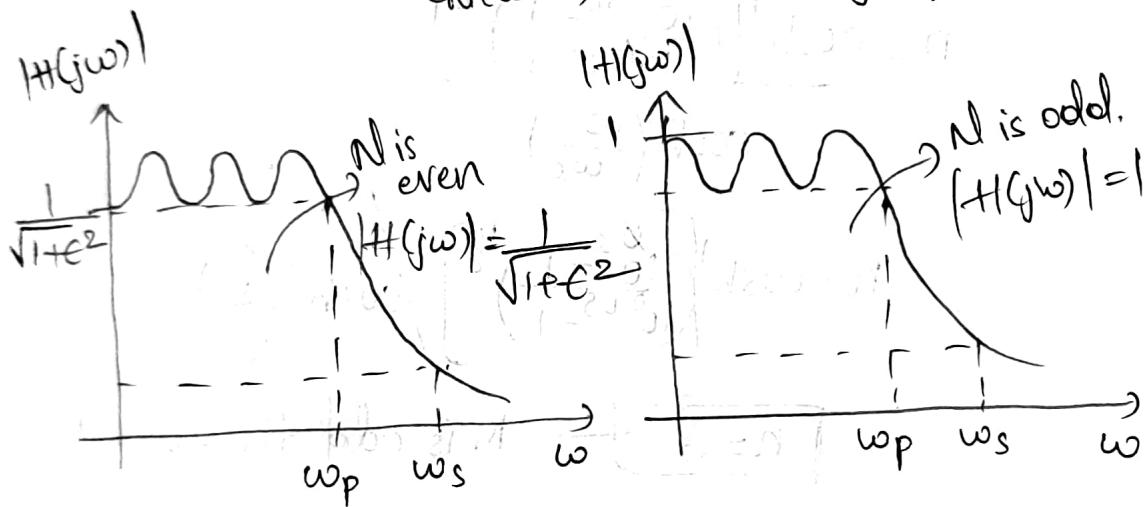

Q: Design a low pass filter with max gain of 5dB, with passband ripple of 0.5 dB & cut-off frequency of 2500 rad/s, stopband frequency of filter is 12,500 rad/s with stopband attenuation of 80dB or more.

Sol:-  $A_{max} = 5 \text{ dB}$      $A_{min} = 80 \text{ dB}$

$$\omega_p = 2500 \text{ rad/s}$$

$$\omega_s = 12,500 \text{ rad/s}$$

$$\epsilon = \left( 10^{\frac{A_{max}}{10}} - 1 \right)^{\frac{1}{2}} = \left( 10^{\frac{0.05}{10}} - 1 \right)^{\frac{1}{2}} = 0.349$$

$$n = \cosh^{-1} \left[ \left( \frac{10^{\frac{A_{min}}{10}} - 1}{10^{\frac{A_{max}}{10}} - 1} \right)^{\frac{1}{2}} \right]$$

$$\cosh^{-1} \left( \frac{\omega_s}{\omega_c} \right)$$

$$n = \cosh^{-1} \left[ \left( \frac{10^{\frac{0.05}{10}} - 1}{10^{\frac{0.05}{10}} - 1} \right)^{\frac{1}{2}} \right] / \cosh^{-1}(5)$$

$$\boxed{n=3} \rightarrow N \text{ is odd } + (s=0) = 1$$

$$H(s) = \frac{0.215}{(s+0.6264)(s^2+0.6264s+1.1424)}$$

$$20 \log_{10} x = 5$$


$$x = 10^{\frac{5}{20}} = 1.7783$$

Final transfer function is,

$$H(s) = \frac{0.215 \times 1.7783}{(s+0.6264)(s^2+0.6264s+1.1424)}$$

2nd order  
1st order

Second order filter,

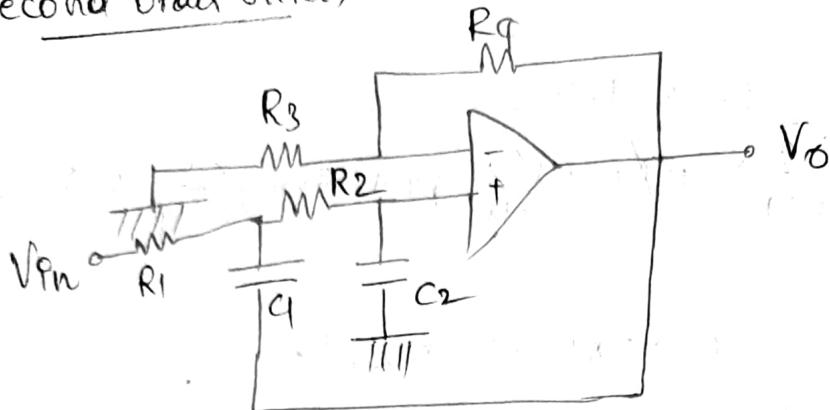

$$\frac{V_o(s)}{V_{in}(s)} = \frac{\frac{A_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{R_1 C_2 + R_2 C_1 + R_1 C_1 (1 - A_0)}{R_1 R_2 C_1 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

where  $R_1 = R_2 = R$  &  $C_1 = C_2 = C$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{\frac{A_0}{R^2 C^2}}{s^2 + \frac{1}{RC} s (3 - A_0) + \left( \frac{1}{RC} \right)^2}$$

On comparing,

$$\left( \frac{1}{RC} \right)^2 = 1.1424$$

$$RC = \sqrt{\frac{1}{1.1424}}$$

$$\frac{3 - A_0}{RC} = 0.6264$$

$$(3 - A_0) \times \sqrt{1.1424} = 0.6264$$

$$\underline{A_0 = 2.41}$$

Set  $A_0 = 1$ ,

$$\text{Then, } \frac{V_o(s)}{V_{in}(s)} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \left[ \frac{R_1 C_2 + R_2 C_1}{R_1 R_2 C_1 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

Since  $\omega_p = 2500 \text{ rad/s}$

$$s \rightarrow \frac{s}{\omega_p}, H(s) = \frac{0.215 \times 1.7783}{\left(\left(\frac{s}{\omega_p}\right)^2 + 0.6264\left(\frac{s}{\omega_p}\right) + 1.1424\right)\left(\frac{s}{\omega_p} + 0.6264\right)}$$

$$H(s) = \frac{0.215 \times 1.7783 \times \omega_p^2}{(s^2 + 0.6264\omega_p s + 1.1424\omega_p^2)(s + 0.6264\omega_p)}$$

On comparing,

$$\frac{1}{R_1 R_2 C_1 C_2} = 1.1424 \times \omega_p^2 = 1.1424 \times (2500)^2$$

$$\frac{R_1 C_2 + R_2 C_1}{R_1 R_2 C_1 C_2} = 0.6264 \times 2500$$

$$\frac{1}{C_1 C_2} = 1.1424 \times (2500) \times (10^{-6})^2$$

Assume  $C_1 = C_2 = 1 \mu F$

$$\frac{1}{R_1 R_2} = 1.1424 \times (2500)^2 \times (10^{-6})^2$$


$$\frac{1}{R_1 R_2} = 7.14 \times 10^{-6}$$

$$R_1 R_2 = \frac{10^6}{7.14}$$

$$\frac{C_2(R_1 + R_2)}{R_1 R_2} = 0.6264 \times 2500$$

$$10^{-6}(R_1 + R_2) \times 7.14 \times 10^{-6} = 0.6264 \times 2500$$

Let  $R_1 = R_2 = R$

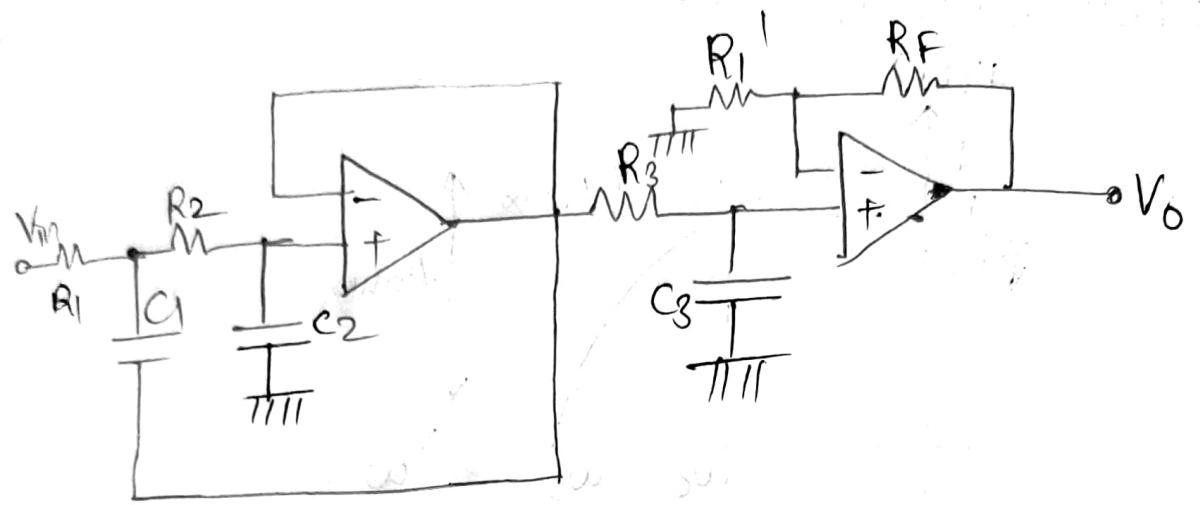

op-amp bandwidth =  $\omega_n$   
before bypassing the  $C_2$

so  $\omega_n = \frac{1}{R_2 C_2}$   $\text{rad/sec}$   
so  $\omega_n = \frac{1}{(R_2 + R_f) C_2}$   $\text{rad/sec}$

$$\omega_n = \frac{1}{(R_2 + R_f) C_2} = \frac{1}{(R_2 + R_f) \cdot 10^{-6}}$$

$$10^6 = \frac{1}{(R_2 + R_f) \cdot 10^{-6}}$$

$$10^{12} = (R_2 + R_f) \cdot 10^{-6}$$

$$10^{12} = 10^6 \cdot 34$$

$$10^6 = (R_2 + R_f) \cdot 10^6$$


$$10^6 = (R_2 + R_f) \cdot 10^6$$

so  $R_2 + R_f = 10^6 \Omega$   $\text{each}$   
so  $R_2 = 10^6 \Omega$   $\text{each}$

so  $R_f = 10^6 \Omega$

$$R_f = 10^6 \Omega$$

## Butterworth Approximation:

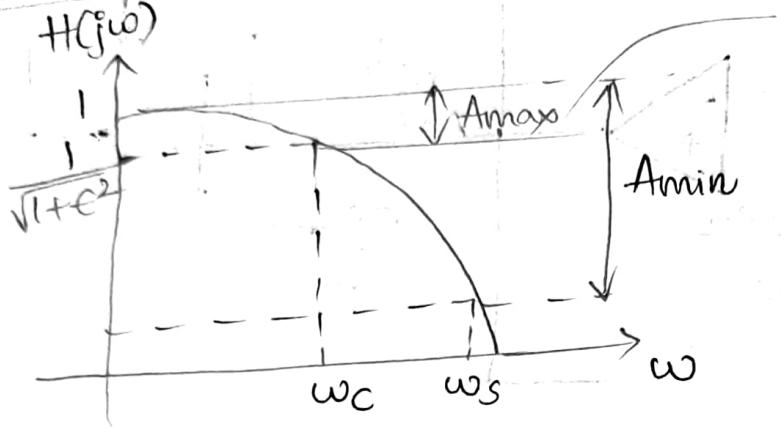

$w_c \rightarrow$  passband edge

$w_s \rightarrow$  stopband edge

$A_{\text{max}} \rightarrow$  Maximum passband attenuation. } (dB)

$A_{\text{min}} \rightarrow$  Minimum stopband attenuation. }

$$|H(j\omega)| = \frac{1}{\sqrt{1+\epsilon^2\omega^{2n}}}$$

$$|A_{\text{max}}| = 10 \log_{10} (1 + \epsilon^2)$$

$$\epsilon = \left( 10^{\frac{A_{\text{max}}}{10}} - 1 \right)^{1/2} \quad \textcircled{1}$$

$$\text{At } \omega = \frac{w_s}{w_c}$$

$$|A_{\text{min}}| = 10 \log_{10} (1 + \epsilon^2 \omega^{2n}) \quad \textcircled{2}$$

Substituting eq \textcircled{1} in \textcircled{2}

$$A_{\text{min}} = 10 \log_{10} \left( 1 + \frac{10^{A_{\text{max}}/10}}{10^{\frac{A_{\text{min}}}{10}}} - 1 \right) (\omega^{2n})$$

$$\omega^{2n} = \left\{ \frac{10^{\frac{A_{\text{min}}}{10}} - 1}{10^{\frac{A_{\text{max}}}{10}} - 1} \right\}$$

$$\omega = \frac{w_s}{w_c}$$

$$n = \frac{1}{2 \log_{10} \left( \frac{\omega_s}{\omega_c} \right)} \times \log_{10} \left\{ \frac{\frac{A_{min}/10}{-1}}{\frac{A_{max}/10}{-1}} \right\}$$

Q: A Butterworth LPF is required to provide the following specifications passband upto 10 kHz with 3dB of loss, stopband to be at least 100 dB down at 100 kHz. Calculate the order of filter & roots of butterworth polynomials.

Sol:  $A_{max} = 8 \text{ dB}$

$A_{min} = 100 \text{ dB}$

$f_s = 100 \text{ kHz}$

$f_c = 10 \text{ kHz}$

$n = 5,$


$$H(s) = \frac{1}{(s+1)(s^2 + 1.618s + 1)(s^2 + 0.618s + 1)}$$

# Bandpass filters

Wideband pass  
( $Q < 10$ )

$$Q = \frac{f_c}{B.W}$$

Wideband

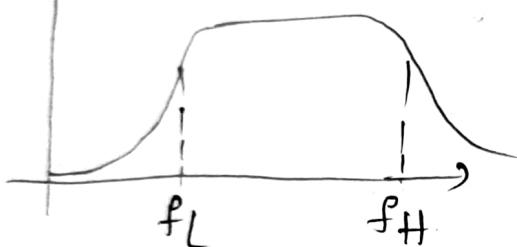


Narrow band pass  
( $Q > 10$ )

→ Bandwidth is much smaller than the center frequency. The quality factor is very large. The filter is highly selective.


$$\begin{aligned} Q &= \frac{f_c}{B.W} \\ &= \frac{f_c}{f_H - f_L} \\ &= \frac{f_c}{\Delta f} \\ &= \frac{f_c}{\frac{1}{2\pi C_0 L}} = 2\pi C_0 L f_c \\ &= 2\pi C_0 L \cdot \omega_c \\ &= 2\pi C_0 L \cdot \omega_c \cdot \sqrt{1 + (\frac{R}{2L})^2} \end{aligned}$$

→ Wideband pass filters:

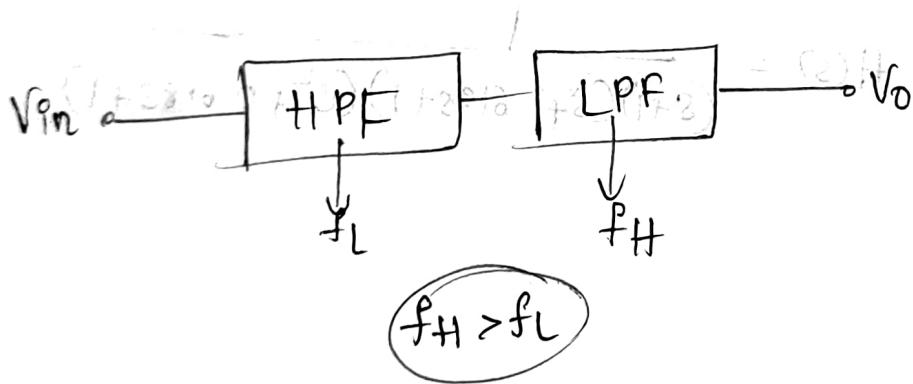

Q: Design a widebandpass filter so that,  
 $f_L = 200\text{Hz}$ ,  $f_H = 1\text{kHz}$  & passband gain=4

SOL:

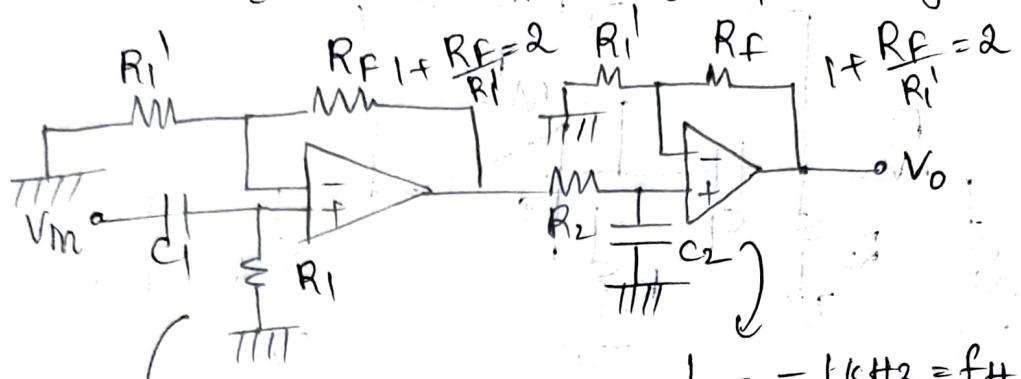

$$\frac{1}{2\pi R_2 C_2} = 1\text{kHz} = f_H$$

$$C_2 = 0.1\mu\text{F}$$

$$C_1 = 0.1\mu\text{F}$$

$$R_2 = \frac{1}{2\pi \times 10^3 \times 10^3}$$

$$R_1 = \frac{1}{2\pi \times 10 \times 200} \approx 8\text{k}\Omega$$


$$R_1 \approx 1.6\text{k}\Omega$$

$$Q = \frac{f_C}{BW} = \frac{\sqrt{f_L f_H}}{(f_H - f_L)} = 0.56 //$$

Design  
Must AC


AC Design  
must AC

## Narrow Bandpass Filter:

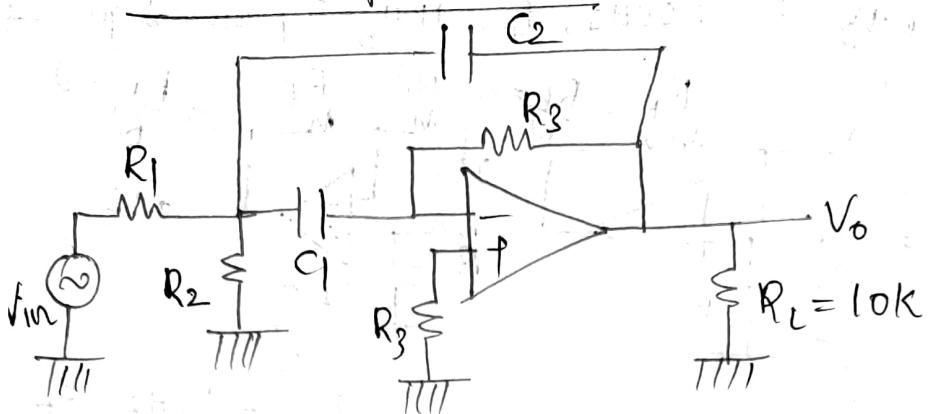

At low frequencies,  $\omega = 0$ ,

Impedance is  $\infty$

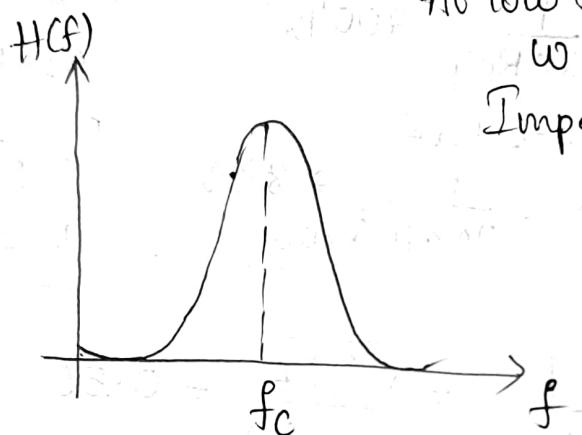

Given  $f_c$ ,  $Q$ , B.W. Design equations are

Assume  $C_1 = C_2 = C$

$$R_1 = \frac{Q}{2\pi f_c C A_f}$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_f)}$$

$$R_3 = \frac{Q}{\pi f_c C}$$

$$\text{Passband gain} = A_f = \frac{R_3}{2R_1} \quad A_f < 2Q^2$$

Condition must be satisfied.

Center frequency  $f_c$  can be changed to new center frequency  $f'_c$ , keep gain & B.W. constant by changing  $R_2$  to  $R'_2$ .

$$R'_2 = R_2 \left( \frac{f_c}{f'_c} \right)^2$$

Q: (a) Design a narrow bandpass filter with  $f_C = 1\text{kHz}$

$$Q = 8, A_F = 10$$

(b) change the center freq to 1.5 kHz keeping  $A_F \& B.W$  constant.

Solt:  $C_1 = C_2 = C = 0.01\mu\text{F}$

$$R_1 = 4.72\text{k}\Omega$$

$$R_2 = 5.97\text{k}\Omega$$

$$R_3 = 95.5\text{k}\Omega$$

$$R_2' = 5.97 \times \left( \frac{1\text{k}}{1.5\text{k}} \right)^2 = 2.65\text{k}\Omega$$

## Band Reject filters (Band stop)



Wideband  
( $Q < 10$ )

$$Q = \frac{f_c}{B.W}$$

Narrow band  
( $Q > 10$ )


$$Q = \frac{f_c}{B.W}$$

→ Wideband reject filter

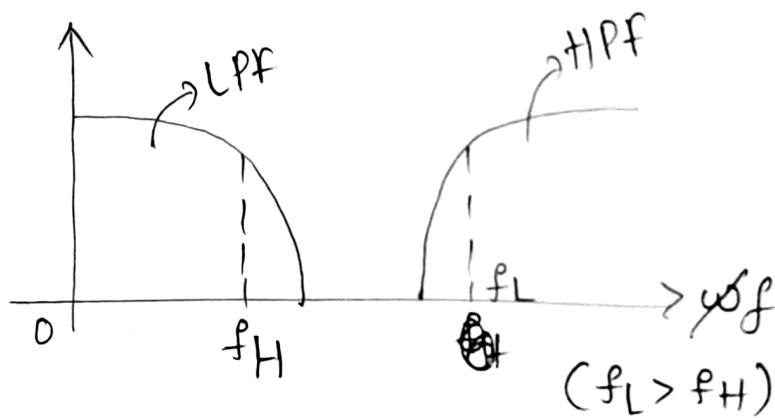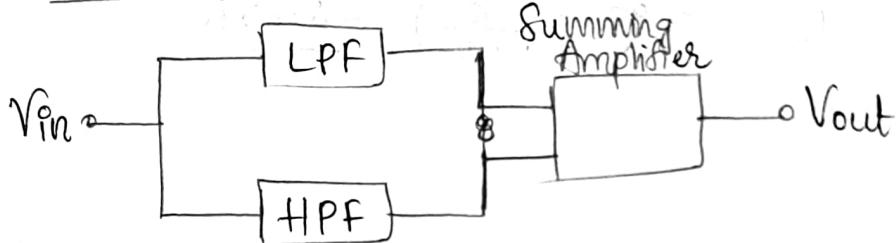


→ Narrow Band Reject filter: (Notch filter)

→ It is called as  
Twin-T network.

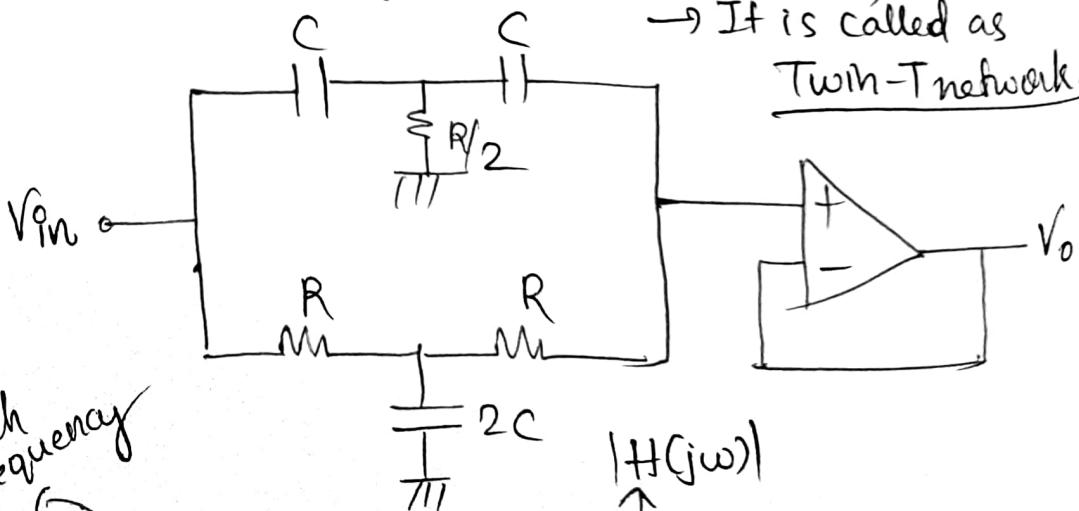


Notch frequency

$$f_N = \frac{1}{2\pi RC}$$

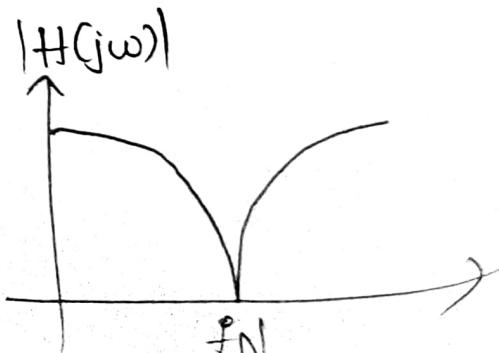

Q: Design a wide band reject filter with  $f_H = 200\text{Hz}$   
and  $f_L = 1\text{kHz}$

Solt

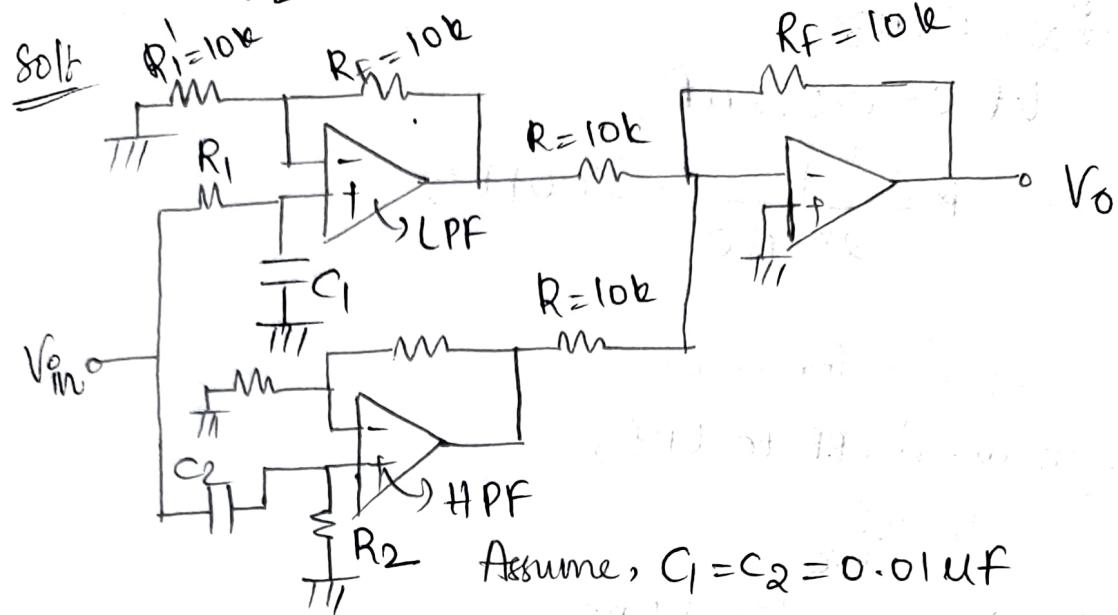

$$\frac{1}{2\pi R_1 C_1} = 200$$

$$R_1 = \frac{1}{2\pi \times 200 \times 10^{-8}}$$

$$\underline{R_1 = 79.5\text{k}\Omega}$$

$$\frac{1}{2\pi R_2 C_2} = 1000$$

$$R_2 = \frac{1}{2\pi \times 10 \times 10^{-8}}$$

$$\underline{R_2 = 15.9\text{k}\Omega}$$

Q: Design a 60Hz active notch filter

Solt  $f_N = 60\text{Hz}$

let  $C = 0.068\mu\text{F}$

$$R = \frac{1}{2\pi f_N C} = \frac{89.01\text{k}\Omega}{}$$

### \* Frequency Transformations:

#### ① Normalised LPF to LPF,

$$s \rightarrow \frac{s}{\omega_c}$$

$H(s) \rightarrow$  Normalized LPF

$$\text{LPF} \leftarrow H(s) = H\left(\frac{s}{\omega_c}\right)$$

#### ② Normalised LPF to HPF,

$$s \rightarrow \frac{\omega_c}{s} \quad H(s) \rightarrow \text{Normalized LPF}$$

$$H^1(s) = H\left(\frac{\omega_c}{s}\right) \rightarrow \text{HPF}$$

#### ③ Normalised LPF to BPF,

$$s \rightarrow \frac{s^2 + \omega_l \omega_h}{s(\omega_h - \omega_l)}$$

$$H^1(s) = H\left(\frac{s^2 + \omega_l \omega_h}{s(\omega_h - \omega_l)}\right) \rightarrow \text{Band pass filter.}$$


#### ④ Normalised LPF to BSF,

$$s \rightarrow \frac{s(\omega_h - \omega_l)}{s^2 + \omega_l \omega_h}$$

$$H^1(s) = H\left(\frac{s(\omega_h - \omega_l)}{s^2 + \omega_l \omega_h}\right) \rightarrow \text{Band stop filter.}$$

Q: A Butterworth HPF has  $f_C = 60 \text{ MHz}$ ,  $f_S = 80 \text{ MHz}$ ,  $A_{\min} = 40 \text{ dB}$ ,  $A_{\max} = 8 \text{ dB}$ . Find order of filter.

Sol:

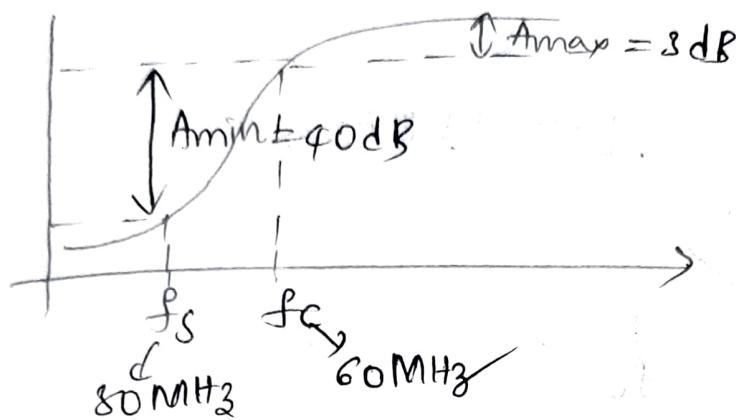


$$n = \frac{1}{2 \log_{10} \left( \frac{\omega_C}{\omega_S} \right)} \times \log_{10} \left( \frac{10^{\frac{A_{\min}}{10}} - 1}{10^{\frac{A_{\max}}{10}} - 1} \right)$$

$$\underline{n = 6.64}$$

Q: A chebyshov HPF has  $f_c = 60 \text{ MHz}$ ,  $A_{\min} = 40 \text{ dB}$   
 $f_s = 30 \text{ MHz}$ ,  $A_{\max} = 0.5 \text{ dB}$

Find order of filter.



Solt:

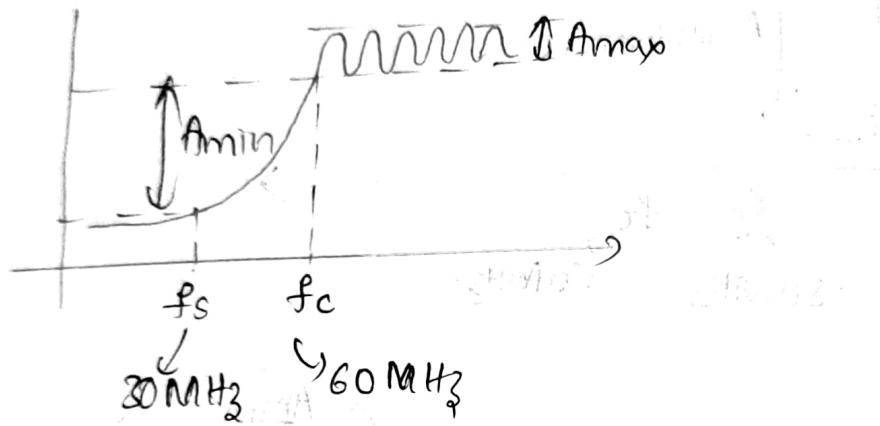

$$n_b = \frac{\cosh^{-1}\left(\frac{A_{\min}}{10^{10}-1}/\frac{A_{\max}}{10^{10}-1}\right)}{\cosh^{-1}\left(\frac{w_s}{w_c}\right)}$$



Normalized  
HPF.


# IC555:

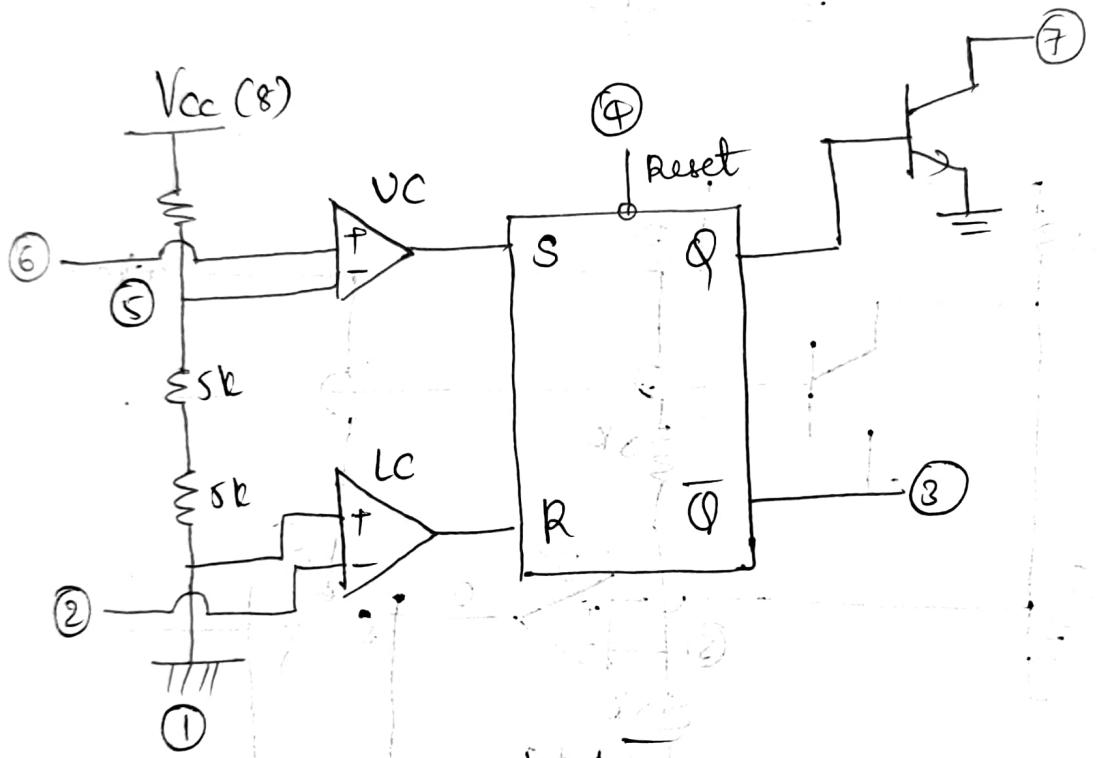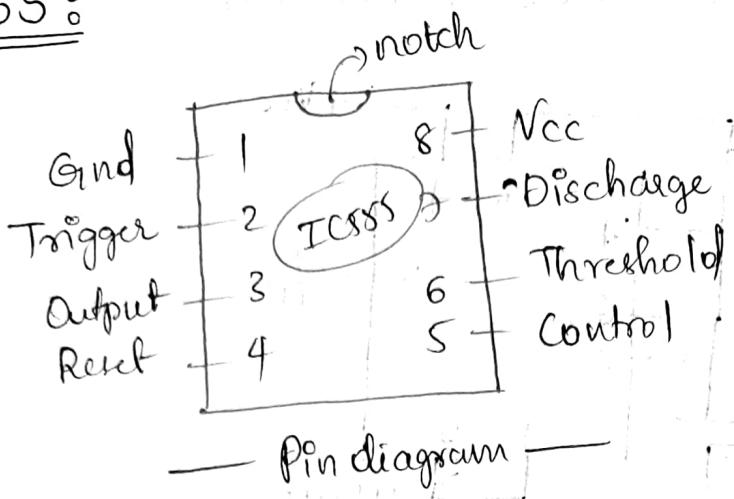

S	R	Q	$\bar{Q}$
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1		Invalid

# (\*) IC555 as monostable multivibrator

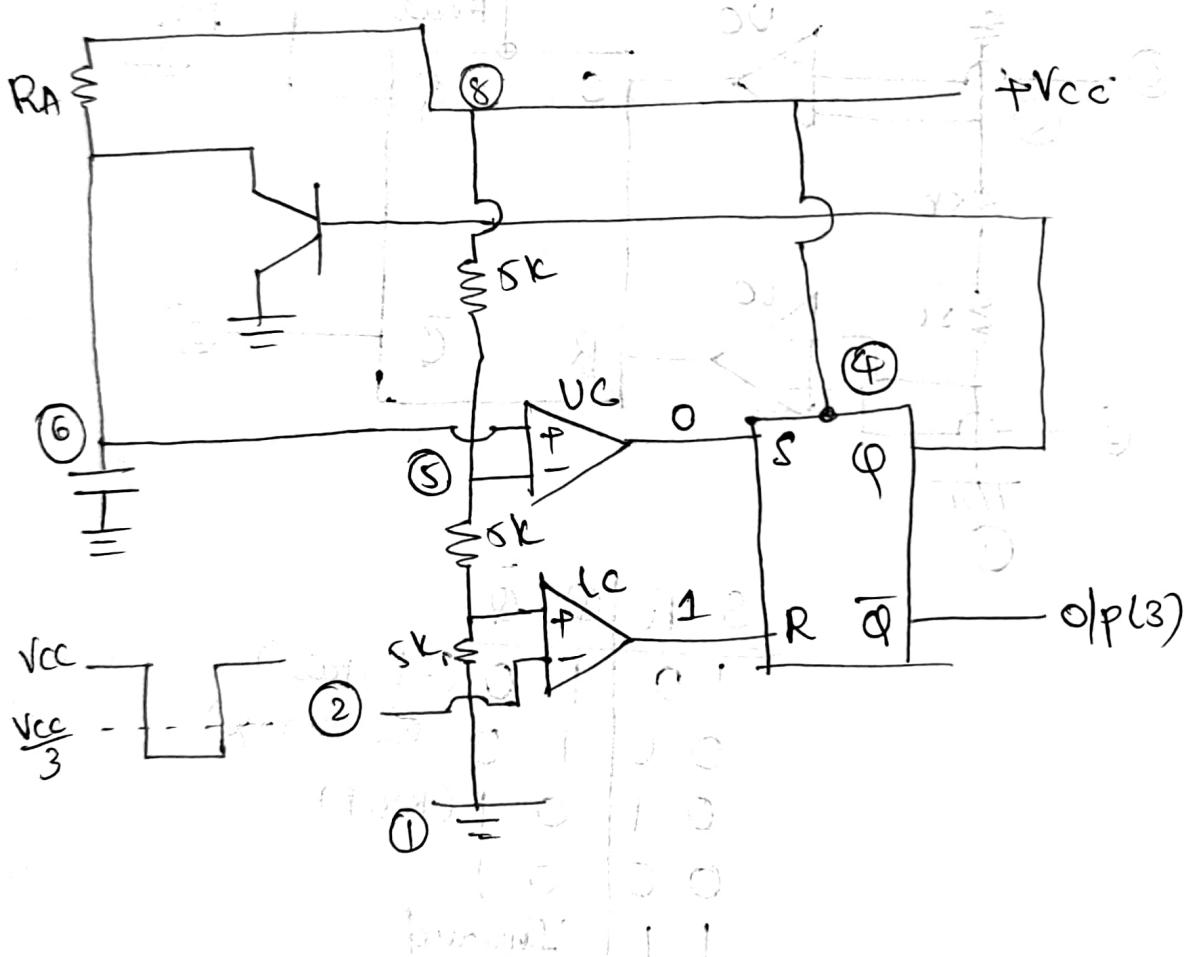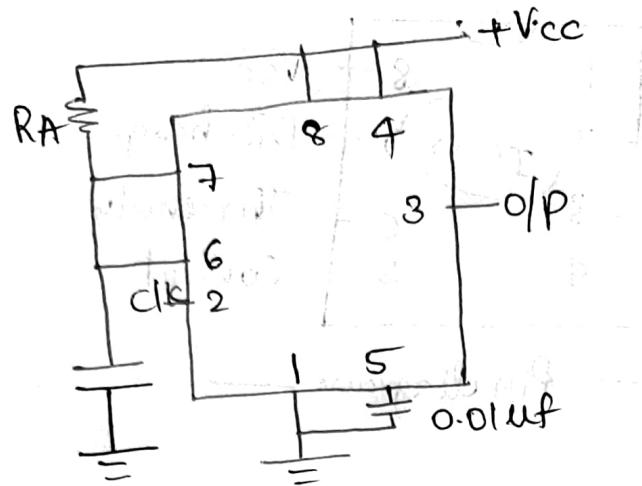

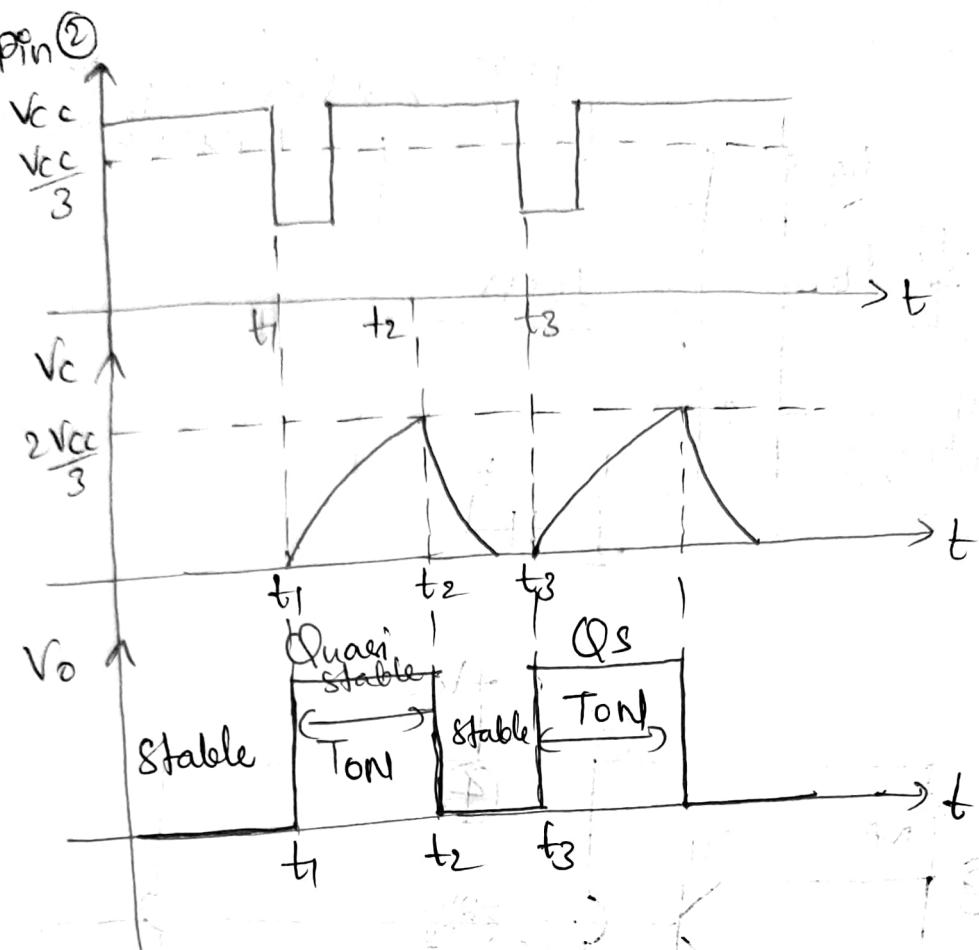

Time duration ( $T_{ON}$ )

$$V_c = V_{CC} \left( 1 - e^{-t/RC} \right)$$




$$\text{at } t = T_{ON}, V_c = \frac{2V_{CC}}{3}$$

$$\frac{2V_{CC}}{3} = V_{CC} \left( 1 - e^{-T_{ON}/R_A C} \right)$$

$$\underline{T_{ON} = 1.01 R_A C}$$



# Astable operation using IC555 timer:

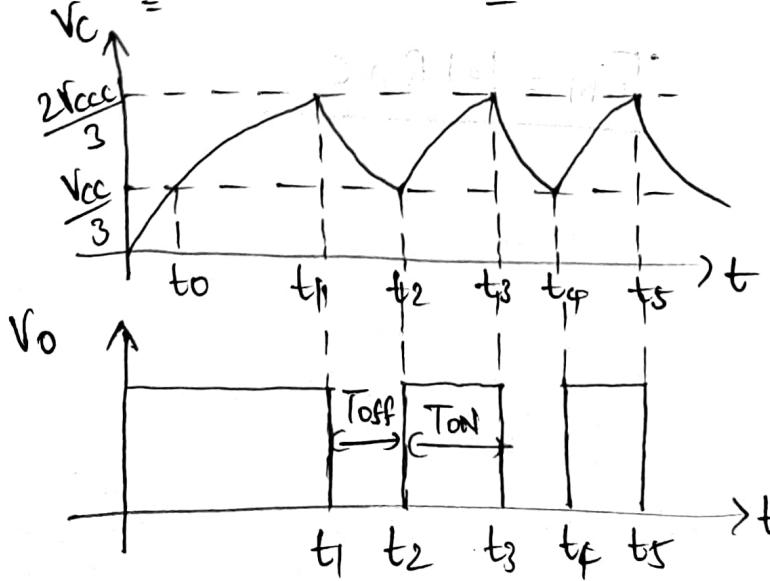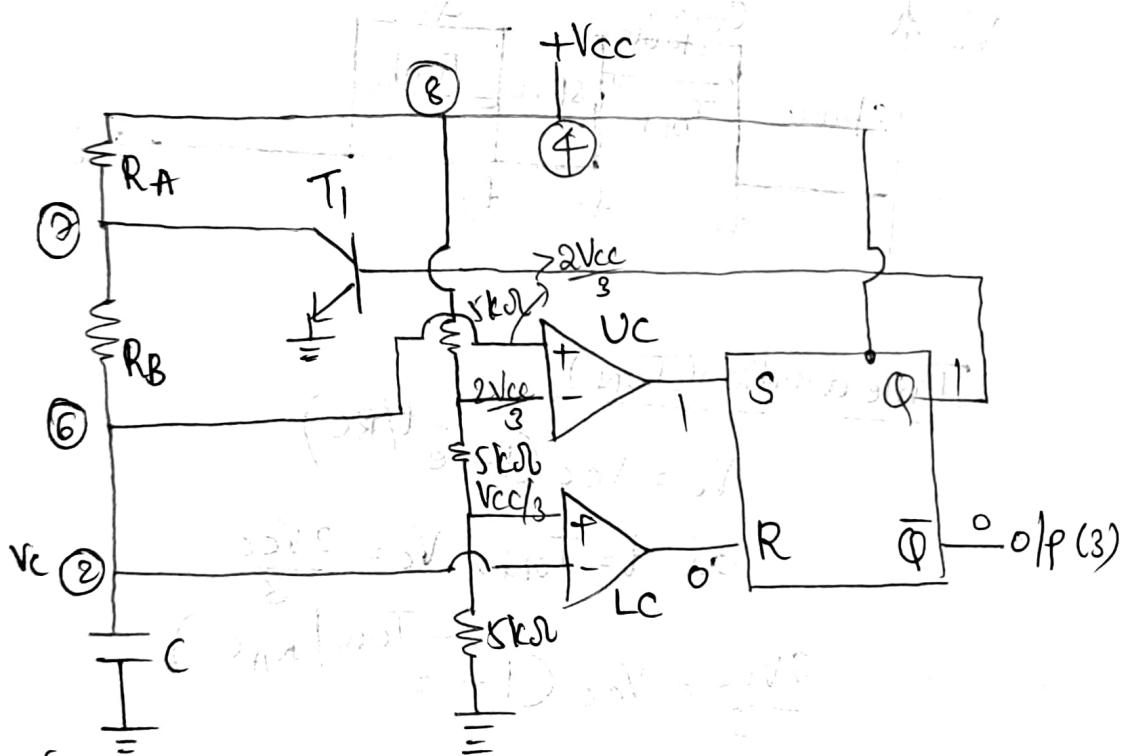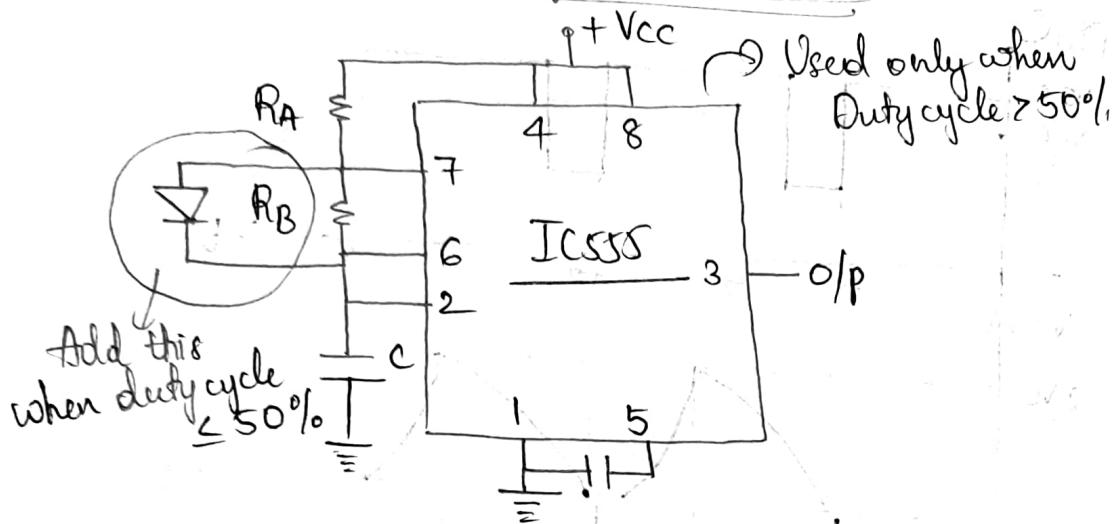

$T_{ON}(t_2 - t_3)$

$$R_A \frac{1}{I} \\ R_B \frac{1}{I} \\ C \frac{1}{I}$$

$$T_{ON} = 0.693(R_A + R_B)C$$

$T_{OFF}(t_1 - t_2)$

$$R_B \frac{1}{I} \\ V_C \frac{1}{I}$$

$$T_{OFF} = 0.693 R_B C$$

Time period ( $T$ ) =  $T_{ON} + T_{OFF}$

$$T = 0.693(R_A + 2R_B)C$$

$$f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

Frequency of oscillation.

Duty cycle ( $D$ ) =  $\frac{T_{ON}}{T}$

$$= \frac{0.693(R_A + R_B)C}{0.693(R_A + 2R_B)C}$$

$$(D) = \frac{R_A + R_B}{R_A + 2R_B}$$

Q: Design a astable multivibrator using IC555 timer which generates a signal with frequency 1kHz & duty cycle 75%.

Solt:  $f = 1\text{kHz} = \frac{1.45}{(R_A + 2R_B)C}$

$$(R_A + 2R_B)C = 1.45 \times 10^{-3} \quad \text{--- (1)}$$

$$D = \frac{R_A + R_B}{R_A + 2R_B} = 0.75$$

$$(R_A + R_B) = 0.75(R_A + 2R_B)$$

$$R_A(0.75) = R_B(1.5 - 1)$$

$$\boxed{R_A = 2R_B}$$

from (1),  $4R_B C = 1.45 \times 10^{-3}$

Assume  $C = 0.1 \mu\text{F}$

$$4R_B(10^{-9}) = 1.45 \times 10^{-3}$$

$$4R_B = 1.45 \times 10^6$$

$$R_B = 1.45 \times 25 \times 10^2$$

$$\boxed{R_B = 3625 \Omega}$$

$$\boxed{R_A = 7.25 \text{ k}\Omega}$$

$$\boxed{R_B = 3.625 \text{ k}\Omega}$$

Q) Design a astable multivibrator using IC555 timer which generates a signal with  $f = 1k\text{Hz}$  &  $D = 25\%$

Solt

$$\left. \begin{array}{l} T_{ON} = 0.693 R_A C \\ T_{OFF} = 0.693 R_B C \end{array} \right\} \text{when } D \leq 50\%$$

$$T = 0.693 (R_A + R_B) C$$

$$D = \frac{T_{ON}}{T} = \frac{R_A}{R_A + R_B}$$

$$f = 1\text{kHz} = \frac{1.45}{(R_A + R_B) C}$$

$$(R_A + R_B) C = 1.45 \times 10^{-3} \quad \text{--- (1)}$$

$$0.25 = \frac{R_A}{R_A + R_B}$$

$$0.25 R_B = 0.25 R_A$$

$$R_B = 3 R_A$$

from (1),


$$4R_A C = 1.45 \times 10^{-3}$$

$$\text{Assume } C = 0.1\mu\text{F}$$

$$4R_A (10^{-8}) = 1.45 \times 10^{-3}$$

$$\frac{R_A = 3.625 \text{k}\Omega}{R_B = 10.875 \text{k}\Omega}$$


## • PHASE LOCKED LOOP:

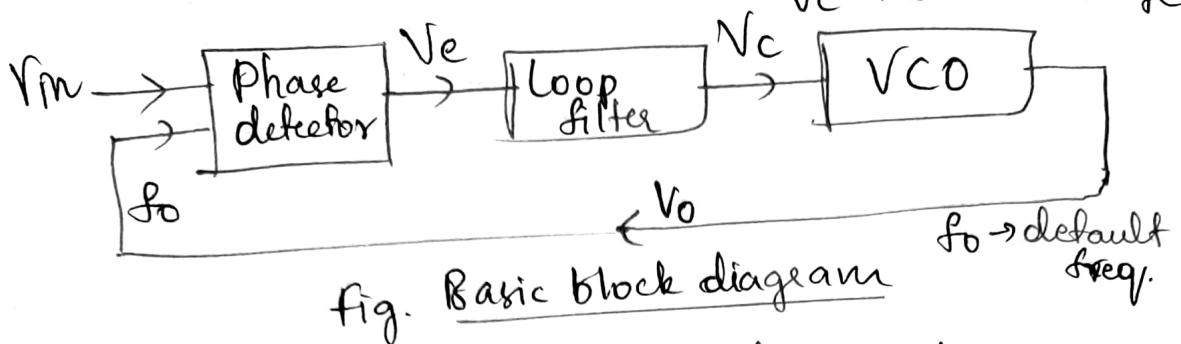

$VCO \rightarrow$  Voltage Controlled Oscillator.
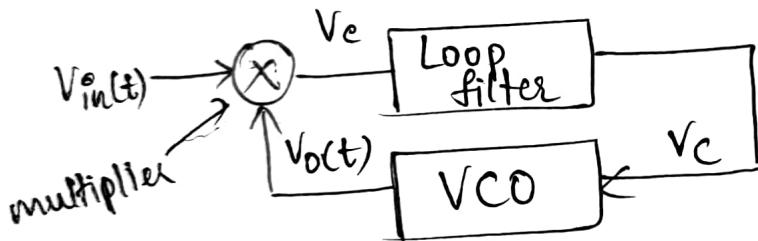
### → Modes of operation:

- ① free running state. ( $f_0$ )
- ② Capture state (when  $V_{in}$  is non-zero)
- ③ Lock state. ( $VCO$  frequency has changed to  $f_l$  from  $f_0$ )



$$e(t) \rightarrow VCO \rightarrow B \cos(\omega_c t + \theta_o(t))$$

$$VCO \text{ o/p} \rightarrow V_o(t) = B \cos(\omega_c t + \theta_o(t))$$

$$\begin{aligned} \text{Instantaneous angular freq of VCO o/p} \\ = \dot{\omega}_c + \dot{\theta}_o(t) \end{aligned}$$

$$\text{where, } \dot{\theta}_o(t) = c e(t)$$

$$\text{when } e(t) = 0 \rightarrow \dot{\theta}_o(t) = 0$$

so, instantaneous angular freq  
of VCO o/p is  $\omega_c = 2\pi f_c$

where  $f_c \rightarrow$  free running frequency of VCO.

$$\text{Let } V_{in}(t) = A \sin(\underline{\omega_i t} + \psi_0) = A \sin(\underline{\theta_i(t)} + \underline{\omega_i t})$$

$$V_{in}(t) = A \sin(\underline{\omega_c t} + (\omega_i - \omega_c)t + \psi_0)$$

$$\boxed{\theta_i^o(t) = (\omega_i - \omega_c)t + \psi_0}$$

$$\theta_i^o(s) = \frac{(\omega_i - \omega_c)}{s^2 + \omega_c^2} + \frac{\psi_0}{s}$$

$$V_o(t) = B \cos(\underline{\omega_c t} + \theta_o(t))$$

$$V_e(t) = AB \sin(\underline{\omega_c t} + \theta_i^o(t)) \cos(\underline{\omega_c t} + \theta_o(t))$$


$$V_e(t) = \frac{1}{2} AB \left[ \sin(\theta_i^o(t) - \theta_o(t)) + \sin(2\underline{\omega_c t} + \theta_i^o(t) + \theta_o(t)) \right]$$

Since loop filter is LPF,

$$V_c = \frac{1}{2} AB \left[ \sin(\theta_i^o(t) - \theta_o(t)) \right]$$

Let  $H(s)$  be Transfer function of loop filter,

In terms of phase,

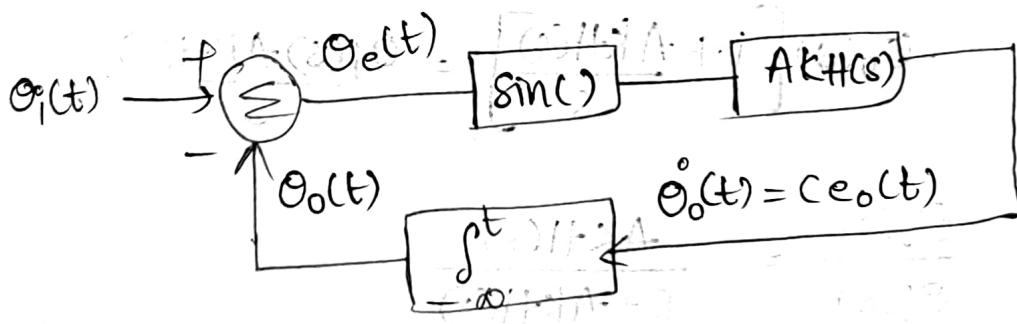

$$\theta_o^o(t) = ce_o(t)$$

$$e(t) = h(t) * \frac{1}{2} AB \sin(\theta_i^o(t) - \theta_o(t))$$


$$ce(t) = ch(t) * \frac{1}{2} AB \sin(\theta_i^o(t) - \theta_o(t))$$

$$\Theta_0(t) = C \theta_e(t) \quad (K = \frac{1}{2} CB)$$

$$\dot{\Theta}_0(t) = \frac{CAB}{2} \int_{-\infty}^t h(t-x) \sin(\Theta_i(x) + \Theta_0(x)) dx$$

$$\dot{\Theta}_0(t) = AK \int_{-\infty}^t h(t-x) \sin(\theta_e(t)) dx$$

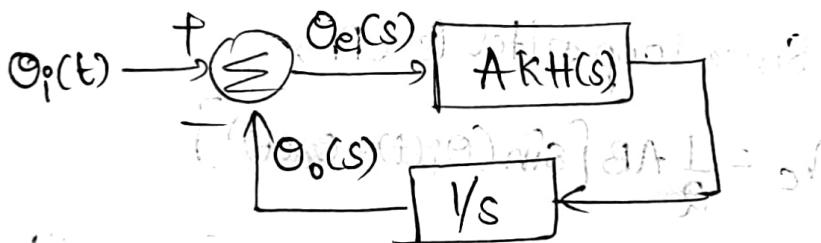If  $\sin(\theta_e(t)) \approx \theta_e(t)$ , then  
 entire circuit becomes linear & we can apply convolution. Assume  $\theta_e(t) \ll \pi/2$ , then  
 $\sin(\theta_e) \approx \theta_e$



$$\Theta_0(s) = [\Theta_i(s) - \Theta_0(s)] \frac{AKH(s)}{s}$$

$$\Theta_0(s) \left[ 1 + \frac{AKH(s)}{s} \right] = \frac{\Theta_i(s) AKH(s)}{s}$$

$$\frac{\Theta_0(s)}{\Theta_i(s)} = \frac{AKH(s)}{s + AKH(s)}$$

$$\Theta_e(s) = \Theta_i(s) - \Theta_0(s)$$

$$\Theta_e(s) = \frac{s \Theta_i(s)}{s + AKH(s)}$$

$$\Theta_i(t) = (\omega_0 - \omega_c)t + \Psi_0$$

$$\Theta_i(s) = \frac{\omega_i - \omega_c}{s^2} + \frac{\Psi_0}{s}$$

$$\Theta_e(s) = \frac{s}{s+Ak} \left[ \frac{\omega_i - \omega_c}{s^2} + \frac{\Psi_0}{s} \right]$$

Let  $H(s) = 1$ , (1st order LPF)

$$\Theta_e(s) = \frac{s}{s+Ak} \left[ \frac{\omega_i - \omega_c}{s^2} + \frac{\Psi_0}{s} \right]$$

$$\Theta_e(s) = \frac{\omega_i - \omega_c}{s(s+Ak)} + \frac{\Psi_0}{(s+Ak)}$$

$$\Theta_e(t) = \frac{\omega_i - \omega_c/Ak}{s} - \frac{(\omega_i - \omega_c)/Ak}{(s+Ak)}$$

$$+ \frac{\Psi_0}{(s+Ak)}$$

$$\Theta_e(t) = \frac{\omega_i - \omega_c}{Ak} - \frac{(\omega_i - \omega_c)}{Ak} e^{-Akt} + \Psi_0 e^{-Akt}$$

$\boxed{\lim_{t \rightarrow \infty} \Theta_e(t) = \left( \frac{\omega_i - \omega_c}{Ak} \right)}$  → steady state response.

$$\text{Let } H(s) = \frac{s+a}{s}$$

$$\Theta_e(s) = \frac{s}{s+Ak\left(\frac{s+a}{s}\right)} \left[ \frac{\omega_i - \omega_c}{s^2} + \frac{\Psi_0}{s} \right]$$

from final value theorem,

$$\Theta_e(t=\infty) = \lim_{s \rightarrow 0} s \Theta_e(s)$$

$$\Theta_e(t=\infty) = 0$$

There is an exact phase difference of  $\pi/2$  between i/p & o/p.

### IC PLL 565

(3A+3) (3A+2) 1


	1	2	3	4	5	6	7	8
-Vcc								
input								
input								
VCO o/p								
phase comparator								
Reference o/p								
Demodulated o/p								
External o/p								

NE/SE 565

14 (Nc),  
13 (Nc)  
12 (Nc)  
11 (Nc)  
10 (+Vcc)  
9 (External capacitor  
for VCO)  
8 (External resistor  
for VCO)

Pin Diagram

→ NE/SE 565 PLL Block diagram:

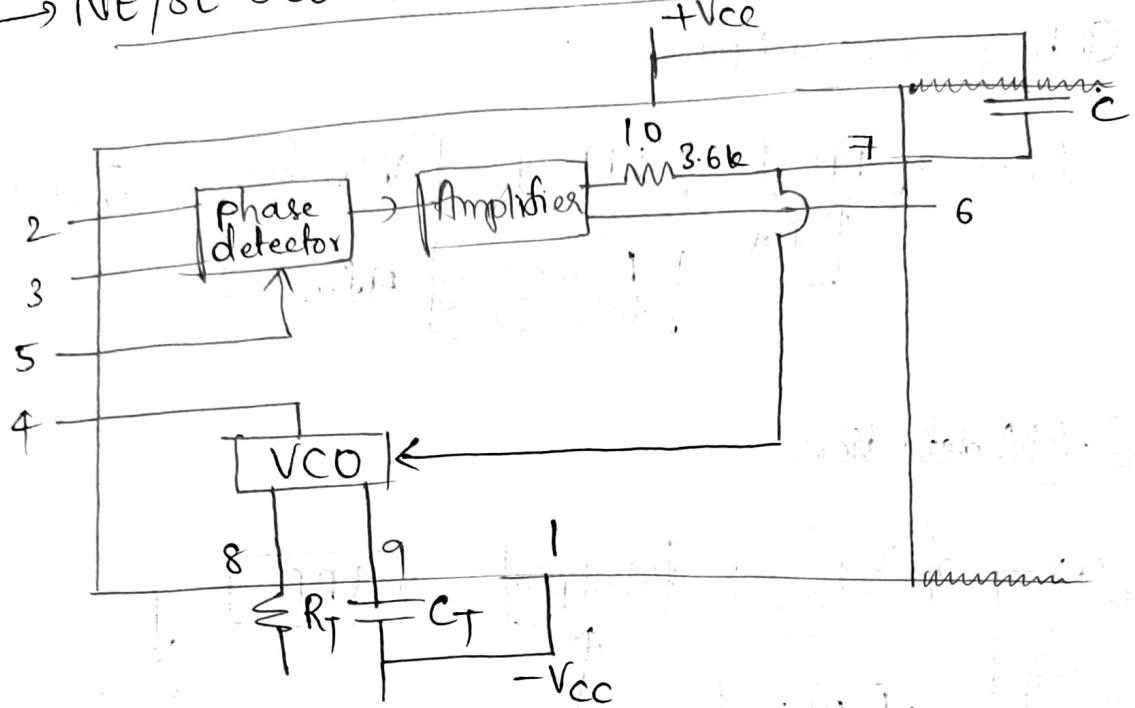

→ Important electrical parameters of 565 PLL,

- operating freq range = 0.001 Hz to 500 kHz
- operating voltage range =  $\pm 6V$  to  $\pm 12V$
- Input level  $\approx 10\text{mV}$  rms (min) to 3V (p-p) max.
- O/p sink current = 1 mA (typical)
- I/p impedance =  $\pm 10\text{k}\Omega$ .

lock in range

$$\Delta f_L = \pm \frac{7.8 f_0}{V}$$

$$V = +V_{cc} - (-V_{cc})$$

Capture range


$$\Delta f_C = \pm \left[ \frac{\Delta f_L}{(2\pi)(3.6)10^3 C} \right]^{1/2}$$

free running frequency.


$$f_0 = \frac{0.25}{R_T C_T} \text{ Hz}$$

## Applications of PLL


### ① frequency multiplier

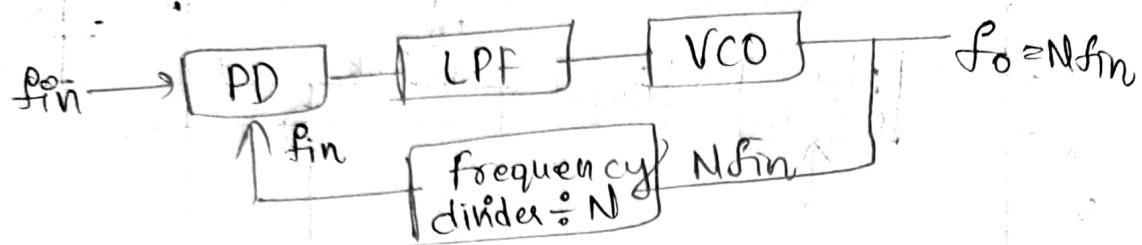


### ② AM detection

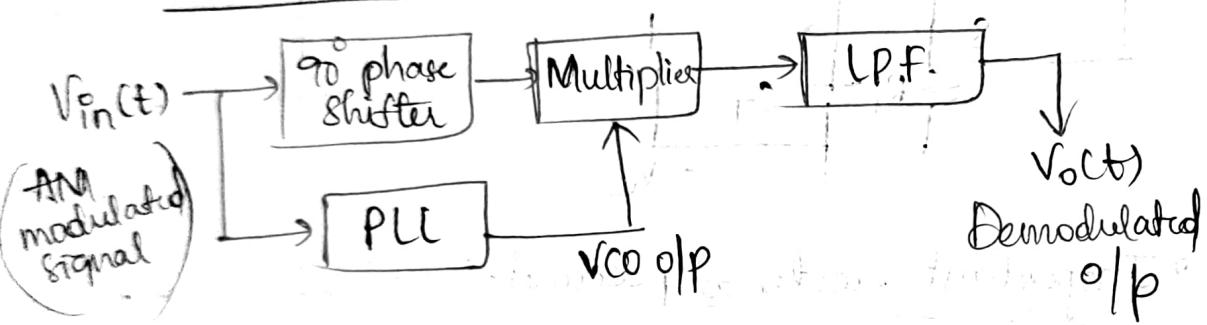

### ③ FM detection

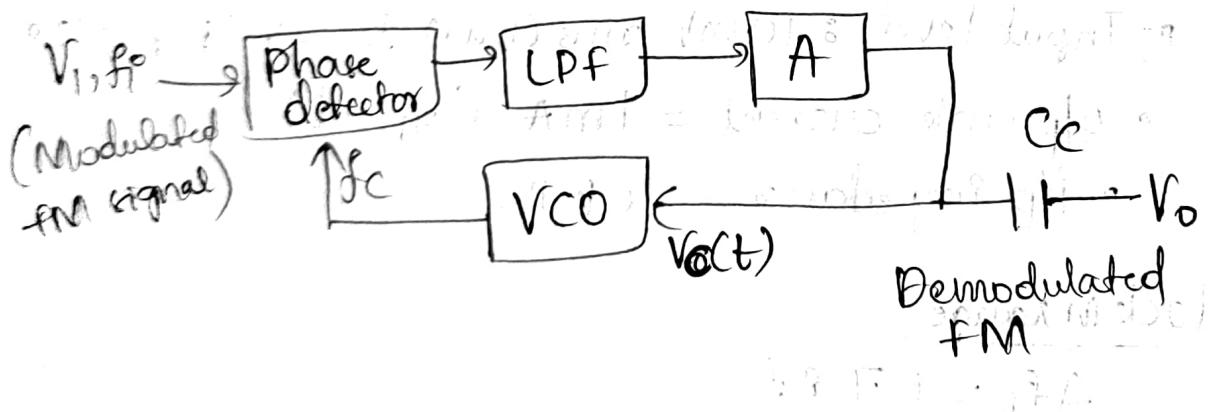

#### ④ FSK Demodulation

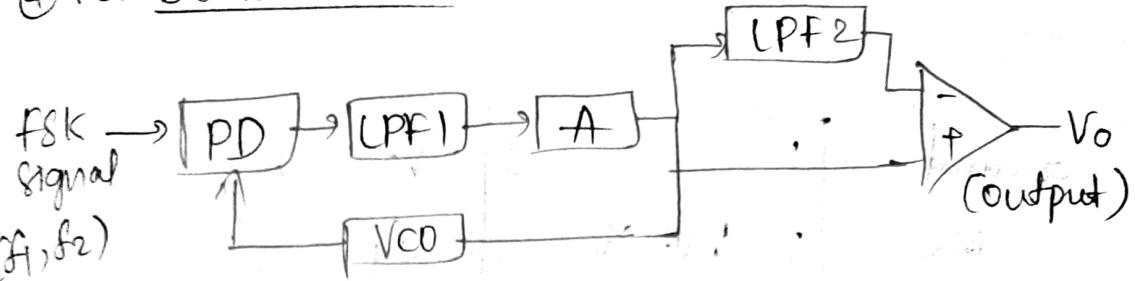



$$V_{f_1} = \frac{f_1 - f_0}{k_0}, \quad V_{f_2} = \frac{f_2 - f_0}{k_0}$$

$$\Delta V_f = \frac{f_2 - f_1}{k_0}$$



$k_0$  — parameter of VCO.

$$V_{CC} = +5V$$

RC ladder filters:  
LPF2

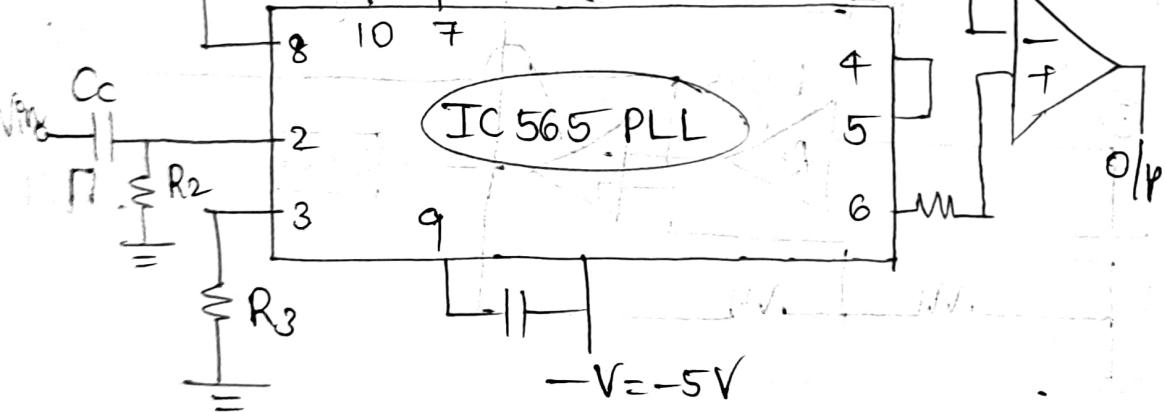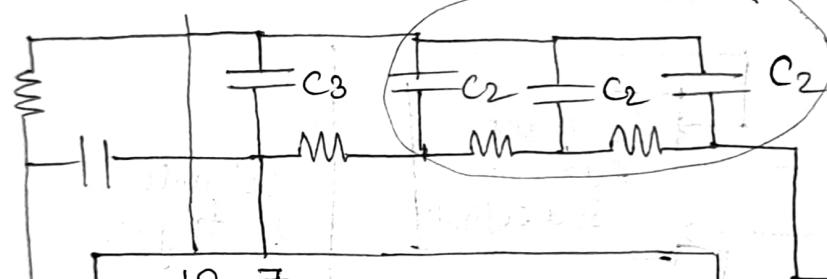
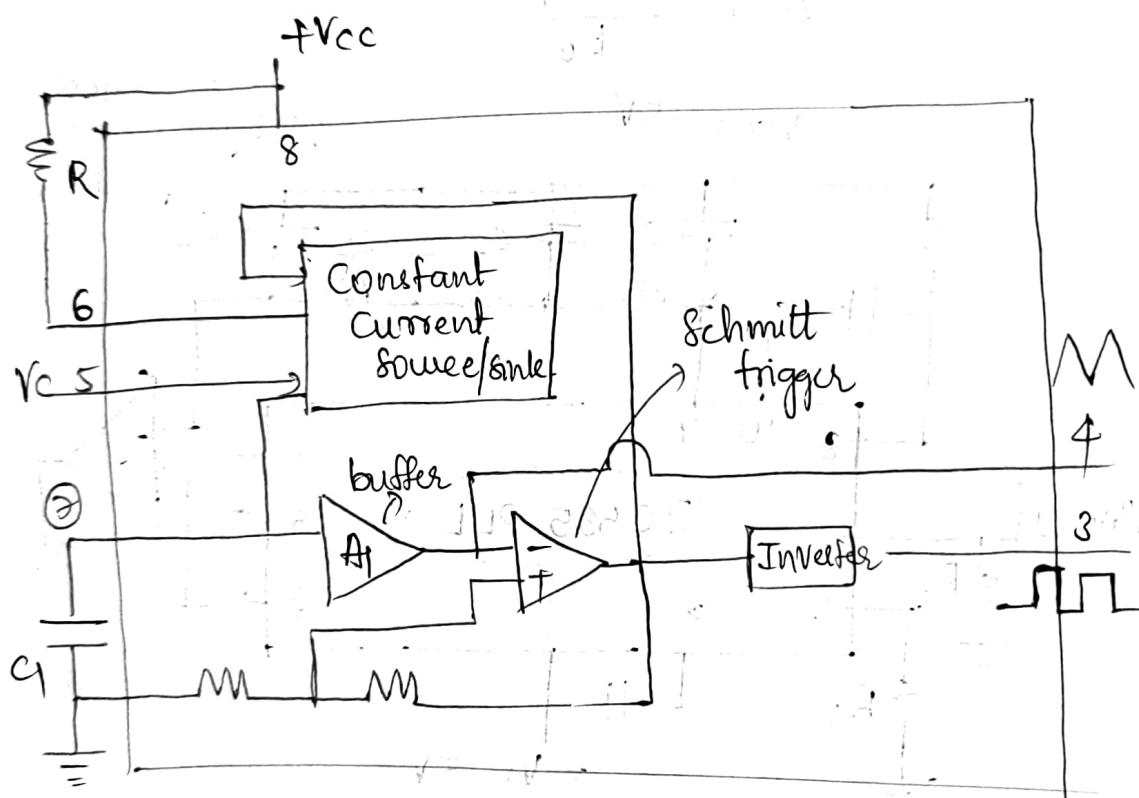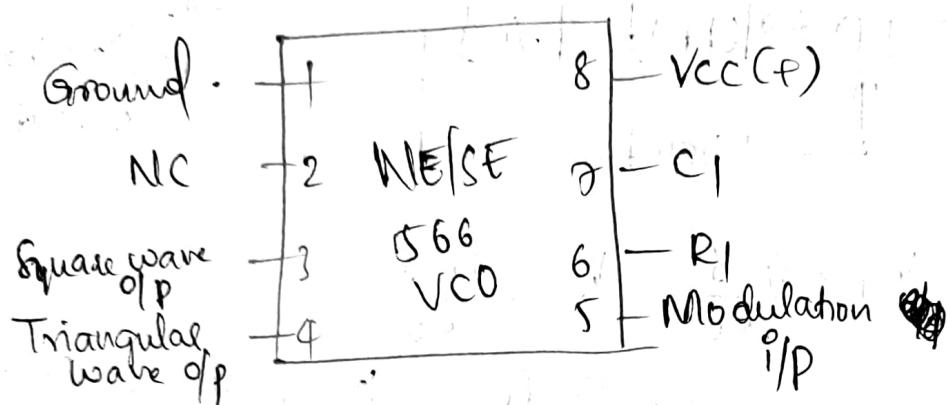
# • IC Voltage controlled oscillator NE/SE 566




$V_c$  - modulating input voltage

$$V_Q = \text{opf of OPAMP } A_2 = +V_{\text{sat}} = +V_{\text{cc}}$$
$$-V_{\text{sat}} = 0.5 V_{\text{cc}}$$

when  $V_Q = +V_{\text{cc}}$ , block behaves as

constant current source.

$$i = \frac{V_{\text{cc}} - V_c}{R_1}$$

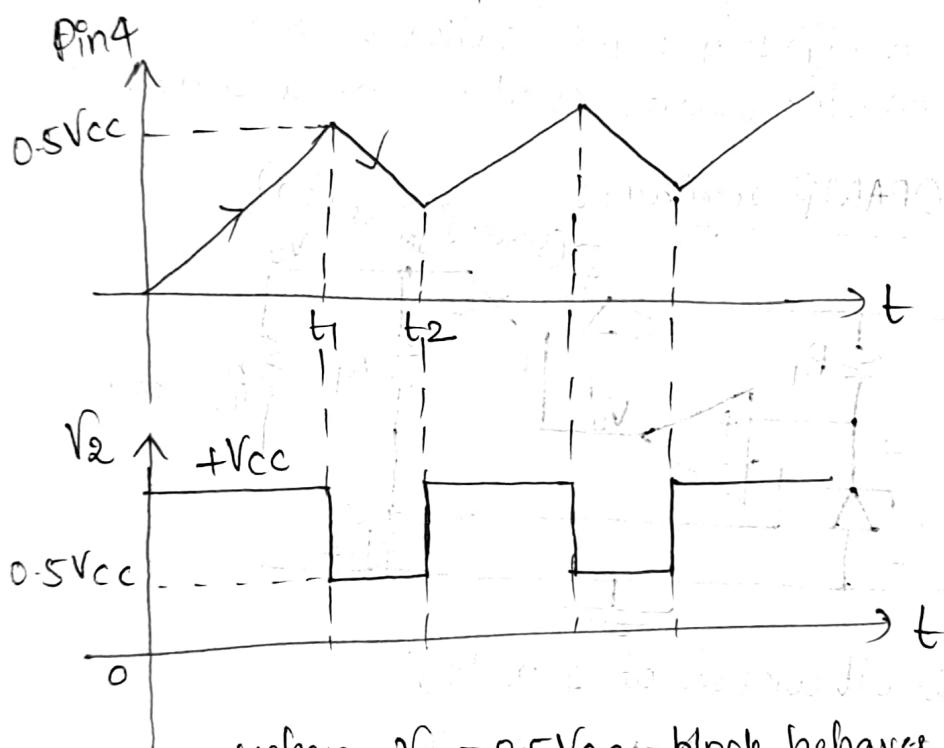

when  $V_Q = 0.5V_{\text{cc}}$ , block behaves as constant current sink.

$$Q = CV$$

$$i = C \frac{dV}{dt}$$

$$i = C_1 \frac{\Delta V}{\Delta t} = \frac{C_1 (0.25V_{\text{cc}})}{\Delta t}$$


$$\Delta t = \frac{C_1 (0.25V_{\text{cc}})}{i}$$

$$i = \frac{V_{\text{cc}} - V_c}{R_1}$$

## • Voltage regulator:

- It is a electronic circuit that provides a stable dc voltage independent of load current, temp etc.
- They can be classified as ,
  - 1) Series regulator.
  - 2) Switching regulator.
- Series regulators use a power transistor connected in series b/w the unregulated dc input & the load.
- Switching regulators operate the power transistor as a high freq on/off switch so that power transistor doesn't conduct current continuously.

## • Series OPAMP regulator:

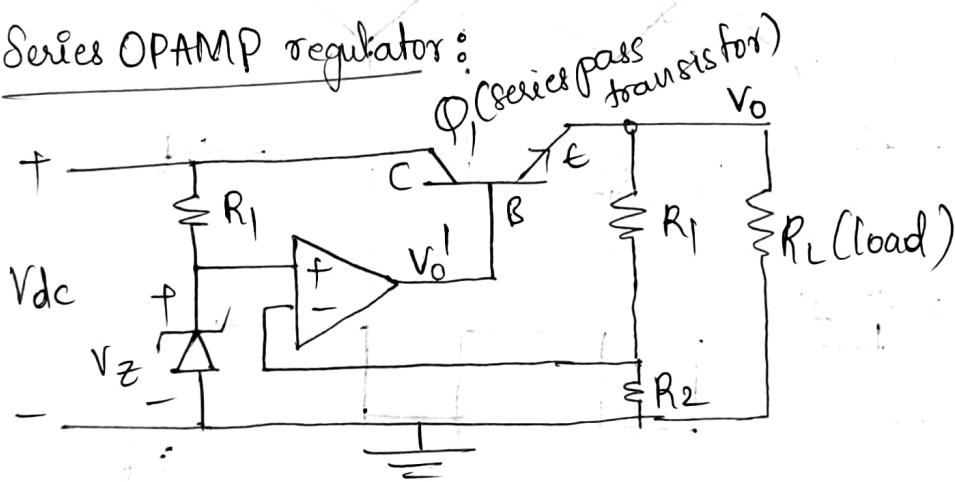

→ Circuit consists of 4 parts ,

- ① Reference Voltage circuit.
- ② Error amplifier.
- ③ Series pass transistor
- ④ Feedback w/w

$$V_o^+ = A(V_z - \beta V_o)$$

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$V_o^+ = V_o = A(V_z - \beta V_o)$$

$$V_o = \frac{AV_z}{1 + A\beta}$$

## • IC Voltage regulators:

### • Fixed Voltage Series Regulators:

- 78XX series are 3 terminal, positive voltage fixed regulators.
- In 78XX, the last 2 numbers (XX) indicate the o/p voltage.
- There are seven o/p voltage options available such as 5, 6, 8, 12, 15, 18 & 24V.
- 79XX series generates -ve voltage (-ve DC voltage)

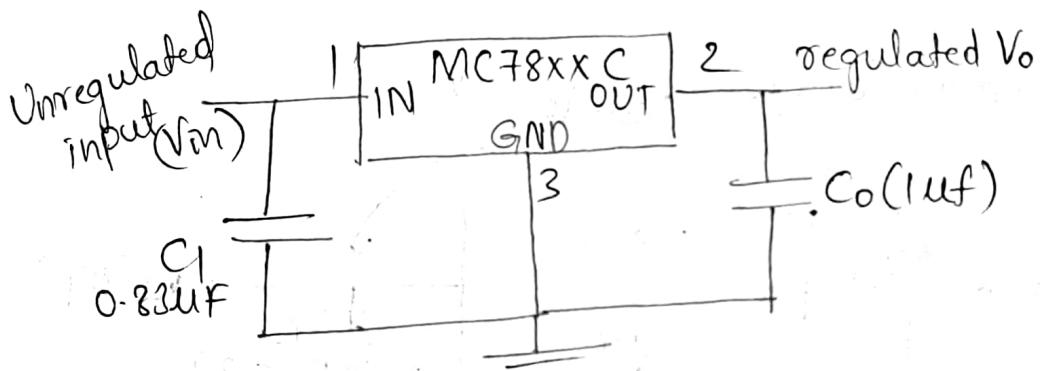


fig. Standard representation of a 3-terminal positive regulator.

### Characteristics:

- ①  $V_o$ : The regulated o/p voltage is fixed value specified by manufacturer.
- ②  $|V_{in}| \geq |V_o| + 2$  volts  
The unregulated input voltage must be at least 2V more than regulated o/p voltage.
- ③  $I_o(\text{max})$ : The load current may vary from '0' to rated maximum output current.
- ④ Thermal shutdown: The IC has temp sensor, which turns off the IC when it becomes hot ( $125^\circ\text{C}$  to  $150^\circ\text{C}$ )

## • Line Input regulation:

→ It is defined as percentage change in o/p voltage for a change in input voltage.

## • Load regulation:

→ It is defined as the change in o/p voltage for a change in load current.

## • Ripple rejection:

→ The IC regulator not only keeps the o/p voltage constant but also reduces the amount of ripple.

## • Current Source:

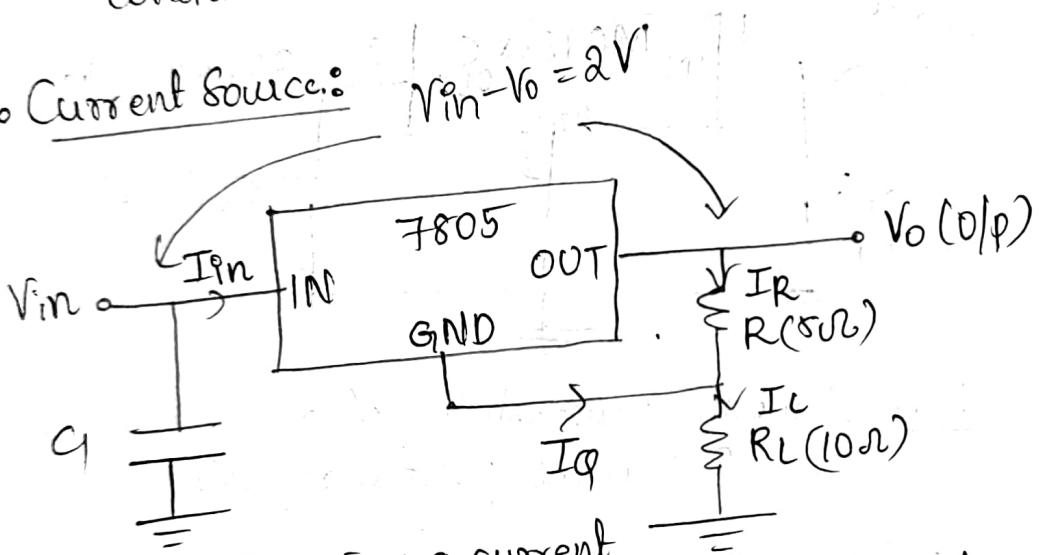


Fig. IC7805 as a current source.

→ The circuit is wired to supply a current of 1 Ampere to a  $10\Omega$ , 10 Watt load.

$$I_L = I_R + I_Q$$

where  $I_Q$  is Quiescent current & is about 4.2mA for 7805

$$I_L = \frac{V_R}{R} + I_Q$$

Since  $I_L = 1A$ ,  $\frac{V_R}{R} \approx 1A$   
(neglecting  $I_Q$ )

- Line/Input regulation:

→ It is defined as percentage change in o/p voltage for a change in input voltage.

- Load regulation:

→ It is defined as the change in o/p voltage for a change in load current.

- Ripple rejection:

→ The IC regulator not only keeps the o/p voltage constant but also reduces the amount of ripple.

- Current Source:

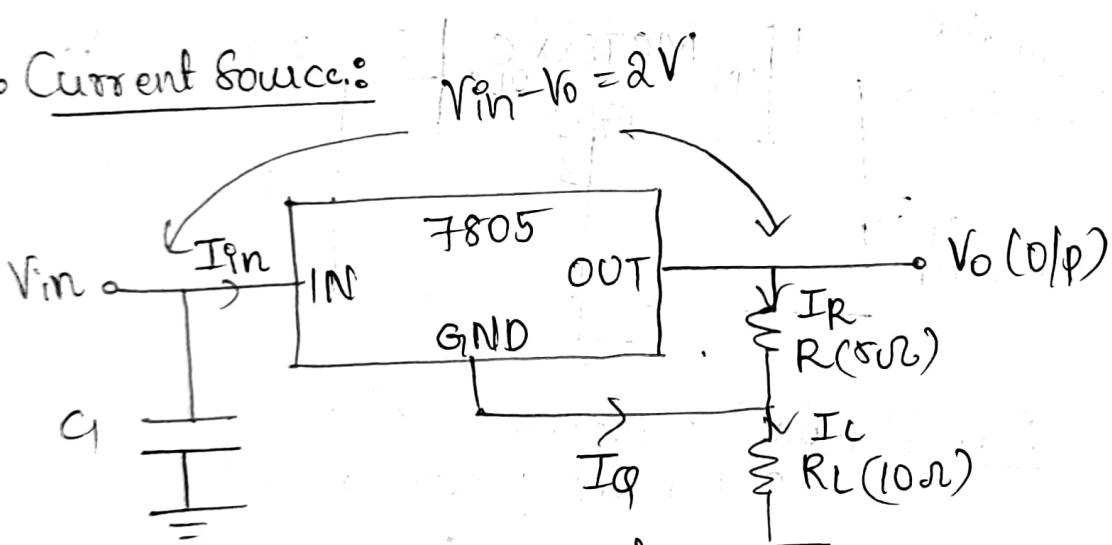


fig. IC7805 as a current source.

→ The circuit is wired to supply a current of 1 Ampere to a  $10\ \Omega$ , 10 Watt load.

$$I_L = I_R + I_Q$$


where  $I_Q$  is Quiescent current & is ~~about~~ about 4.2mA for 7805

$$I_L = \frac{V_R}{R} + I_Q$$

Since  $I_L = 1A$ ,  $\frac{V_R}{R} \approx 1A$   
(neglecting  $I_Q$ )
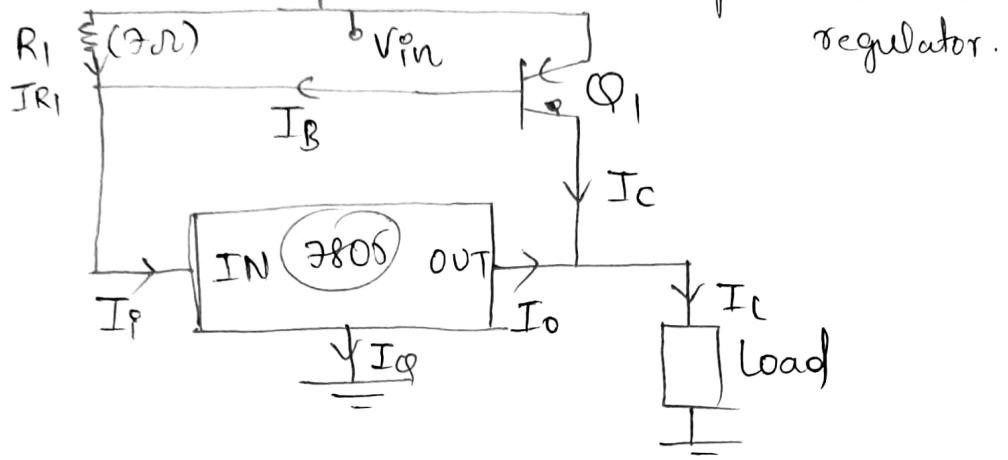
## • Boosting IC regulator o/p current:

→ It is possible to boost the o/p current of a 3 terminal regulator simply by connecting an external pass transistor in parallel with



fig(b). Boosting a 3 terminal regulator

① For low load currents, the voltage drop across 'R' is insufficient ( $< 0.7V$ ) to turn on transistor  $Q_1$ , & regulator itself is able to supply the load current.

If  $I_L$  increases,  $V_{R1}$  increases when  $V_{R1} = 0.7V$ , transistor is turned 'on'

If  $I_L = 100\text{mA}$ ,  $V_{EB} = V_{R1} = 0.7V$

If  $I_L > 100\text{mA}$ , the transistor  $Q_1$  is turned 'ON' & it supplies extra current.

→ When  $Q_1$  is ON,  $V_{EB(\text{ON})}$  remains fairly constant, & excess current comes from  $Q_1$

$$I_L = I_C + I_O$$


$$I_C = \beta I_B$$

for regulator  $\rightarrow I_O = I_L^o - I_Q$ ,  $I_O \approx I_L^o$

$$I_B = I_L^o - I_{R1} = I_O - I_{R1}$$

$$I_B \approx I_O - \frac{V_{EB(\text{ON})}}{R_1}$$
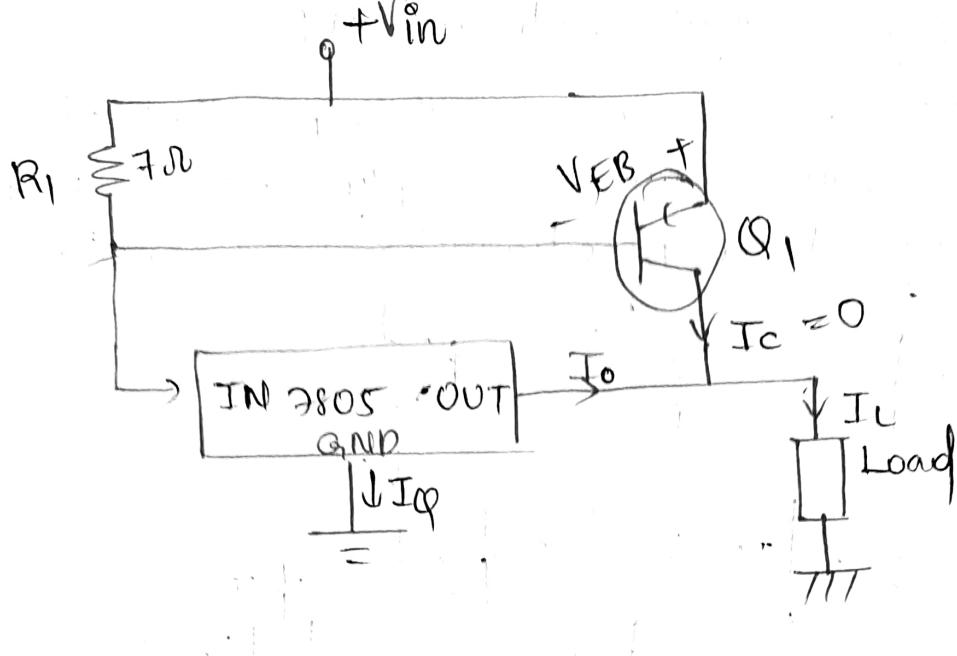
$$I_L = (\beta + 1) I_O - \frac{\beta V_{EB(\text{ON})}}{R_1}$$



Let  $V_{EB(ON)} = 1V$  &  $\beta = 15$ .

Calculate the o/p current coming from 7805 &  $I_c$  coming from transistor  $Q_1$  for loads  $(100\Omega, 5\Omega, 1\Omega)$

Sol: o for load  $100\Omega$ ,

for 7805, the o/p voltage across load will be 5V.

$$I_L = \frac{5V}{100} = 50mA$$

Let  $Q_1$  be off, then  $V_{EB} = 50mA \times 7\Omega$

$$V_{EB} = 350mV$$

Since  $350mV < 1V$ ,  $Q_1$  is OFF,

$$I_c = 0 ; I_L = I_o = 50mA$$

o For load  $5\Omega$ , Assume  $Q_1$  is OFF! ( $I_c = 0$ )

$$I_L = \frac{5}{5} = 1A$$

$$V_{EB} = 1A \times 7\Omega \\ = 7V$$

Here  $Q_1$  is 'ON'.

$$I_L = (\beta + 1) I_0 - \frac{\beta V_{EB}(\text{ON})}{R_I}$$

$$I = (16) I_0 - \frac{15 \times 1}{7}$$

$$\underline{I_0 = 196 \text{ mA}}$$

$$I_0 + I_C = I_L$$

$$196 \text{ mA} + I_C = 1 \text{ A}$$

$$\underline{I_C = 804 \text{ mA}}$$

• For load 1Ω, Assume Q<sub>1</sub> is OFF ( $I_C = 0$ )

$$I_L = \cancel{5} = 5 \text{ A}$$

$$V_{EB} = \cancel{0.5} \times 7 = +4 \cancel{V} 35 \text{ V}$$

so, Q<sub>1</sub> is (ON).


$$I_L = (\beta + 1) I_0 - \frac{\beta V_{EB}(\text{ON})}{R_I}$$

$$\cancel{35} = 16 I_0 - \frac{15 \times 1}{7}$$

$$\underline{I_0 = 446 \text{ mA}}$$

$$\underline{I_C = 454 \text{ mA}}$$

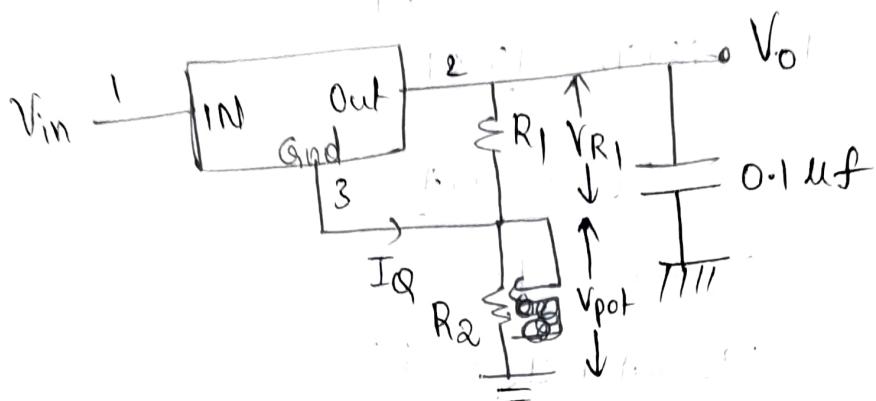Fixed Regulator used as Adjustable regulator:



$$V_0 = V_R + V_{pot}$$

$$V_0 = V_R + (I_q + I_{R1})R_2$$

$$V_0 = V_R + I_q R_2 + \frac{V_R}{R_1} R_2$$

$$V_0 \approx V_R \left( 1 + \frac{R_2}{R_1} \right); I_q \text{ is neglected.}$$

Eg: Specify suitable component value to get  $V_0 = 7.5V$  in the circuit of fig. 1, using a 7805 regulator.

Sol: from datasheet, of 7805,

$$I_q = 4.2 \text{ mA}$$

$$\text{we choose } I_{R1} = 25 \text{ mA}$$




$$\text{As } V_R = 5V \text{ for 7805}$$

$$R_1 = \frac{5V}{25 \text{ mA}} = 200 \Omega$$

$$V_{R2} = 2.5 \text{ V}$$


$$R_2 = \frac{V_{R2}}{I_{R1} + I_q} \rightarrow R_2 = 856 \Omega$$

IC723

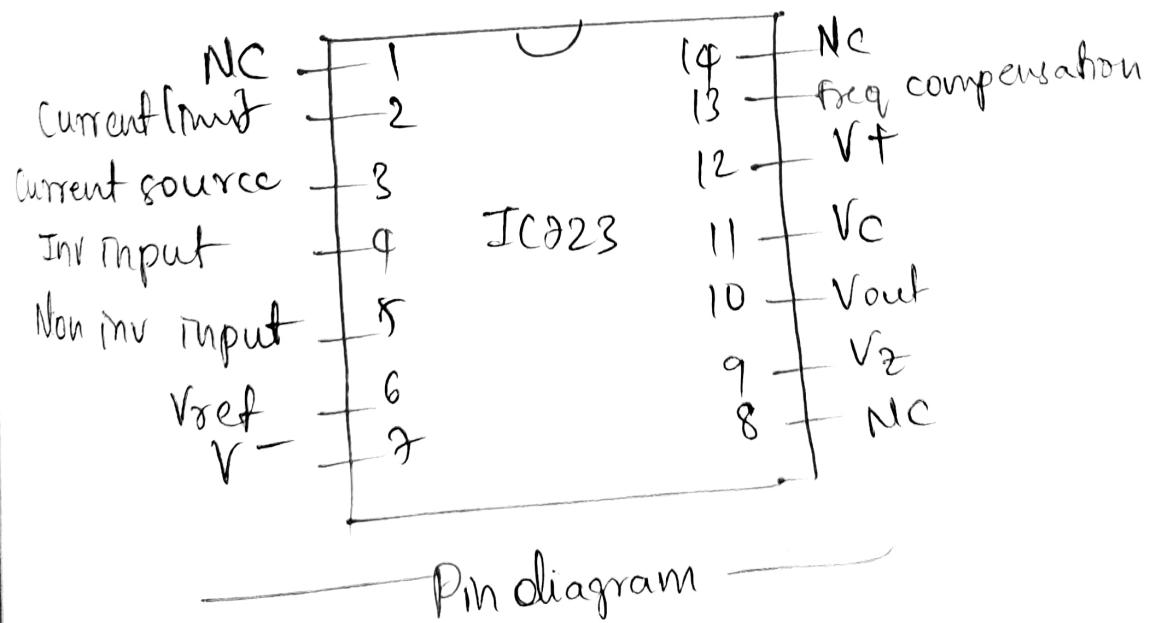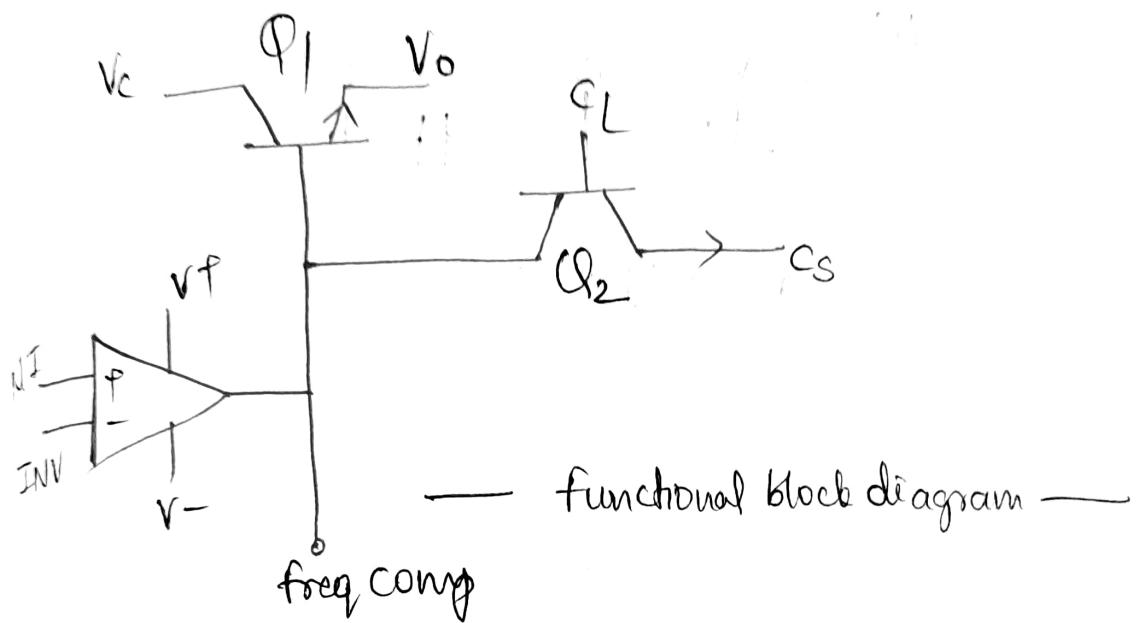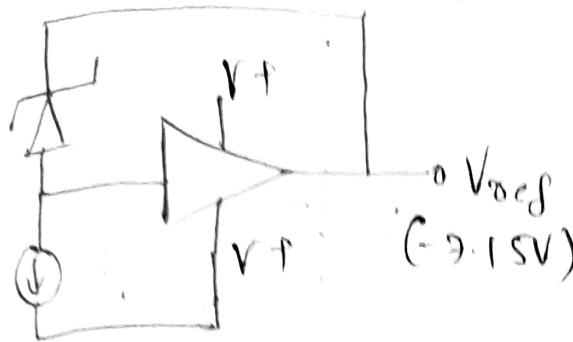





## Low voltage regulator:

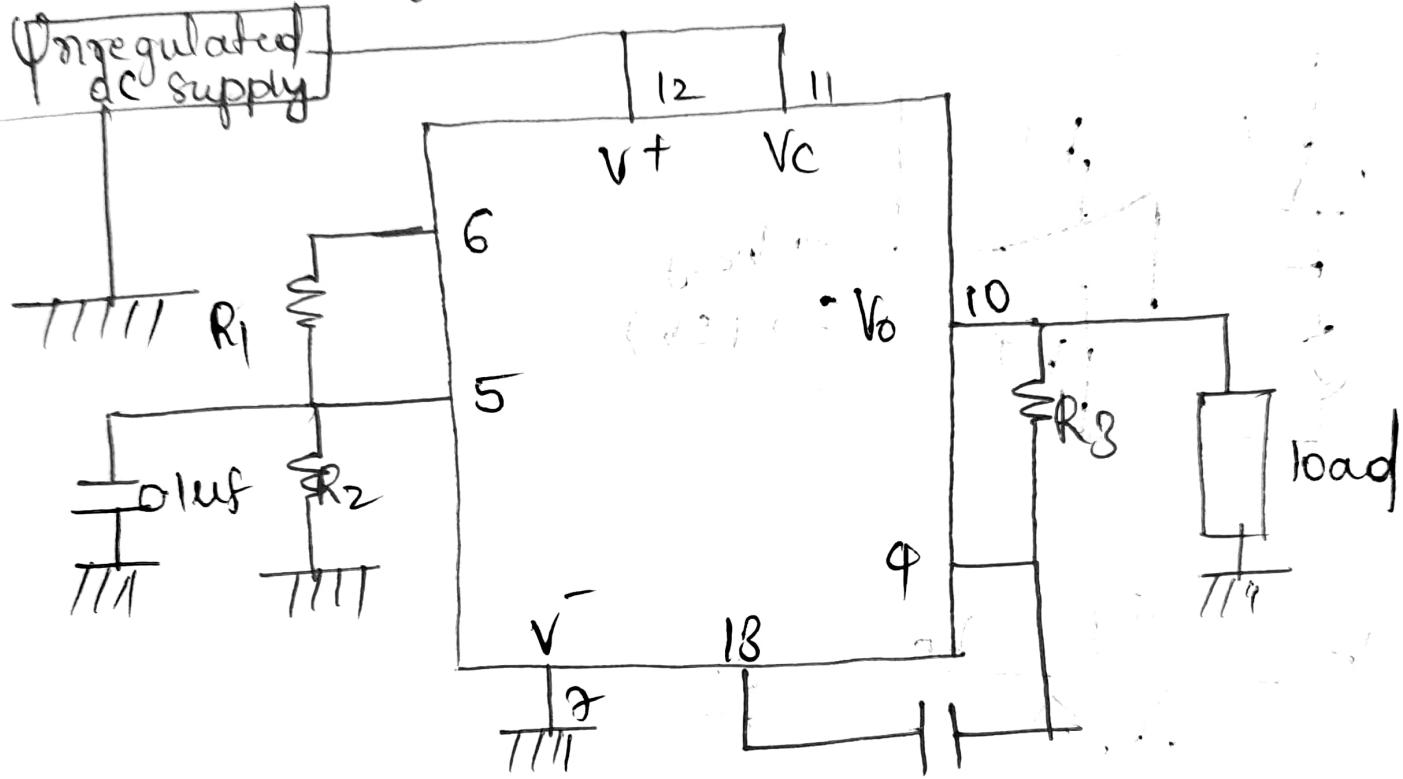

— Pin diagram —

## D/A converter:


① Weighted resistor type D/A converter,

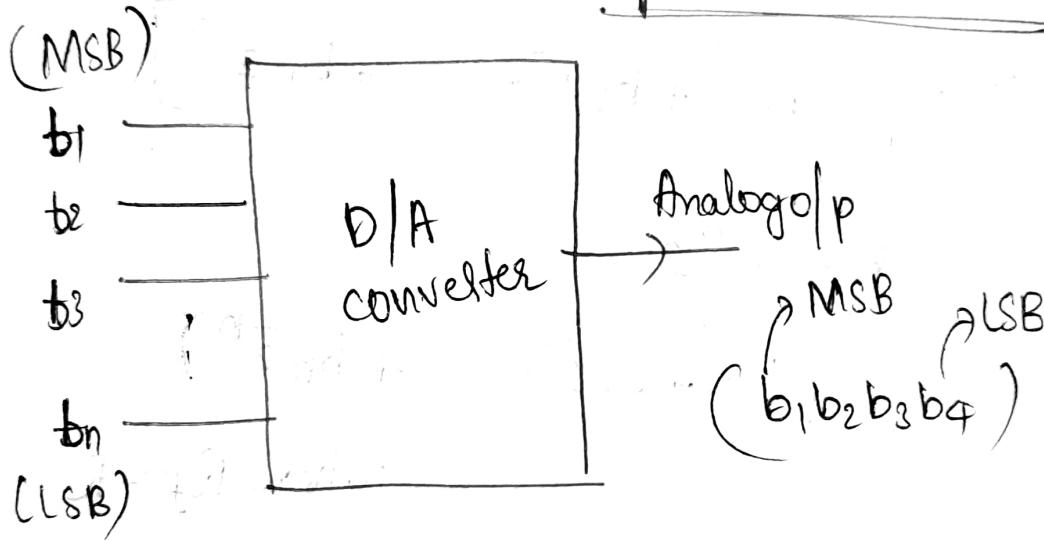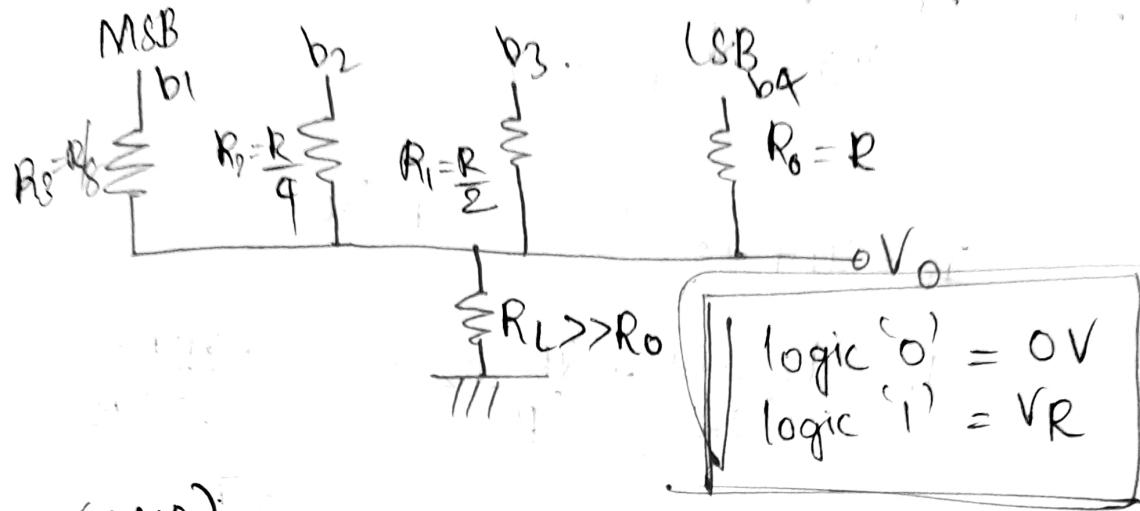

from miller's theorem,

Voltage at any node in a resistive N/w is equal to sum of currents entering the node divided by sum of conductors connected at the node.
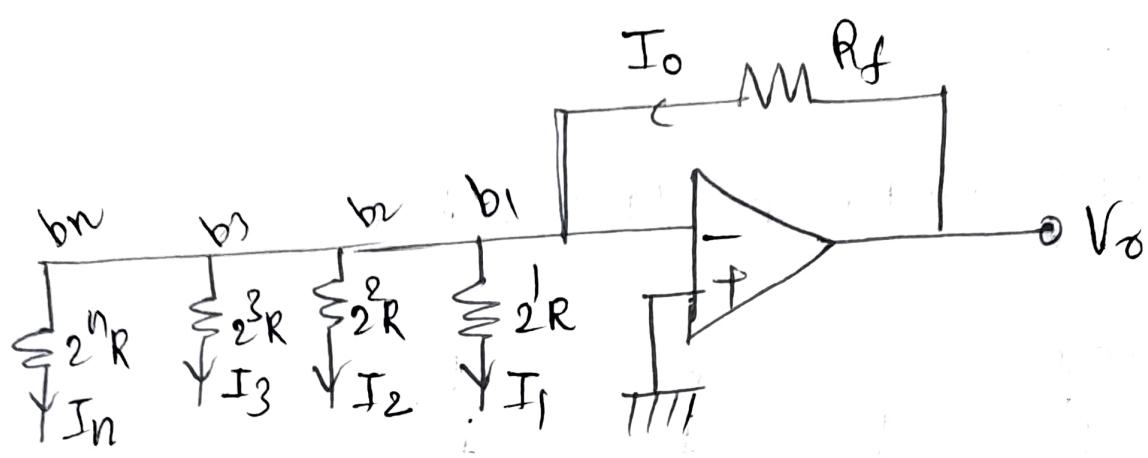
$$V_o = \frac{\frac{V_R}{R} + \frac{V_R}{R/2} + \frac{V_R}{R/4} + \frac{V_R}{R/8}}{\frac{1}{R} + \frac{1}{R/2} + \frac{1}{R/4} + \frac{1}{R/8}}$$



$$I_0 = I_1 + I_2 + I_3 + \dots + I_n$$

$$I_0 = \frac{V_R \times b_1}{2R} + \frac{V_R}{2^2 R} b_2 + \dots + \frac{V_R b_n}{2^n R}$$

$$I_0 = \frac{V_R}{R} \left[ b_1 \frac{-1}{2} + b_2 \frac{-2}{2^2} + \dots + b_n \frac{-n}{2^n} \right]$$

$$V_0 = I_0 R_f$$


$$V_0 = V_R \left( b_1 \frac{-1}{2} + b_2 \frac{-2}{2^2} + \dots + b_n \frac{-n}{2^n} \right)$$

where  $R_f = R$

• Disadvantage of binary weighted D/A converter:

- 1) Requirement of wide range of resistors.
- 2) fabrication of resistors beyond 'MΩ' is not practical.

# (8) R-2R ladder D/A converter

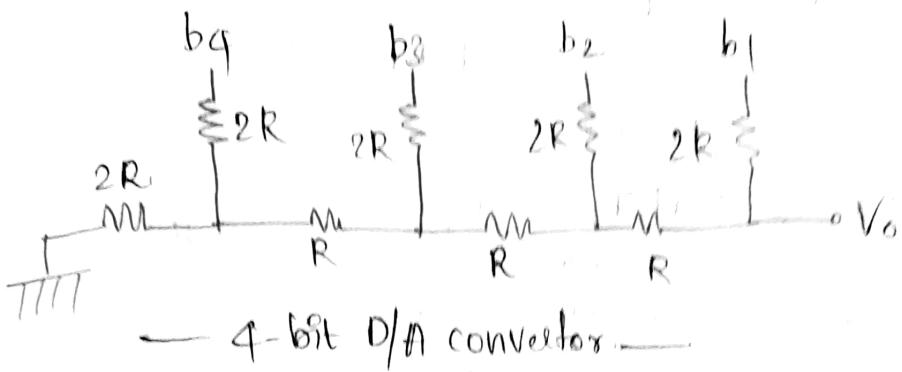

b<sub>1</sub> b<sub>2</sub> b<sub>3</sub> b<sub>4</sub>

$\begin{cases} \text{logic '1'} \rightarrow V_R \\ \text{logic '0'} \rightarrow 0 \end{cases}$

$$1000 \rightarrow V_0 = V_R/2$$


b<sub>1</sub> b<sub>2</sub> b<sub>3</sub> b<sub>4</sub>

$$0100 \rightarrow V_0 = V_R/4$$

$$0010 \rightarrow V_0 = V_R/8$$

$$(+) \quad 0001 \rightarrow V_0 = V_R/16$$
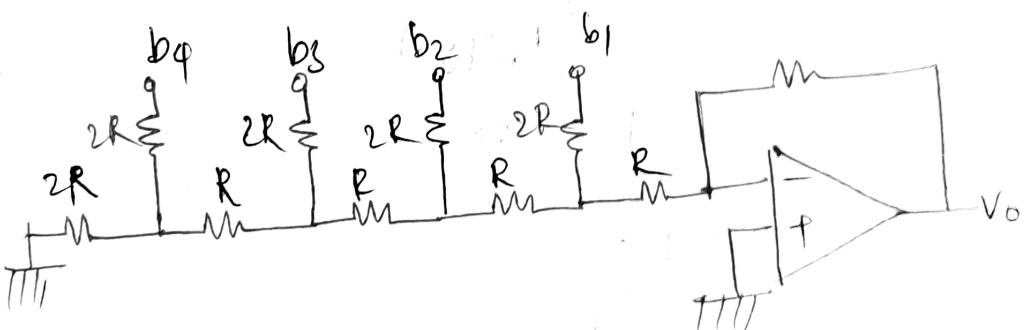
$$\underline{\hspace{2cm}} \rightarrow V_0 = \frac{V_R}{2} + \frac{V_R}{4} + \frac{V_R}{8} + \frac{V_R}{16}$$



$$V_0 = -\frac{V_R \times R_f}{R} \left( \frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} + \frac{b_4}{2^4} \right)$$

Assume R<sub>f</sub> = R<sub>1</sub>

$$V_0 = -\frac{V_R}{2^n} \left( b_1 2^{n-1} + b_2 2^{n-2} + \dots + b_n 2^0 \right)$$

resolution  $\rightarrow \frac{V_R \times R_f}{2^n \times R}$

Q: Consider R-2R 4-bit converter  $R_f$  is variable

$$R = 10k\Omega, V_R = 10V$$

Determine the value of  $R_f$  that should be connected to achieve

(a) Value of 1LSB at o/p is 0.5V

(b) Analog o/p of 6V for binary input 1000.

(c) full scale o/p voltage of 10V.

Solt- (a)  $V_o = \frac{V_R \times R_f}{2^n \times R}$        $\begin{matrix} 000 \\ b_1 b_2 b_3 b_4 \end{matrix}$

$$0.5 = \frac{10 \times R_f}{2^4 \times 10k\Omega}$$

$$\underline{R_f = 8k\Omega}$$

(b)  $\begin{matrix} 1000 \\ b_1 b_2 b_3 b_4 \end{matrix}$

$$V_o = \frac{R_f \times V_R}{2^n \times R}$$

$$6 = \frac{R_f \times 10}{2^4 \times (10^4)}$$

$$\underline{R_f = 12k\Omega}$$

(c)  $\begin{matrix} 1111 \\ b_1 b_2 b_3 b_4 \end{matrix}$

$$V_o = \frac{R_f \times V_R}{2^n \times R}$$

$$10 = \frac{R_f \times 10}{10^4} \left( \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right)$$

$$R_f = \frac{10^4}{\frac{15}{16}} \rightarrow R_f = \frac{16}{15} \times 10^4$$

$$\underline{R_f = 10.667k\Omega}$$