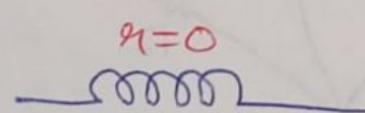
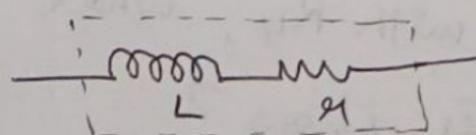


INDUCTORS

Properties

$$V = L \frac{di}{dt}$$

- ① For dc excitation, $\frac{di}{dt} = 0$
 $\therefore V = 0$ → inductor is s.c. for ideal DC
- ② An inductor never allows sudden change in current through it.
- ③ An ideal inductor is a coiled wire with zero internal resistance, so power dissipated is zero.

- ④ Practical inductors will have small internal resistance and they are represented as coil shown below which allow some power losses.


⑤ Inductors are available in different shapes and sizes and they are classified on the basis of type of core material on which winding is done.

⑥ Inductors are used as filters, compensator etc in communication and power system.

#Capacitors

Properties

$$i = C \frac{dv}{dt}$$


① For dc excitation, $\frac{dv}{dt} = 0$, $i_c = 0$

capacitor acts as open circuit for ideal D.C.

② capacitor never allows sudden change in voltage across it.


③ Ideal capacitors are considered to have infinite dielectric resistance b/w electrodes so dielectric losses are zero but conduction is through polarization $R = \infty$

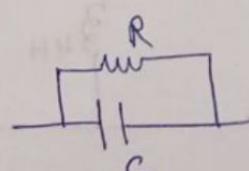④ Practical capacitors are considered to have very large dielectric resistance b/w electrodes so they undergo losses.



⑤ Capacitors are available in different shapes and sizes and they are classified on the basis of dielectric material b/w the electrodes

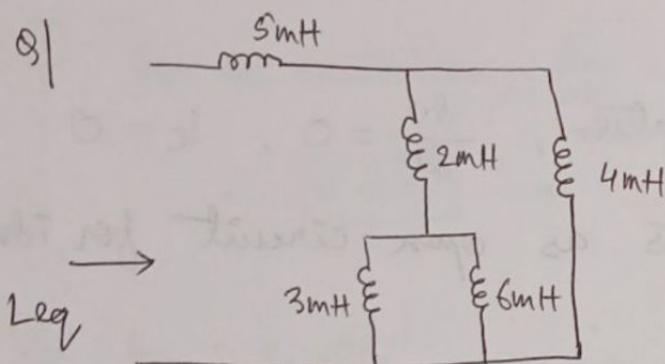⑥ They are used as filters, compensators, power factor correcting equipments, wave shaping etc in communication system



$$3 \parallel 6 = 2 \text{ mH}$$

$$2 + 2 = 4 \text{ mH}$$

$$4 \parallel 4 = 2 \text{ mH}$$

$$5 + 2 = 7 \text{ mH}$$


$$\text{Leg} = 5 + \left\{ [2 + (3 \parallel 6)] \parallel 4 \right\}$$


$$= 5 + [(2+2) \parallel 4]$$

$$= 5 + 2$$

$$= 7 \text{ mH}$$

Q1 Find Leg.

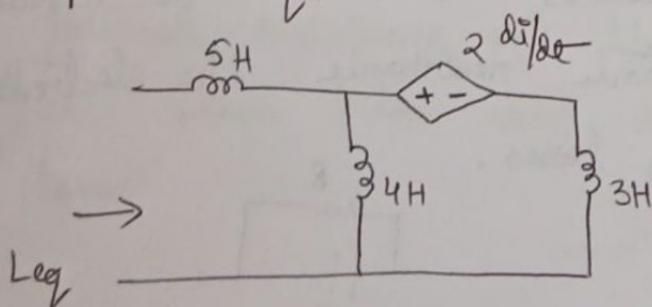

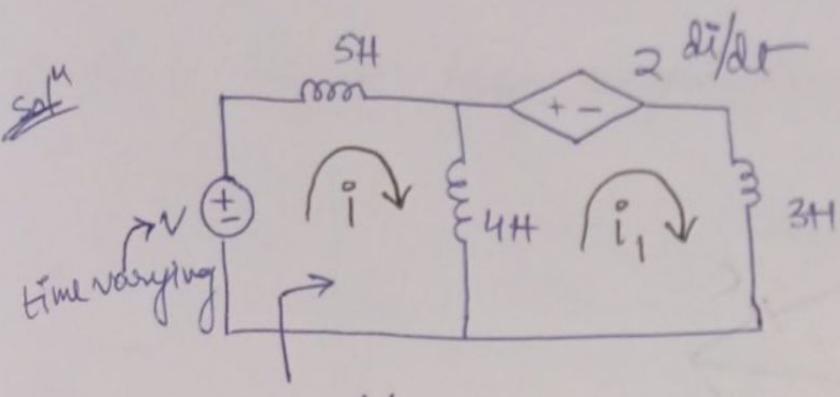

$$L_{eq} = \frac{V}{(di/dt)}$$

Mesh

$$-V + 5 \frac{di}{dt} + 4 \left(\frac{di}{dt} - \frac{di_1}{dt} \right) = 0$$

$$\text{let } X = \frac{di}{dt}$$

$$Y = \frac{di_1}{dt}$$

$$\therefore 9X - 4Y = V \rightarrow \textcircled{1}$$

$$4 \left(\frac{di_1}{dt} - \frac{di}{dt} \right) + 2 \frac{di}{dt} + 3 \frac{di_1}{dt} = 0$$


$$\Rightarrow -2X + 7Y = 0 \rightarrow \textcircled{2}$$

\therefore solving $\textcircled{1}$ and $\textcircled{2}$,


$$V = \left(\frac{63-8}{7} \right) X = \frac{55}{7} \frac{di}{dt}$$

$$\therefore L_{eq} = \frac{55}{7} \text{ H}$$

Q1 Find C_{eq}

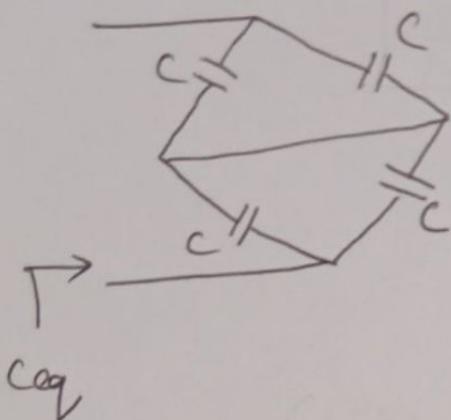
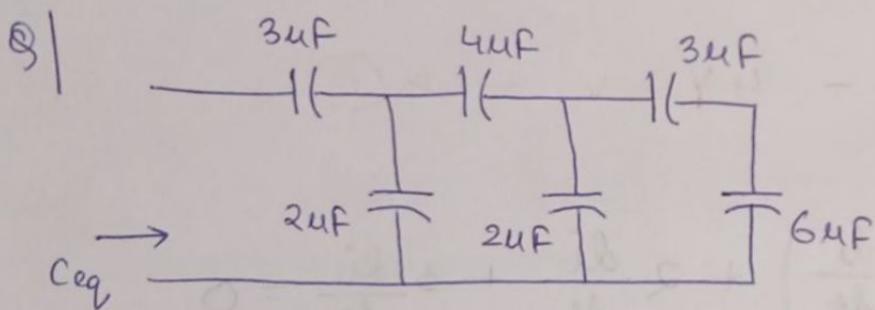
$$C_{eq} = 2C \parallel 2C$$
$$= \frac{4C^2}{4C} = C$$



$$3 \text{ series } 6 = 2\mu F$$

$$2 \parallel 2 = 4\mu F$$


$$4 \text{ series } 4 = 2\mu F$$

$$2 \parallel 2 = 4\mu F$$


$$\therefore C_{eq} = \frac{12}{7}\mu F$$

$$3 \text{ series } 4 = \frac{12}{7}\mu F$$

Q) Find input loop capacitance.

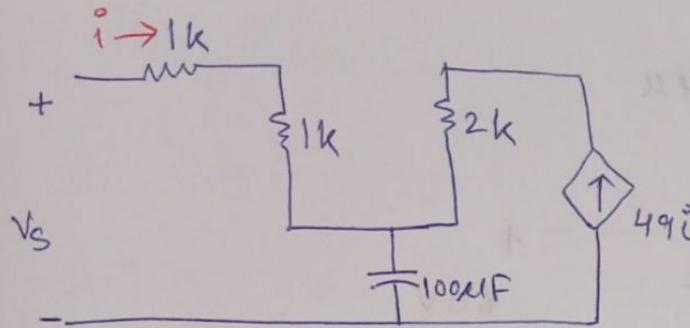

Solⁿ

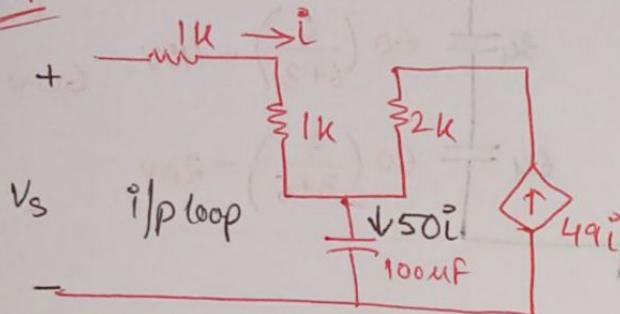

KVL


$$V = \frac{1}{C} \int idt$$

$$-Vs + 2000i + \frac{1}{100\mu} \int 50idt = 0$$

$$\Rightarrow Vs = 2000i + \frac{1}{50\mu} \int idt$$


$$\therefore C_{loop} = 2\mu F, R_{loop} = 2000 \Omega$$

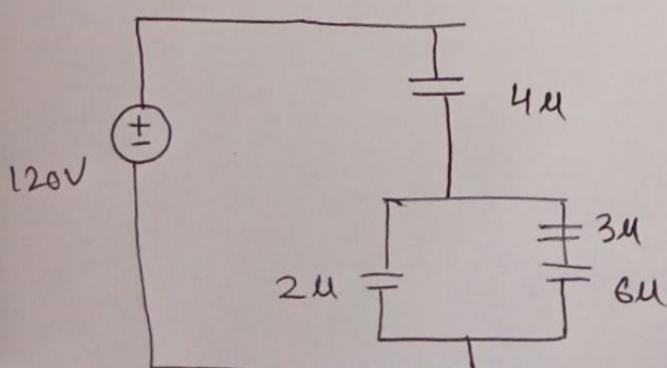Q) Determine steady state voltage across each capacitor and energy stored in each. Also find charge.



$$3 \text{ series } 6 = 2\mu$$

$$2 \parallel 2 = 4\mu$$

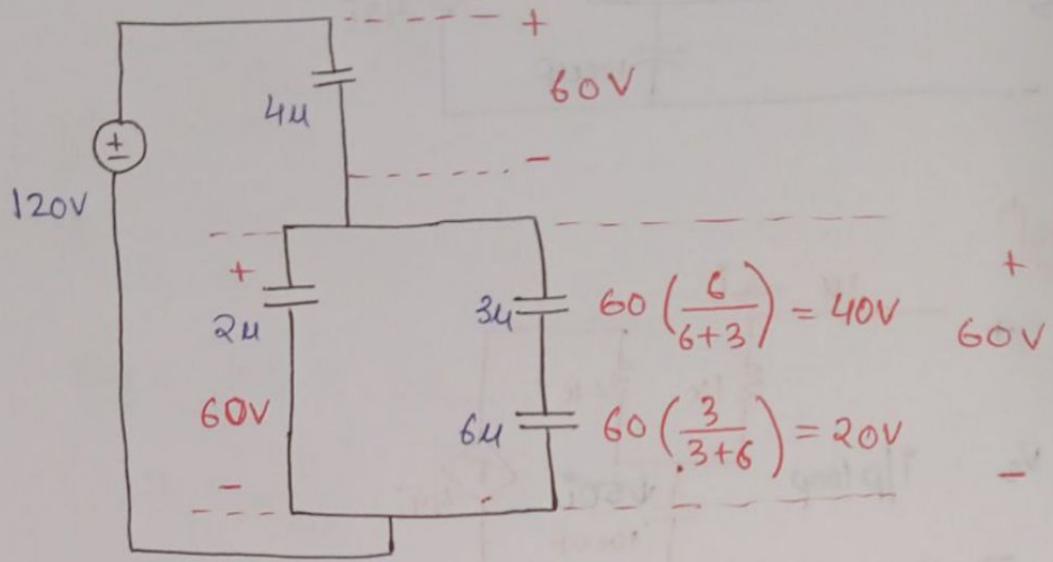

$4\mu F$

$$q_4 = CV = 4 \times 60 = 240 \mu C$$

$$E_4 = \frac{1}{2} CV^2 = \frac{1}{2} \times 4 \times (60)^2 = 7200 \mu J$$

$$q_2 = CV = 2 \times 60 = 120 \mu C$$

$$E_2 = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times (60)^2 = 3600 \mu J$$

$$q_3 = \cancel{q_2} \cdot CV =$$


$$E_3 = \frac{1}{2} CV^2 =$$

$$q_6 = CV =$$

$$E_6 = \frac{1}{2} CV^2 =$$

Unit 5 - steady state Analysis of Circuits for sinusoidal Excitations

→ Radian

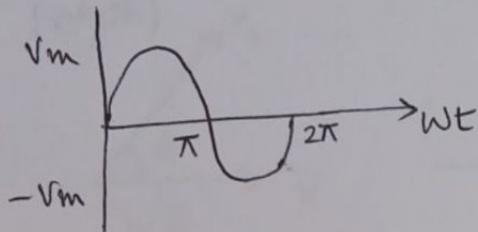


$V_m \rightarrow$ amplitude

$\omega \rightarrow$ angular frequency
(radian / sec)

$$V = V_m \sin \omega t$$


$$\omega = 2\pi f = \frac{2\pi}{T}$$

→ Degree

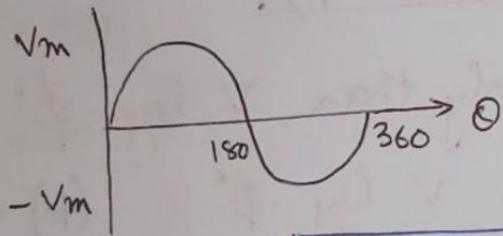

$$V = V_m \sin \theta$$

→ Time

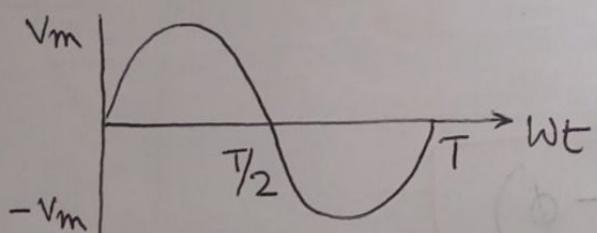

$$V = V_m \sin \left(\frac{2\pi}{T} \cdot t \right)$$

India

$$\text{Power frequency} = 50 \text{ Hz} \Rightarrow T = \frac{1}{50} = 20 \text{ ms}$$

$$1T = 2\pi = 360^\circ = 20 \text{ ms}$$


$$100 = 0$$

Standard sine wave

$$V_x = V_m \sin(\omega t + \phi)$$

$\phi \rightarrow$ phase shift (degree)

①

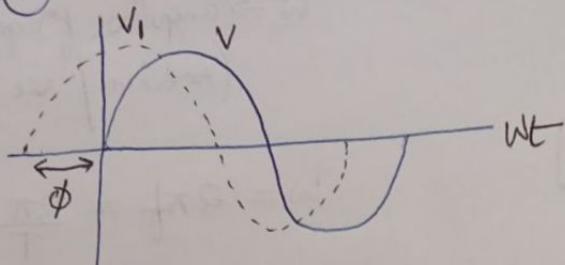


$$V_1 = V_m \sin(\omega t + \phi)$$

V_1 comes early than V by ϕ° .

$\therefore V_1$ leads V by ϕ° . (+) \rightarrow leading

②

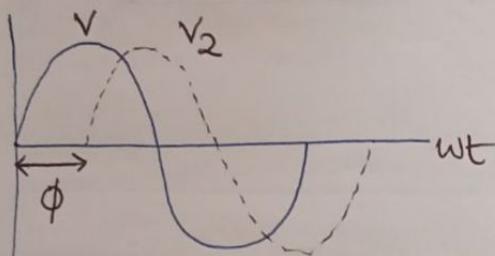

$$V_2 = V_m \sin(\omega t - \phi)$$

V_2 lags V by ϕ° .

(-) \rightarrow lagging

India


$$\phi = 60^\circ$$

$360^\circ = 20 \text{ msec}$ (Already we know)

$$60^\circ = t_{\text{shift}}$$

$$\therefore t_{\text{shift}} = \frac{60}{360} \times 20 \text{ ms} = 3.33 \text{ ms}$$
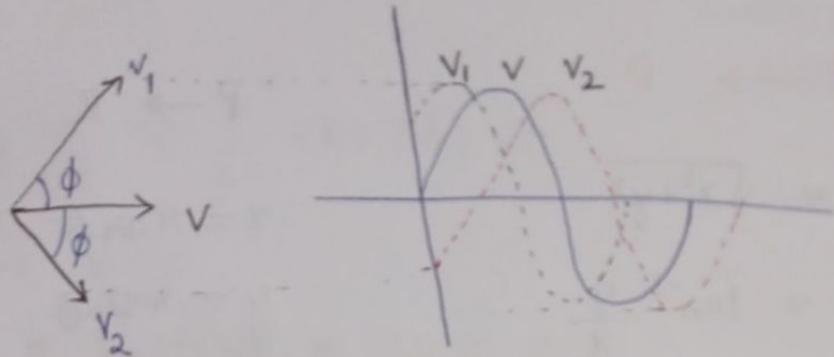
$$\omega = 2\pi f = 2\pi(50) = 100\pi \text{ rad/sec}$$




$$V = |V_m| \angle 0^\circ$$

$$V_1 = |V_m| \angle \phi^\circ$$

$$V_2 = |V_m| \angle -\phi^\circ$$

S plane

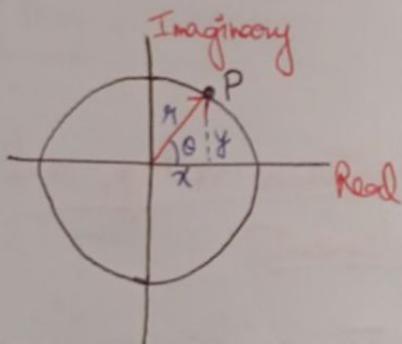

rectangular form

$$P = x + iy$$

polar form

$$P = r \angle \theta$$

Euler's form

$$P = re^{j\theta}$$

Rectangular \rightarrow Polar

$$0 + jo \rightarrow 0 \angle 0^\circ$$

$$1 + jo \rightarrow 1 \angle 0^\circ$$

$$0 + ji \rightarrow 1 \angle 90^\circ$$

$$1 + ji \rightarrow \sqrt{2} \angle 45^\circ$$

$$0 - ji \rightarrow 1 \angle -90^\circ$$

$j \rightarrow$ powerful operator

$+j \rightarrow lead$

$-j \rightarrow lag$

Rectangular coordinates $\rightarrow x, y$

Polar coordinates $\rightarrow r, \theta$

$$R \rightarrow P$$

$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

$$P \rightarrow R$$

$$x = r \cos \theta$$

$$y = r \sin \theta$$


Ex $\rightarrow 1 + j0$ to polar

$$r = \sqrt{1^2 + 0^2} = 1$$

$$\theta = \tan^{-1} \frac{0}{1} = 0$$


$$\therefore 1 + j0 = 1 \angle 0^\circ$$

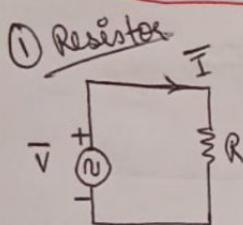Phasor relationship between voltages and current in passive elements



$$\text{let } \bar{V} = V_m \sin \omega t \rightarrow ①$$

$$V = IR$$

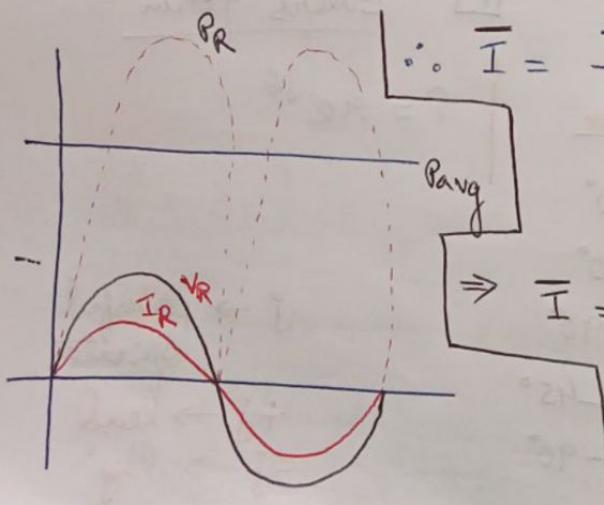


$$\therefore \bar{I} = \frac{\bar{V}}{R} = \frac{V_m \sin \omega t}{R}$$

$$= \frac{V_m}{R} \sin \omega t$$

$$\Rightarrow \bar{I} = I_m \sin \omega t \rightarrow ②$$

Phasor diagram

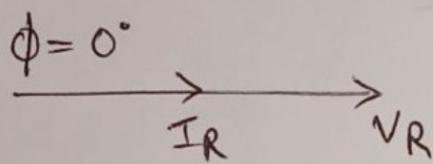

Power factor

$$\cos \phi = \cos 0^\circ = 1$$


(unity power factor)

$$P_{avg} = \frac{1}{T} \int_0^T v(t) i(t) dt$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = V_{rms} \cdot I_{rms}$$

② Inductor

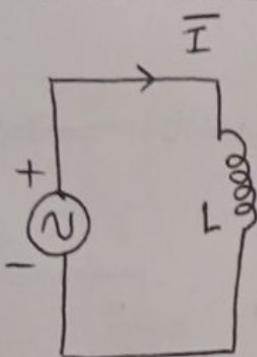

$$\text{Let } \bar{I} = I_m \sin \omega t \rightarrow ①$$

$$\text{Now } V = L \frac{dI}{dt}$$

$$\therefore V = L \frac{d}{dt} (I_m \sin \omega t)$$

$$= L \omega I_m \cos \omega t$$

$$= \omega L I_m \sin(\omega t + 90^\circ)$$


$$= \omega L I_m \sin(\omega t) [j]$$

$$\therefore \begin{cases} \bar{V} = j \omega L \bar{I} \\ \bar{V} = +j X_L \bar{I} \end{cases} \rightarrow \begin{array}{l} \text{voltage is } \underline{j \text{ operator}} \text{ times} \\ \text{the current} \end{array}$$


$\rightarrow V$ leads I by 90°

where $X_L = \omega L = 2\pi fL$
 \hookrightarrow inductive reactance


Phasor diagram

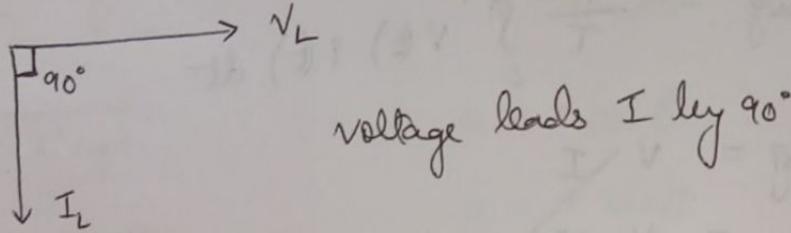
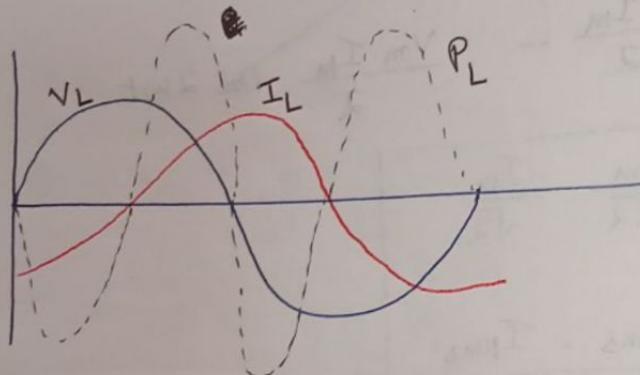
$$\text{power factor} = \cos \phi = \cos 90^\circ = 0$$



③ capacitor

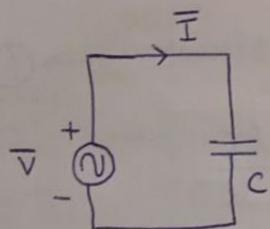

$$\text{Let } \bar{V} = V_m \sin \omega t \rightarrow ①$$

$$I = C \frac{dV}{dt}$$

$$\Rightarrow \bar{I} = C \frac{d}{dt} (V_m \sin \omega t)$$

$$= C \cdot \omega \cdot V_m \cos \omega t$$

$$= \omega C V_m \sin(\omega t + 90^\circ) \rightarrow ②$$

$$= \omega C V_m \sin \omega t [j]$$

$$\bar{I} = j \omega C \bar{V}$$


$$\bar{V} = \frac{\bar{I}}{j \omega C} = \frac{-j}{\omega C} \bar{I}$$

$$\bar{V} = -jX_C \bar{I} \rightarrow \text{voltage lags } I \text{ by } 90^\circ$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$


↳ capacitive reactance

Phasor diagram

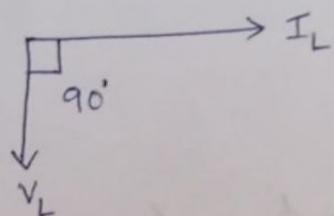


Power factor

$$\cos \phi = \cos 90^\circ = 0$$

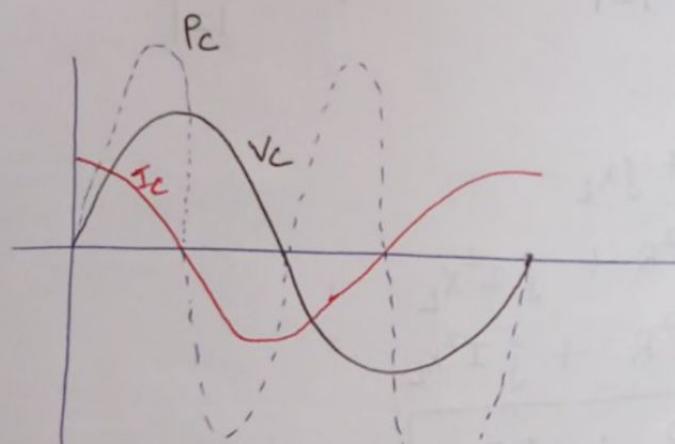

series R-L

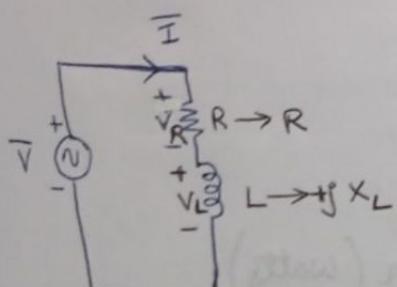

KVL

$$-\bar{V} + \bar{V}_R + \bar{V}_L = 0$$

$$\Rightarrow \bar{V} = I(R + jX_L)$$

$$\Rightarrow \bar{V} = I(R + jX_L)$$

$$\Rightarrow \boxed{\bar{V} = IZ}$$

$$\boxed{\text{Impedance } Z (\Omega) = R + jX_L}$$


Impedance triangle

$$Z = R + jX_L$$

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$
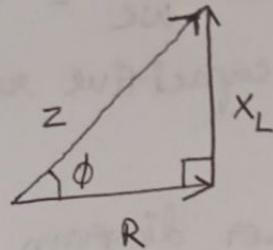
$$= \tan \left(\frac{\omega L}{R} \right)$$



Power factor

$$\cos \phi = \frac{R}{|Z|} \quad \sin \phi = \frac{X_L}{|Z|}$$



$$Z = R + jX_L$$

$$I^2 Z = I^2 R + j I^2 X_L$$

$$VI = I^2 R + j I^2 X_L$$

$$S = P + jQ_L$$

Total / Apparent power (VA)
(associated with source)


Reactive power (VAR)
(flux, charge)

Active / Real / True power (Watts)
(consumable part of energy)

Power Triangle

$$|S| = \sqrt{P^2 + Q_L^2}$$
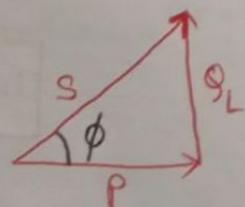
$$\phi = \tan^{-1} \left(\frac{Q_L}{P} \right)$$



$$\cos \phi = \frac{P}{S} \Rightarrow P = \cos \phi \times S = VI \cos \phi \text{ Watts}$$


$$\sin \phi = \frac{Q_L}{S} \Rightarrow Q_L = S \sin \phi = VI \sin \phi \text{ VARs}$$

Here $V, I \rightarrow \text{rms value}$


$$[81 - 9 = 2]$$

Phasor diagram

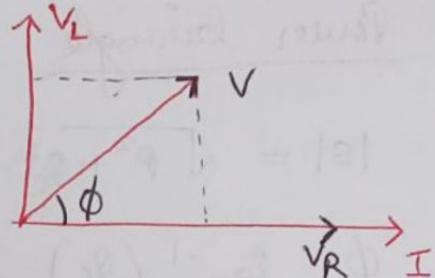I lags V by $\phi < 90^\circ$
↓
less than



Series RC

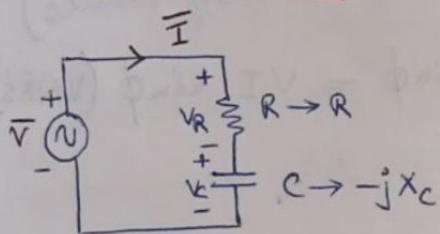


$$Z = R - jX_C$$

$$\begin{aligned} \text{KVL} \\ -\bar{V} + \bar{V}_R + \bar{V}_C &= 0 \\ \Rightarrow \bar{V} &= IR - jX_C I \\ \Rightarrow \bar{V} &= \bar{I} (R - jX_C) \\ \Rightarrow \boxed{\bar{V} = \bar{I} Z} \end{aligned}$$

Impedance triangle

$$|Z| = \sqrt{R^2 + X_C^2}$$
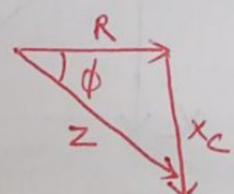
$$\phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{1}{\omega R C}\right)$$



Power factor

$$\cos \phi = \frac{R}{|Z|}$$

$$\sin \phi = \frac{X_C}{|Z|}$$

$$I^2 Z = I^2 R - j X_C I^2$$

$$VI = I^2 R - j I^2 X_C$$


$$S = P - j Q_C$$

reactive power (VARs)

Power triangle

$$|S| = \sqrt{P^2 + Q_C^2}$$
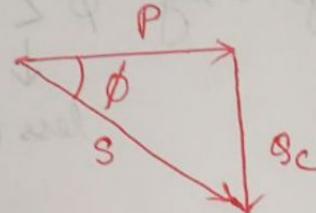
$$\phi = \tan^{-1} \left(\frac{Q_C}{P} \right)$$




$$\cos \phi = \frac{P}{S} \Rightarrow P = S \cos \phi = VI \cos \phi \text{ (watts)}$$

$$\sin \phi = \frac{Q_C}{S} \Rightarrow Q_C = S \sin \phi = VI \sin \phi \text{ (VARs)}$$


V, I → rms value

Phasor diagram

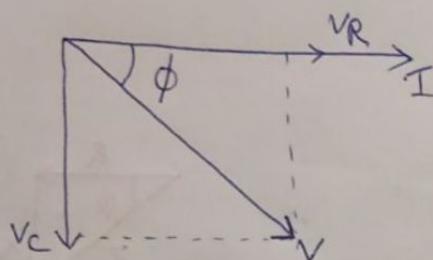

I leads V, by $\phi < 90^\circ$
less than

RLC circuit (series)

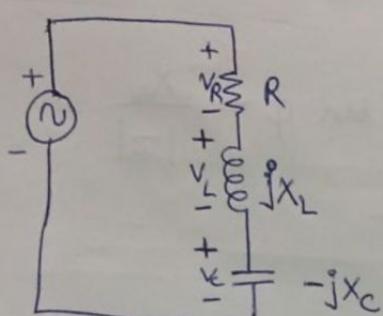

KVL

$$-\bar{V} + \bar{V}_R + \bar{V}_L + \bar{V}_C = 0$$

$$\Rightarrow \bar{V} = IR + jX_L I - jX_C I$$

$$\Rightarrow \bar{V} = I [R + j(X_L - X_C)]$$

$$V = IZ$$

Here,

$$Z = R + j(x_L - x_C)$$

$x_{\text{net}} \rightarrow \text{net reactance}$

$$|Z| = \sqrt{R^2 + (x_L - x_C)^2}$$

$$\phi = \tan^{-1} \left(\frac{x_L - x_C}{R} \right)$$

net impedance angle

Power factor


$$\cos \phi = \frac{R}{|Z|}$$

$$\sin \phi = \frac{|x_L - x_C|}{|Z|}$$

Case 1: If $x_L > x_C \rightarrow$ General nature of electrical system

$$Z = R + jx_{\text{net}}$$

series RL circuit

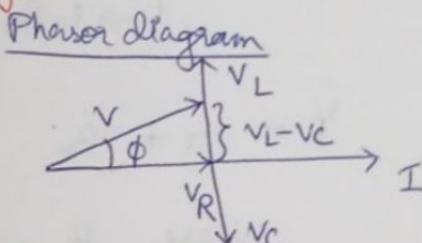


I lags V by $\phi < 90^\circ$ (lagging power factor)

Case 2: If $x_L < x_C$

$$Z = R - jx_{\text{net}}$$

series RC circuit

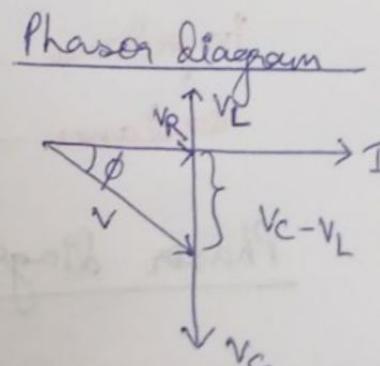

I leads V by $\phi < 90^\circ$ (leading power factor)

Case 3: If $X_L = X_C$

$$Z = R \rightarrow \text{purely resistive}$$

I in phase with V $\rightarrow \phi = 0^\circ$, PF = 1

unity power factor

$$Z = R \pm jX$$

$$\begin{cases} Z = R + jX_L \\ Z = R - jX_C \end{cases}$$

$$Y = G \pm jB$$

Y = admittance = $\frac{1}{Z}$

$$Y = G - jB_L$$

G = conductance = $\frac{1}{R}$

$$\text{where } B_L = \frac{1}{X_L} = \frac{1}{\omega L} = \frac{1}{2\pi f L}$$

B = susceptance = $\frac{1}{X}$

\hookrightarrow inductive susceptance (W)

$$Y = G + jB_C$$


$$\text{where } B_C = \frac{1}{X_C} = \frac{1}{1/\omega C} = \omega C = 2\pi f C$$

\hookrightarrow capacitive susceptance (V)

Impedance \rightarrow admittance

Resistance \rightarrow susceptance


Phasor diagram

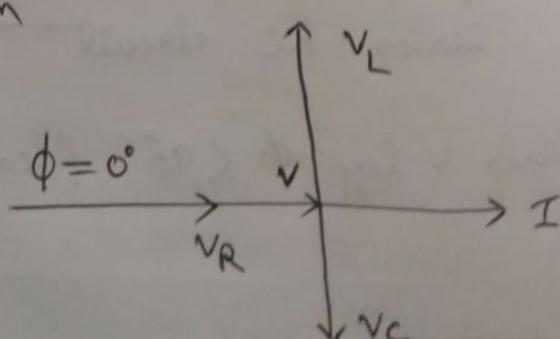

PARALLEL CIRCUITS

→ V - reference

→ Parallel RL

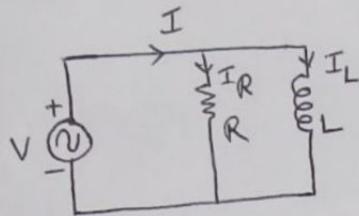

$$I_R = \frac{V}{R} \angle 0^\circ$$


$$I_L = \frac{V}{jX_L} = \frac{V}{X_L} \angle -90^\circ$$

$$I = I_R + I_L$$


$$|I| = \sqrt{I_R^2 + I_L^2}$$

$$\phi = \tan^{-1} \left(\frac{I_L}{I_R} \right)$$


$$\cos \phi = \frac{I_R}{I}$$

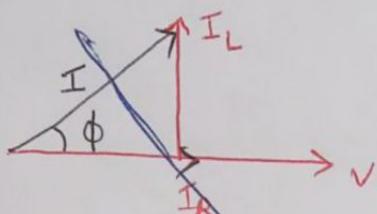

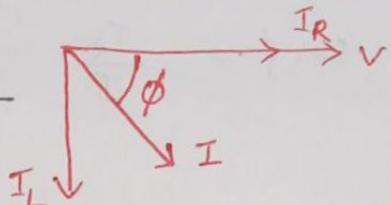V lags I by $\phi < 90^\circ$
V leads current by $\phi < 90^\circ$




→ Parallel RC

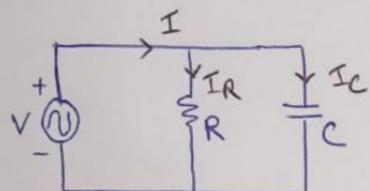

$$I_R = \frac{V}{R} \angle 0^\circ$$
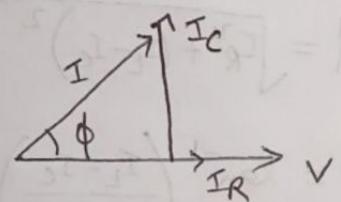
$$I_C = \frac{V}{-jX_C} = \frac{V}{X_C} \angle 90^\circ$$



V lags I by $\phi < 90^\circ$


$$I = I_R + I_C$$

$$|I| = \sqrt{I_R^2 + I_C^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C}{I_R} \right)$$

$$\cos \phi = \frac{I_R}{I}$$

→ Parallel RLC

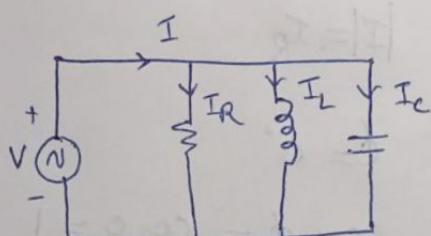


$$I_R = \frac{V}{R} \angle 0^\circ$$

$$I_L = \frac{V}{X_L} \angle -90^\circ$$

$$I_C = \frac{V}{X_C} \angle 90^\circ$$

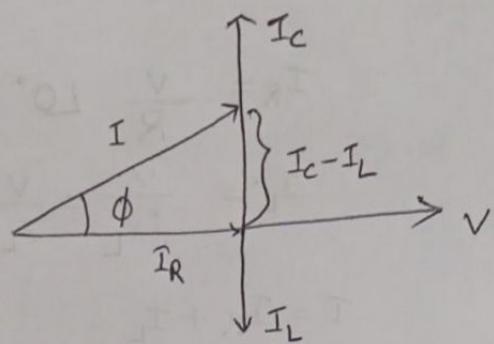Case 1 : $x_L > x_C \rightarrow I_L < I_C$




$$|I| = \sqrt{I_R^2 + (I_C - I_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$$

$$\cos \phi = \frac{I_R}{I}$$

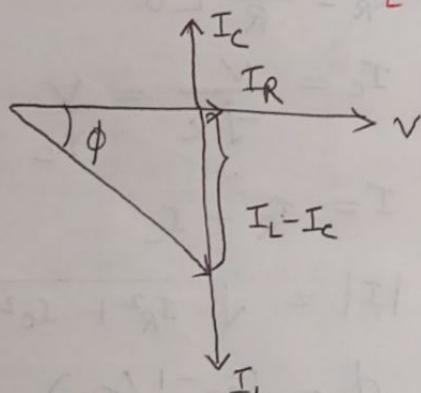
Case 2 : $x_L < x_C \rightarrow I_L > I_C$



$$|I| = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$\phi = \tan^{-1} \left(\frac{I_L - I_C}{I_R} \right)$$

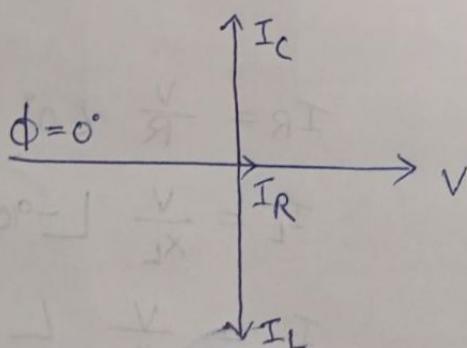Case 3 : $x_L = x_C \Rightarrow I_L = I_C$




$$|I| = I_R$$

$$\phi = 0^\circ$$


$$\cos \phi = \cos 0^\circ = 1$$

Unity power factor.

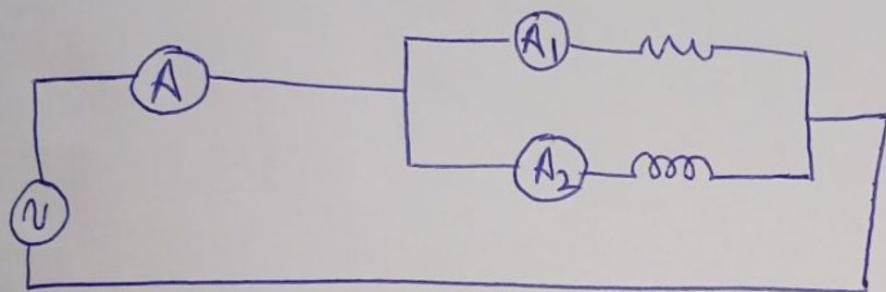Q) If A_1 reads 8A
 A_2 reads 6A
 A reads ?? Also find pf.



Solⁿ

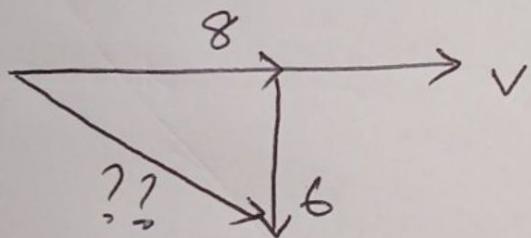

$$I = \sqrt{I_R^2 + I_L^2} = \sqrt{8^2 + 6^2} = \sqrt{100} = 10$$

$$\text{P.F.} = \frac{I_R}{I} = \frac{8}{10} = 0.8 \text{ (lagging)}$$

RMS value | True | Effective value


It is that steady value of a time varying voltage or current waveform which could produce the same value of heat as given by the original waveform for definite period of time.

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T [V(t)]^2 dt}$$

Average value / Mean value

It is that steady value of time varying voltage or current waveform which could develop same amount of charge as given by the original waveform for a definite period of time in a circuit.


Concept of Symmetry

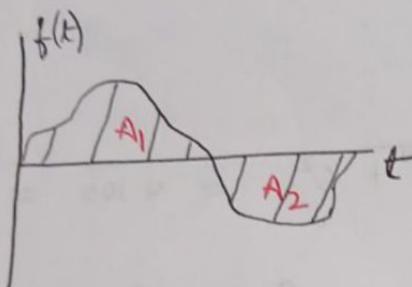

$$|A_1| = |A_2| \Rightarrow \text{Symmetrical}$$

$$|A_1| \neq |A_2| \Rightarrow \text{Asymmetrical}$$

Ex

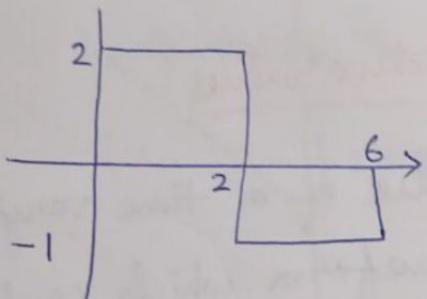

$$\text{+ve area} = |2 \times 2| = 4$$

$$-\text{ve area} = |4 \times (-1)| = 4$$

\therefore Symmetrical

NOTE

Average value of any symmetrical waveform for one full cycle is always zero.

I. For symmetrical waveform

$$V_{avg} = \begin{cases} 0 & \xrightarrow{\text{full cycle}} \\ \frac{1}{T/2} \int_0^{T/2} v(t) dt & \xrightarrow{\text{half cycle}} \end{cases}$$

2. For asymmetrical waveform

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt \longrightarrow \text{Full cycle}$$

Peak factor / Crest factor

$$\frac{V_{max}}{V_{rms}}$$

$$\Rightarrow \text{Form factor / Shape factor} = \frac{V_{rms}}{V_{avg}}$$

$$\Rightarrow \text{Peak to peak value } V_{P-P} = |V_{max} - V_{min}|$$

NOTE


Most of our electrical applications involves heat generation so we talk RMS values in general.

Ex → 1 ϕ , domestic supply in India
 $= 230V \rightarrow \text{RMS value}$

However applications like battery charging, electroplating, electrorefining etc involves charge so we calculate average values.

STANDARD WAVEFORMS

1.

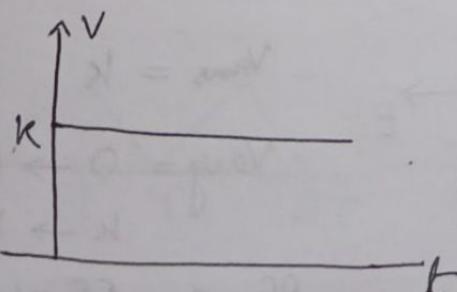


$$V_{rms} = K$$

$$V_{avg} = K$$

$$P.F. = 1$$

$$F.F. = 1$$

$$V_{P-P} = K$$

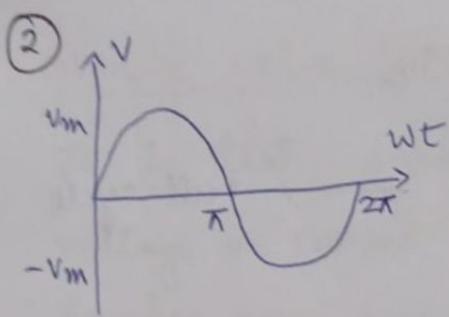


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\begin{aligned} V_{avg} &= 0 \rightarrow \text{full cycle} \\ &= \frac{2V_m}{\pi} \rightarrow \text{half cycle} \end{aligned}$$

$$PF = \sqrt{2}$$

$$FF = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$V_{pp} = 2V_m$$

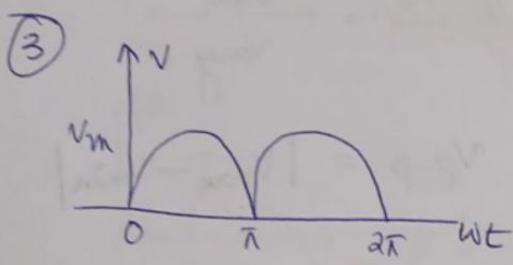


$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{avg} = \frac{2V_m}{\pi}$$

$$PF = \sqrt{2}$$

$$FF = 1.11$$


$$V_{pp} = V_m$$

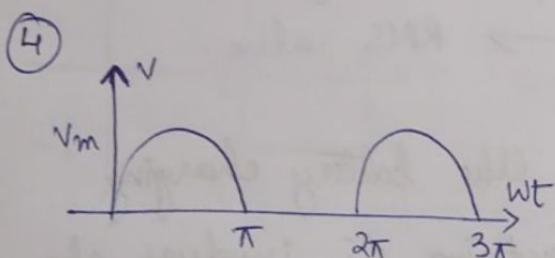

$$V_{rms} = \frac{V_m}{2}$$

$$V_{avg} = \frac{V_m}{\pi}$$


$$PF = 2 \quad FF = 1.57$$

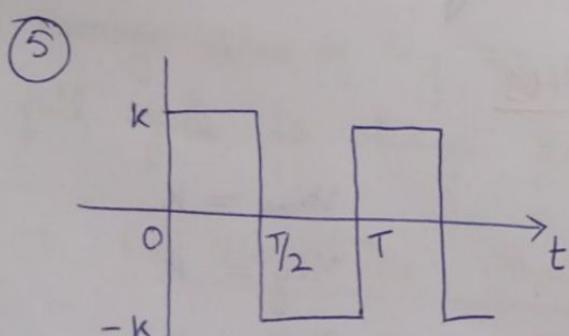

$$V_{rms} = k$$


$$\begin{aligned} V_{avg} &= 0 \rightarrow \text{full cycle} \\ &\quad k \rightarrow \text{half cycle} \end{aligned}$$
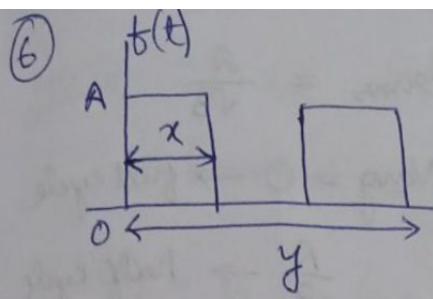
$$\begin{aligned} PF &= 1 \quad FF = 1.57 \\ V_{pp} &= V_m \end{aligned}$$



$$I_{\text{rms}} = A \sqrt{\frac{x}{y}}$$
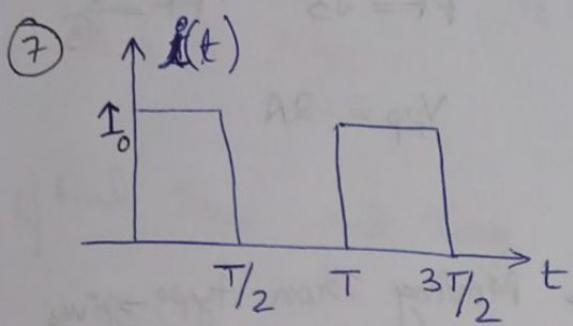
$$I_{\text{avg}} = A \left(\frac{x}{y} \right)$$




$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$I_{\text{avg}} = \frac{I_0}{2}$$

$$\text{PF} = \sqrt{2} \quad \text{FF} = \sqrt{2}$$


$$I_{\text{pp}} = I_0$$

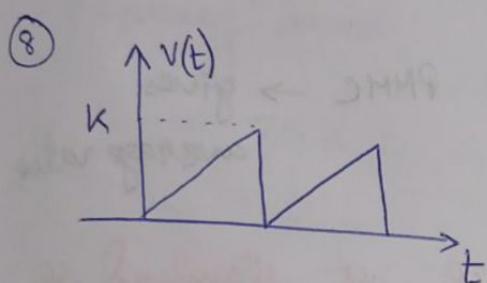

$$V_{\text{rms}} = \frac{k}{\sqrt{3}}$$

$$V_{\text{avg}} = \frac{k}{2}$$
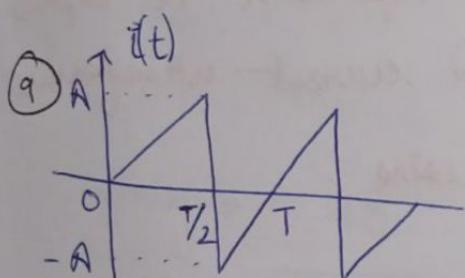
$$\text{PF} = \sqrt{3} \quad V_{\text{pp}} = k$$




$$I_{\text{rms}} = \frac{A}{\sqrt{3}}$$

$$I_{\text{avg}} = \begin{aligned} & 0 \rightarrow \text{full cycle} \\ & = \frac{A}{2} \rightarrow \text{half cycle} \end{aligned}$$

$$\text{PF} = \sqrt{3} \quad \text{FF} = \frac{2}{\sqrt{3}}$$

$$I_{\text{pp}} = 2A$$

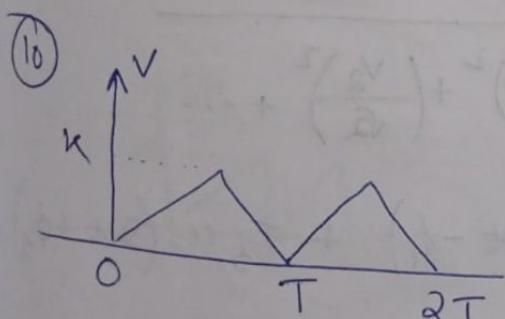


$$V_{\text{rms}} = \frac{k}{\sqrt{3}}$$

$$V_{\text{avg}} = \frac{k}{2}$$

$$\text{PF} = \sqrt{3} \quad \text{FF} = \frac{2}{\sqrt{3}}$$

$$V_{\text{pp}} = k$$

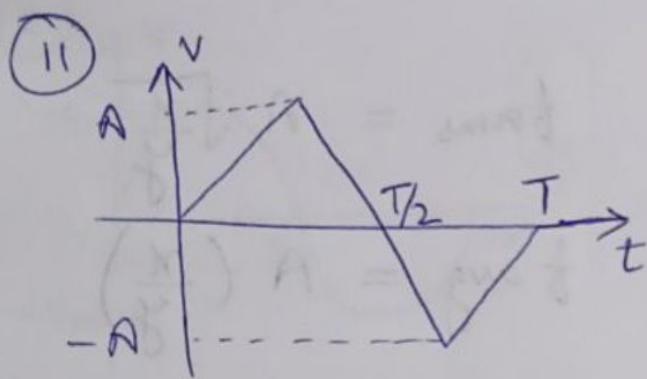

$$V_{\text{rms}} = \frac{A}{\sqrt{3}}$$

$V_{\text{avg}} = 0 \rightarrow \text{full cycle}$

$\frac{A}{2} \rightarrow \text{half cycle}$

$$\text{PF} = \sqrt{3} \quad \text{FF} = \frac{2}{\sqrt{3}}$$

$$V_{\text{pp}} = 2A$$

NOTE

- * AC Analog meters \rightarrow Moving Iron type \rightarrow gives RMS values
- * DC analog meters \rightarrow PMMC \rightarrow gives average value
- * Practical waveforms are not standard so we use Fourier series expansion to express the practical voltages and current waveforms in terms of Sine or cosine.

* Practical waveforms are not standard so we use Fourier series expansion to express the practical voltages and current waveforms in terms of sine or cosine.

Ex : $V(t) = V_0 + V_1 \sin \omega t + V_2 \sin 2\omega t + \dots$

$$\therefore V_{avg} = V_0$$

$$V_{rms} = \sqrt{V_0^2 + \left(\frac{V_1}{\sqrt{2}}\right)^2 + \left(\frac{V_2}{\sqrt{2}}\right)^2 + \dots}$$

$$i(t) = I_0 + I_1 \cos(\omega t - \phi_1) + I_3 \cos(3\omega t + \phi_3)$$

$$\therefore I_{avg} = I_0$$

$$I_{rms} = \sqrt{I_0^2 + \left(\frac{I_1}{\sqrt{2}}\right)^2 + \left(\frac{I_3}{\sqrt{2}}\right)^2}$$

NOTE : If frequency are same, dont use Fourier series concept.

$$v(t) = v_1 \sin(\omega t + \phi) + v_2 \sin(\omega t - \phi)$$

$$= v_1 L \phi + v_2 L - \phi$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

Q) find I_{rms} and I_{avg}

$$i(t) = 20 + 10 \sin(\underline{\omega t - 30^\circ}) + 7 \cos(\underline{\omega t + 40^\circ})$$

frequency same

$$= 20 + 10 \sin(\omega t - 30^\circ) + 7 \sin(\omega t + 130^\circ)$$


$$= 20 + (10 L - 30^\circ) + (7 L + 130^\circ)$$


$$= 20 + 4.16 + 0.36j$$

$$= 20 + [4.17 L 4.94^\circ]$$

$$I_{avg} = 20$$

$$I_{rms} = \sqrt{(20)^2 + \left(\frac{4.17}{\sqrt{2}}\right)^2} = 20.21$$


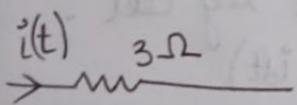
Q)  Find P_{lost}

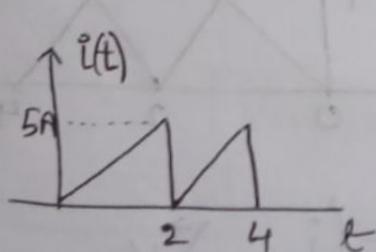

$$P_{lost} = I_{rms}^2 \times R$$

$$= \left(\frac{5}{\sqrt{3}}\right)^2 \times 3$$

$$= 25 W$$

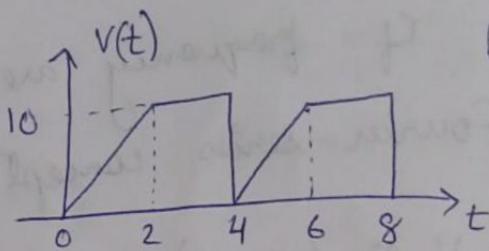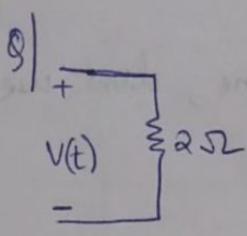

Find P_{lost}
for $t = 4$

$$P_{\text{lost}} = \frac{V_{\text{rms}}^2}{R}$$

$0 < t < 2$

$$V(t) = 5t$$

$$\begin{aligned} &\text{at } t=0, V=0 \\ &\text{at } t=2, V=10 \\ &\frac{10-0}{2-0} = 5 \end{aligned}$$



$2 < t < 4$

$$V(t) = 10$$

$$\begin{aligned} V_{\text{rms}} &= \sqrt{\frac{1}{T} \left[\int_0^2 V(t)^2 dt + \int_2^4 V(t)^2 dt \right]} \\ &= \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (10)^2 dt \right]} \\ &= \sqrt{66.66} \end{aligned}$$

$$P_{\text{lost}} = \frac{(V_{\text{rms}})^2}{R} = \frac{66.66}{2} = 33.33 \text{ W}$$

Q1 Find total power absorbed by cell

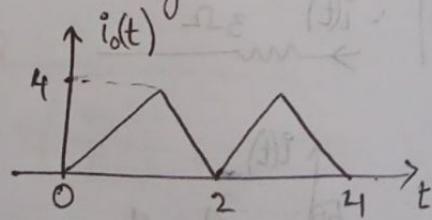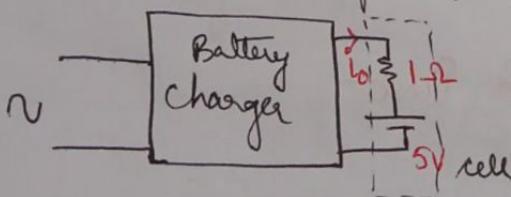


$$P_{\text{absorbed}} = (i_{\text{o rms}})^2 R + (i_{\text{o avg}}) V$$

Now, from standard waveforms,
 $i_{\text{o rms}} = \frac{4}{\sqrt{3}}$
 $i_{\text{o avg}} = \frac{4}{2} = 2$

$$P_{\text{loss}} = \left(\frac{4}{\sqrt{3}}\right)^2 \times 1 + 2 \times 5$$

$$= \frac{16}{3} + 10 = 15.33 \text{ W}$$

Q) find Z_{eq} .

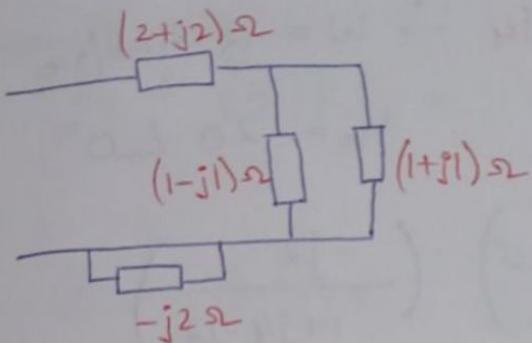


$$Z_{eq} = (2+j2) + [(1-j1) \parallel (1+j1)]$$

$$= (2+j2) + \frac{(1-j1)(1+j1)}{(1+j1)+(1-j1)}$$

$$= (2+2j) + \frac{1+j1-j1-j^2}{1+j1+1-j1}$$


$$= (2+2j) + \frac{2}{2}$$

$$Z_{eq} = 3+j2$$

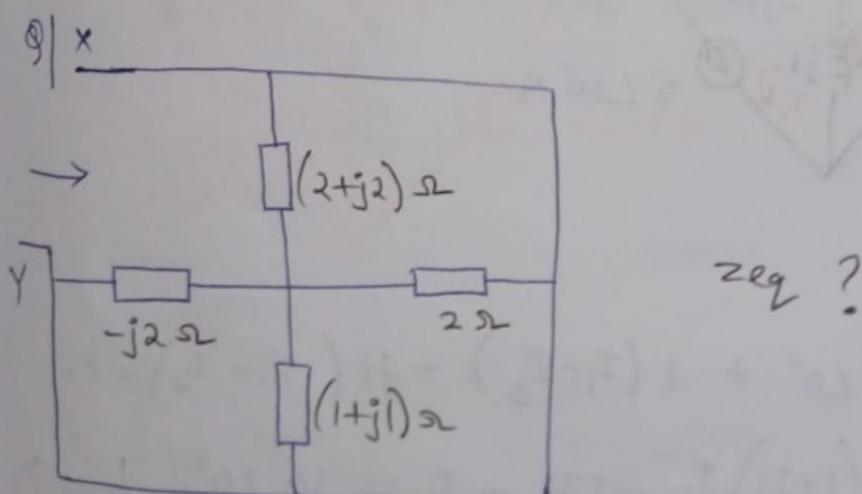

$$Z_{eq} = 0$$

Q1 find V_o .

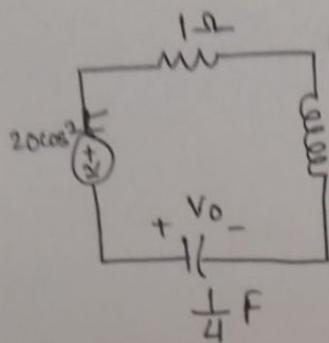

$$2H = +j\omega L \quad V = 20 \cos 2t$$

$$\text{Here, } \omega = +j 2 \times 2 = j4 \quad \therefore \omega = 2 \text{ rad/sec}$$

$$= -j\omega C$$

$$V_m = 20 \angle 0^\circ$$

$$\therefore V_o = - \left(\frac{20 \angle 0^\circ}{\sqrt{2}} \right) \left(\frac{-j2}{1+j4-j2} \right)$$


voltage division rule

\uparrow
 V_{rms}

$$= \frac{-(10\sqrt{2} \angle 0^\circ)(-j2)}{1+j2}$$

$$= (11.3 + 5.6j) \text{ V}$$

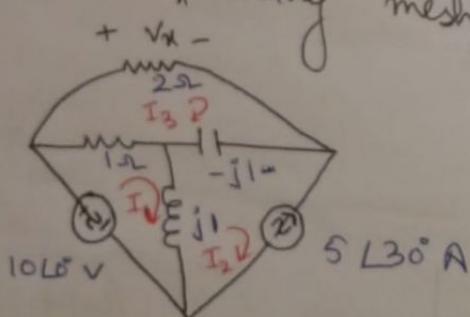Q1 find V_x using mesh and nodal analysis.



Mesh

$$-10 \angle 0^\circ + 1(I_1 - I_3) + j1(I_1 - I_2) = 0$$

$$\Rightarrow (1+j1)I_1 - jI_2 - I_3 = 10 \angle 0^\circ \quad \rightarrow ①$$

$$2I_3 - j1(I_3 - I_2) + 1(I_3 - I_1) = 0$$

$$\therefore -I_1 + jI_2 + (3-j)I_3 = 0 \quad \rightarrow ②$$

$$I_2 = -5 \angle 30^\circ \rightarrow \textcircled{3}$$

From ① and ③,

$$(1+j1) I_1 - I_3 = \underbrace{12.5 - j4.33}_{10 - 5 \angle 120^\circ} \rightarrow \textcircled{A}$$

From ② and ③

$$-I_1 + (3-j) I_3 = \underbrace{5 \angle 120^\circ}_{-2.5 + j4.33} \rightarrow \textcircled{B}$$


$$\therefore \textcircled{A} \Rightarrow (1+j1) I_1 - I_3 = 12.5 - j4.33$$

$$\textcircled{B} \times (1+j) \Rightarrow -(1+j) I_1 + (4+2j) I_3 = -6.83 + j1.83$$

$$(3+j2) I_3 = 5.67 - j2.5$$

$$\therefore I_3 = 1.71 \angle -57.48^\circ \text{ A}$$

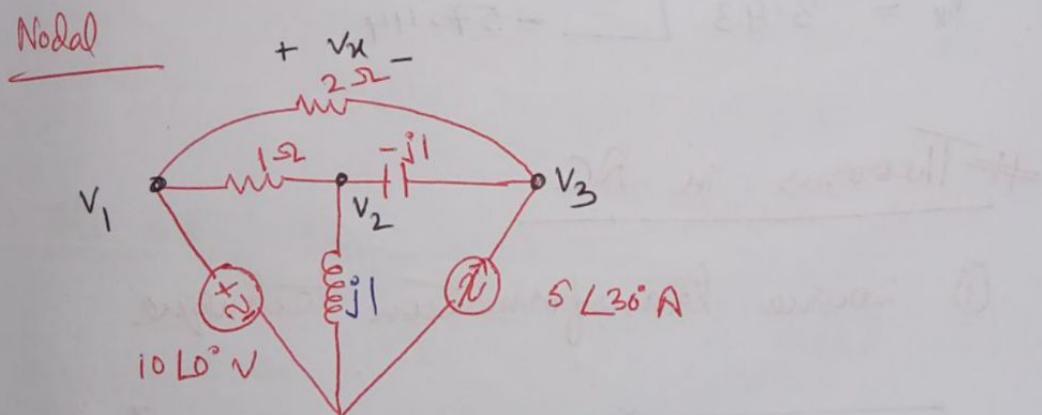Now, $V_u = 2I_3 = 3.42 \angle -57.48^\circ \text{ V}$



$$V_1 = 10 \rightarrow \textcircled{1}$$

$$\frac{V_2 - 10}{1} + \frac{V_2}{j} + \frac{V_2 - V_3}{-j1} = 0$$

$$\Rightarrow V_2 - 10 + jV_2 + j(V_2 - V_3) = 0$$

$$\Rightarrow V_2 - jV_3 = 10 \rightarrow \textcircled{2}$$

$$-(\text{---} \angle 30^\circ) + \frac{v_3 - v_2}{-j1} + \frac{v_3 - 10}{2} = 0$$

$$\Rightarrow \frac{j(v_3 - v_2)}{1} + \frac{v_3 - 10}{2} = 5 \angle 30^\circ$$

$$\Rightarrow -j2 v_2 + (1+j2) v_3 = 10 + 10 \angle 30^\circ$$

$$= 18.66 + j5 \rightarrow ③$$

$$② \times j2 \Rightarrow j2 v_2 + 2 v_3 = j20$$

$$③ \Rightarrow -j2 v_2 + (1+j2) v_3 = 18.66 + j5$$

$$v_3 = \frac{18.66 + j5}{3+j2}$$


$$v_3 = 8.65 \angle 19.57^\circ$$

$$v_x = v_1 - v_3 = 10 - (8.66 \angle 19.57^\circ)$$

$$v_x = 3.43 \angle -57.44^\circ$$

Theorems in AC

① source transformation technique

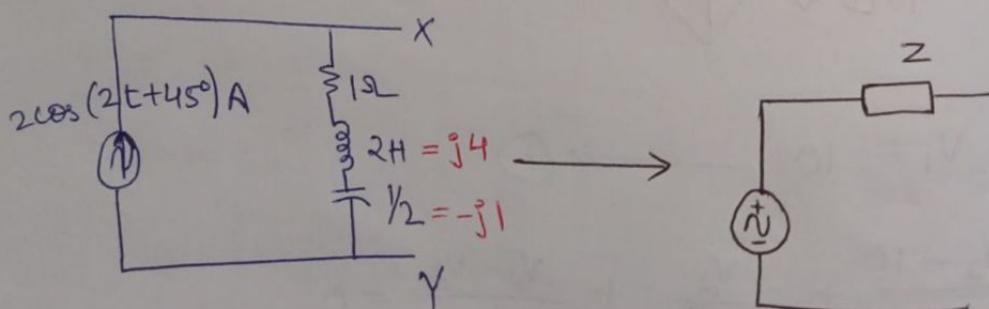

Here, $I = 2 \cos(2t + 45^\circ) = 2 \angle 45^\circ$
 $w = 2$

$$z = 1+j4 - j1 = (1+j3) \Omega$$

$$V = I \cdot z$$


$$= 2 \angle 45^\circ (1+j3)$$

$$= 2 \angle 45^\circ \times 3.16 \angle 71.56^\circ$$

$$= 6.32 \angle 116.56^\circ$$

$$\therefore V = 6.32 \cos(2t + 116.56^\circ) V$$

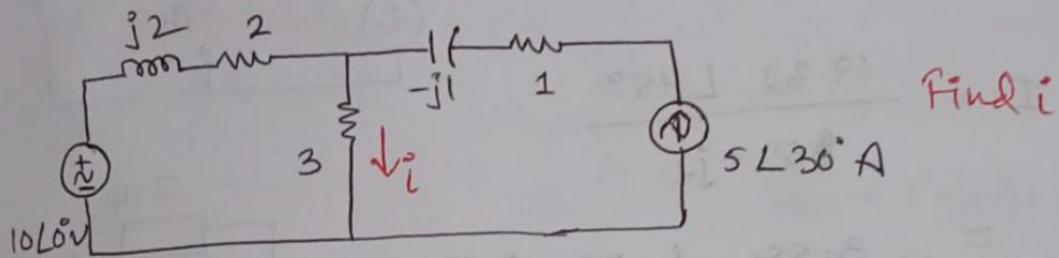② Superposition, Thevenins, Nortons theorem



① Superposition Theorem

$$\text{10V only} : i^1 = \frac{10 \angle 0^\circ}{5+j2} \text{ or } \frac{10 \angle 0^\circ}{5\sqrt{5}} \angle -21.8^\circ$$

$$i^1 = 1.857 \angle 21.8^\circ$$

$$\text{5A only} : i^{11} = 5 \angle 30^\circ \left(\frac{2+j2}{5+j2} \right)$$


$$= 5 \angle 30^\circ (+$$

$$= 2.61 \angle 53.19^\circ$$

$$i = i^1 + i^{11} = 3.58 \angle 23.2^\circ$$

Thevenin theorem


$$Z_{TH} = (2 + j2) \Omega$$

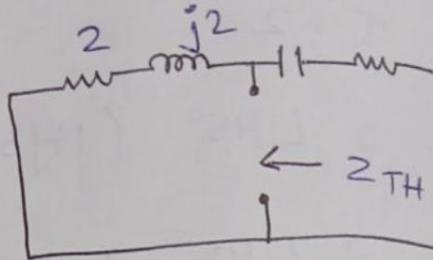

KVL


$$-10 \angle 0^\circ + V_{TH} - (2+j2) 5 \angle 30^\circ = 0$$

$$V_{TH} = 19.32 \angle 45^\circ$$

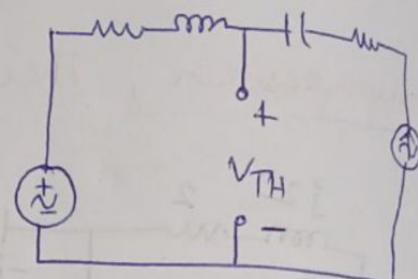

$$I = \frac{19.32 \angle 45^\circ}{2.82 + j2}$$

$$= 3.58 \angle 23.2^\circ A$$

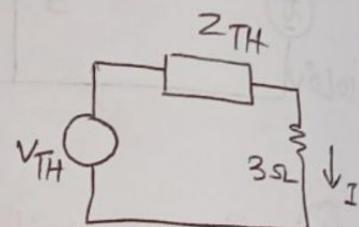


Norton theorem

$$I_N = \frac{10 \angle 0^\circ + 5 \angle 30^\circ}{2 + j2}$$


$$= \frac{10 \angle 0^\circ}{2.82 \angle 45^\circ} + 5 \angle 30^\circ$$

$$= 6.83 \angle 0^\circ$$

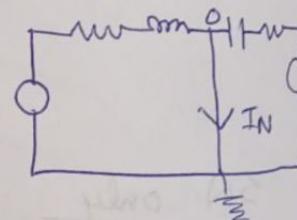

$$I = 6.83 \angle 0^\circ \left(\frac{2+j2}{5+j2} \right)$$

$$= 3.58 \angle 23.2^\circ A$$

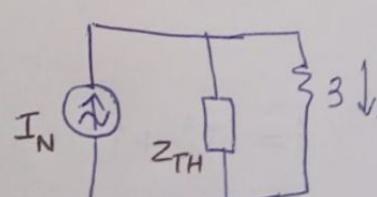

Maximum Power Transfer Theorem in AC

Though there are 3 types of physical power existing in AC steady state n/w, the power that is consumable / utilizable / convertible in any other form is Active power or real power in Watts.


Max^m. power transfer theorem is confined to active power only.

General case


P_{max} occurs in the load when $Z_L = Z_{TH}^*$

$$P_{max} = \frac{|V_{TH}|^2}{4 R_{TH}}$$
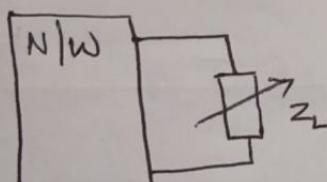
$$R_{TH} = \text{Real part } [Z_{TH}^*]$$




Z_L is controllable

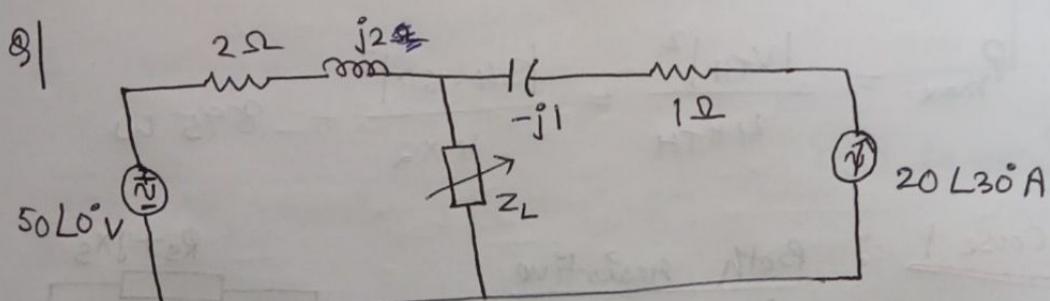


Find value of Z_L for which P_{max} occurs and find P_{max} .

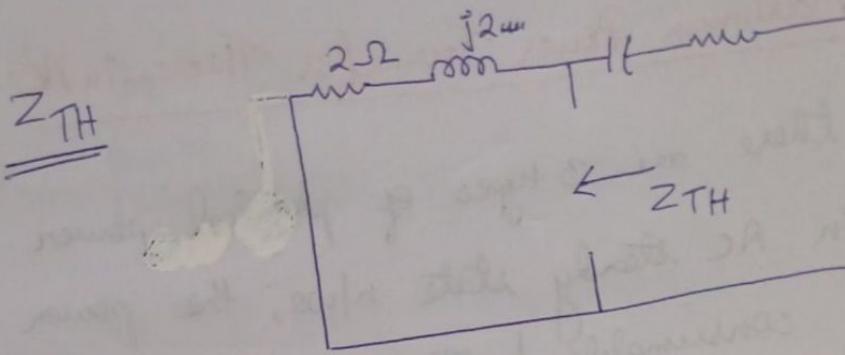Determine Thvenin equivalent across Z_L .



$$Z_{TH} = (2 + j2) \Omega$$

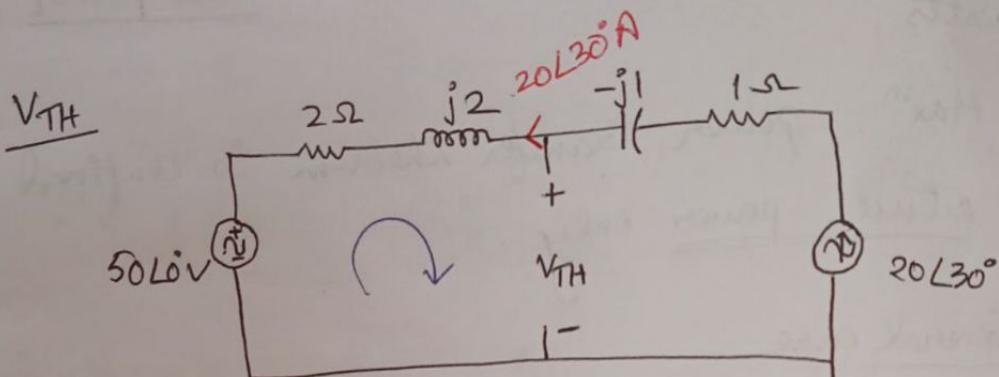

$$-(50L0) - (2 + j2) 20L30^\circ + V_{TH} = 0$$

$$\Rightarrow V_{TH} = 84.64 \angle 40.2^\circ$$

Now,


$$Z_L = Z_{TH}^* = (2 - j2) \Omega$$

\uparrow
 R_{TH}

$$P_{max} = \frac{|V_{TH}|^2}{4R_{TH}} = \frac{|84.64|^2}{4 \times 2} = 895 \text{ W}$$

Case 1 : Both resistive and reactive part are controllable

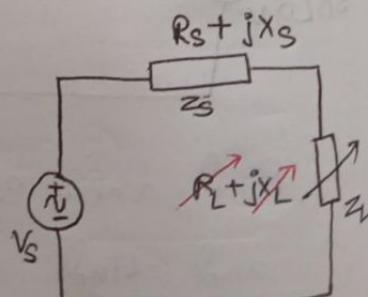
P_{max} occurs in load if load impedance is complex conjugate of equivalent source impedance seen by it.



$$Z_L = Z_S^* = R_S - jX_S$$

$$P_{\max} = \frac{|V_S|^2}{4R_S} \quad V_S \rightarrow \text{RMS value}$$

Case 2 : Load is controllable resistor

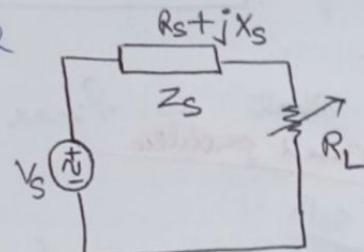

Load is purely resistive but source has some reactance, we cannot avoid reactive power in n/w.


P_{\max} occurs in load if

$$R_L = |Z_S| = \sqrt{R_S^2 + X_S^2}$$

$$P_{\max} = I_{\text{rms}}^2 \times R_L$$

Case 3 : R_L variable, X_L non variable

$$\begin{aligned} R_L &= |R_S + jX_S + jX_L| \\ &= \sqrt{R_S^2 + (X_L + X_S)^2} \end{aligned}$$

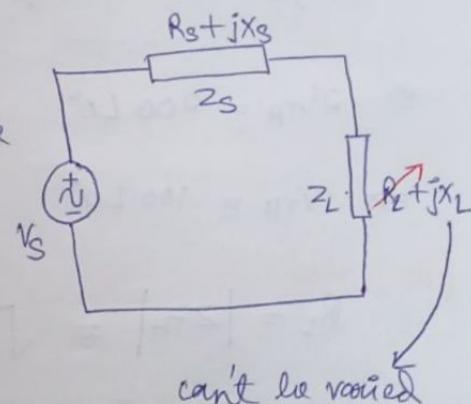


Case 4 : X_L variable, R_L constant


For P_{\max} ,

$$X_L = -X_S$$

$$\Rightarrow X_L + X_S = 0$$

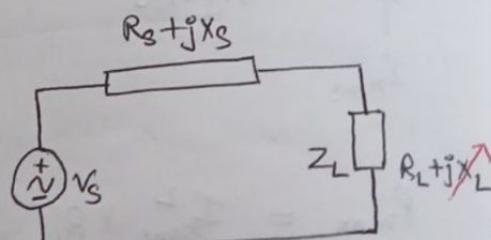


P_{\max} occurs if $X_L = -X_S$
in load

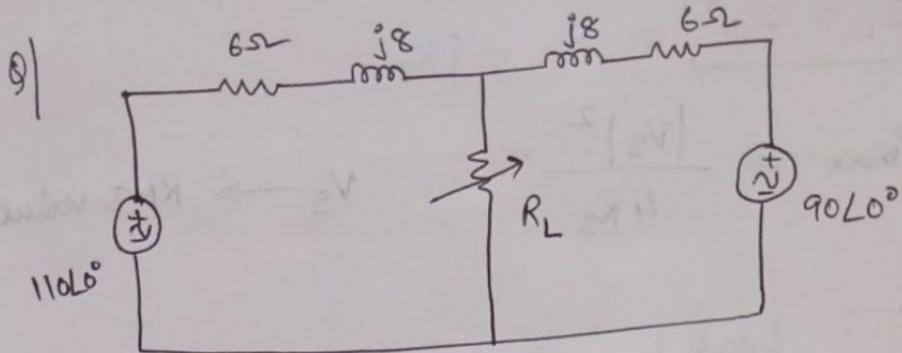

What is P_{max} transferred to load?
Cube 2 problem

Sol^u
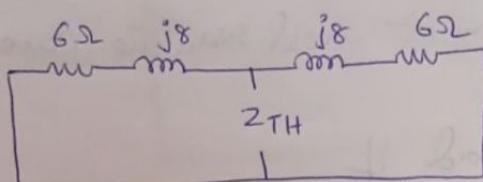
$$Z_{TH} = (6+j8) \parallel (6+j8) = (3+j4) \Omega$$



V_{TH}

Nodal Analysis

$$\frac{V_{TH} - 110 L0^\circ}{6+j8} + \frac{V_{TH} - 90 L0^\circ}{6+j8} = 0$$

$$\Rightarrow 2V_{TH} = 200 L0^\circ$$

$$\Rightarrow V_{TH} = 100 L0^\circ$$

$$R_L = |Z_{TH}| = \sqrt{3^2 + 4^2} = 5 \Omega$$


$$I_{5\Omega} = \frac{100 L0^\circ}{3+j4+5} = 11.18 \angle -28.56^\circ$$

I_{rms}


$$P_{max} = I_{rms}^2 \times R_L$$

$$= |11.18|^2 \times 5$$

$$= 625 W$$

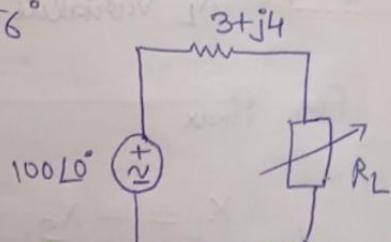


Q/ Find P_{max} transferred to load.

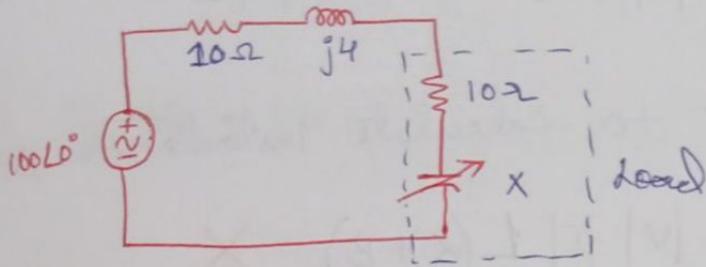

Case 4 problem

Sol^M
 $Z_{TH} =$

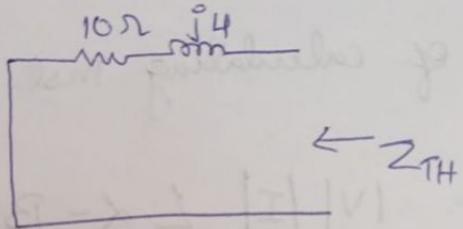

$$\therefore Z_{TH} = 10 + j4$$

$$\therefore X_L = -X_S$$

$$\Rightarrow X = -j4$$

$$P_{max} = \left(\frac{100 \angle 0^\circ}{10 + j4 + 10 - j4} \right)^2 \times 10 = I^2 R$$

$$= 250 \text{ W}$$

Complex Power (S^*) \rightarrow volt amperes (VA)

$$S^* = VI^*$$

It is used to calculate instantaneous power in AC circuit.

I^* \rightarrow complex conjugate of I

$$I = 10 \angle 20^\circ \text{ A} \Rightarrow I^* = 10 \angle -20^\circ \text{ A}$$

~~NOTE~~ ① If $V = |V| \angle \alpha$, $I = |I| \angle \beta$

If we want to calculate instantaneous power

$$V \cdot I = |V| |I| \angle (\alpha + \beta) \times$$

Correct way of calculating inst. power


$$V \cdot I^* = |V| |I| \angle \alpha - \beta \checkmark$$

② If $V = |V| \angle \alpha$, $I = |I| \angle -\beta$

$$V \cdot I = |V| |I| \angle \alpha - \beta \times$$

Correct way : $V \cdot I = |V| |I| \angle (\alpha + \beta)$

✓

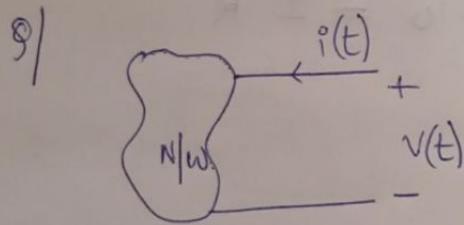

$$\text{Here, } V(t) = 20 + j12$$

$$i(t) = 5 + j4$$

Calculate P and Q.

Sol^u

$$V(t) = 20 + j12 = 23.32 \angle 30.96^\circ V$$

$$i(t) = 5 + j4 = 6.4 \angle 38.65^\circ A$$


Complex power, $S^* = V I^*$

$$= |23.32| |6.4| \angle (30.96 - 38.65)$$

$$P = 147.9 - j19.97$$

$$P = 147.9 \text{ watts}, Q = 19.97 \text{ VARs}$$

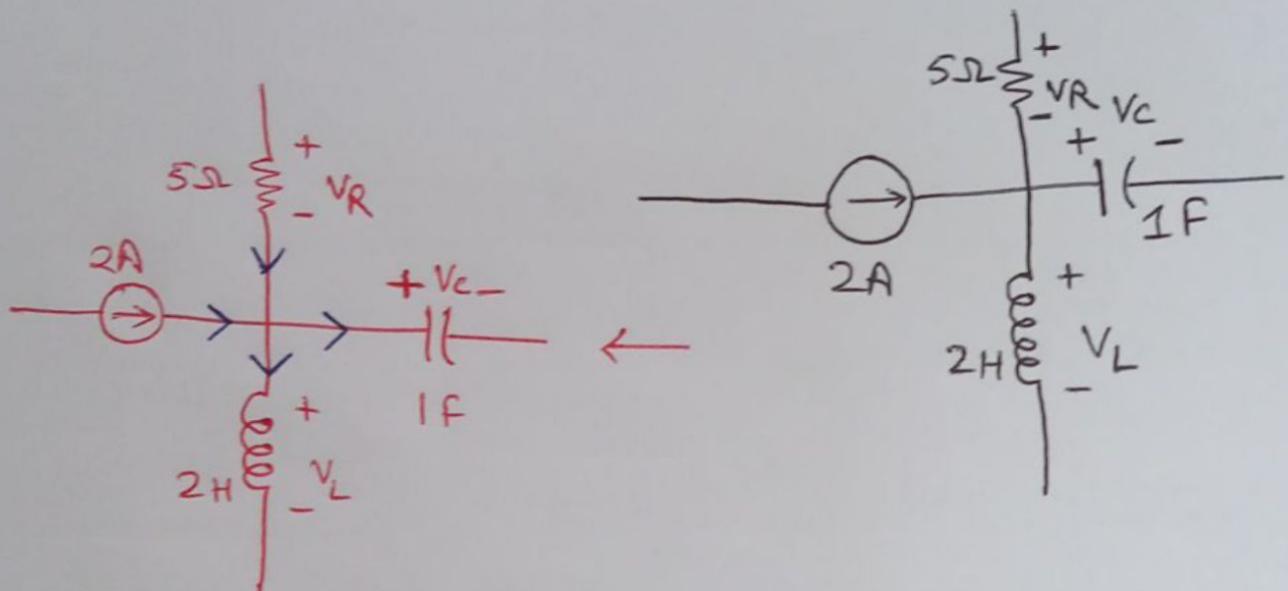Q) If $V_R = 5V$, $V_C = 4\sin 2t \text{ V}$, $V_L = ?$



Using KCL, $2 + \frac{V_R}{5} = -\frac{dV_C}{dt} + \frac{1}{2} \int V_L dt$

$$\Rightarrow \frac{1}{2} \int V_L dt = 2 + 1 - 8 \cos 2t$$

$$\Rightarrow \int V_L dt = 6 - 16 \cos 2t$$

$$\Rightarrow V_L = \frac{d}{dt} (6 - 16 \cos 2t)$$

$$\Rightarrow V_L = 32 \sin 2t \text{ V}$$