


Practice Set 1 Answer

1.

$$-V + \frac{I}{3} \times 6 + \frac{I}{6} \times (6) + \frac{I}{3} (6) = 0$$

$$\Rightarrow V = I (2 + 1 + 2)$$

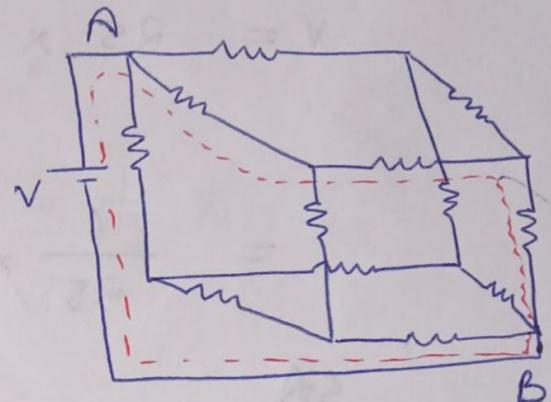
$$\Rightarrow \frac{V}{I} = R_{AB} = 5 \Omega$$



2. $R_{AB} = 0 \Omega$

3.


R_{XY}

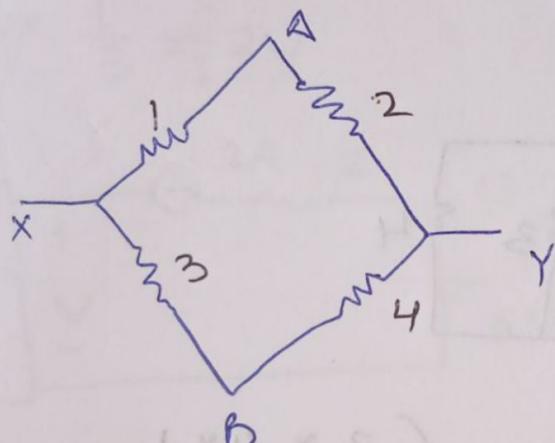

$$R_{XY} = 3117$$



$$= \frac{21}{10}$$

R_{AB}

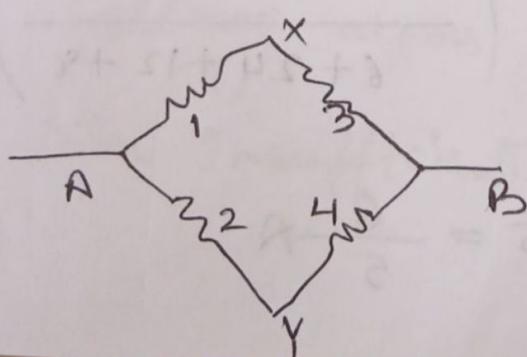


$$R_{AB} = 4116$$


$$= \frac{12}{5}$$

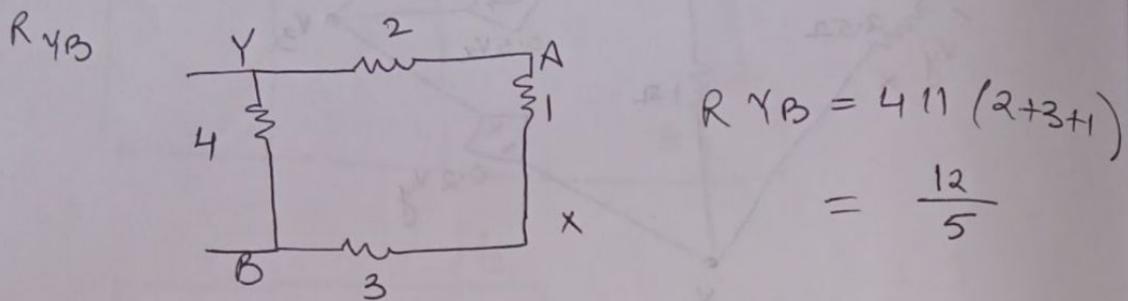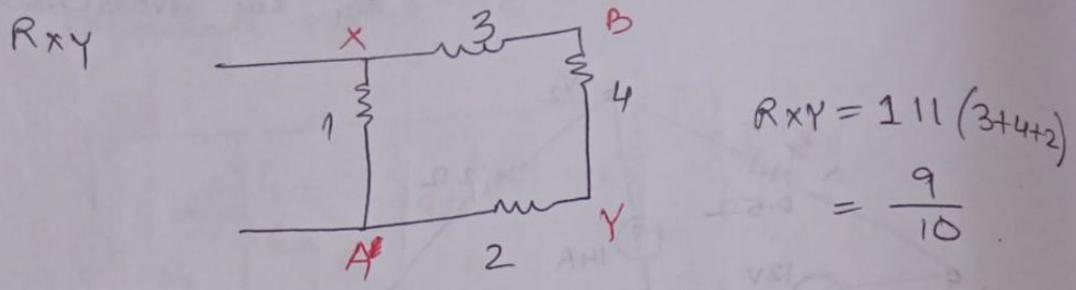

4.

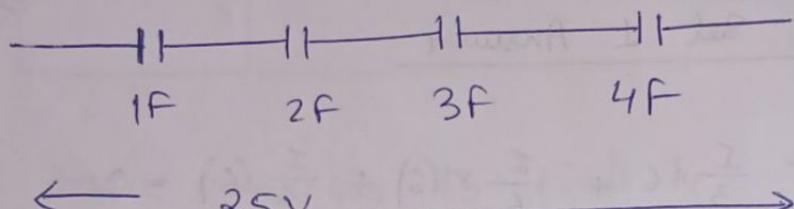

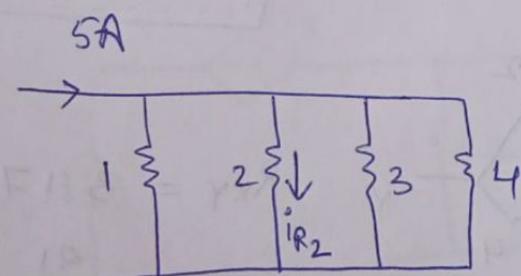
$$V = 25 \times \left[\frac{\frac{1}{2}}{\frac{1}{1} + \frac{1}{2} + \frac{1}{3} + \frac{1}{4}} \right] = \frac{6}{25} \times 25 = 6 V$$



$$i_{R2} = 5 \times \left(\frac{3 \times 4 \times 1}{6 + 24 + 12 + 8} \right) = \frac{6}{25} \times 5 = \frac{6}{5} A$$

7.


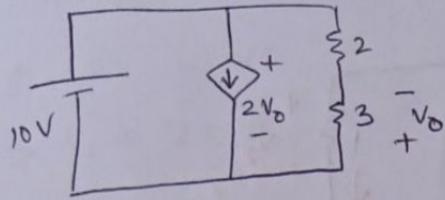


$$V_o = -10 \left(\frac{3}{2+3} \right) = -6V$$

$$P = V \times I$$

$$= 10 \times 12 = 120 W$$

8.

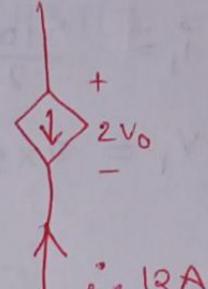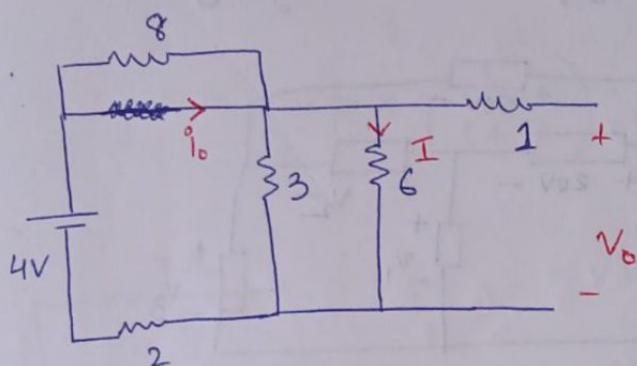

$$6113 = 2\Omega$$


8Ω is redundant (useless)

$$i_o = \frac{V}{R} = \frac{4}{2+2} = 1A$$

$$I = 1 \left(\frac{3}{6+3} \right) = \frac{3}{9} = \frac{1}{3} A$$

$$V_o = 6 \times \frac{1}{3} = 2V$$


9.

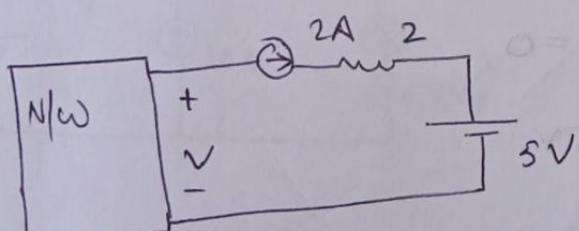

$$\frac{V-5}{2} = 2$$

$$\Rightarrow V = 9V \quad X$$

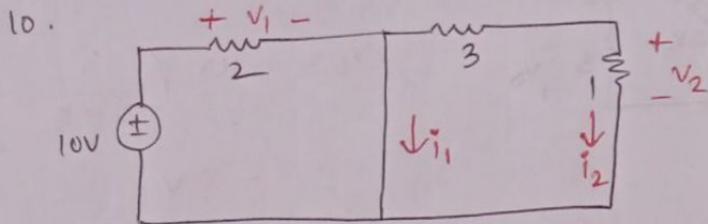voltage across 1 source not given
data insufficient.




$$i_1 = \frac{10}{2} = 5A$$

$$i_2 = 0$$

$$v_1 = 2 \times 5 = 10V$$

$$v_2 = 0$$

11.

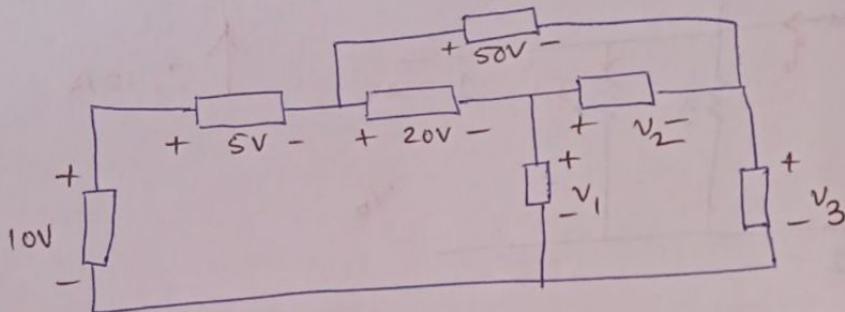

$$-10 + 25 + v_1 = 0$$

$$\Rightarrow v_1 = -15V$$

$$-20 + 50 - v_2 = 0$$


$$\Rightarrow -v_2 = -30$$

$$\Rightarrow v_2 = 30V$$

$$+15 + 30 + v_3 = 0$$

$$\Rightarrow v_3 = -45V$$

12.

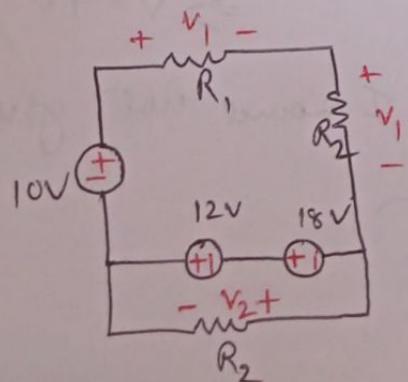

$$v_2 + 12 + 18 = 0$$


$$\Rightarrow v_2 = -30V$$

$$-10 + 2V_1 - 18 - 12 = 0$$

$$\Rightarrow 2V_1 = 40$$

$$\Rightarrow V_1 = 20 \text{ V}$$


13.

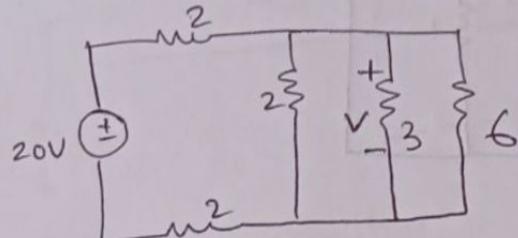

$$6/13/11/2 = 1\Omega$$

$$\therefore V = 20 \times \left(\frac{1}{1+4} \right) = 5 \text{ V.}$$

14.

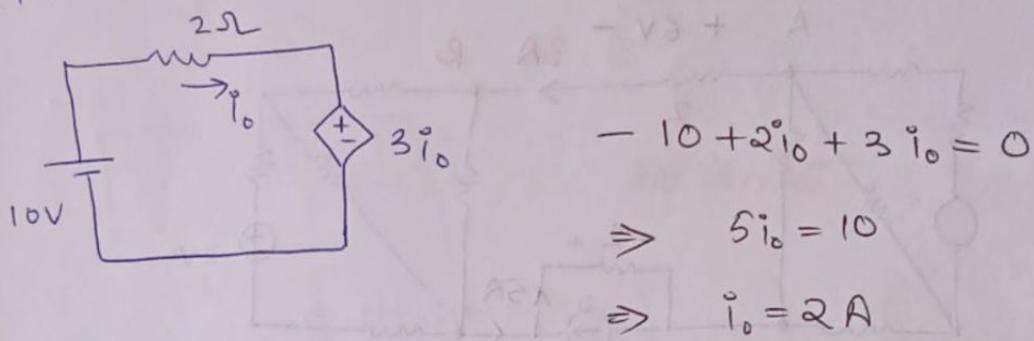

$$-V_3 + A$$

$$-10 + 2i_o + 3i_o = 0$$

$$\Rightarrow 5i_o = 10$$



$$\Rightarrow i_o = 2 \text{ A}$$

$$\therefore P_{\text{delivered}} = + 6 \times 2 = 12 \text{ W}$$

Since i flowing inwards [sink]

$$P_{\text{delivered}} = - 6 \times 2 = 12 \text{ W}$$


15.

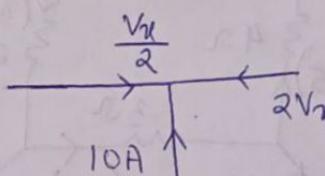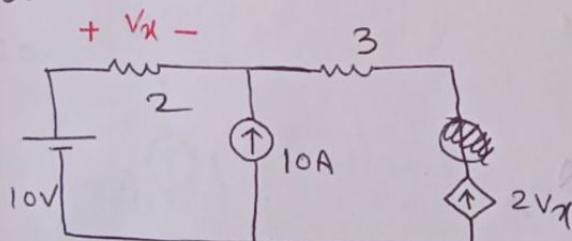

$$\frac{V_x}{2} + 10 + 2V_x = 0$$

$$\Rightarrow V_x = -4 \text{ V}$$


16.

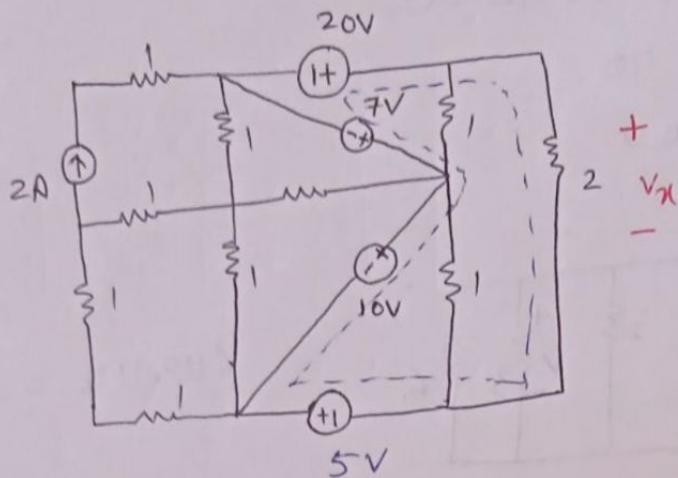

$$-5 - 10 + 7 - 20 + V_x = 0$$


$$\Rightarrow V_x = 28V$$

17.

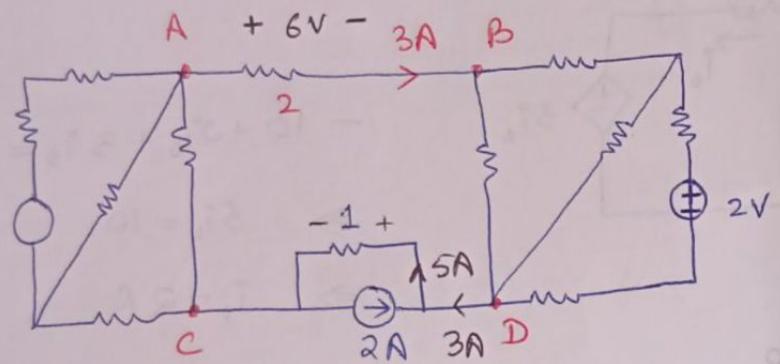

$$V_C - V_D = -5V$$

18.

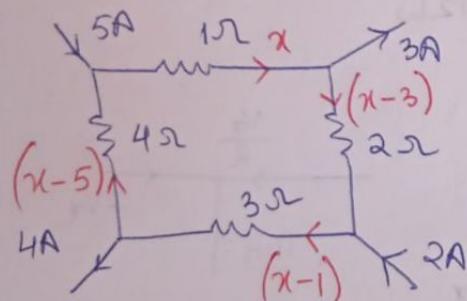


$$x + (x-3)2 + (x-1)3 + (x-5)4 = 0$$

$$\Rightarrow x = 2.9A$$

$$P_T = (2.9)^2(1) + (2.9-1)^2(2) + (2.9-5)^2(4)$$


$$P_T = (2.9)^2(1) + (0.1)^2(2) + (1.9)^2(3) + (2.1)^2(4) = 36.9W$$

19.

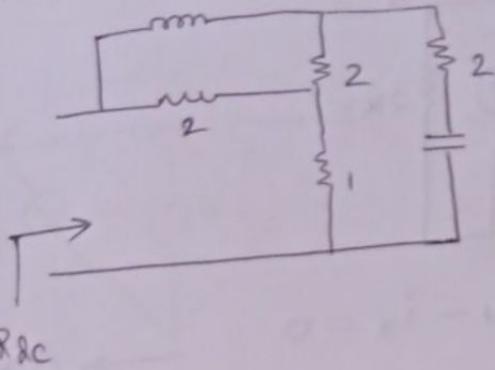



under dc condition,

inductor becomes s.c.

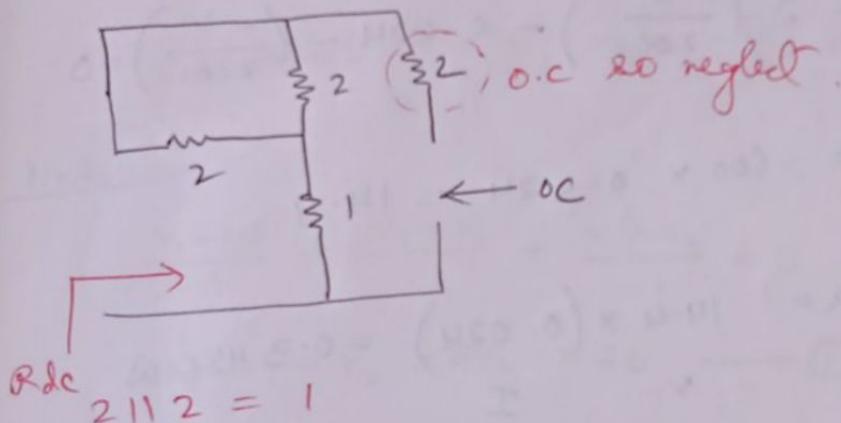—m—capacitor \rightarrow o.c. becomes o.c.

$$\therefore R_{dc} = 1 + 1 = 2 \Omega$$

20.

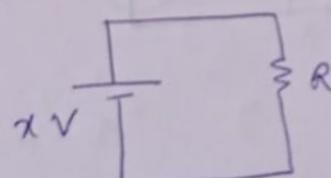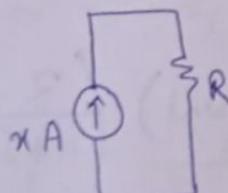

$$P = I^2 R = x^2 R = 18$$

$\hookrightarrow ②$


$$P = \frac{V^2}{R} = \frac{x^2}{R} = 4.5$$

$$\Rightarrow x^2 = 4.5R$$

Put ① in ②,

$$(4.5R) R = 18 \Rightarrow R = \sqrt{\frac{180}{45}} = 2 \Omega$$
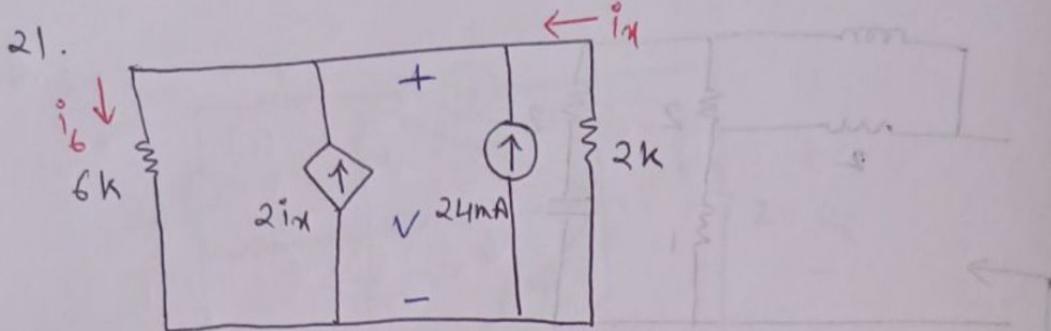
$$② \Rightarrow \frac{x^2 \times 2}{R} = 18 \Rightarrow x = 3$$



$$\text{KCL} \quad i_6 - 2i_x - 0.024 - i_x = 0 \quad \rightarrow \textcircled{1}$$

~~Also~~ we can write,


$$i_6 = \frac{V}{6000} \quad i_x = -\frac{V}{2000}$$

Replacing in $\textcircled{1}$,

$$\frac{V}{6000} - 2 \left(-\frac{V}{2000} \right) - 0.024 - \left(\frac{-V}{2000} \right) = 0$$

$$\Rightarrow V = 600 \times 0.024 = 14.4$$

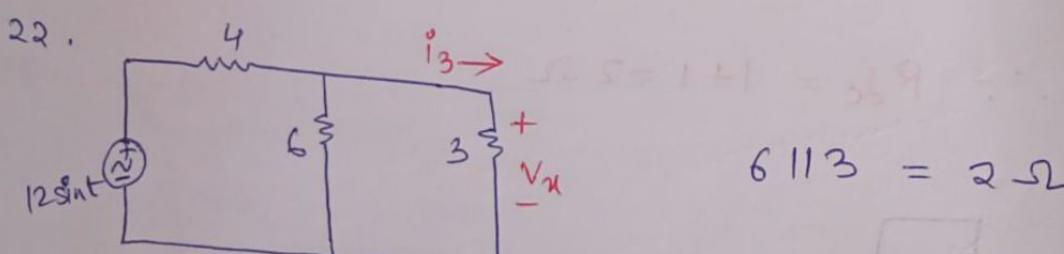
$$\therefore \text{Power} = \frac{14.4}{V} \times (0.024) = 0.3456 \text{ W}$$



$$V_x = (12 \sin t) \left(\frac{2}{4+2} \right)$$

$$= 4 \sin t \text{ volts.}$$

Practice set 2 answers

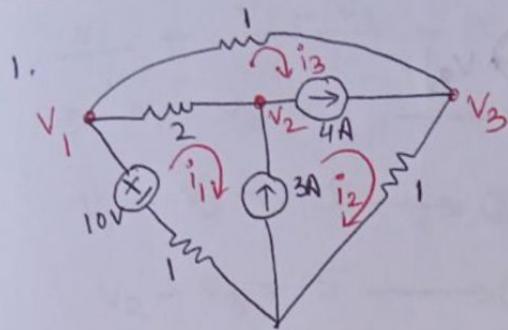

Mesh

$$i_1 - 10 + i_3 + i_2 = 0$$



$$\Rightarrow i_1 + i_2 + i_3 = 10 \rightarrow ①$$

$$i_2 - i_1 = 3 \rightarrow ②$$

$$i_2 - i_3 = 4 \rightarrow ③$$

$$\text{Solving we get, } i_1 = \frac{8}{3}$$

$$\therefore P_{\text{delivered}} = 10 \times \frac{8}{3} = \frac{80}{3} \text{ W}$$

Nodal

$$\frac{V_1 - 10}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{1} = 0$$

$$\Rightarrow 5V_1 - V_2 - 2V_3 = 20 \rightarrow ①$$

$$\frac{V_2 - V_1}{2} - 3 + 4 = 0$$

$$\Rightarrow V_2 - V_1 = -2 \rightarrow ②$$


$$\frac{V_3}{1} + \frac{V_3 - V_1}{1} - 4 = 0$$


$$\Rightarrow -V_1 + 2V_3 = 4 \rightarrow ③$$

$$\therefore V_1 = \frac{22}{3}$$

$$\therefore I = \frac{10 - \frac{22}{3}}{1} = \frac{8}{3} \text{ A}$$
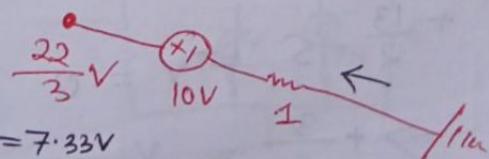
$$P = 10 \times \frac{8}{3} = \frac{80}{3} \text{ W}$$



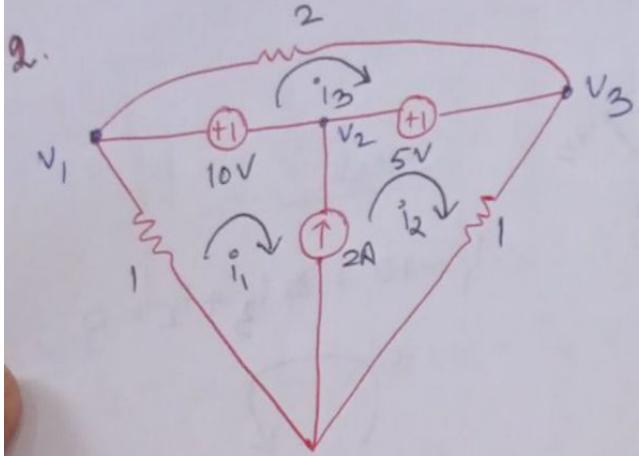

Mesh

$$i_1 + 2i_3 + i_2 = 0 \rightarrow ①$$

$$-5 - 10 + 2i_3 = 0$$

$$\Rightarrow 2i_3 = 15$$


$$\Rightarrow i_3 = \frac{15}{2} \rightarrow ②$$

$$\therefore ① \Rightarrow i_1 + i_2 + 2 \times \frac{15}{2} = 0$$

$$\Rightarrow i_1 + i_2 = -15 \rightarrow ③$$

$$\text{Also, } i_2 - i_1 = 2 \rightarrow ④$$
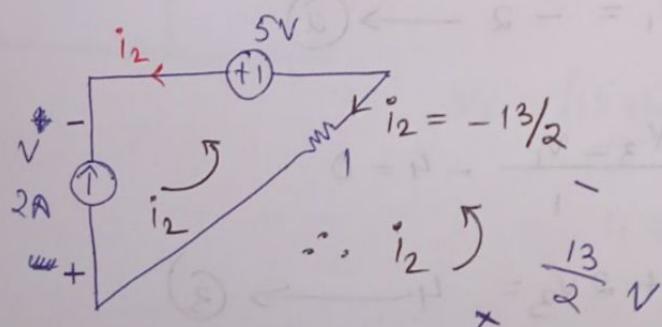
$$\therefore i_2 = -\frac{13}{2} \quad i_1 = -\frac{17}{2}$$



$$+\frac{13}{2} - 5 - V = 0$$

$$\Rightarrow +\frac{3}{2} = V$$

$$\therefore P_{\text{del}} = -2 \times \frac{3}{2} = -3 \text{ W}$$

Nodal

$$\frac{v_1}{1} + \frac{v_1 - v_3}{2} - 2 + \frac{v_3}{1} + \frac{v_3 - v_1}{2} = 0$$

$$\Rightarrow v_1 + v_3 = 2 \rightarrow \textcircled{1}$$


$$v_1 - v_2 = 10 \rightarrow \textcircled{2}$$

$$v_2 - v_3 = 5 \rightarrow \textcircled{3}$$

$$\therefore v_1 = \frac{17}{2} \checkmark \quad v_2 = \frac{17}{2} - 10 \\ = -\frac{3}{2} \checkmark$$

$$P_{\text{del}} = -\frac{3}{2} \times 2 = -3W.$$

Also


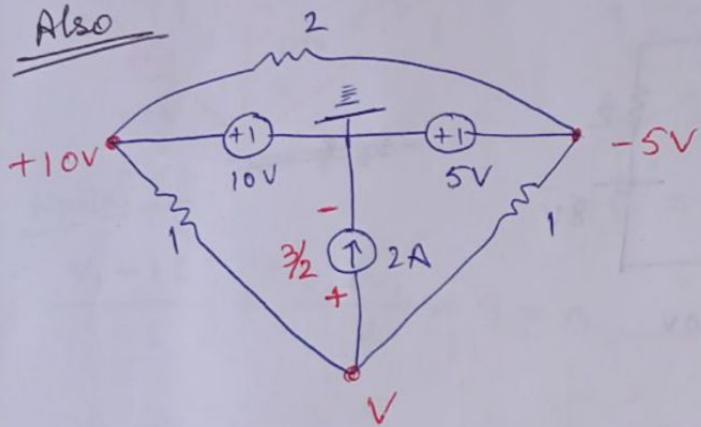








$$\frac{v - 10}{1} + \frac{v + 5}{1} + 2 = 0$$



$$\Rightarrow v = -\frac{3}{2} \checkmark$$

$$\therefore P_{\text{del}} = -\frac{3}{2} \times 2 = -3W$$

4.

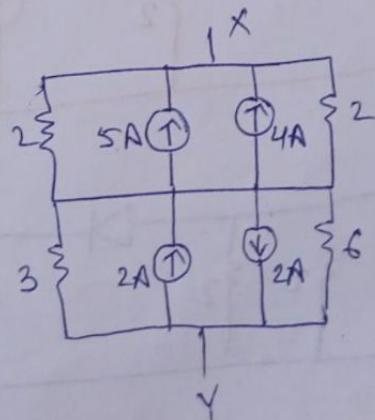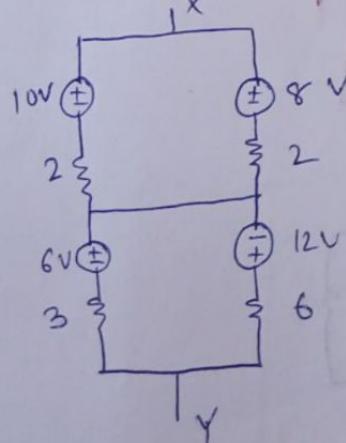


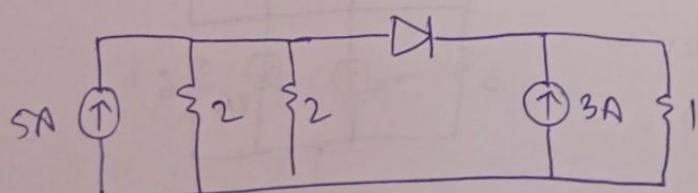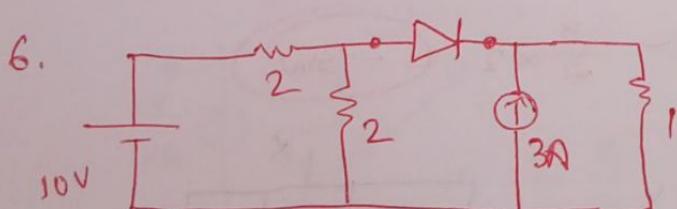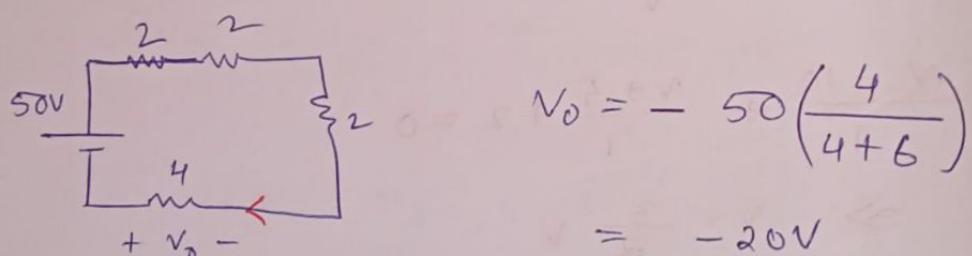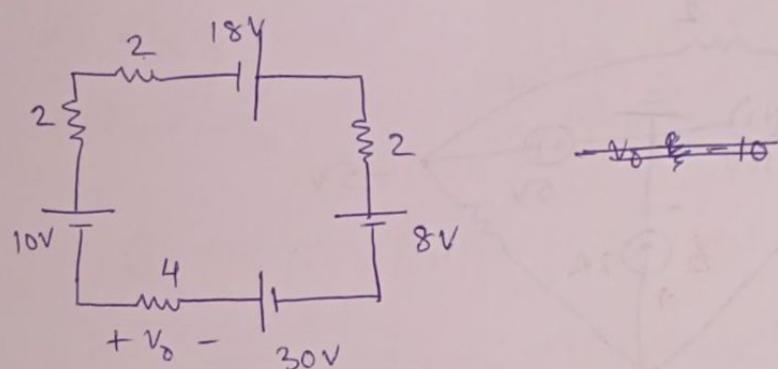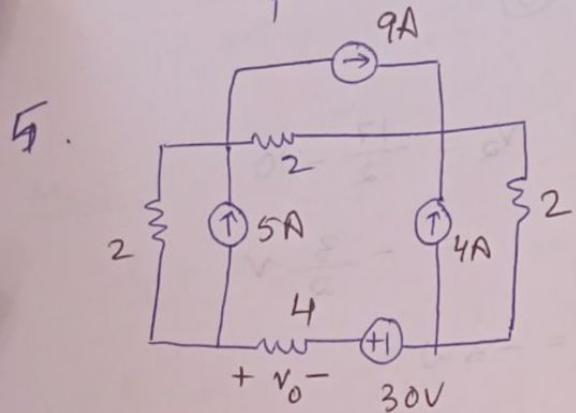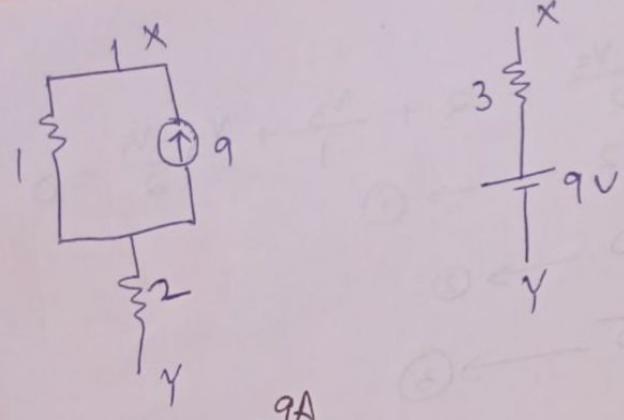

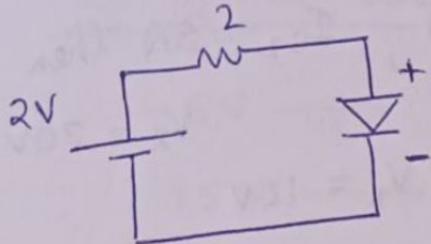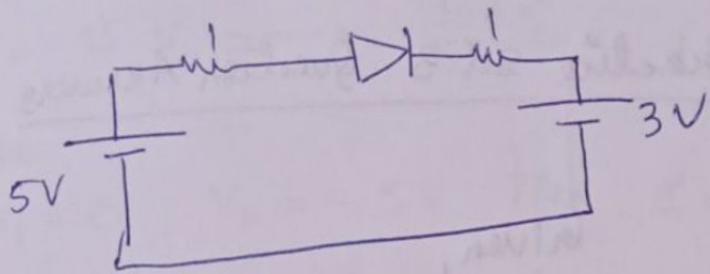

Forward bias $\therefore R = 0$

$$\therefore I_D = \frac{2}{2} = 1A$$

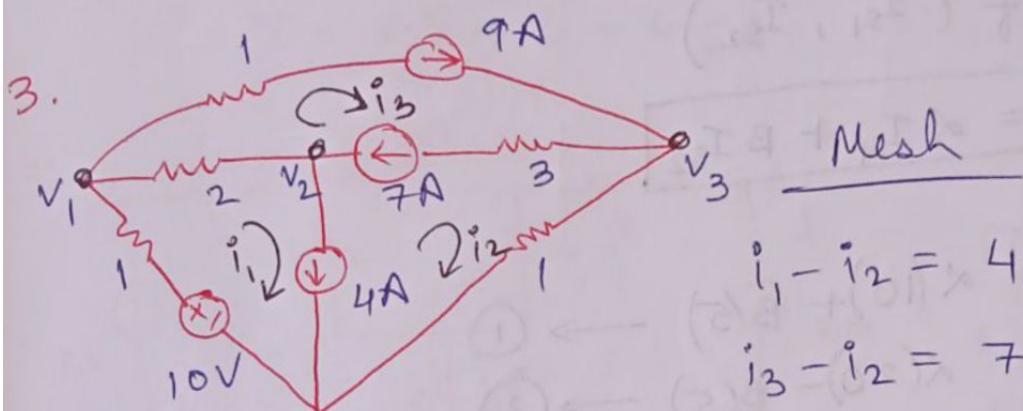

$$i_1 - i_2 = 4 \rightarrow ①$$

$$i_3 - i_2 = 7 \rightarrow ②$$

$$i_3 = 9 \rightarrow ③$$


$$\frac{v_1 - 10}{1} + \frac{v_1 - v_2}{2} + 9 = 0 \rightarrow ①$$

$$\frac{v_2 - v_1}{2} + 4 - 7 = 0 \rightarrow ②$$

$$\frac{v_3}{1} - 9 + 7 = 0 \rightarrow ③$$

Practice set 3 Question Answers

1.

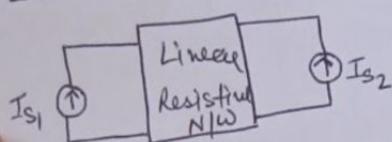

Given,

$$I_{S1} = 10A, I_{S2} = 5A \text{ then } V_x = 20V$$

$$I_{S1} = 20A, I_{S2} = -5A \text{ then } V_x = 10V$$

$$\text{If } I_{S1} = I_{S2} = 15A \text{ then } V_x = ?$$

Now,

$$V_x = f(I_{S1}, I_{S2})$$

$$\Rightarrow V_x = \alpha I_{S1} + \beta I_{S2}$$

$$20 = \alpha(10) + \beta(5) \rightarrow ①$$

$$10 = \alpha(20) - \beta(5) \rightarrow ②$$

$$\text{solving } ① \text{ and } ② \Rightarrow 30 = 30\alpha$$

$$\Rightarrow \alpha = 1$$

$$\therefore \beta = 2$$

Again,

$$V_x = 1 I_{S1} + 2 I_{S2}$$

$$= 1 \times 15 + 2 \times 15 = 45$$

$$\boxed{V_x = 45V}$$

Given,


$$V_1 = 10V, V_2 = 0V \text{ and } I = 5A$$

$$\text{Also, } V_1 = 0V, V_2 = -5V \text{ then } I = 1A$$

$$\text{To find : If } V_1 = V_2 = 15V, I = ?$$

$$\curvearrowleft V_1 = 10, V_2 = 0V \text{ then } I = 5A$$
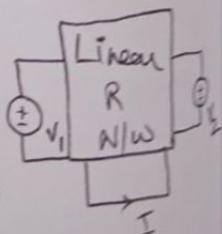
$$\rightarrow \text{If } V_1 \text{ act alone } \rightarrow 10 \rightarrow 5A$$



$$\therefore 15V \rightarrow \frac{15 \times 5}{10} = 7.5A \quad (\text{Homogeneity})$$

Also,

$$V_1 = 0, V_2 = -5V \text{ Then } I = 1A$$


If V_2 act alone

$$-5V \rightarrow 1A$$

$$15V \rightarrow \frac{15 \times 1}{-5} = -3A \quad (\text{Homogeneity})$$

By S.P.T

$$I = 7.5 - 3 = 4.5A$$

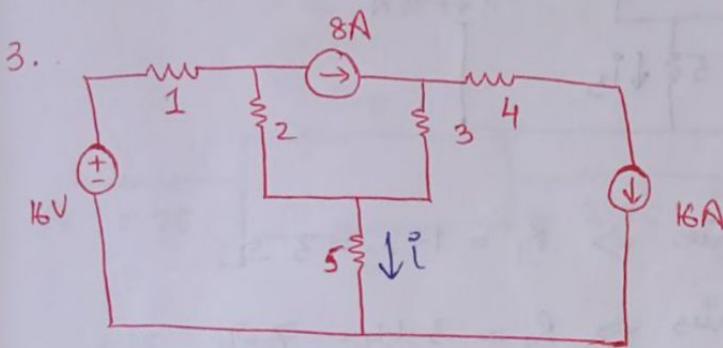


Find Power in
5Ω resistor
using SPT
and KVL.

NOTE : Power is a non linear parameter and hence can't be calculated directly using SPT.

Solⁿ

Step 1: 16V only

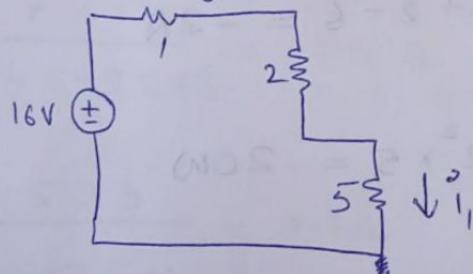



$$i_1 = \frac{16}{8} = 2A$$

Step 2

8A only

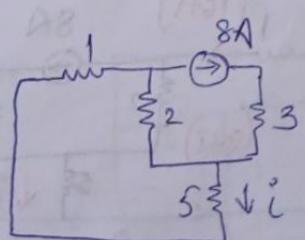
$$5 \text{ and } 1 \text{ in series } R = 5 + 1 = 6$$



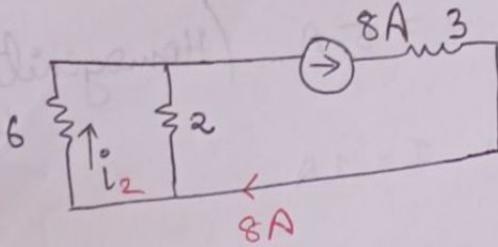


$$\therefore i_2 = 8 \left(\frac{2}{6+2} \right) = 2A$$

step 3 : 16A only

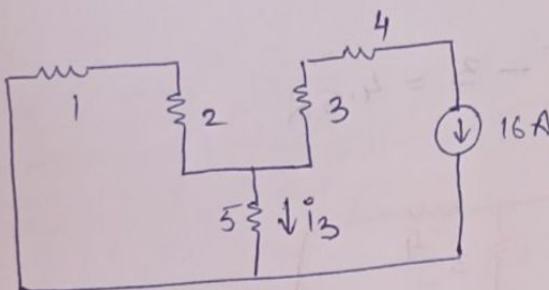

$$1 \text{ and } 2 \text{ in series} \Rightarrow R_1 = 1+2 = 3 \Omega$$

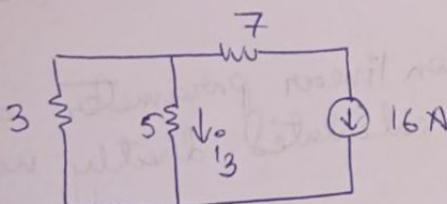
$$3 \text{ and } 4 \text{ in series} \Rightarrow R_2 = 3+4 = 7 \Omega$$



$$i_3 = -16 \left(\frac{3}{5+3} \right) = -6A$$

$$\therefore i = i_1 + i_2 + i_3 = 2 + 2 - 6 = -2A$$



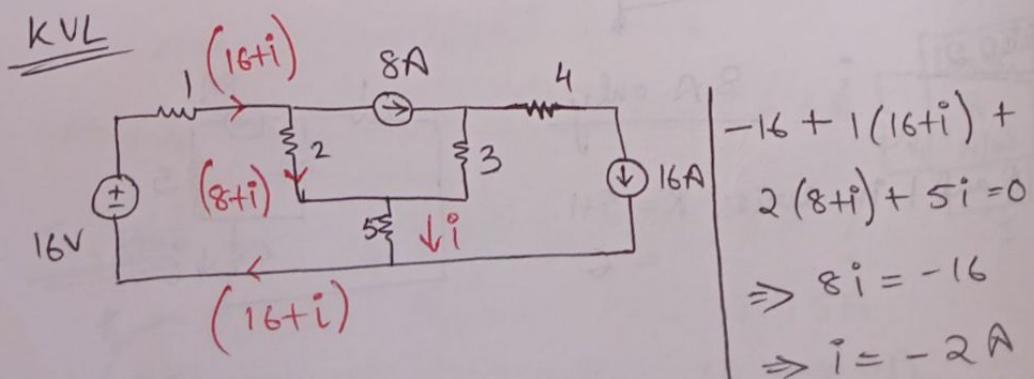
$$P_{\text{Lost}} = I^2 R = 2^2 \times 5 = 20W$$



$$\begin{aligned} -16 + 1(16+i) + \\ 2(8+i) + 5i &= 0 \\ \Rightarrow 8i &= -16 \\ \Rightarrow i &= -2A \end{aligned}$$

$$\therefore P_{\text{lost}} = i^2 R$$

$$= 4 \times 5 = 20 \text{ W}$$

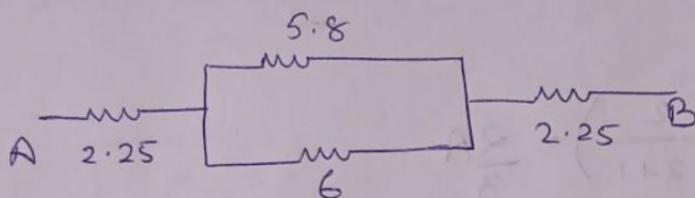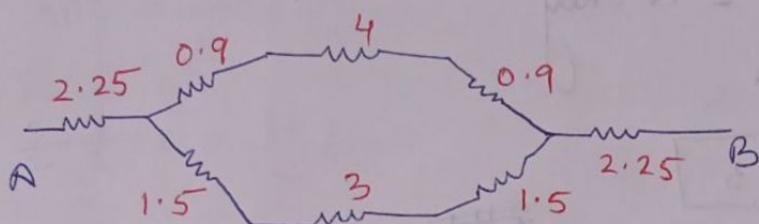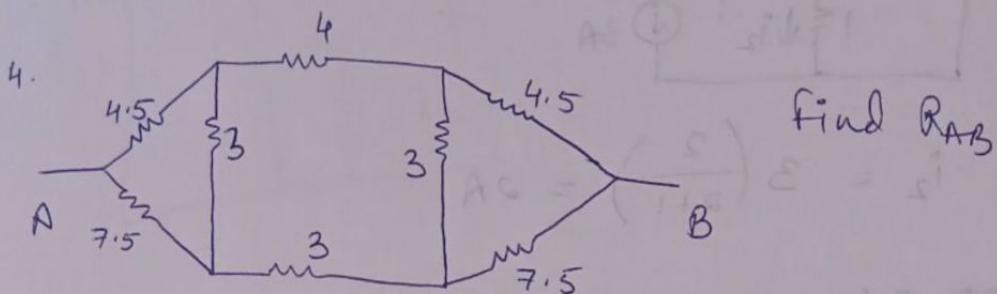

$$\frac{2.25 \parallel 2.95 \parallel 2.25}{A \qquad \qquad \qquad B} \qquad R_{AB} = 7.45 \Omega$$

Delta to Star

$$\frac{4.5 \times 7.5}{4.5 + 7.5 + 3} = 2.25 \Omega$$


$$\frac{7.5 \times 3}{4.5 + 7.5 + 3} = 1.5 \Omega$$

$$\frac{4.5 \times 3}{4.5 + 7.5 + 3} = 0.9 \Omega$$

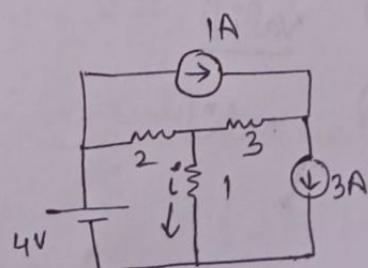
5. Find i in 1Ω using SPT

Soln step 1: 4V only

$$4V \qquad \qquad \qquad i_1 = \frac{4}{3} A$$




Step 2 : 3A only

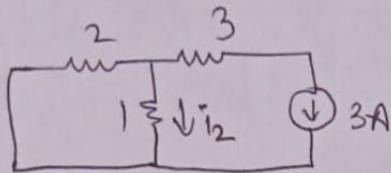

$$i_2 = 3 \left(\frac{2}{2+1} \right) = 2A$$

Step 3 : 1 A only

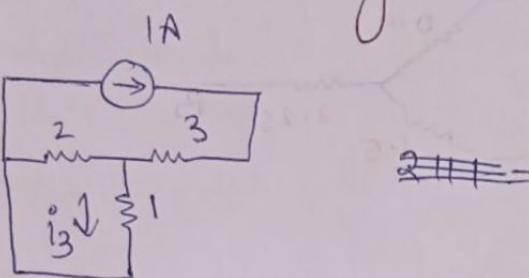

$$i_3 = 1 \left(\frac{2}{2+1} \right) = \frac{2}{3}A$$

$$\therefore i = i_1 + i_2 + i_3$$

$$= \frac{4}{3} + 2 + \frac{2}{3}$$

$$i = 4A$$

6. (a) 2 voltage of different values \rightarrow violates KVL.


(b) valid as resistor in b/w.

(c) unclear what current flows through R.

$$I = 1 - 1 = 0 \rightarrow \text{invalid}$$

(d) valid.

(e) valid

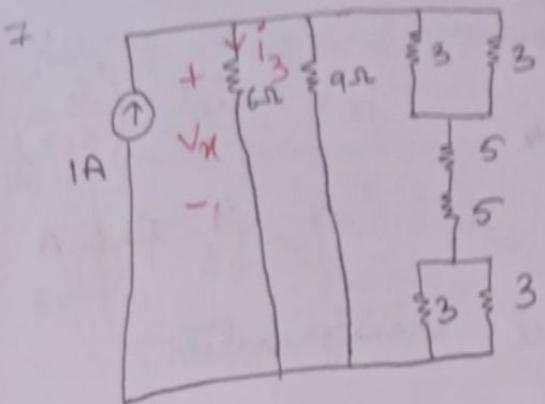


Find V_x .

$$3 \parallel 3 = \frac{9}{6} = \frac{3}{2}$$

$$\frac{3}{2} + \frac{3}{2} + 10 = \frac{26}{2} = 13\Omega$$

$$\left. \begin{array}{c} \frac{1}{3} \\ \parallel \\ \frac{3}{2} \\ \parallel \\ 10 \\ \parallel \\ \frac{3}{2} \end{array} \right\} = \frac{1}{13\Omega}$$
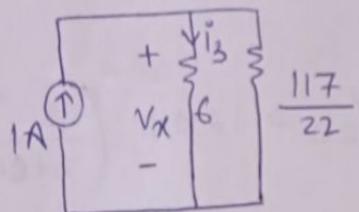
$$13 \parallel 9 = \frac{13 \times 9}{22} = \frac{117}{22}$$



$$i_3 = 1 \left(\frac{\frac{117}{22}}{\frac{117}{22} + 6} \right)$$


$$= \frac{117}{22} \times \frac{22}{249}$$

$$= 0.4698$$

$$\therefore V_x = 6 \times 0.4698$$


$$= 2.8188 \approx 2.819 \text{ V}$$

8.

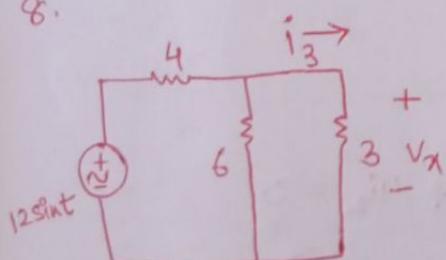

Find i_3 .

$$3 \parallel 6 = 2\Omega$$

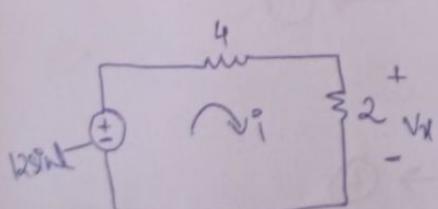


$$i = \frac{12 \sin t}{6} = 2 \sin t \text{ A}$$

↑
total current.

$$i_3 = 2 \sin t \frac{6}{6+3} = \frac{4}{3} \sin t \text{ A}$$

Method 2 : Source transformation

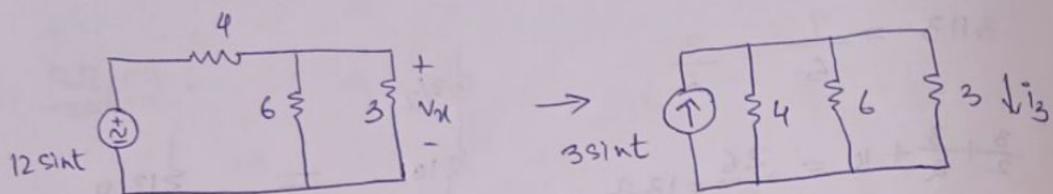


$$i_3 = 3 \sin t \frac{6 \times 4}{24 + 18 + 12} = \frac{4}{3} \sin t \text{ A}$$

Method 3 : Voltage division

$$v_x = 12 \sin t \left(\frac{2}{2+4} \right) = 4 \sin t \text{ V}$$

$$i_3 = \frac{4 \sin t}{3} \text{ A}$$

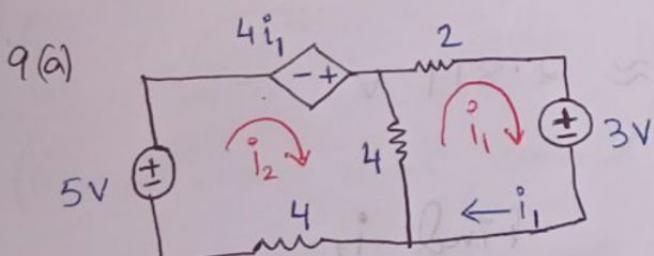

KVL


$$-5 - 4i_1 + 4(i_2 - i_1) + 4i_2 = 0$$

$$\Rightarrow -8i_1 + 8i_2 = 5 \rightarrow ①$$

$$4(i_1 - i_2) + 2i_1 + 3 = 0$$

$$\Rightarrow 6i_1 - 4i_2 = -3 \rightarrow ②$$

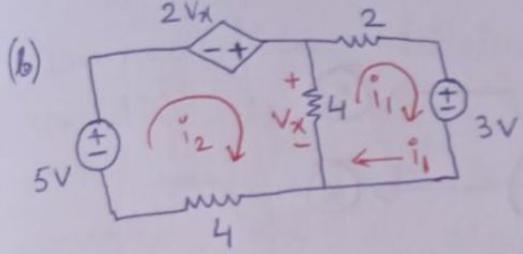solving, $i_1 = -250 \text{ mA}$ $i_2 = 375 \text{ mA}$



$$-5 - 2v_x + 4(i_2 - i_1) + 4i_2 = 0 \rightarrow \textcircled{1}$$

$$\cancel{-4(i_1 - i_2)} \quad 4(i_1 - i_2) + 2i_1 + 3 = 0 \rightarrow \textcircled{2}$$


$$v_x = 4(i_2 - i_1) \rightarrow \textcircled{3}$$

Put \textcircled{3} in \textcircled{1},

$$4i_1 = 5$$

$$\Rightarrow \boxed{i_1 = 1.25 \text{ A}}$$

10.

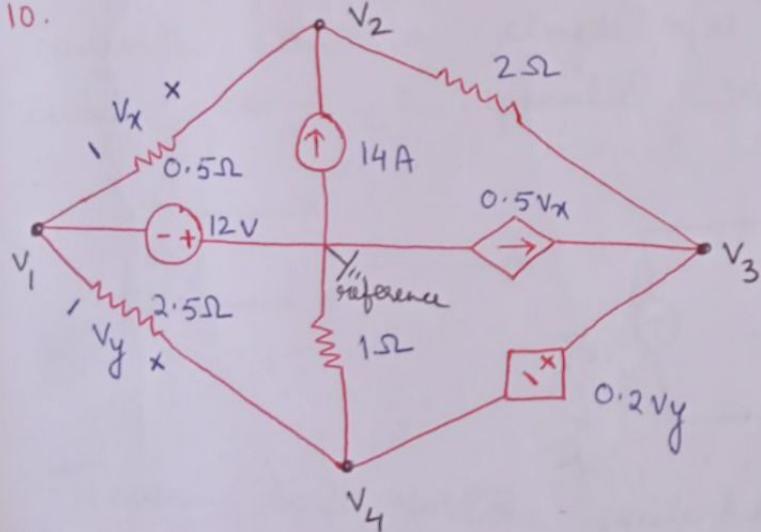

$$V_1 = -12 \rightarrow \textcircled{1}$$

$$\frac{V_2 - V_1}{0.5} - 14 + \frac{V_2 - V_3}{2} = 0$$

$$\Rightarrow \frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2} = 14 \rightarrow \textcircled{2}$$

$$\frac{V_3 - V_2}{2} + \frac{V_4}{1} + \frac{V_4 - V_1}{2.5} - 0.5v_x = 0 \rightarrow \textcircled{3}$$

$$v_3 - v_4 = 0.2 v_y \longrightarrow \textcircled{4}$$

$$0.2 v_y = 0.2 (v_4 - v_1) \longrightarrow \textcircled{5}$$


$$0.5 v_x = 0.5 (v_2 - v_1) \longrightarrow \textcircled{6}$$

\therefore Solving, we get

$$v_1 = -12V, v_2 = -4V, v_3 = 0V, v_4 = -2V$$

PRACTICE SET 4

1. Find v_x with the help of SPT

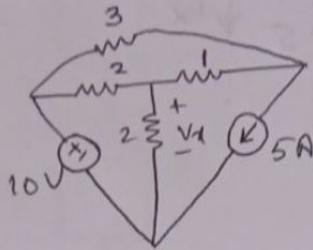

Solⁿ

Step 1 : 10V only

$$v_{x_1} = 10 \left(\frac{2}{2+4/3} \right)$$

$$= 6V$$

$$4/12 = \frac{8}{6} - \frac{4}{3}$$

Step 2 : 5A only

$$v_{x_2} = -2 \left[5 \left(\frac{3}{3+2} \right) \times \frac{2}{4} \right]$$


$$= -3V$$

$$2/12 = 1$$

''. Using SPT

$$v_x = v_{x_1} + v_{x_2} = 6 - 3 = 3V.$$

2. Find v_x using Nodal Analysis

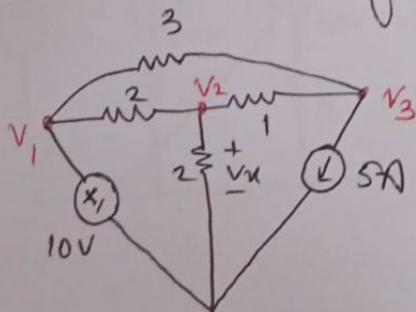

$$v_1 = 10 \rightarrow ①$$

$$\frac{v_2 - 10}{2} + \frac{v_2}{2} + \frac{v_2 - v_3}{1} = 0 \rightarrow ②$$

$$\Rightarrow 4v_2 - 2v_3 = 10$$


$$5 + \frac{V_3 - V_2}{1} + \frac{V_3 - 10}{3} = 0$$

$$\Rightarrow -3V_2 + 4V_3 = -5 \rightarrow (3)$$

$$V_2 = 3$$

$$\therefore V_x = 3V$$

3. Find V_x using SPT

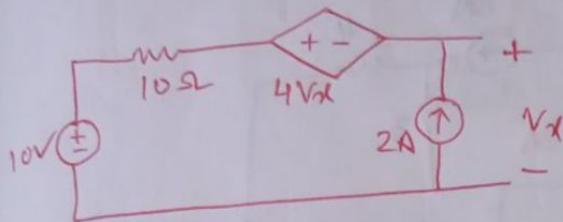

Step 1: 10V only.

$$V_{x_1} = 10 - 4V_{x_1}$$

$$\Rightarrow V_{x_1} = 2V$$

Step 2: 2A only


$$-V_x - 4V_{x_2} + 10(2) = 0$$

$$\Rightarrow 5V_{x_2} = 20$$


$$\Rightarrow V_{x_2} = 4V$$

$$\therefore V_x = V_{x_1} + V_{x_2} = 2 + 4 = 6V$$

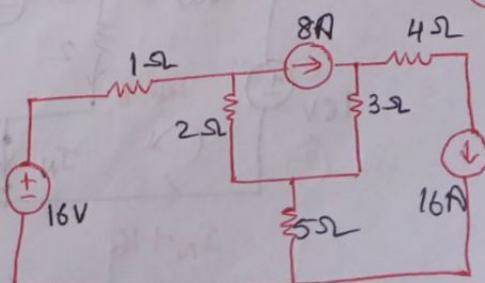
4. Find power lost in 5Ω resistor using
Thevenin and Norton



Sol'n Thevenin

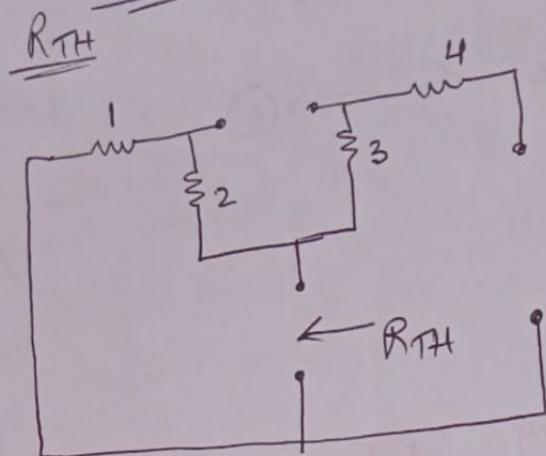


$$R_{TH} = 2 + 1 \\ = 3 \Omega$$

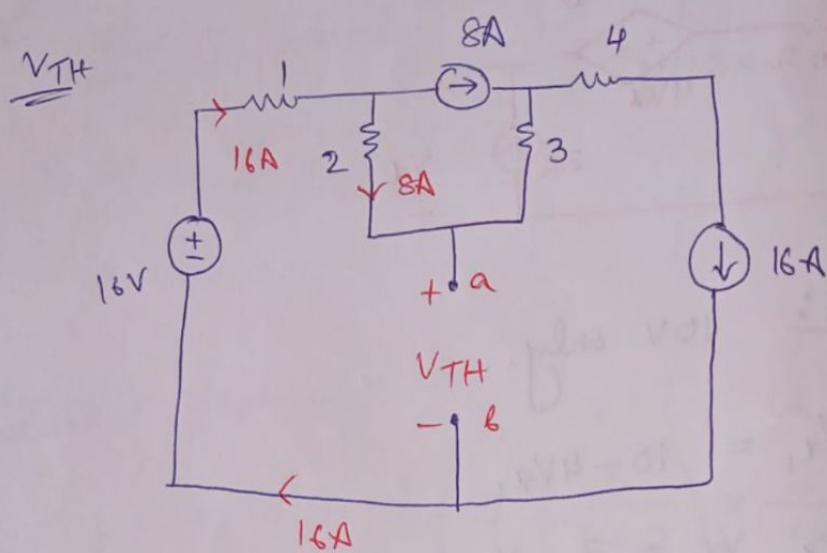

$$-16 + 16 + 16 + V_{TH} = 0$$


$$\Rightarrow V_{TH} = -16 V$$

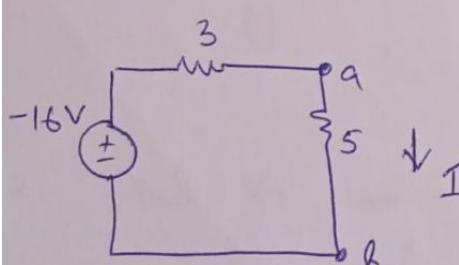

$$I = -\frac{16}{8} = -2 A$$

$$P_{lost} = (-2)^2 \times 5 = 20 W$$

Norton

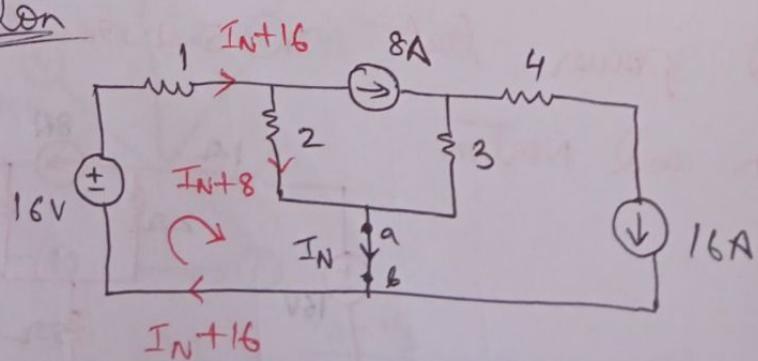


KVL



$$-16 + (I_N + 16) + 2(I_N + 8) = 0$$

$$\Rightarrow 3I_N = -16$$


$$\Rightarrow I_N = \frac{-16}{3} A$$

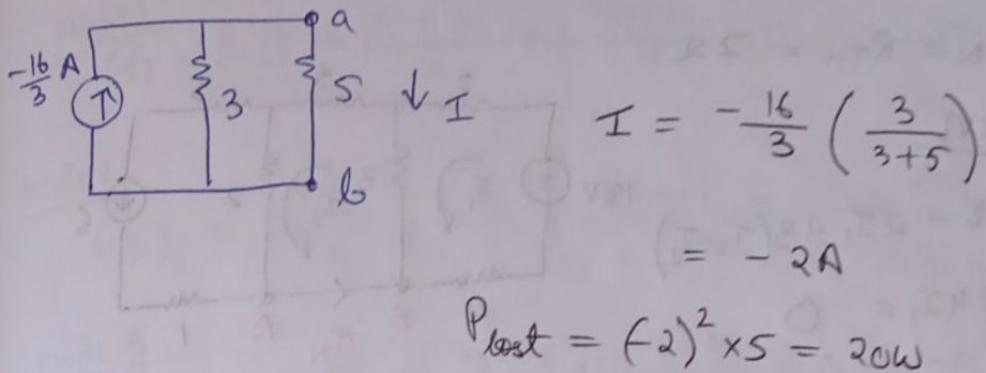

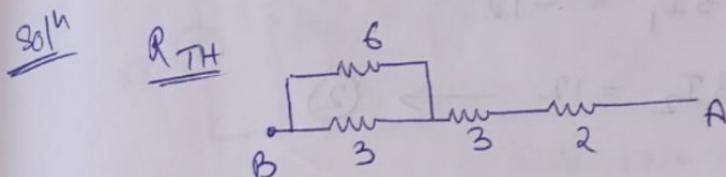
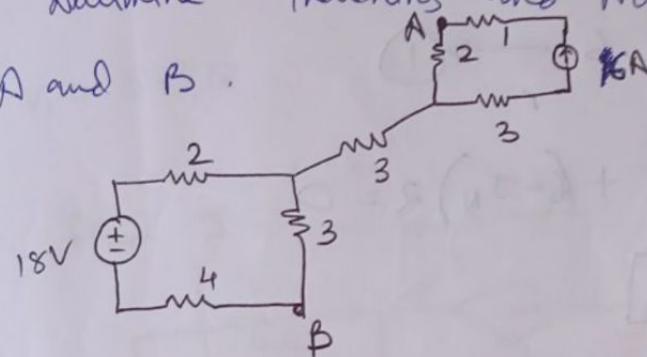
5. Determine Thevenin and Norton equivalent b/w
A and B.


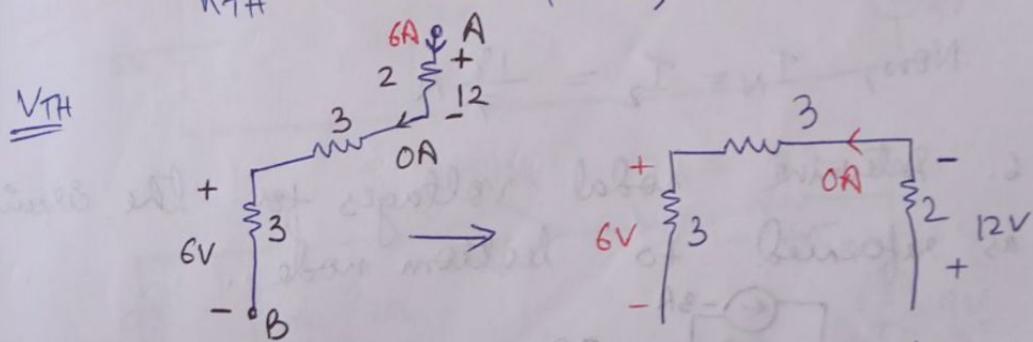
$$R_{TH} = 2 + 3 + \beta(116) = 2 + 3 + 2 = 7 \Omega$$



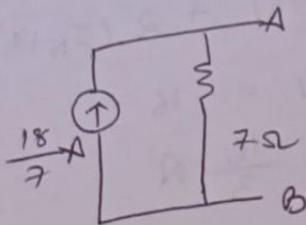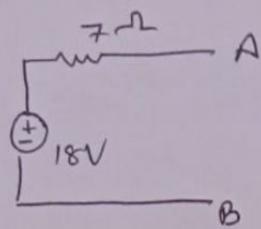
$$V_{TH} - 6 - 12 = 0 \Rightarrow V_{TH} = 18 V$$



Norton's

$$R_N = R_{TH} = 7\Omega$$
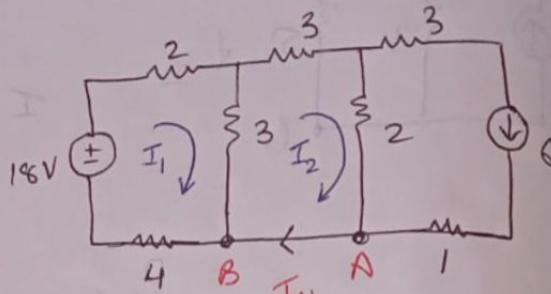
$$\begin{aligned} \text{KVL: } & -18 + 2I_1 + 3(I_1 - I_2) \\ & + 4I_1 = 0 \end{aligned}$$



$$\Rightarrow 9I_1 - 3I_2 = 18$$

$$\Rightarrow 3I_1 - I_2 = 6 \rightarrow \textcircled{1}$$

$$3(I_2 - I_1) + 3I_2 + (6 - I_N)2 = 0$$

Here

$$\boxed{I_N = I_2}$$


$$\Rightarrow 8I_2 - 3I_1 = -12$$


$$\Rightarrow 3I_1 - 8I_2 = 12 \rightarrow \textcircled{2}$$

$$\therefore I_2 = \frac{18}{7} \text{ A}$$

$$\text{Now, } I_N = I_2 = \frac{18}{7} \text{ A}$$

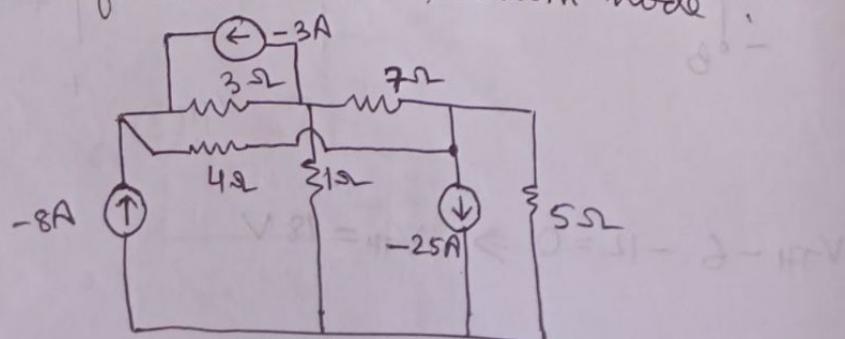6. Determine nodal voltages for the circuit, as referenced to bottom node.



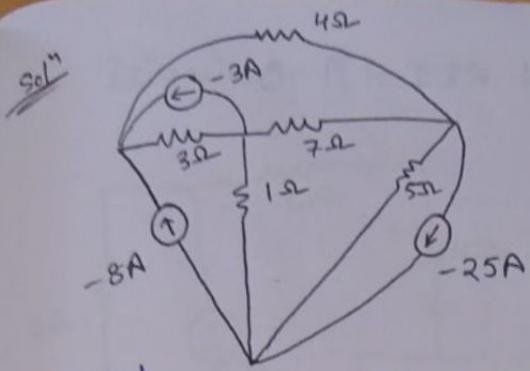

$$\text{Node 1} \quad -(8) - (-3) + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{4} = 0 \rightarrow ①$$

Node 2





$$(-3) + \frac{V_2 - V_1}{3} + \frac{V_2}{1} + \frac{V_2 - V_3}{7} = 0 \rightarrow ②$$

Node 3

$$(-25) + \frac{V_3}{5} + \frac{V_3 - V_2}{7} + \frac{V_3 - V_1}{4} = 0 \rightarrow ③$$

$$V_1 = 5.412, \quad V_2 = 7.736, \quad V_3 = 46.32 \text{ V}$$

7. Find I.

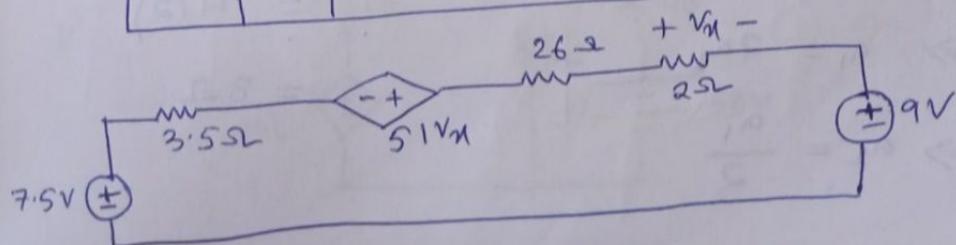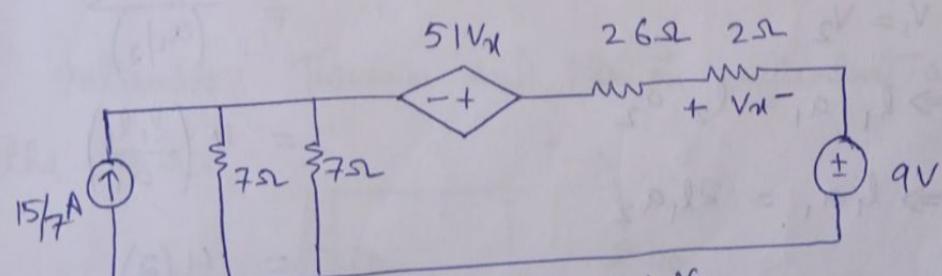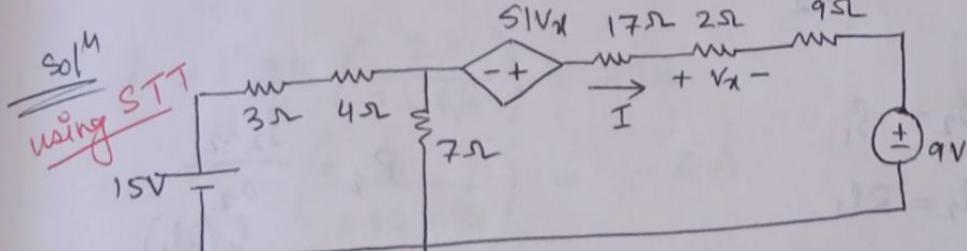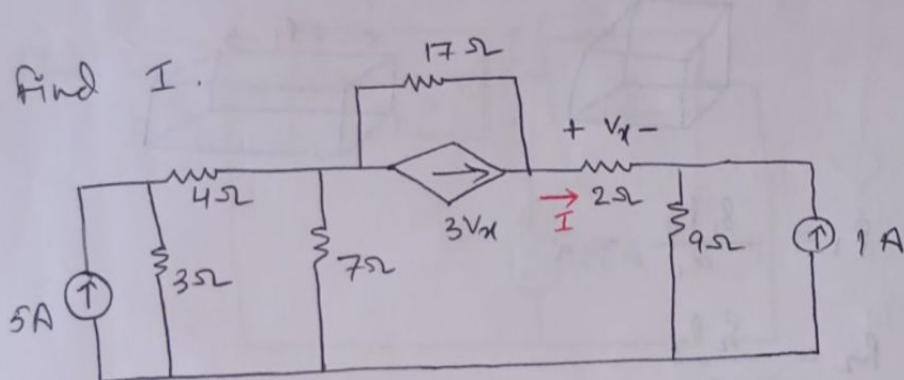



$$-7.5 + 3.5I - 51V_R + 28I + 9 = 0$$

$$V_R = 2I$$

$$\Rightarrow I = 21.28 \text{ mA}$$

8. A cube shaped material has a resistance of 2Ω b/w any of its opposite faces. Now if this material is stretched in one direction by applying linear force to double its original length, then the resistance b/w the opposite stretched face is _____

Soln

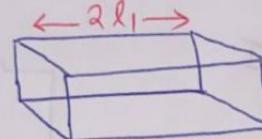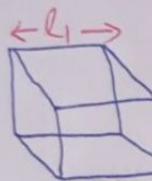

$$R_1 = \frac{\beta_1 l_1}{a_1} = 2$$

$$R_2 = \frac{\beta_2 l_2}{a_2}$$

$$\beta_2 = \beta_1$$

$$l_2 = 2l_1$$

$$V_1 = V_2$$

$$\Rightarrow l_1 \cdot a_1 = l_2 \cdot a_2$$

$$\Rightarrow l_1 a_1 = 2l_1 a_2$$

$$\Rightarrow a_1 = 2a_2$$

$$\Rightarrow a_2 = \frac{a_1}{2}$$


$$R_2 = \frac{\beta_2 l_2}{a_2} = \frac{\beta_1 (2l_1)}{(a_1/2)}$$

$$= 4 \left(\frac{\beta_1 l_1}{a_1} \right)$$

$$= 4(2)$$

$$= 8\Omega$$

q. Determine i .

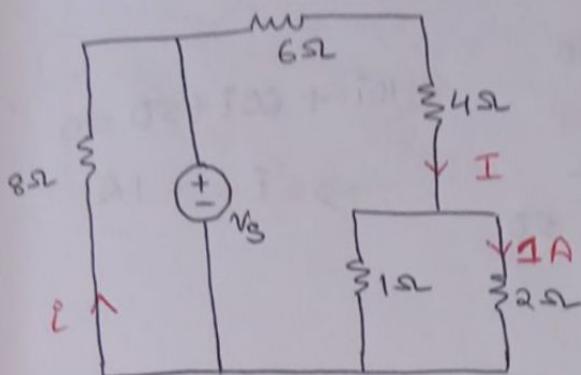


301th

$$i = I \times \frac{1}{3} \Rightarrow I = 3$$

$$V_s = 3 \left(10 + \frac{2}{3} \right) = 32V$$

$$i = -\frac{32}{8} = -4A$$


10. find I

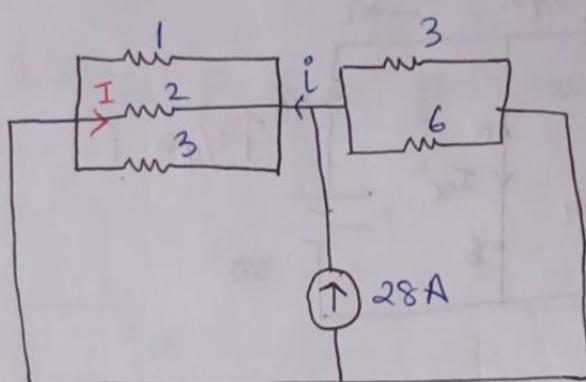


$$i = 28 \left(\frac{2}{2+6//1} \right) = 22A$$

$$I = 22 \left(\frac{3}{6+2+3} \right) = -6A$$

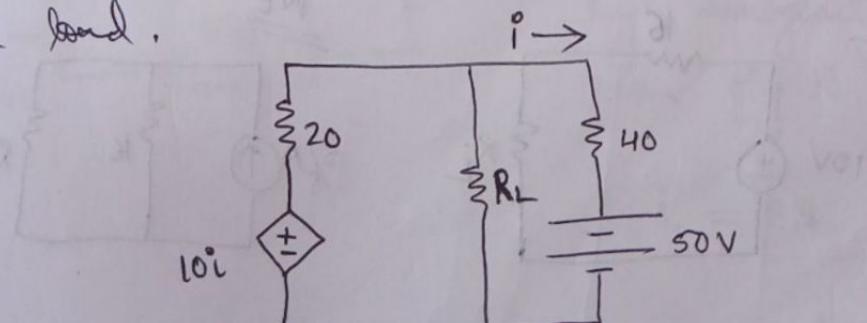11. Determine Thevenin and Norton equivalent across the load.



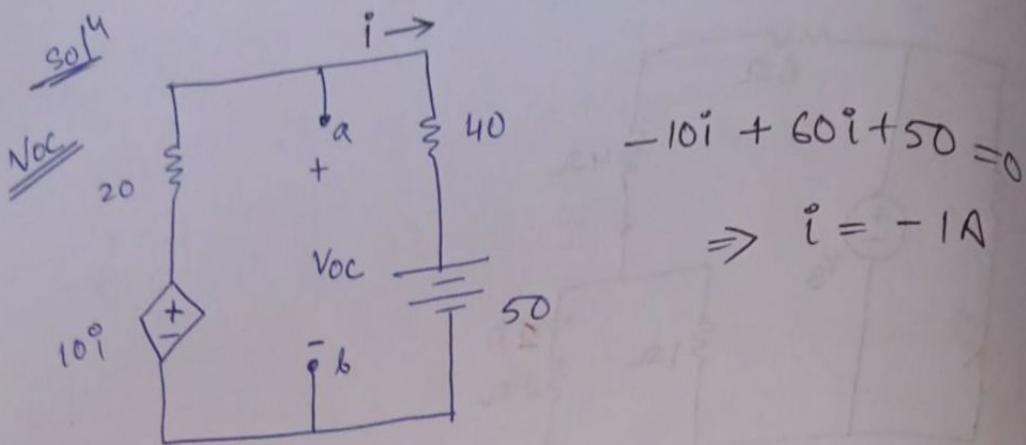


$$-10i + 60i + 50 = 0 \Rightarrow i = -1A$$

KVL

$$-V_{OC} + 40i + 50 = 0$$

$$\Rightarrow -V_{OC} - 40 + 50 = 0$$

$$\Rightarrow V_{OC} = 10V$$

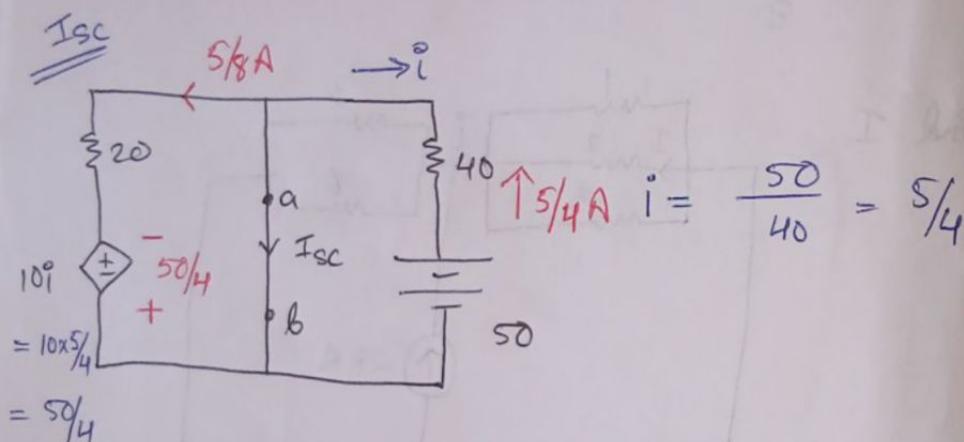


$$\text{KCL} \quad -\frac{5}{4} = \frac{5}{8} + I_{SC}$$


$$\Rightarrow I_{SC} = -\frac{5}{8} A$$


$$R_{TH} = R_N = \frac{V_{OC}}{I_{SC}} = \frac{10 \times 8}{5} = 16\Omega$$

TE

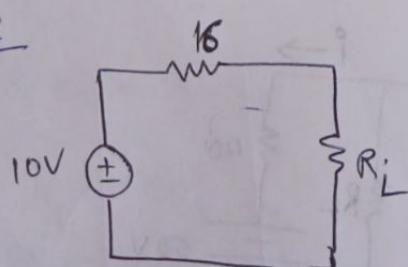


NE

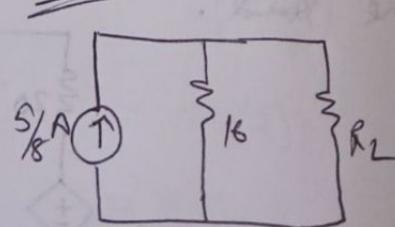

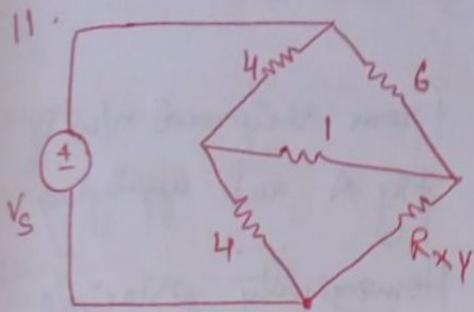

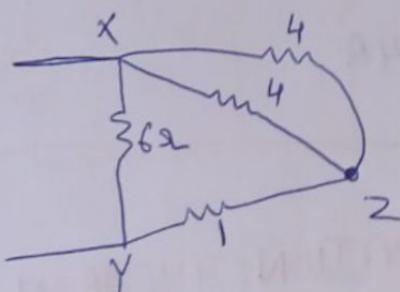what is the value of
R_X for which P_{max}
occurs.



$$4|1|4 = 2$$

$$2+1 = 3$$

$$R_{XY} = R_{TH} = 3|1|6 = 2\Omega$$

12. Use the data in fig A to find current i in fig. B.



fig A


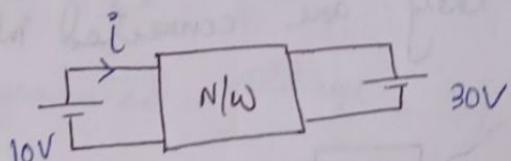


fig B


Solⁿ
Apply Superposition

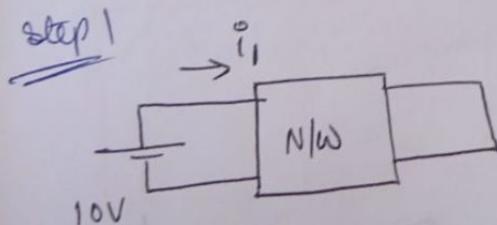

By homogeneity principle
from fig A.

$$i_1 = 8A$$

Step 2 :

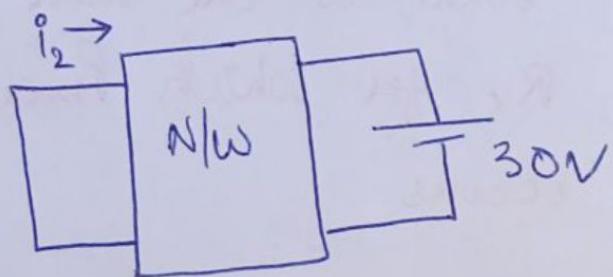


From reciprocal n/w of
fig A and applying
Homogeneity principle

$$\overset{\circ}{i}_2 = -12A$$

$$i = \overset{\circ}{i}_1 + \overset{\circ}{i}_2 = 8 - 12 = -4A$$

Practice set 2 answers

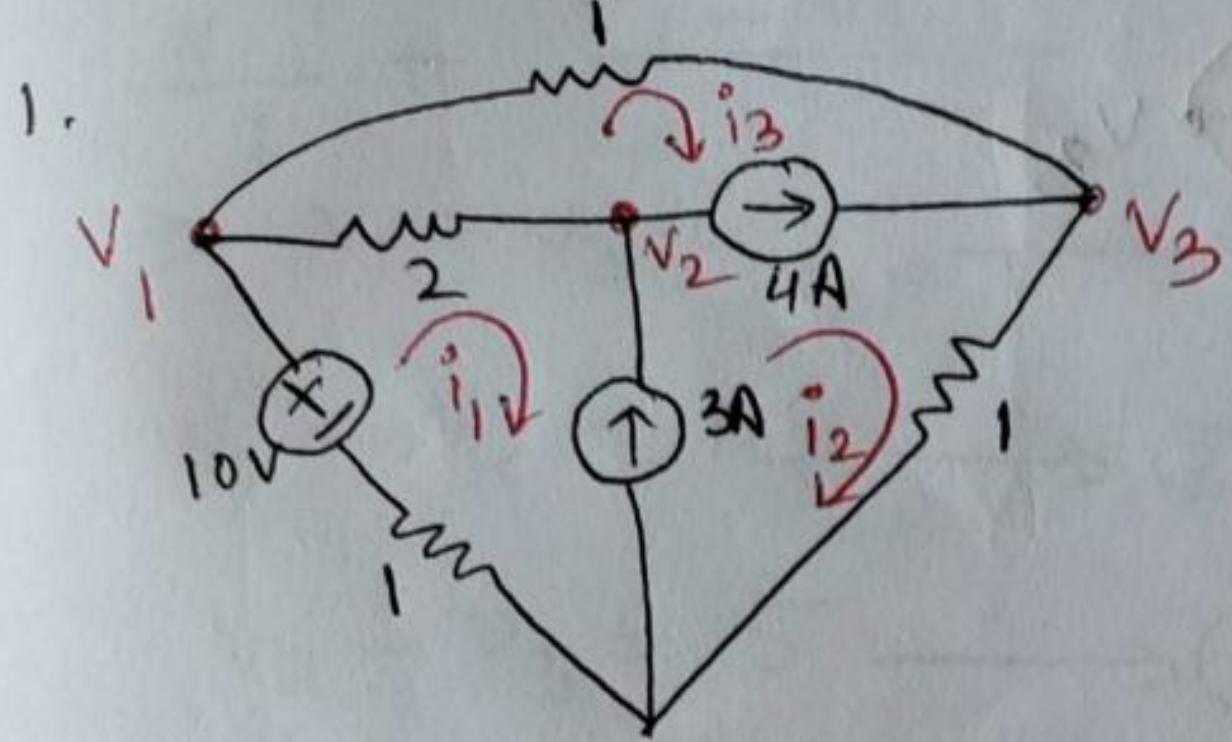

Mesh

$$i_1 - 10 + i_3 + i_2 = 0$$



$$\Rightarrow i_1 + i_2 + i_3 = 10 \rightarrow \textcircled{1}$$

$$i_2 - i_1 = 3 \rightarrow \textcircled{2}$$

$$i_2 - i_3 = 4 \rightarrow \textcircled{3}$$

$$\text{Solving we get, } i_1 = \frac{8}{3}$$

$$\therefore P_{\text{delivered}} = 10 \times \frac{8}{3} = \frac{80}{3} \text{ W}$$

Nodal

$$\frac{v_1 - 10}{1} + \frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{1} = 0$$

$$\Rightarrow 5v_1 - v_2 - 2v_3 = 20 \rightarrow \textcircled{1}$$

$$\frac{v_2 - v_1}{2} - 3 + 4 = 0$$


$$\Rightarrow v_2 - v_1 = -2 \rightarrow \textcircled{2}$$

$$\frac{v_3}{1} + \frac{v_3 - v_1}{1} - 4 = 0$$

$$\Rightarrow -v_1 + 2v_3 = 4 \rightarrow \textcircled{3}$$


$$\therefore v_1 = \frac{22}{3}$$
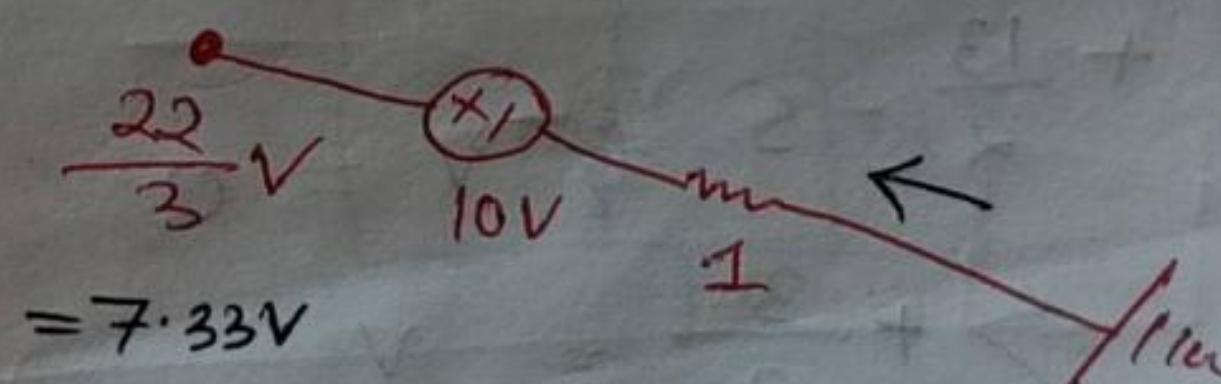
$$\therefore I = \frac{10 - \frac{22}{3}}{\frac{1}{3}} = 8/3 \text{ A}$$



$$P = 10 \times 8/3 = \frac{80}{3} \text{ W}$$

2.

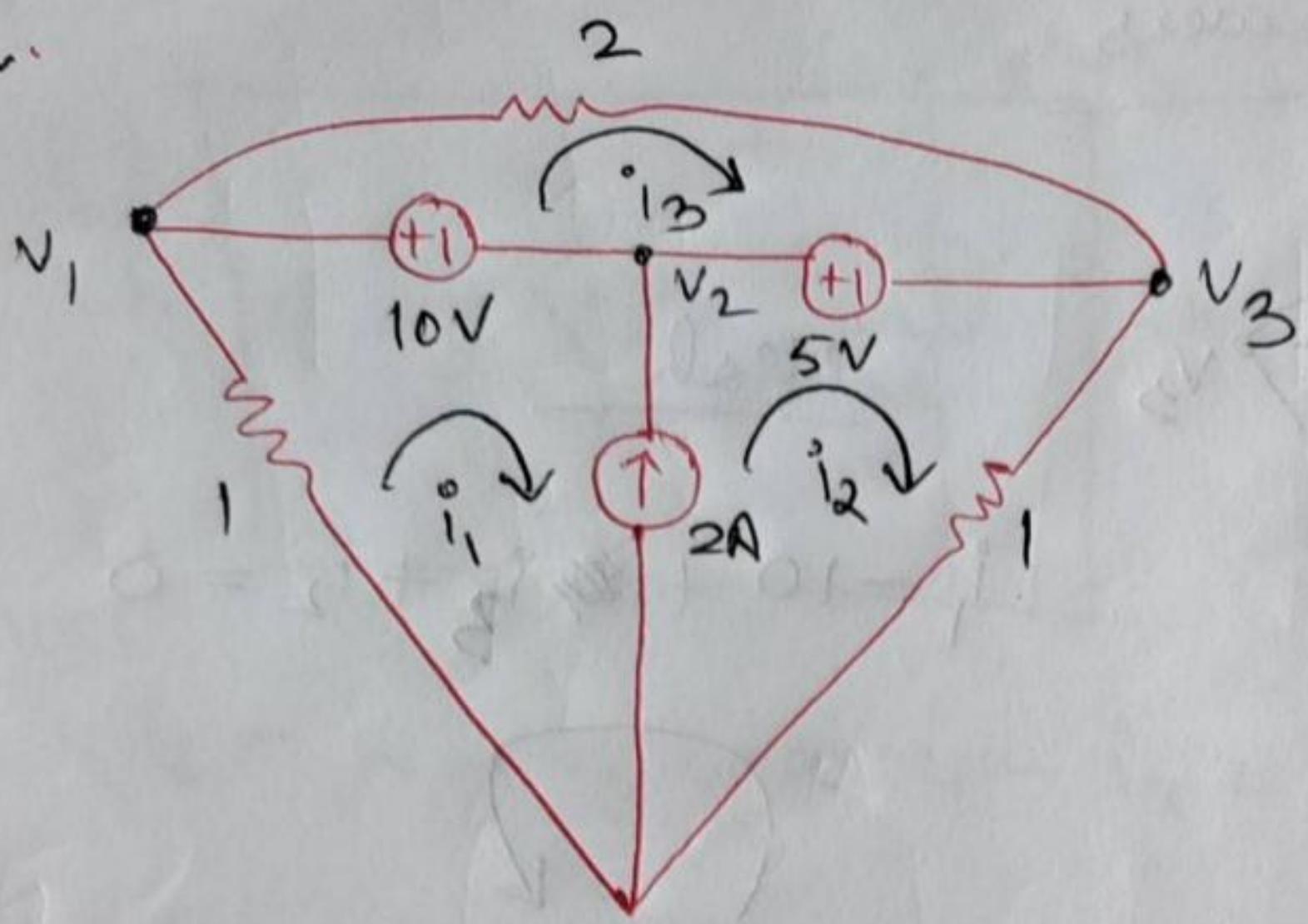Mesh

$$i_1 + 2i_3 + i_2 = 0 \quad \rightarrow \textcircled{1}$$

$$-5 - 10 + 2i_3 = 0$$

$$\Rightarrow 2i_3 = 15$$


$$\Rightarrow i_3 = \frac{15}{2} \rightarrow \textcircled{2}$$

$$\therefore \textcircled{1} \Rightarrow i_1 + i_2 + 2 \times \frac{15}{2} = 0$$

$$\Rightarrow i_1 + i_2 = -15 \rightarrow \textcircled{3}$$

$$\text{Also, } i_2 - i_1 = 2 \rightarrow \textcircled{4}$$
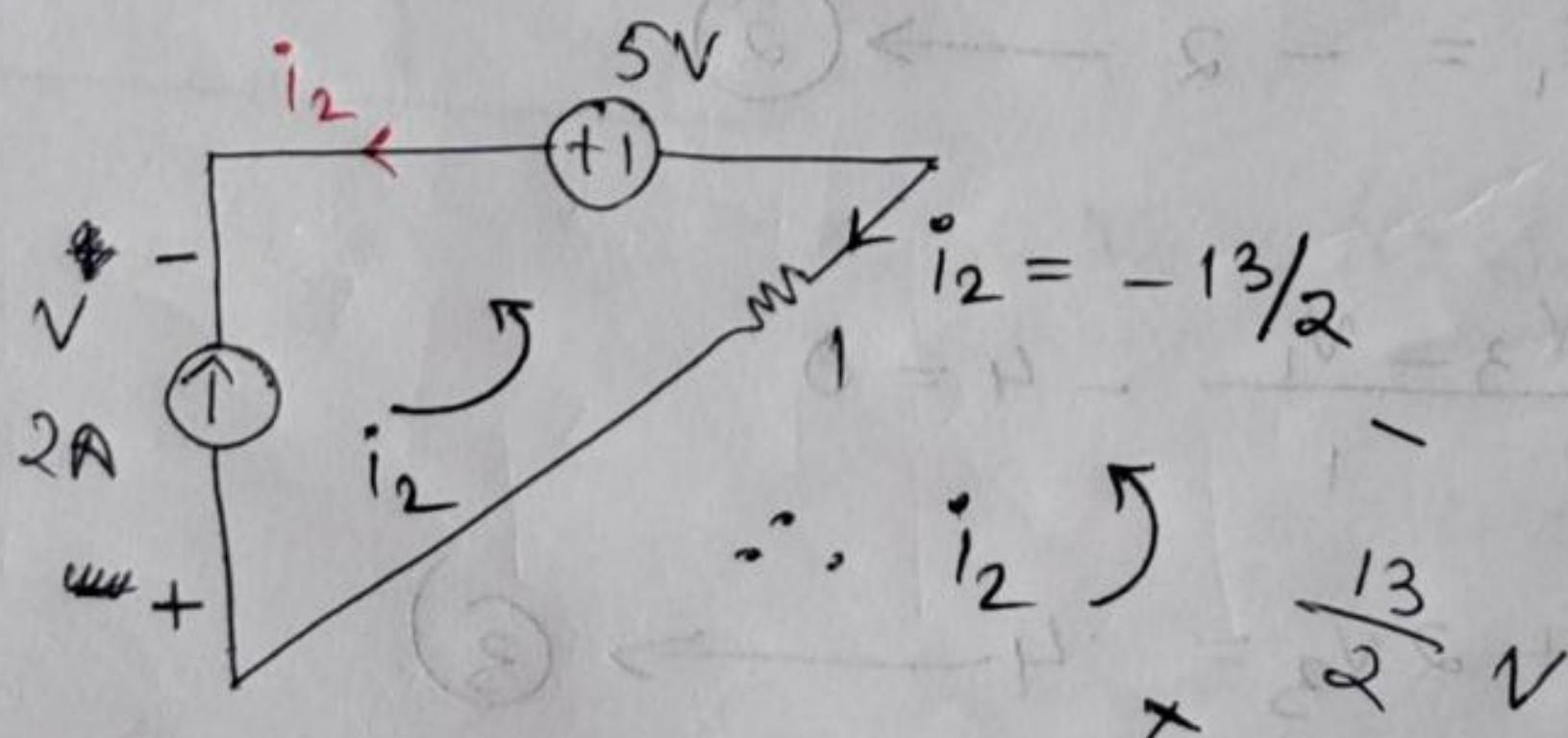
$$\therefore i_2 = -\frac{13}{2} \quad i_1 = -\frac{17}{2}$$



$$+\frac{13}{2} - 5 - v = 0$$

$$\Rightarrow +\frac{3}{2} = v$$

$$\therefore P_{\text{del}} = -2 \times \frac{3}{2} = -3 \text{ W}$$

Nodal

$$\frac{v_1}{1} + \frac{v_1 - v_3}{2} - 2 + \frac{v_3}{1} + \frac{v_3 - v_1}{2} = 0$$

$$\Rightarrow v_1 + v_3 = 2 \quad \rightarrow \textcircled{1}$$

$$v_1 - v_2 = 10 \quad \rightarrow \textcircled{2}$$

$$v_2 - v_3 = 5 \quad \rightarrow \textcircled{3}$$


$$\therefore v_1 = \frac{17}{2} V$$

$$v_2 = \frac{17}{2} - 10$$

$$= -\frac{3}{2} V$$

$$P_{\text{del}} = -\frac{3}{2} \times 2 = -3 W$$



Also







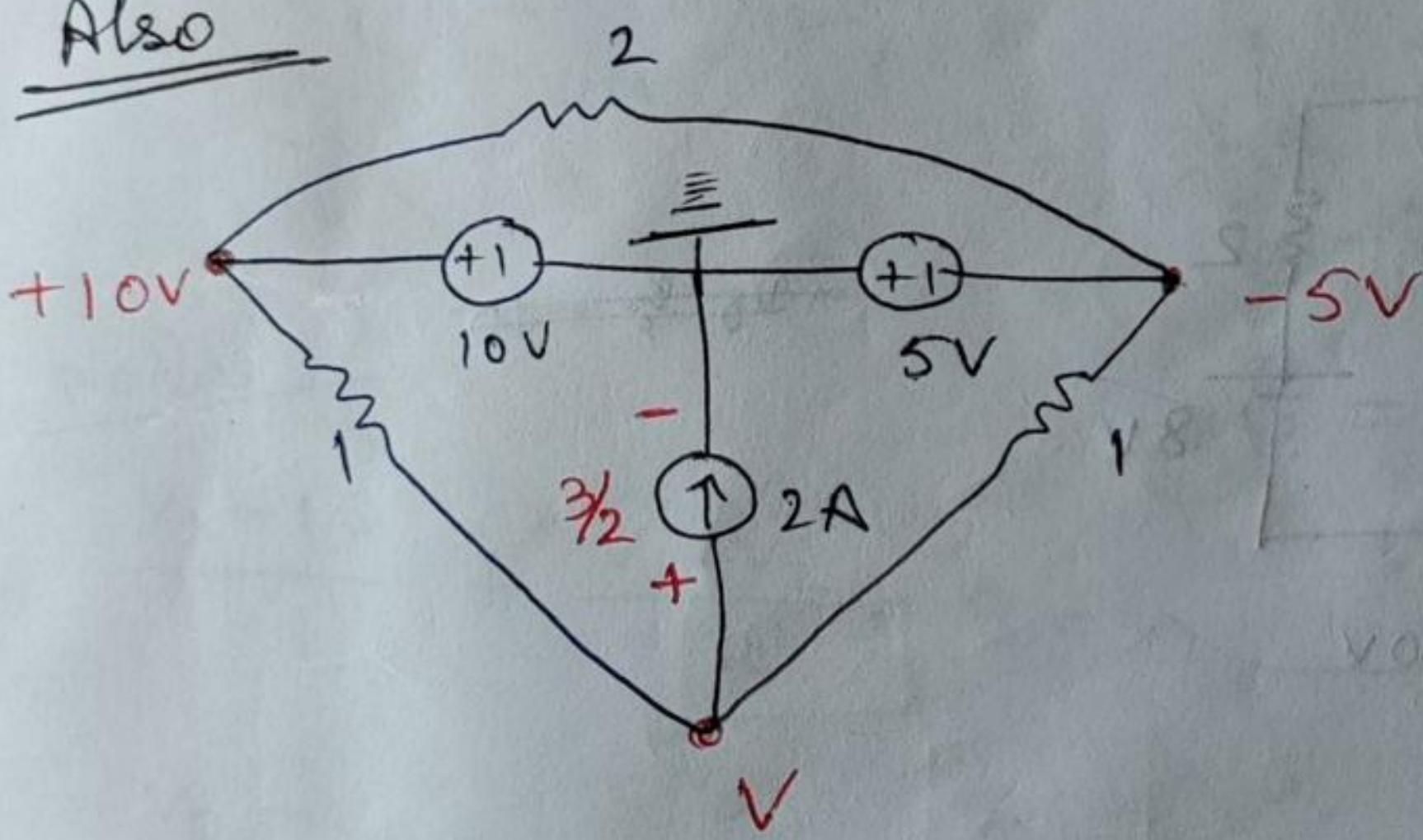




$$\frac{V - 10}{1} + \frac{V + 5}{1} + 2 = 0$$

$$\Rightarrow V = -\frac{3}{2} V$$
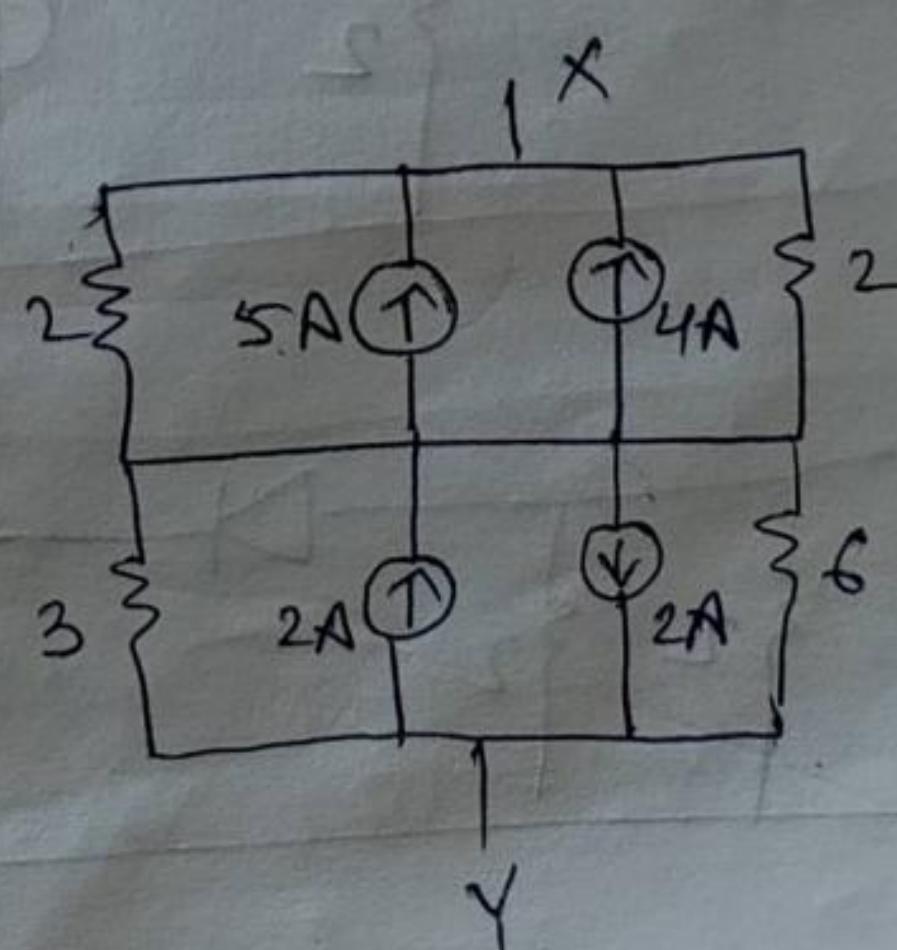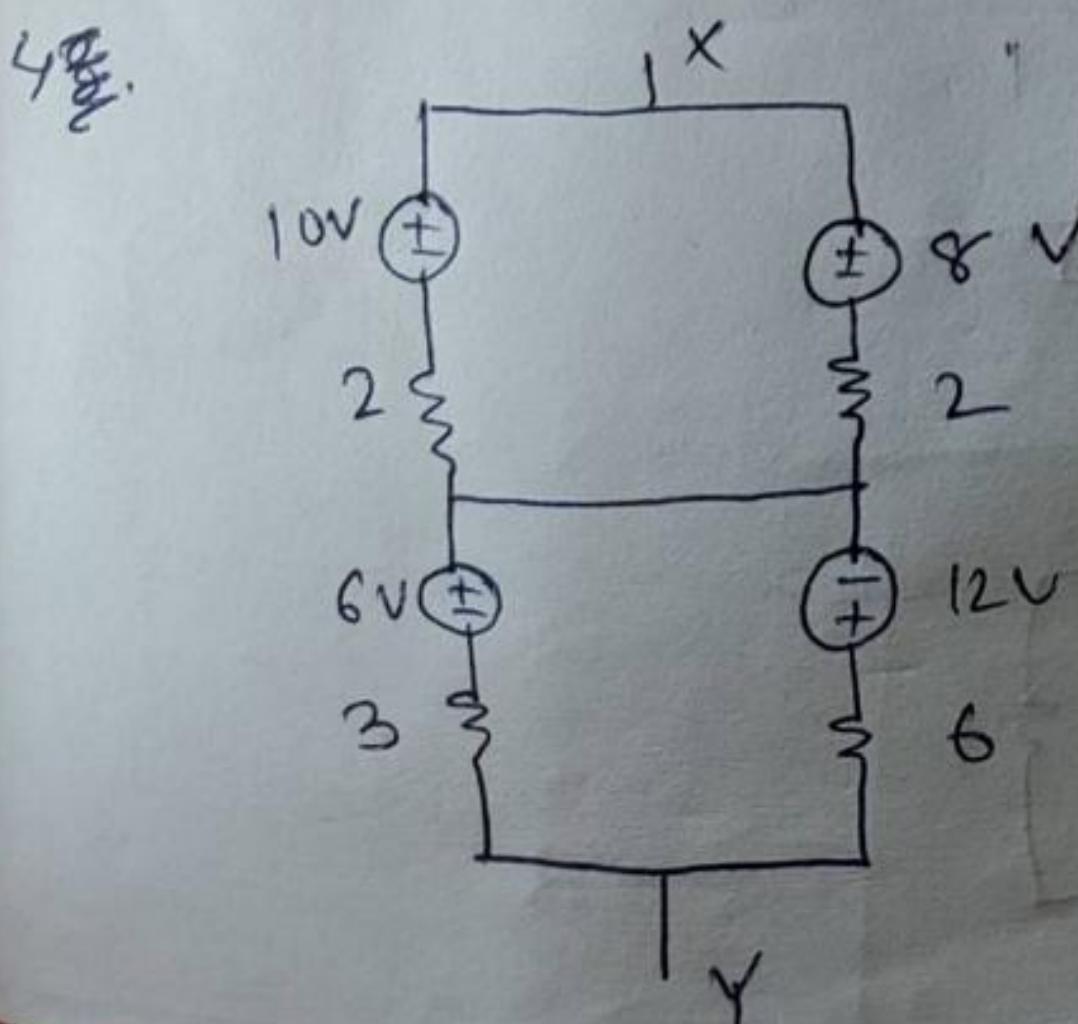
$$\therefore P_{\text{del}} = -\frac{3}{2} \times 2 = -3 W$$




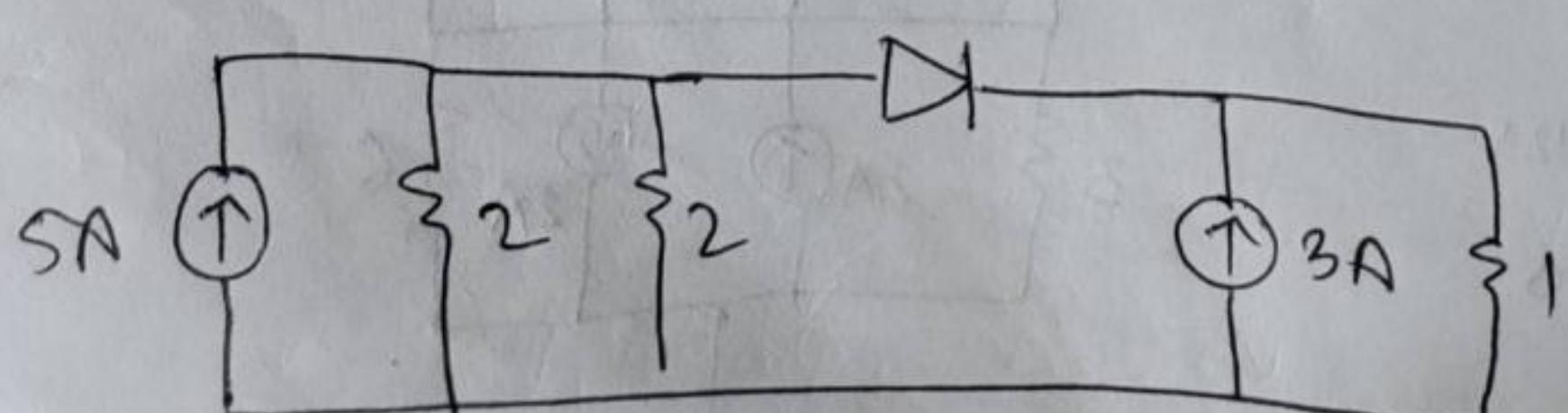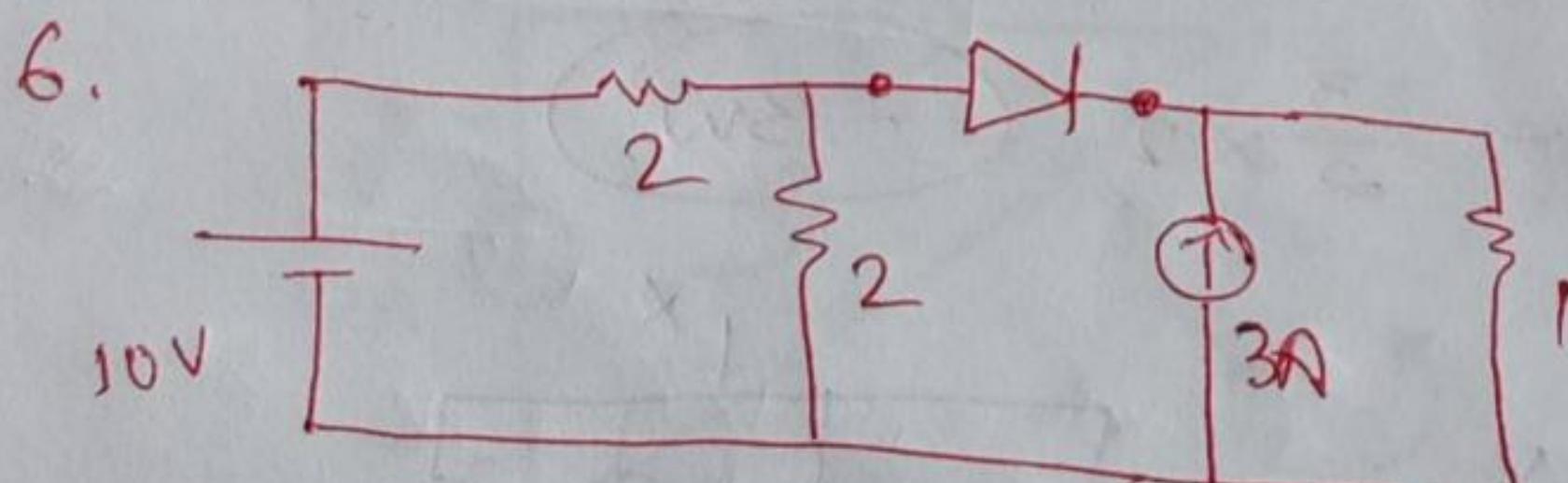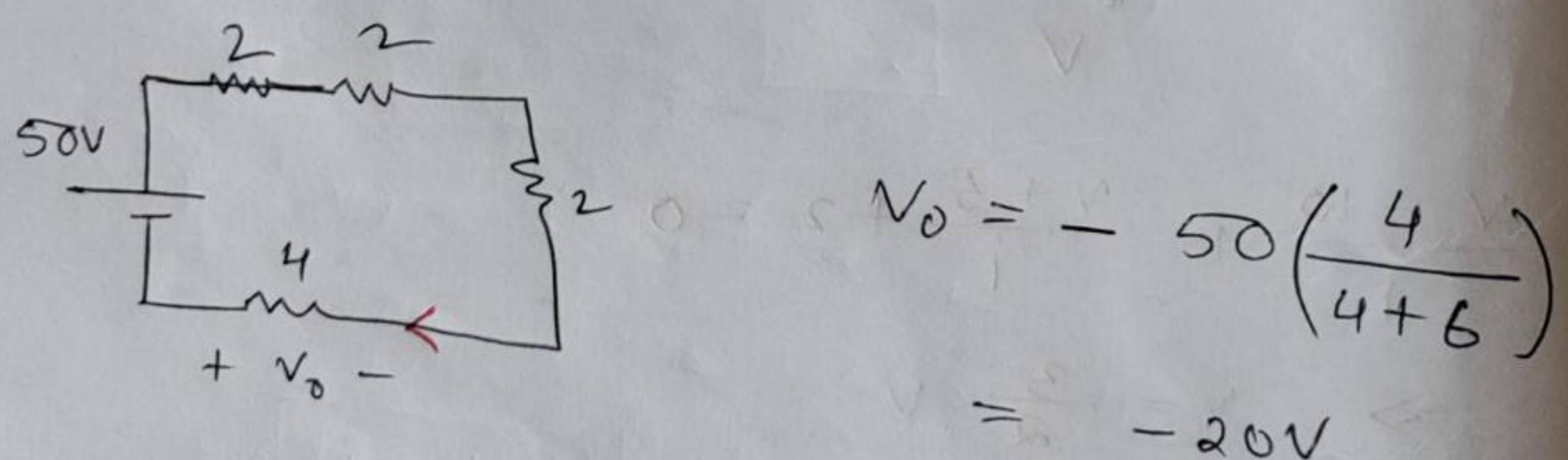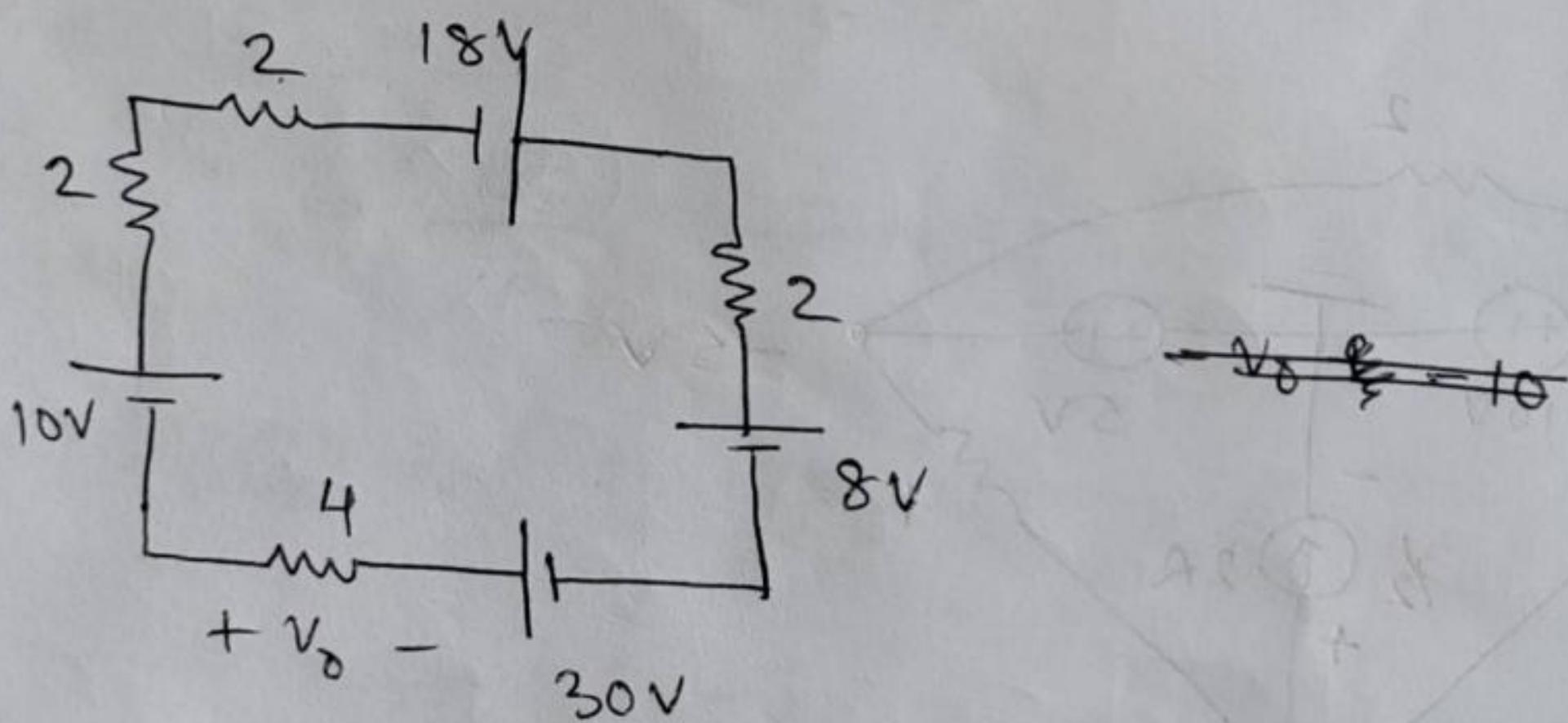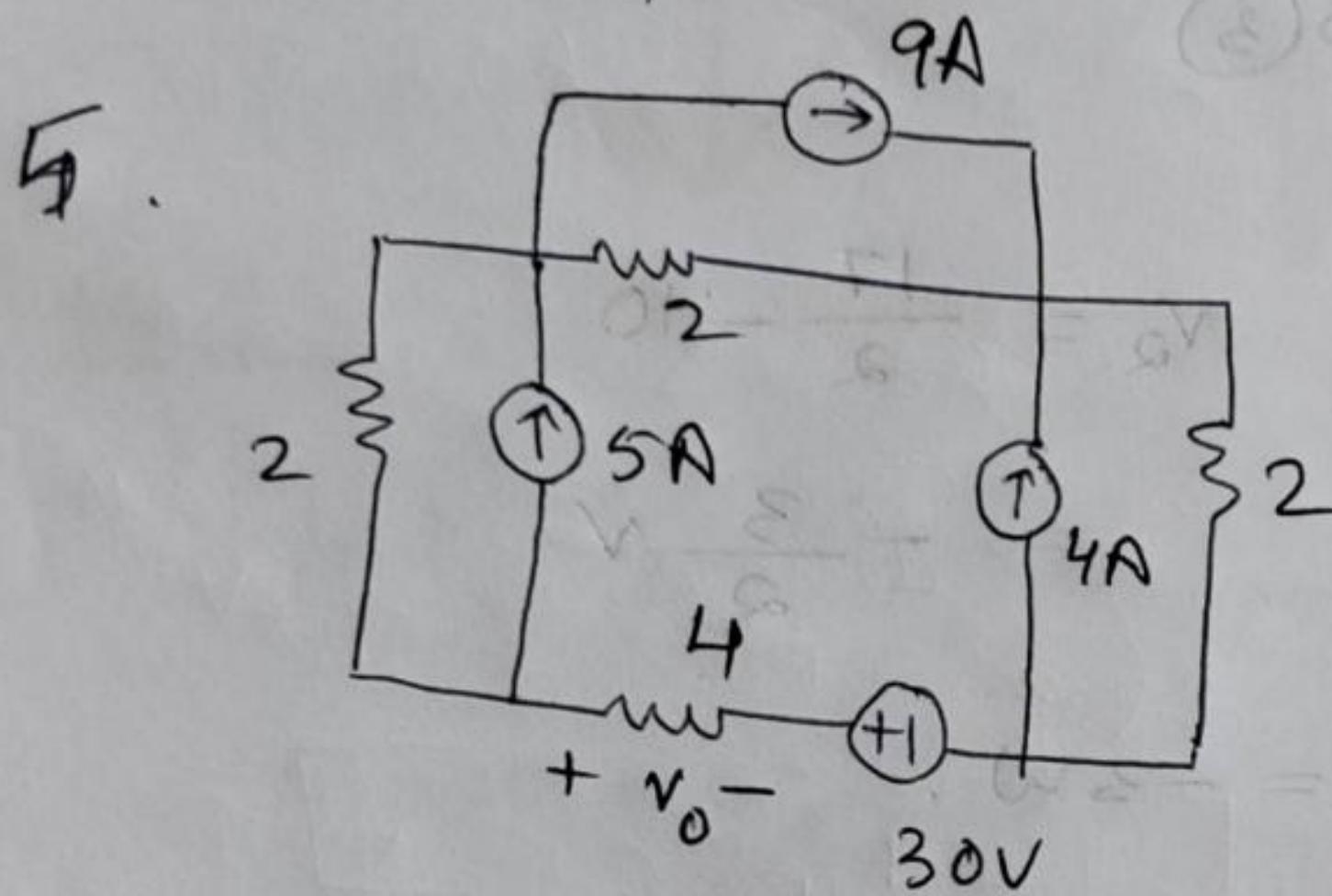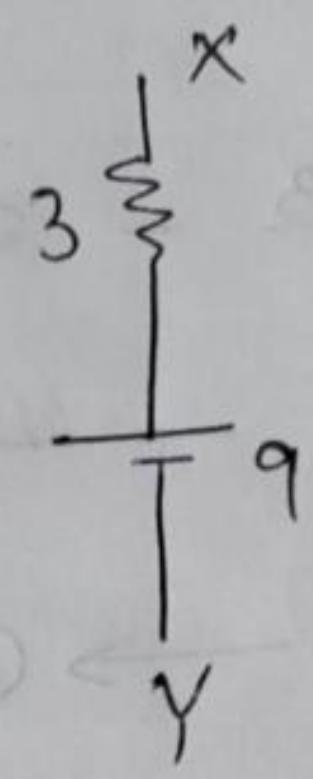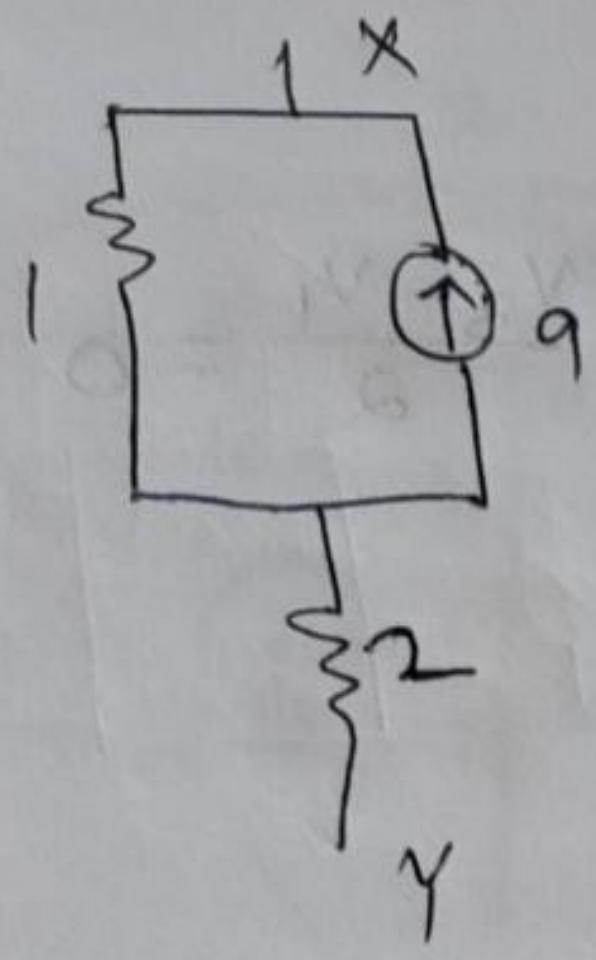

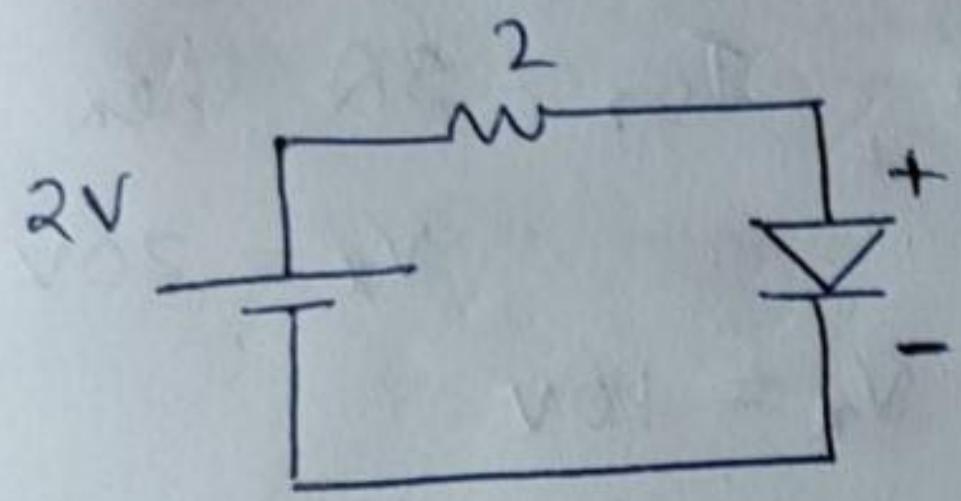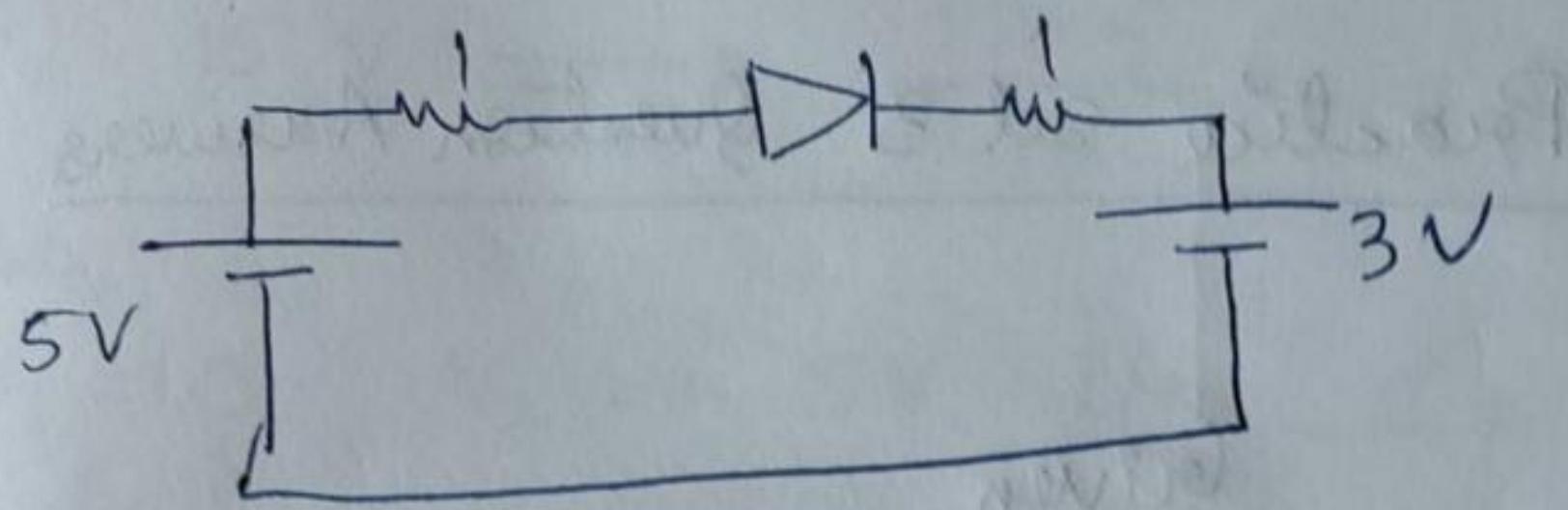

Forward bias $\therefore R = 0$

$$\therefore I_D = \frac{2}{2} = 1A$$

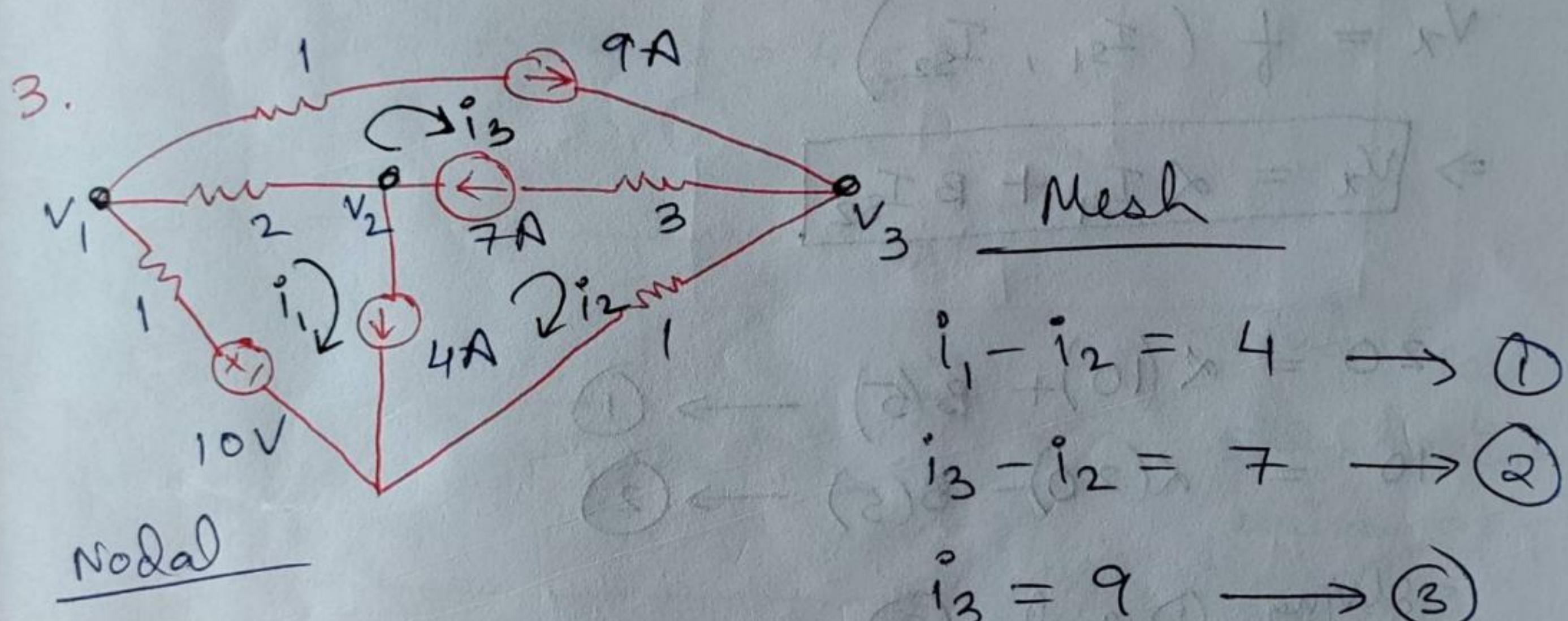

$$\frac{v_1 - 10}{1} + \frac{v_1 - v_2}{2} + 9 = 0 \rightarrow \textcircled{1}$$


$$\frac{v_2 - v_1}{2} + 4 - 7 = 0 \rightarrow \textcircled{2}$$

$$\frac{v_3}{1} - 9 + 7 = 0 \rightarrow \textcircled{3}$$

$$v_2 = 1V$$

Practice set 3 Question Answers

1.

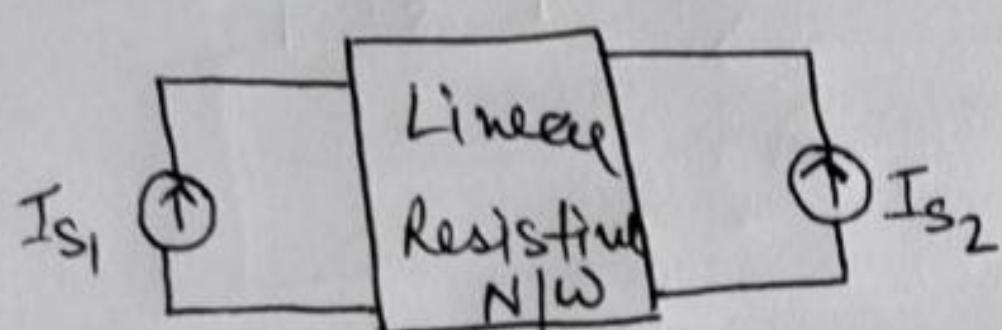

Given,

$$I_{S1} = 10A, I_{S2} = 5A \text{ then}$$

$$V_x = 20V$$

$$I_{S1} = 20A, I_{S2} = -5A \text{ then } V_x = 10V$$

If $I_{S1} = I_{S2} = 15A$ then $V_x = ?$

Now,

$$V_x = f(I_{S1}, I_{S2})$$

$$\Rightarrow V_x = \alpha I_{S1} + \beta I_{S2}$$

$$20 = \alpha(10) + \beta(5) \rightarrow ①$$

$$10 = \alpha(20) - \beta(5) \rightarrow ②$$

Solving ① and ② $\Rightarrow 30 = 30\alpha$

$$\Rightarrow \alpha = 1$$

$$\therefore \beta = 2$$

Again,

$$\begin{aligned} V_x &= 1 I_{S1} + 2 I_{S2} \\ &= 1 \times 15 + 2 \times 15 = 45 \end{aligned}$$

$$V_x = 45V$$

Ques Given,


~~$$V_1 = 10V, V_2 = 0V \text{ and } I = 5A$$~~

~~$$\text{Also, } V_1 = 0V, V_2 = -5V \text{ then } I = 1A$$~~

To find : If $V_1 = V_2 = 15V, I = ?$

$\curvearrowleft V_1 = 10, V_2 = 0V \text{ then } I = ?$

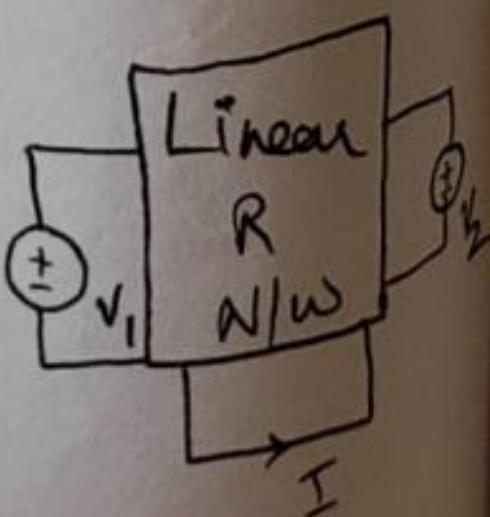$\curvearrowleft \text{If } V_1 \text{ act alone } \rightarrow 10 \rightarrow 5A$



$$\therefore 15V \rightarrow \frac{15 \times 5}{10} = 7.5A \quad (\text{Homogeneity})$$

Also,

$$V_1 = 0, V_2 = -5V \text{ then } I = 1A$$


If V_2 act alone

$$-5V \rightarrow 1A$$

$$15V \rightarrow \frac{15 \times 1}{-5} = -3A \quad (\text{Homogeneity})$$

By S.P.T

$$I = 7.5 - 3 = 4.5A$$

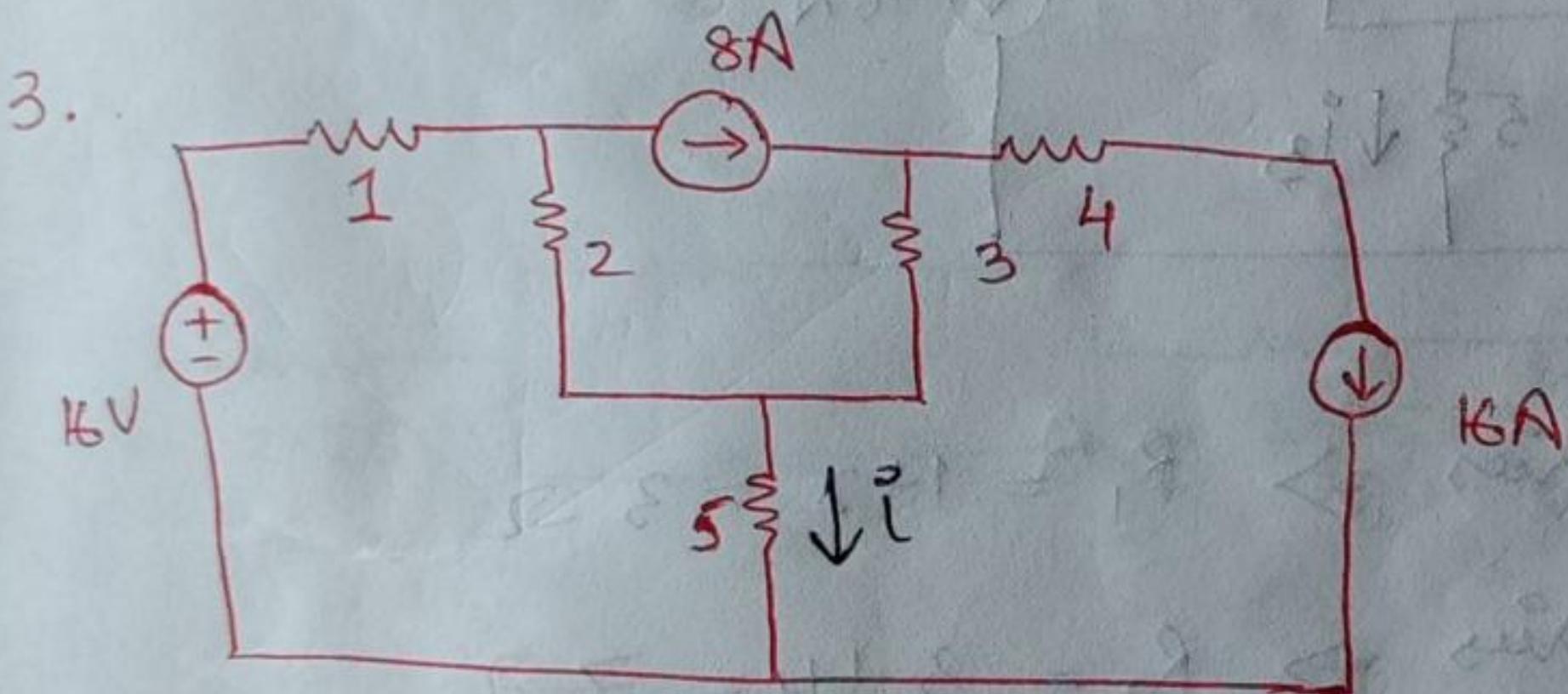


Find Power in
5Ω resistor
using SPT
and KVL.

NOTE : Power is a non linear parameter and hence can't be calculated directly using SPT.

Sol^u

Step 1: 16V only

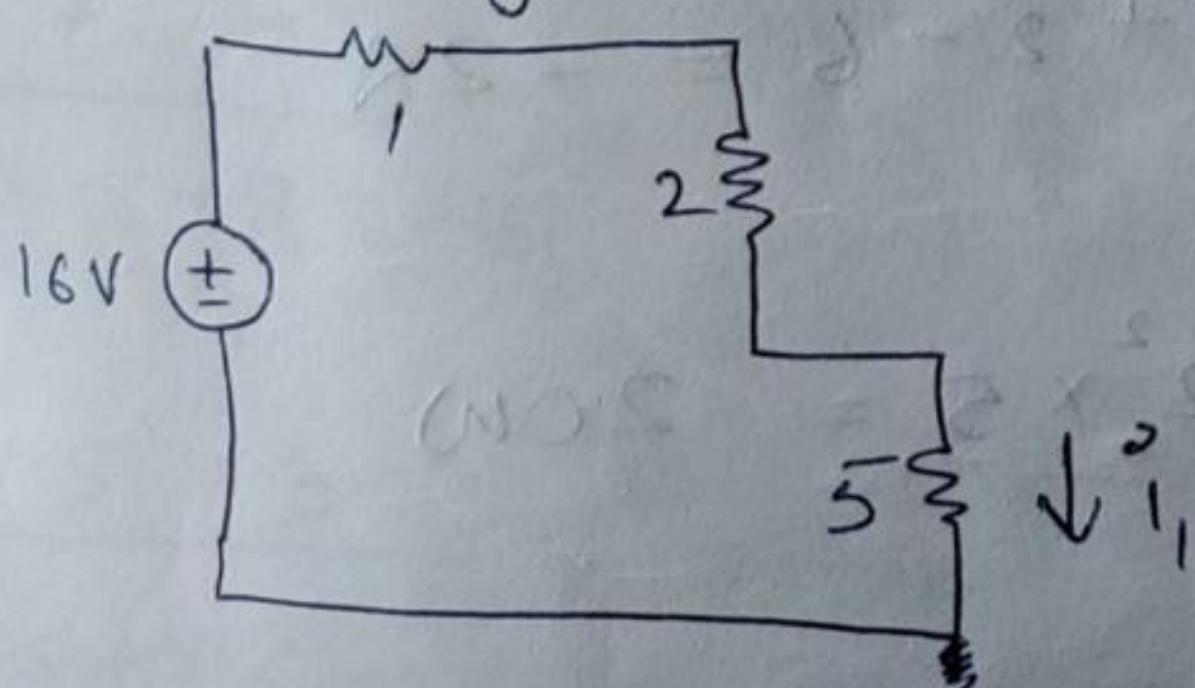



$$i_1 = \frac{16}{8} = 2A$$

Step 2

: 8A only

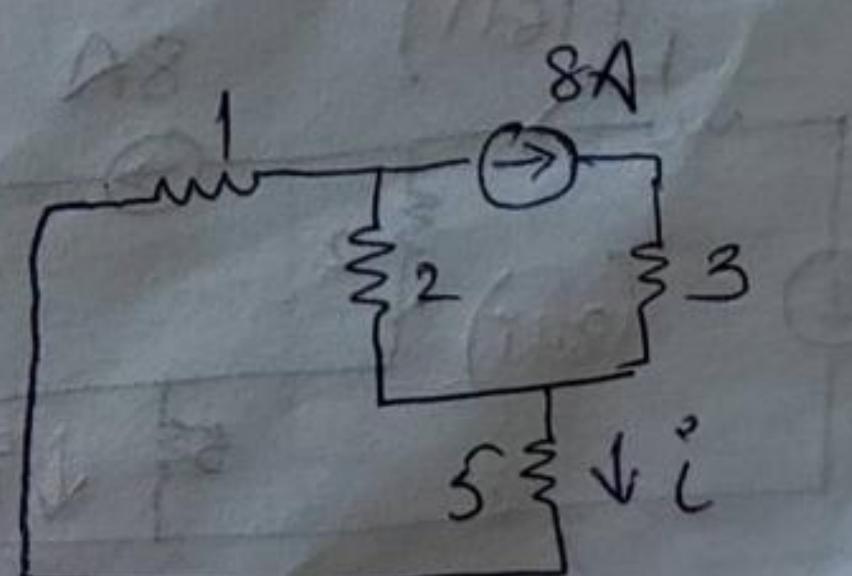
$$\begin{aligned} 3 \text{ and } 1 \text{ in series } R &= 5+1 \\ &= 6 \end{aligned}$$



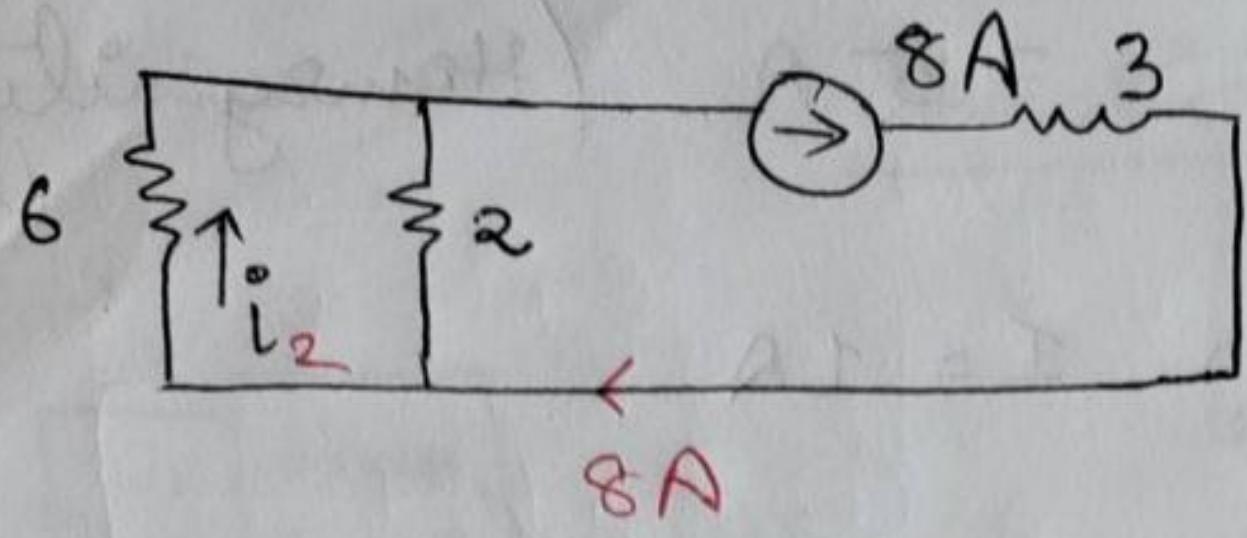


$$\therefore i_2 = 8 \left(\frac{2}{6+2} \right) = 2A$$

Step 3 : 16A only

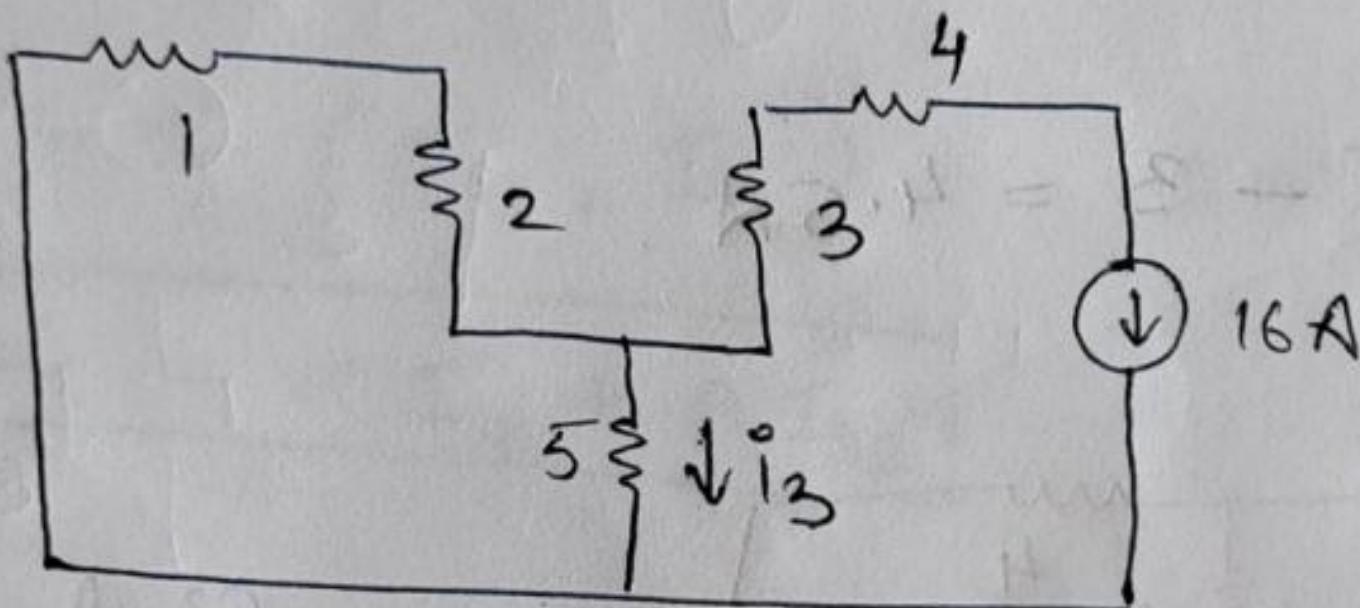

$$1 \text{ and } 2 \text{ in series} \Rightarrow R_1 = 1+2 = 3 \Omega$$
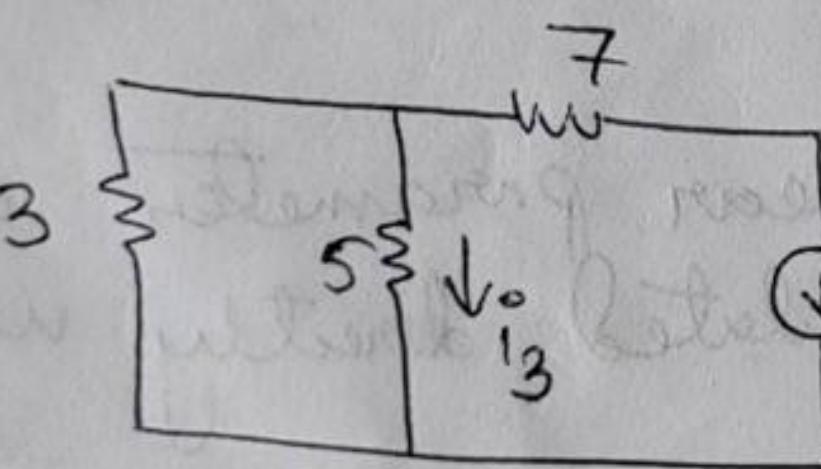
$$3 \text{ and } 4 \text{ in series} \Rightarrow R_2 = 3+4 = 7 \Omega$$




$$i_3 = -16 \left(\frac{3}{5+3} \right)$$

$$= -6A$$

$$\therefore i = i_1 + i_2 + i_3 = 2 + 2 - 6 = -2A$$




$$P_{\text{lost}} = I^2 R = 2^2 \times 5 = 20W$$

KVL

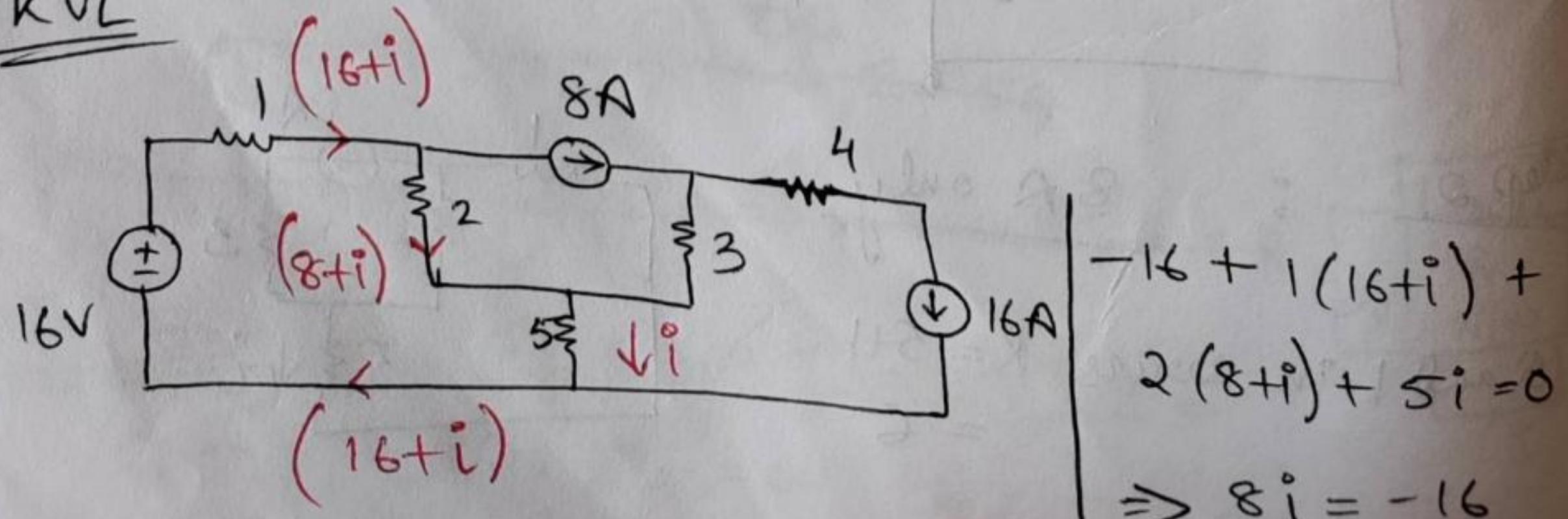

$$\begin{aligned} -16 + 1(16+i) + \\ 2(8+i) + 5i &= 0 \\ \Rightarrow 8i &= -16 \\ \Rightarrow i &= -2A \end{aligned}$$
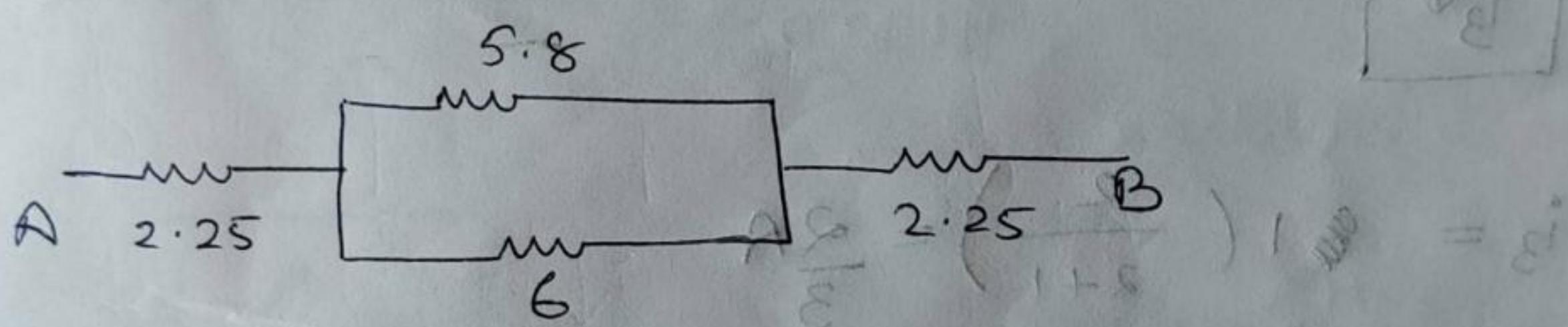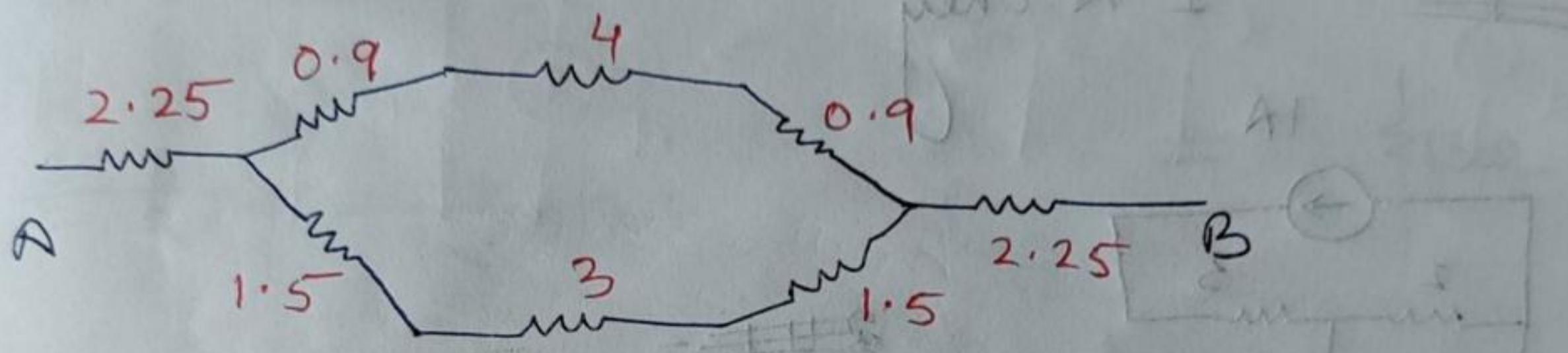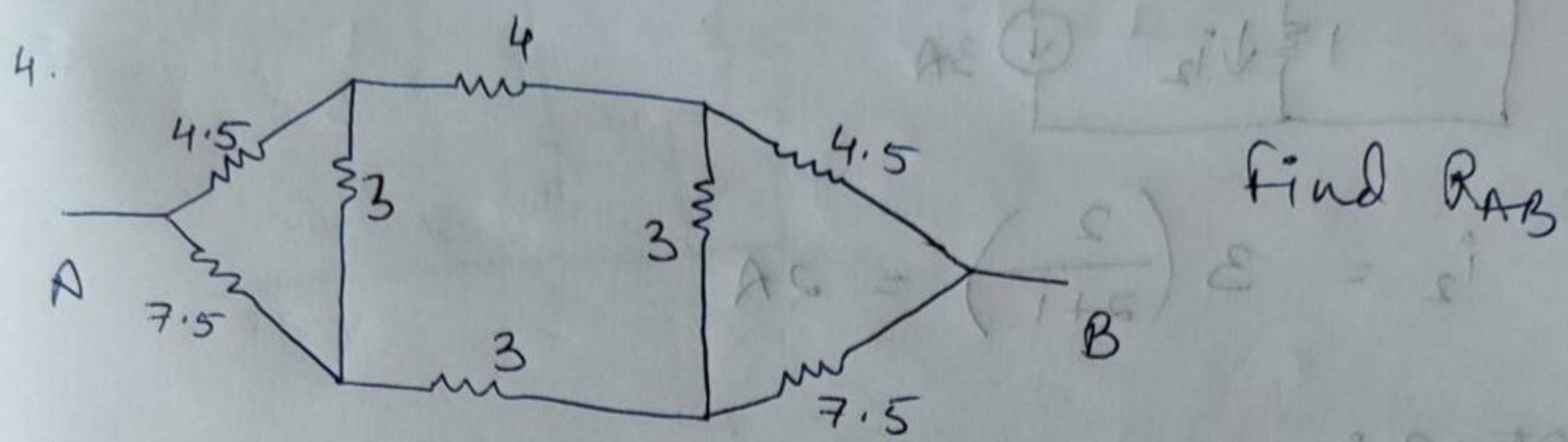
$$\therefore P_{\text{lost}} = i^2 R \\ = 4 \times 5 = 20W$$



$$R_{AB} = 7.45 \Omega$$

Delta to Star

$$\frac{4.5 \times 7.5}{4.5 + 7.5 + 3} = 2.25 \Omega$$


$$\frac{7.5 \times 3}{4.5 + 7.5 + 3} = 1.5 \Omega$$

$$\frac{4.5 \times 3}{4.5 + 7.5 + 3} = 0.9 \Omega$$

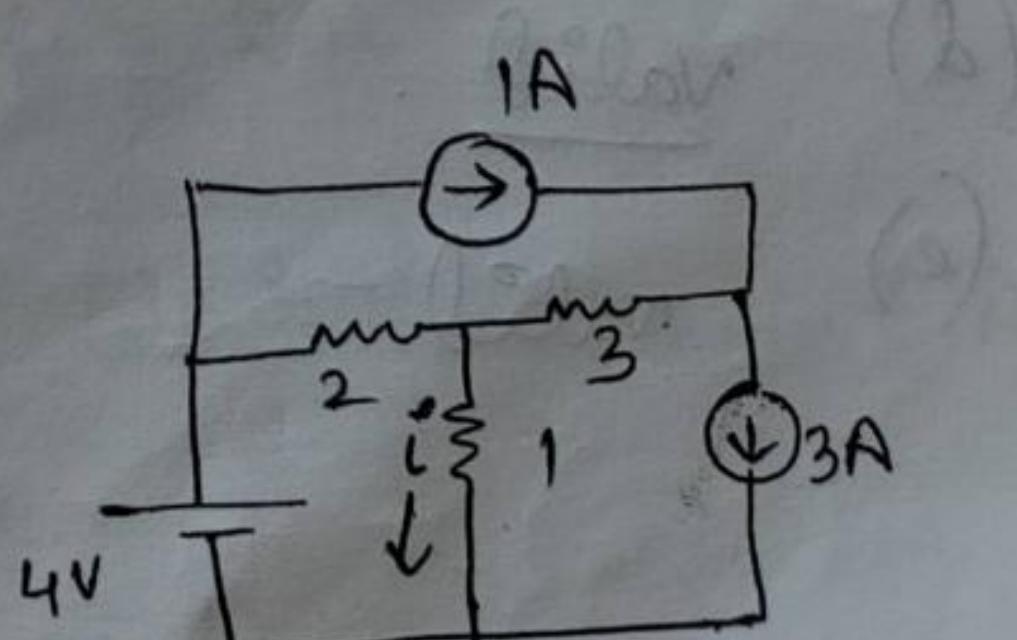
5. Find i in 1Ω using SPT

Soln: step 1: 4V only

$$4V \xrightarrow{\text{1A}} \frac{1}{2} \parallel \frac{1}{3} \parallel 1 \quad i_1 = \frac{4}{3} A$$




Step 2 : 3A only

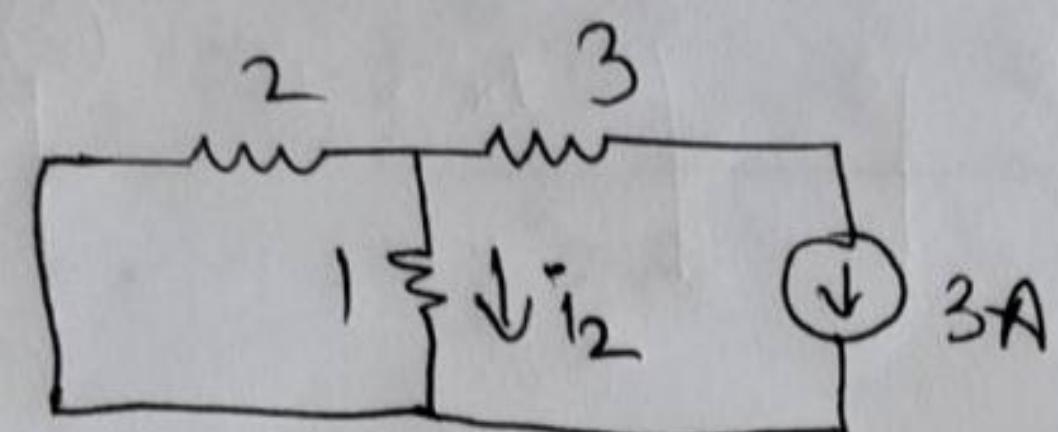

$$i_2 = 3 \left(\frac{2}{2+1} \right) = 2A$$

Step 3 : 1 A only

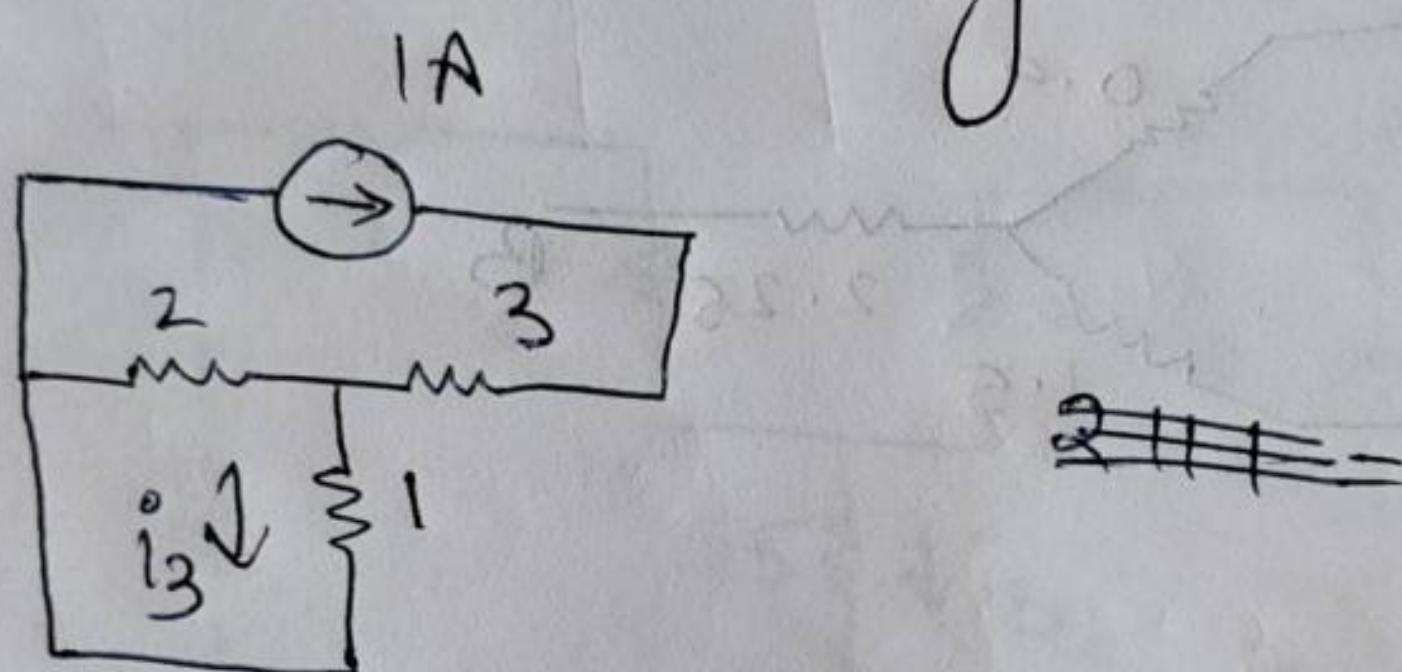

$$i_3 = 1 \left(\frac{2}{2+1} \right) = \frac{2}{3} A$$

$$\therefore i = i_1 + i_2 + i_3$$

$$= \frac{4}{3} + 2 + \frac{2}{3}$$

$$i = 4A$$

6. (a) 2 voltage of different values \rightarrow violates KVL.


(b) valid as resistor in b/w. KVL.

(c) unclear what current flows through R.

$$I = 1 - 1 = 0 \rightarrow \text{invalid}$$


(d) valid.

(e) valid

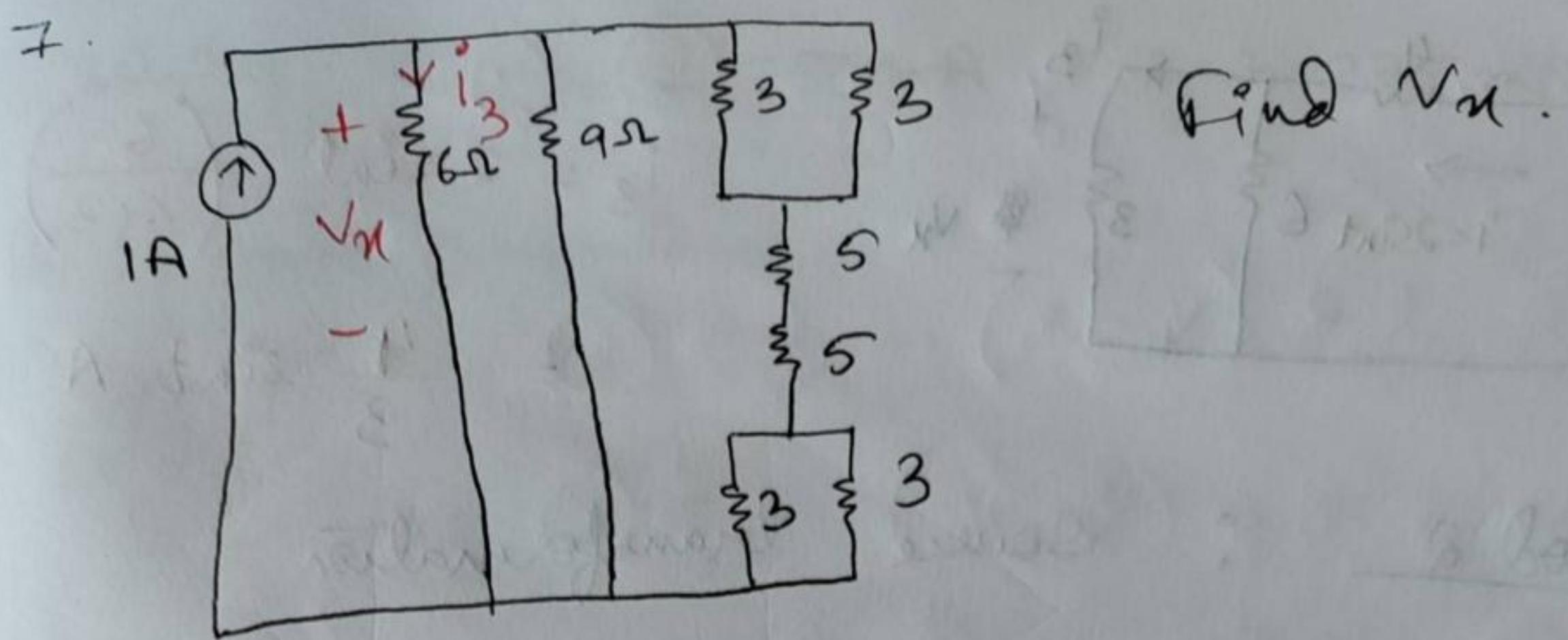


$$3//3 = \frac{9}{6} = \frac{3}{2}$$
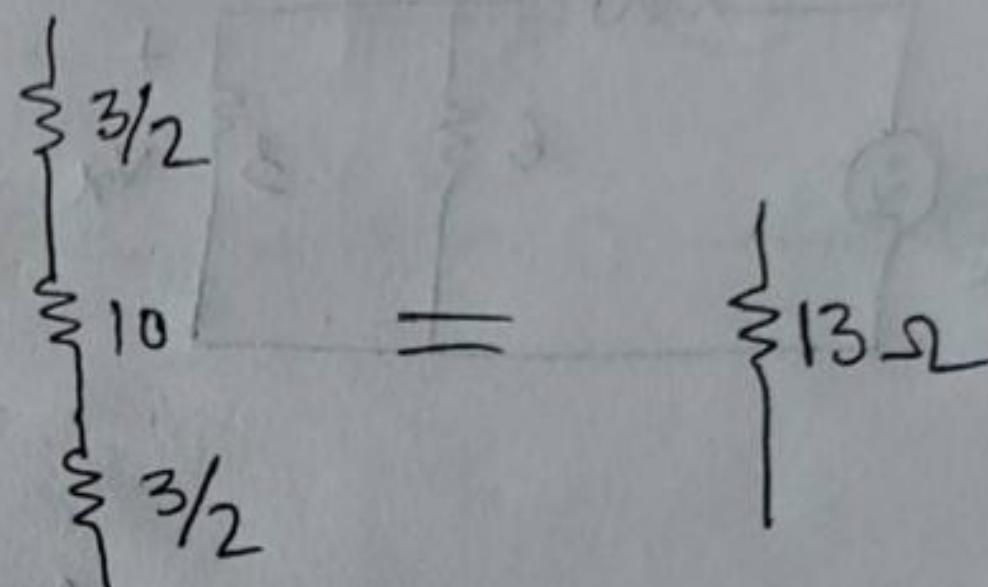
$$\frac{3}{2} + \frac{3}{2} + 10 = \frac{26}{2} = 13\Omega$$


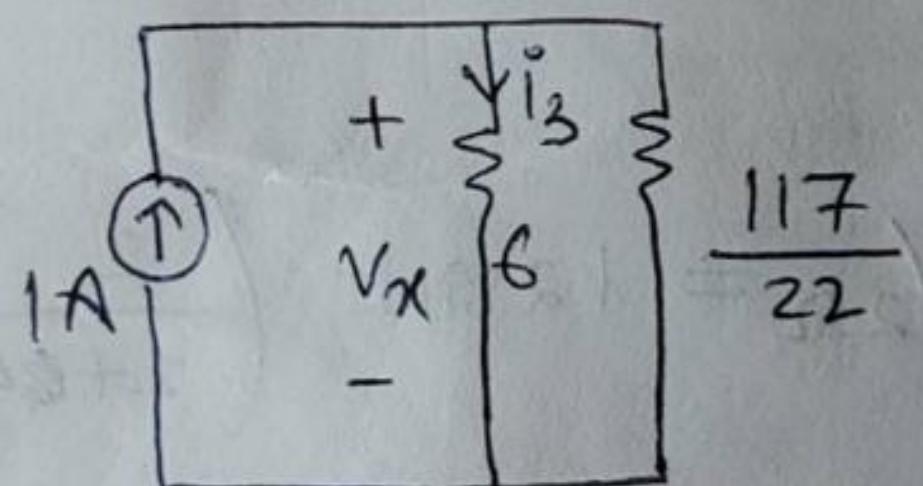
$$13//9 = \frac{13 \times 9}{22} = \frac{117}{22}$$



$$I_3 = 1 \left(\frac{\frac{117}{22}}{\frac{117}{22} + 6} \right)$$


$$= \frac{117}{22} \times \frac{22}{249}$$

$$= 0.4698$$

$$\therefore V_x = 6 \times 0.4698$$


$$= 2.8188 \approx 2.819 \text{ V}$$

8.

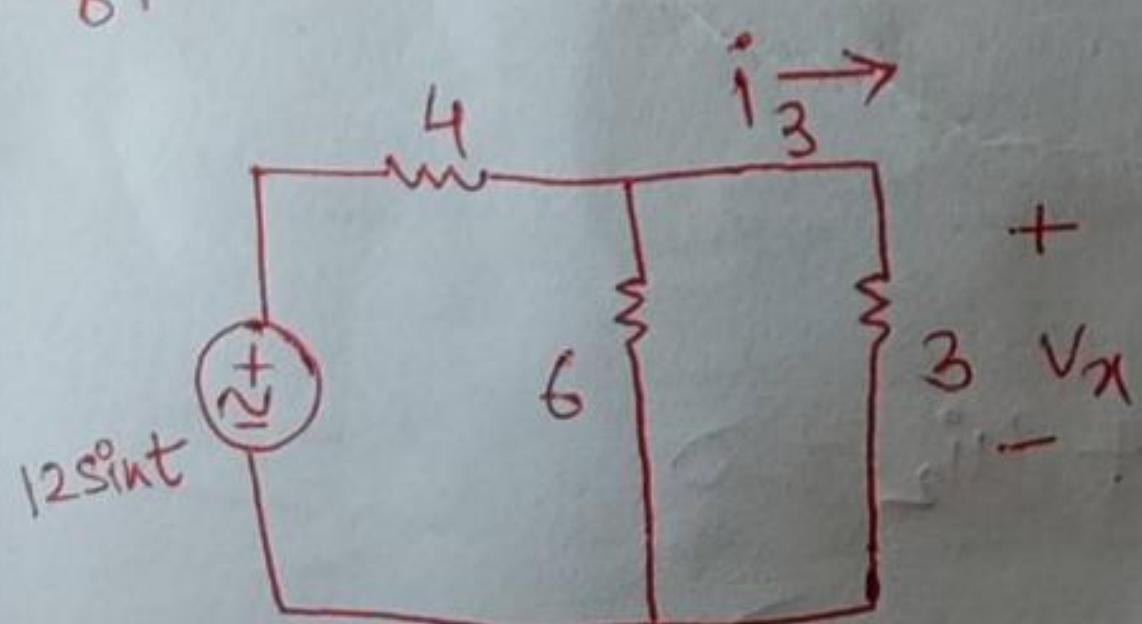


Find i_3 .

$$3//6 = 2\Omega$$

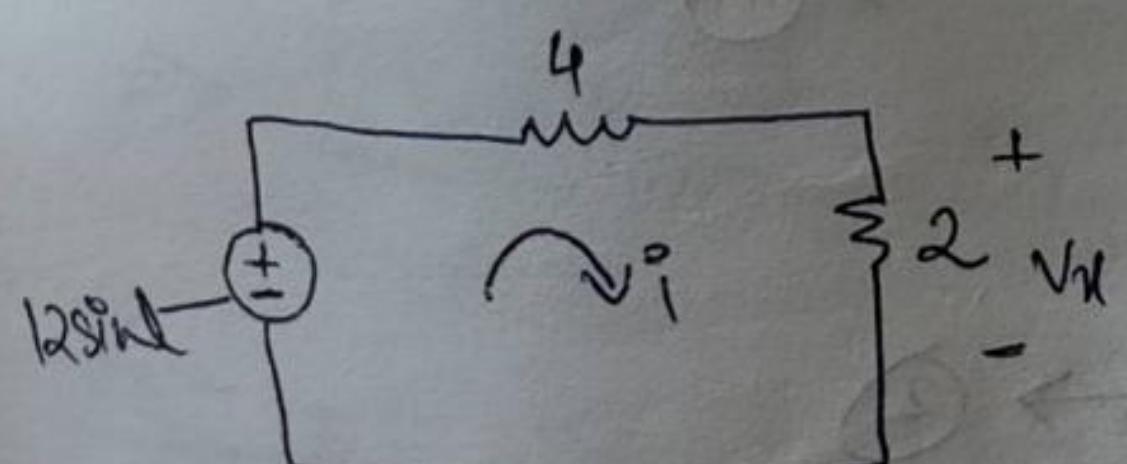


$$i = \frac{12 \sin t}{6} = 2 \sin t \text{ A}$$

↑
total current.


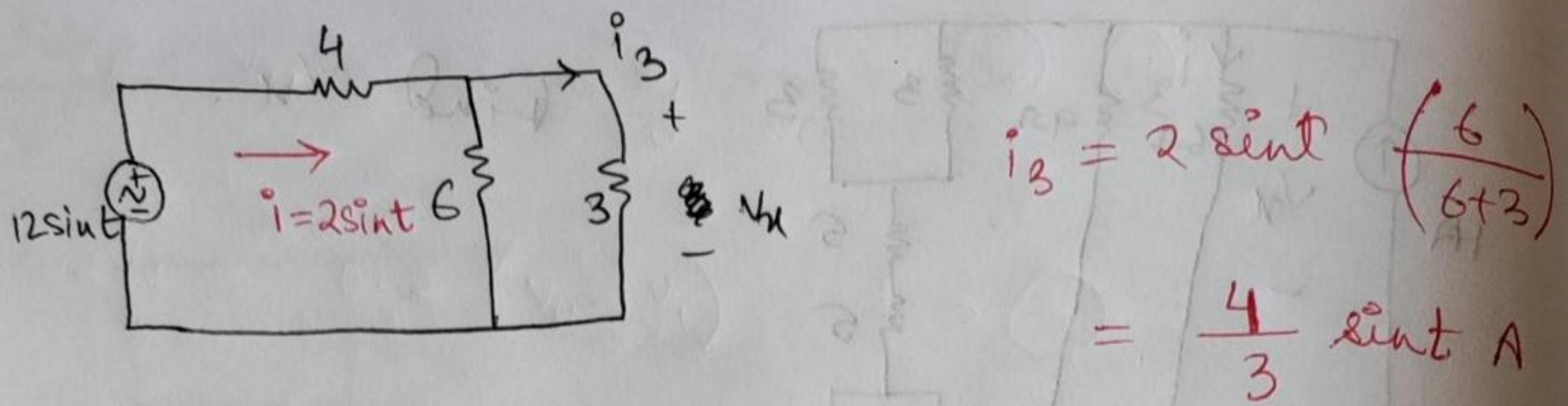


Method 2 : Source transformation

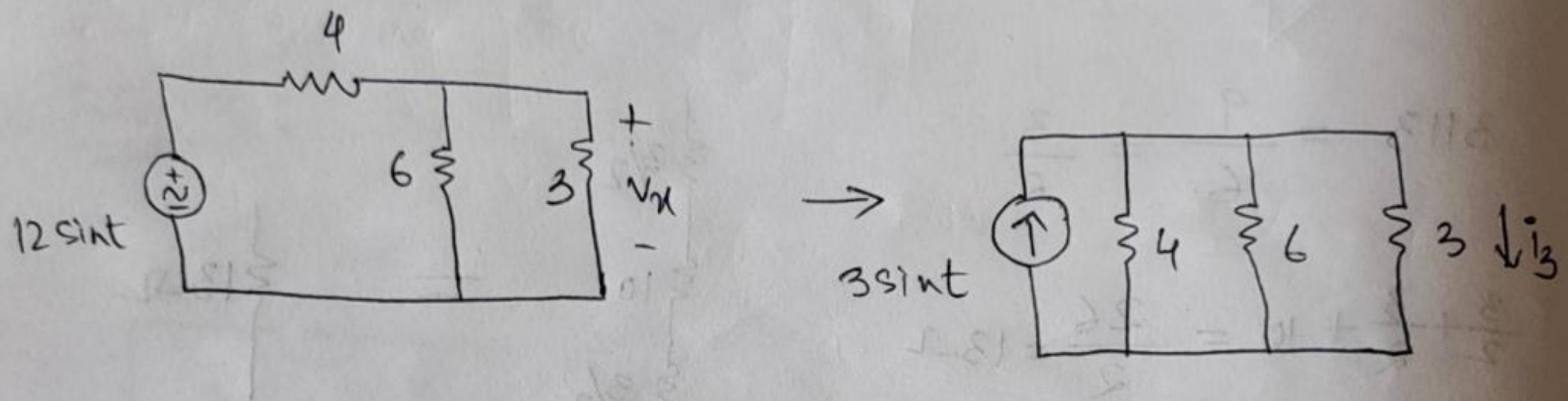

$$i_3 = 3 \sin t \frac{6 \times 4}{24 + 18 + 12} = \frac{6 \times 4}{60} \sin t \text{ A}$$

Method 3 : Voltage division

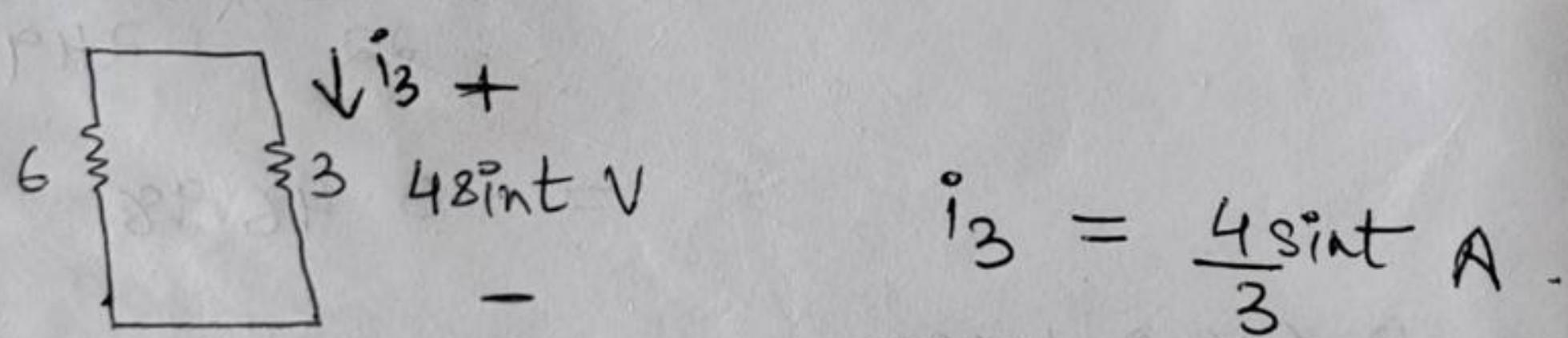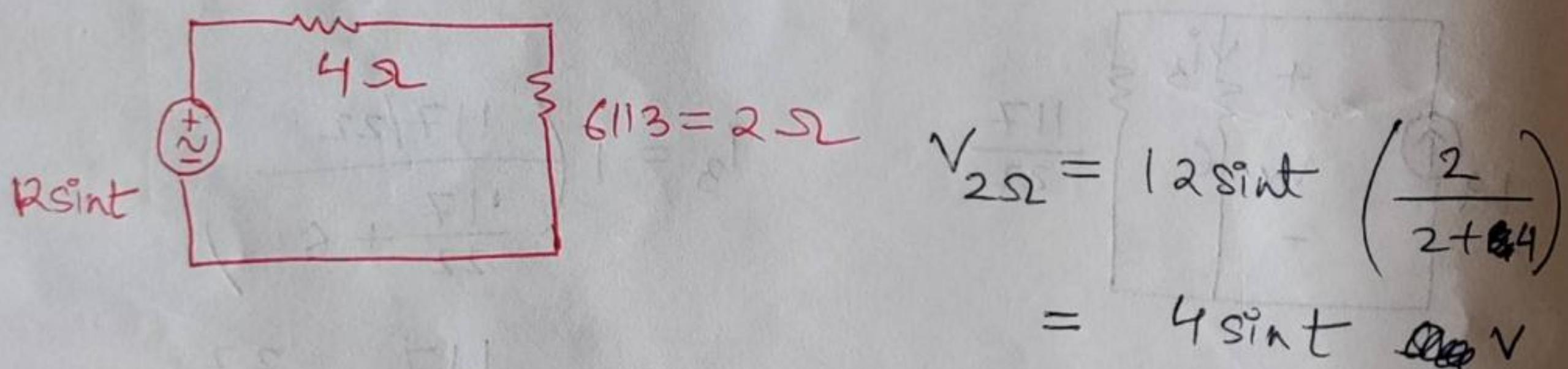

KVL


$$-5 - 4i_1 + 4(i_2 - i_1) + 4i_2 = 0$$

$$\Rightarrow -8i_1 + 8i_2 = 5 \rightarrow ①$$

$$4(i_1 - i_2) + 2i_1 + 3 = 0$$

$$\Rightarrow 6i_1 - 4i_2 = -3 \rightarrow ②$$

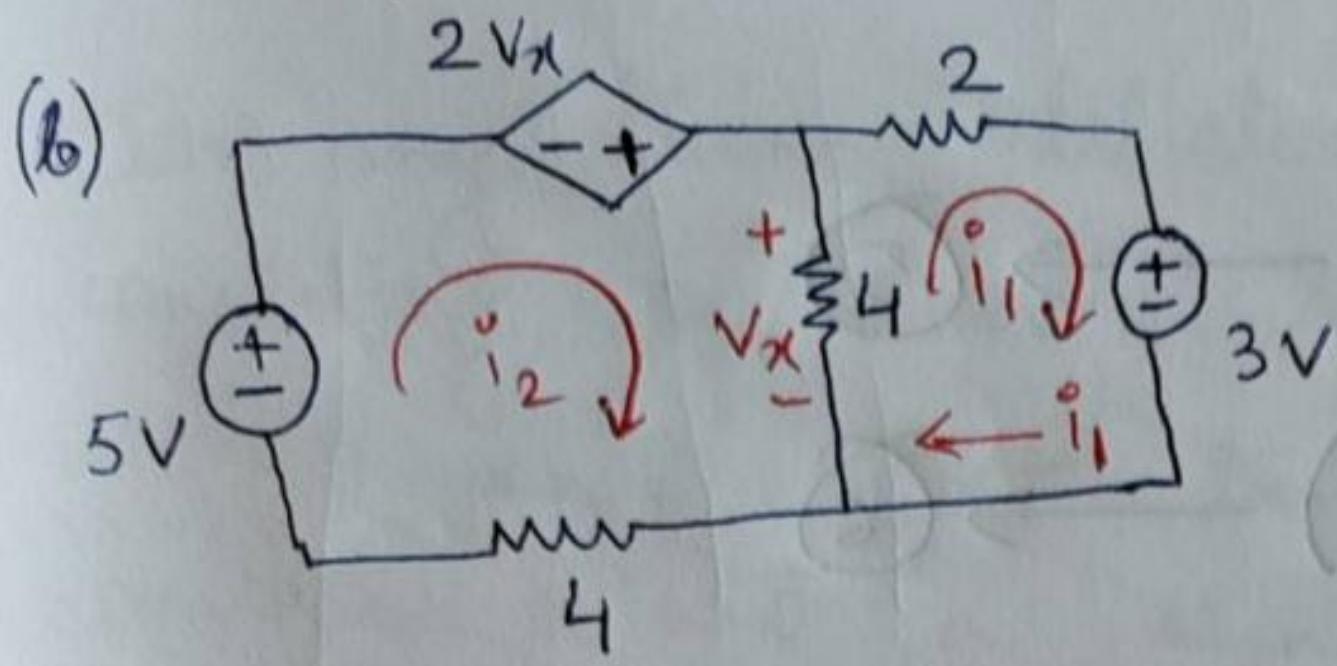solving, $i_1 = -250 \text{ mA}$ $i_2 = 375 \text{ mA}$



$$-5 - 2V_x + 4(i_2 - i_1) + 4i_2 = 0 \rightarrow ①$$

~~$$-4(i_1 - i_2) + 4(i_1 - i_2) + 2i_1 + 3 = 0 \rightarrow ②$$~~


$$V_x = 4(i_2 - i_1) \rightarrow ③$$

Put ③ in ①,

$$4i_1 = 5$$

$$\Rightarrow i_1 = 1.25 \text{ A}$$

10.

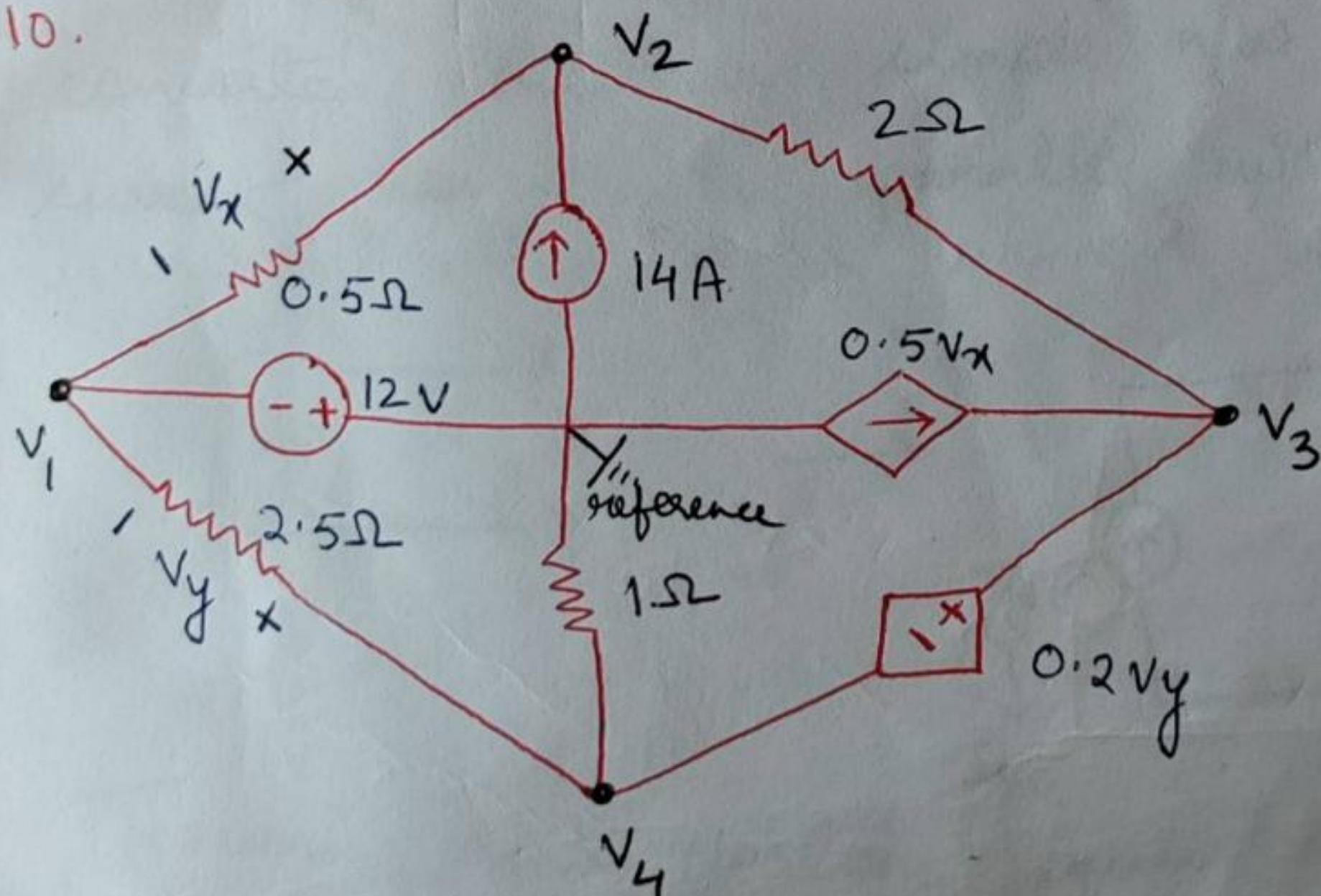

$$v_1 = -12 \rightarrow ①$$

$$\frac{v_2 - v_1}{0.5} - 14 + \frac{v_2 - v_3}{2} = 0$$

$$\Rightarrow \frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 14 \rightarrow ②$$

$$\frac{v_3 - v_2}{2} + \frac{v_4}{1} + \frac{v_4 - v_1}{2.5} - 0.5V_x = 0 \rightarrow ③$$

$$v_3 - v_4 = 0.2 v_y \rightarrow \textcircled{4}$$

$$0.2 v_y = 0.2 (v_4 - v_1) \rightarrow \textcircled{5}$$

$$0.5 v_x = 0.5 (v_2 - v_1) \rightarrow \textcircled{6}$$

\therefore Solving, we get


$$\textcircled{7} \quad v_1 = -12V, v_2 = -4V, v_3 = 0V, v_4 = -2V$$

$$\textcircled{8} \quad (i^o - i^s) H = xV$$

$$\textcircled{9} \quad v_i \text{ due to } \textcircled{8}$$

$$\bar{e} = i^o H$$

$$A \bar{e} = 1$$


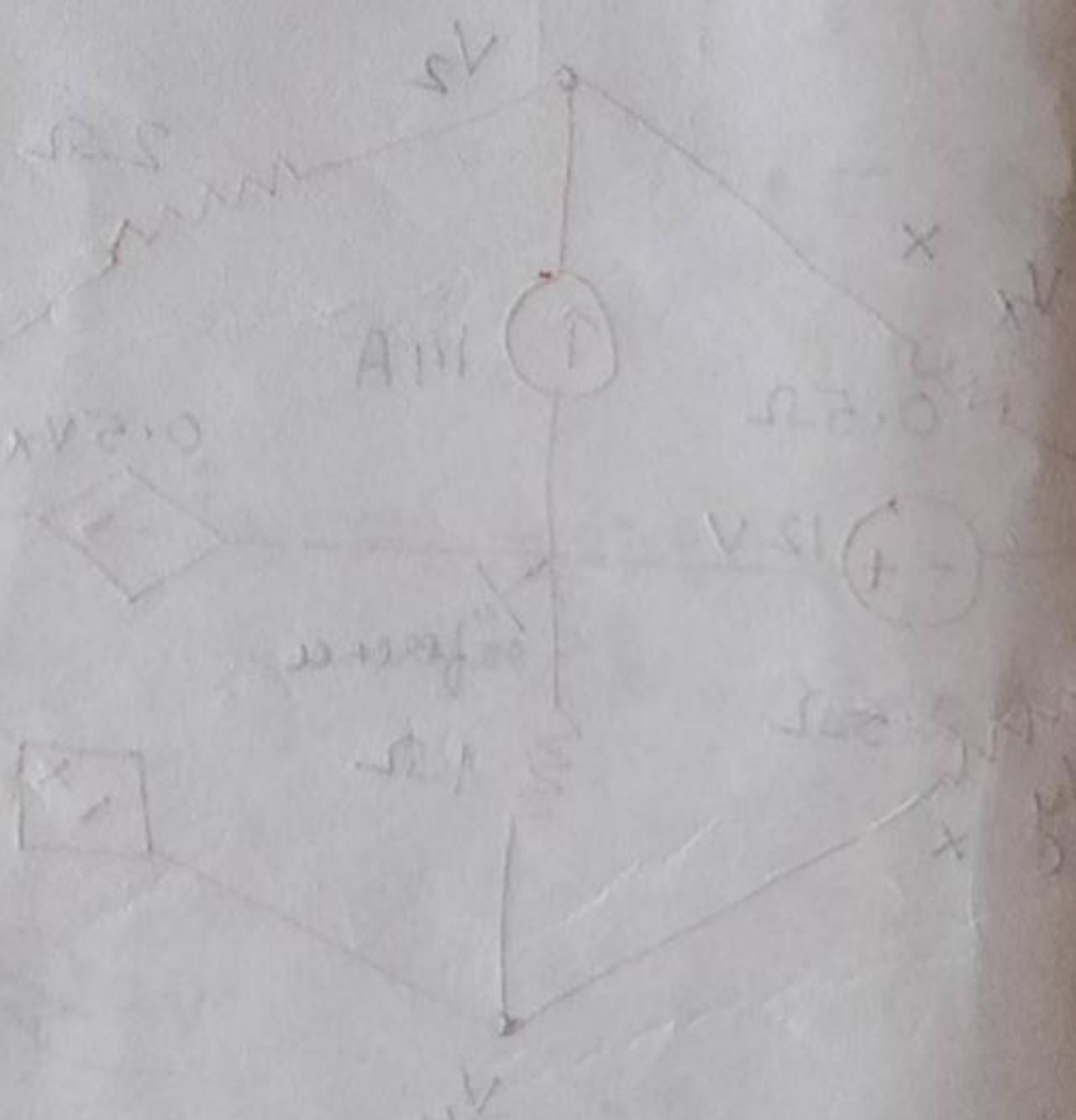


$$\textcircled{10} \quad \bar{e} = i^o H$$

$$0 = \frac{\bar{e} - v}{R} + 10 - \frac{v - \bar{e}}{20}$$

PRACTICE SET 4

1. Find v_x with the help of SPT

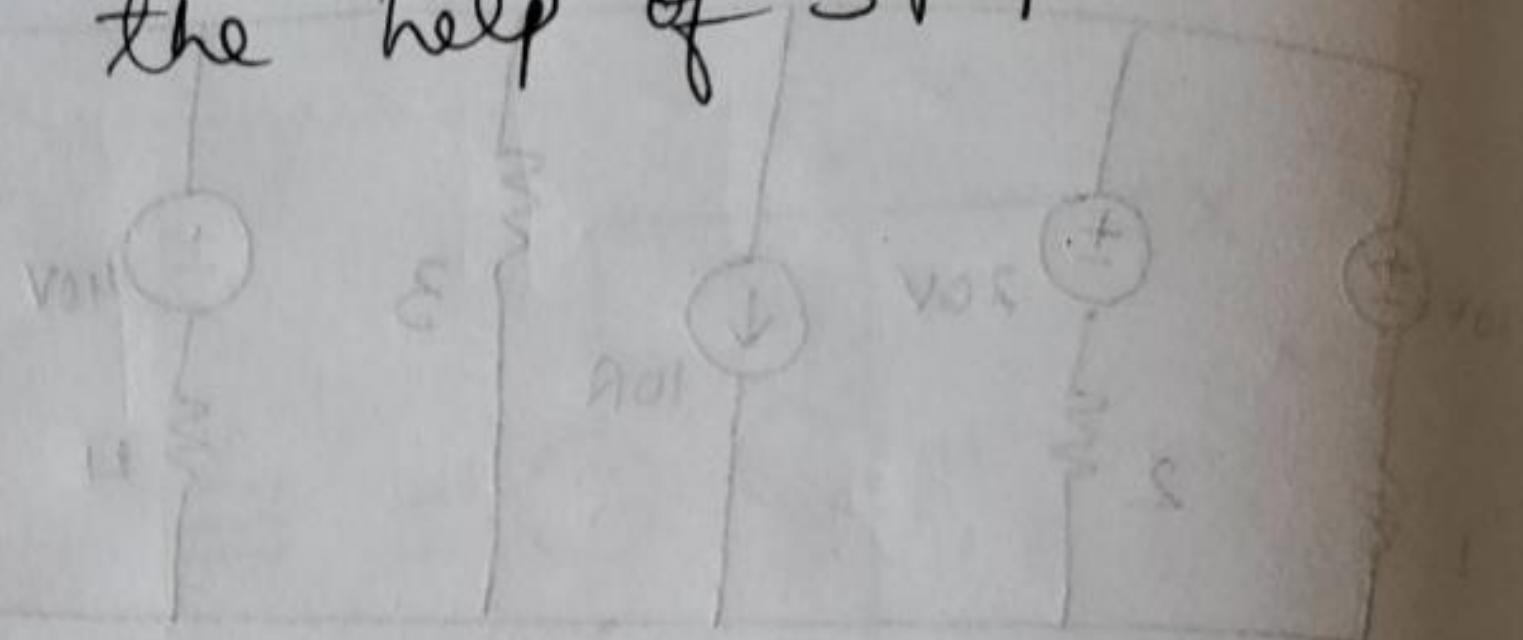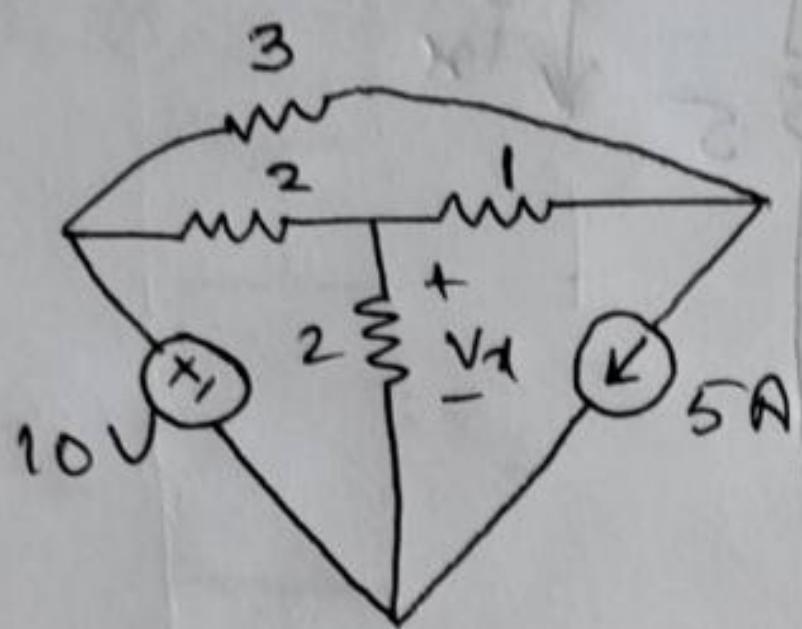

Solⁿ

Step 1 : 10V only

$$v_{x_1} = 10 \left(\frac{2}{2+4/3} \right) \\ = 6V$$

$$4/12 = \frac{8}{6} = \frac{4}{3}$$


Step 2 : 5A only

$$v_{x_2} = -2 \left[5 \left(\frac{3}{3+2} \right) \times \frac{2}{4} \right] \\ = -3V$$

' Using SPT

$$v_x = v_{x_1} + v_{x_2} = 6 - 3 = 3V.$$

2. Find v_x using Nodal Analysis

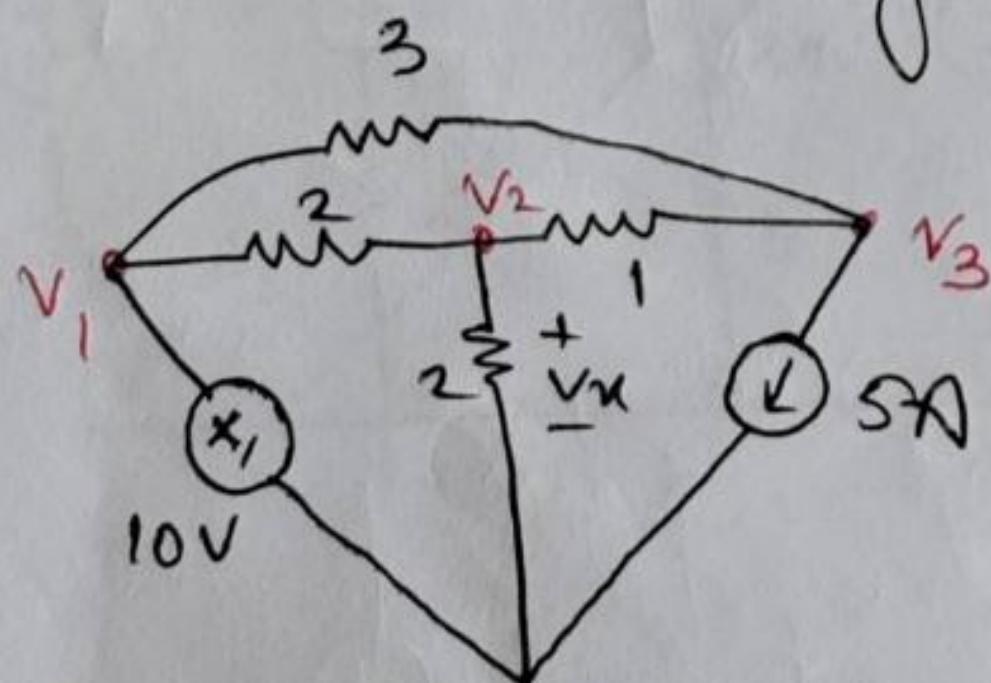

$$v_1 = 10 \rightarrow ①$$

$$\frac{v_2 - 10}{2} + \frac{v_2}{2} + \frac{v_2 - v_3}{1} = 0 \rightarrow ②$$

$$\Rightarrow 4v_2 - 2v_3 = 10$$


$$5 + \frac{V_3 - V_2}{1} + \frac{V_3 - 10}{3} = 0$$

$$\Rightarrow -3V_2 + 4V_3 = -5 \rightarrow (3)$$

$$V_2 = 3$$

$$\therefore V_x = 3V$$

3. Find V_x using SPT

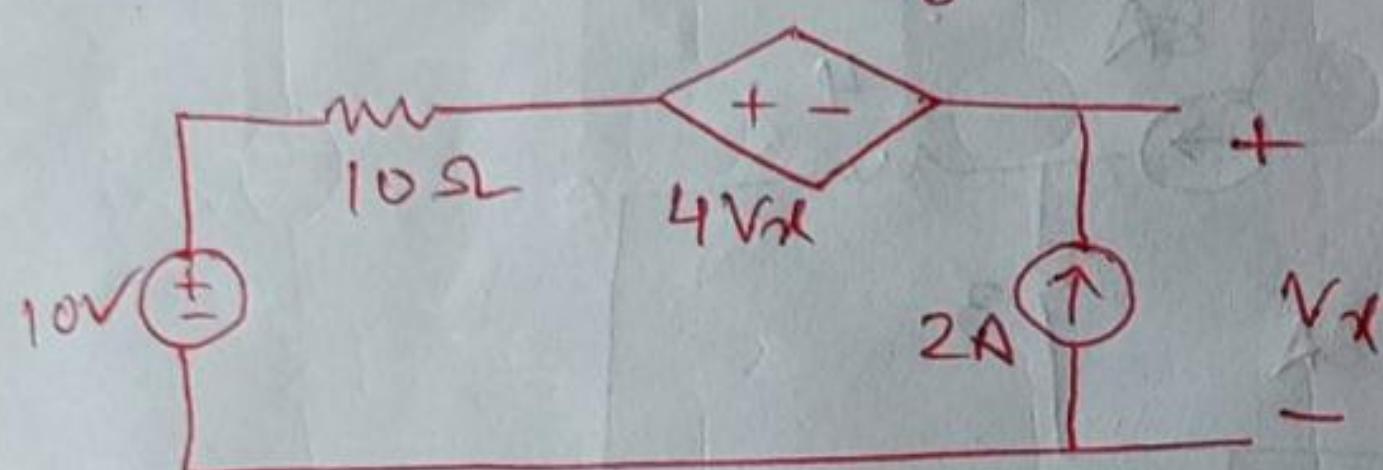

Step 1: 10V only

$$V_{x1} = 10 - 4V_{x1}$$

$$\Rightarrow V_{x1} = 2V$$

Step 2: 2A only


$$-V_x - 4V_{x2} + 10(2) = 0$$

$$\Rightarrow 5V_{x2} = 20$$

$$\Rightarrow V_{x2} = 4V$$


$$\therefore V_x = V_{x1} + V_{x2} = 2 + 4 = 6V$$

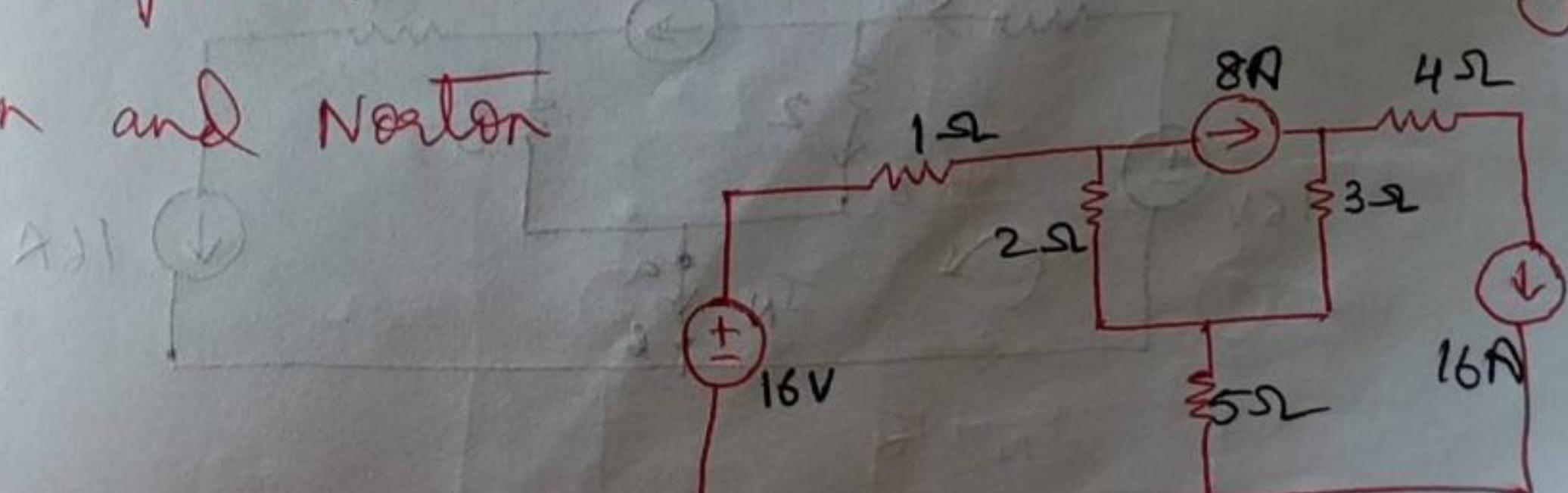4. Find power lost in 5Ω resistor using
Thevenin and Norton




Solⁿ

Thevenin

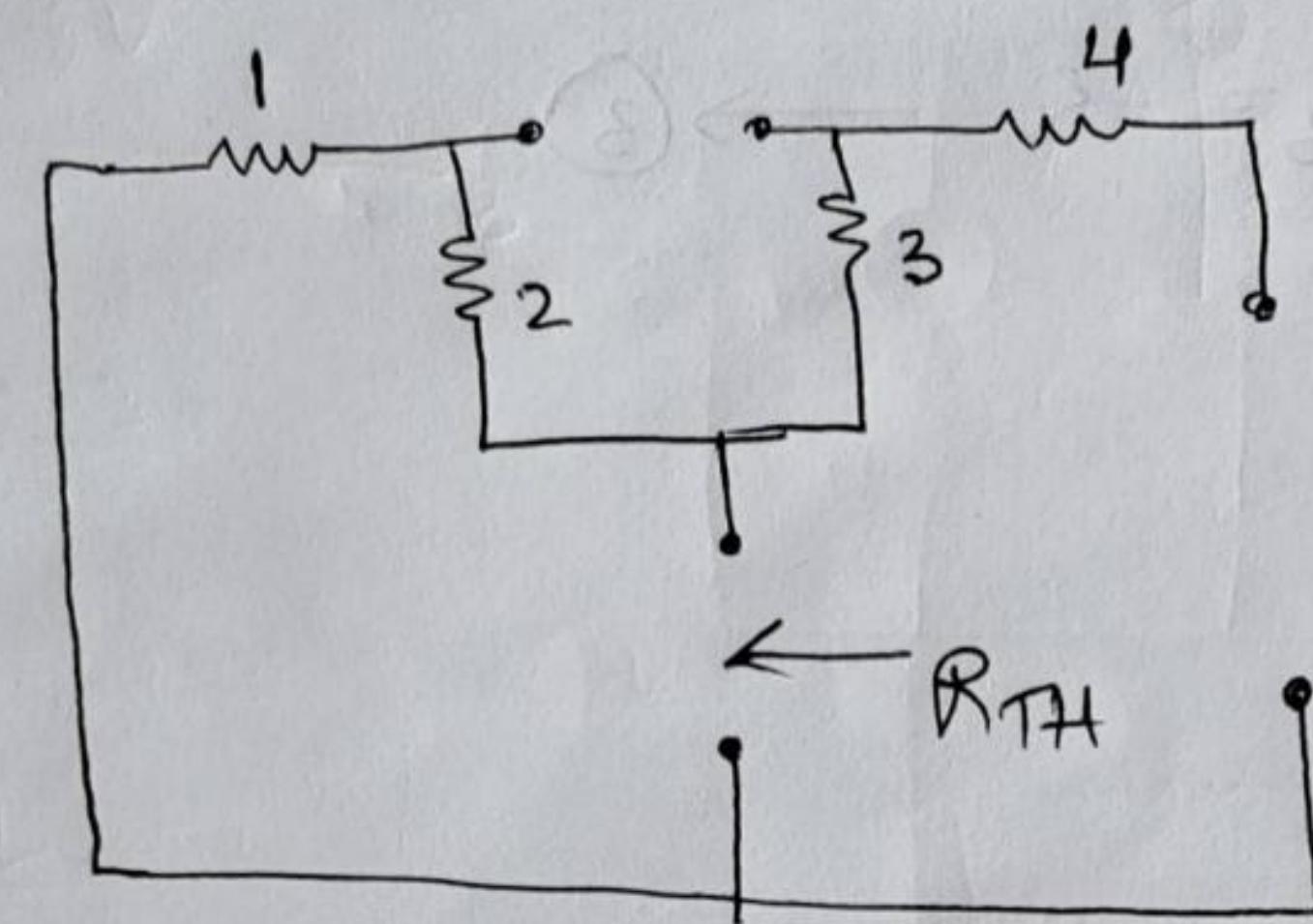


$$R_{TH} = 2 + 1 \\ = 3 \Omega_L$$

V_{TH}

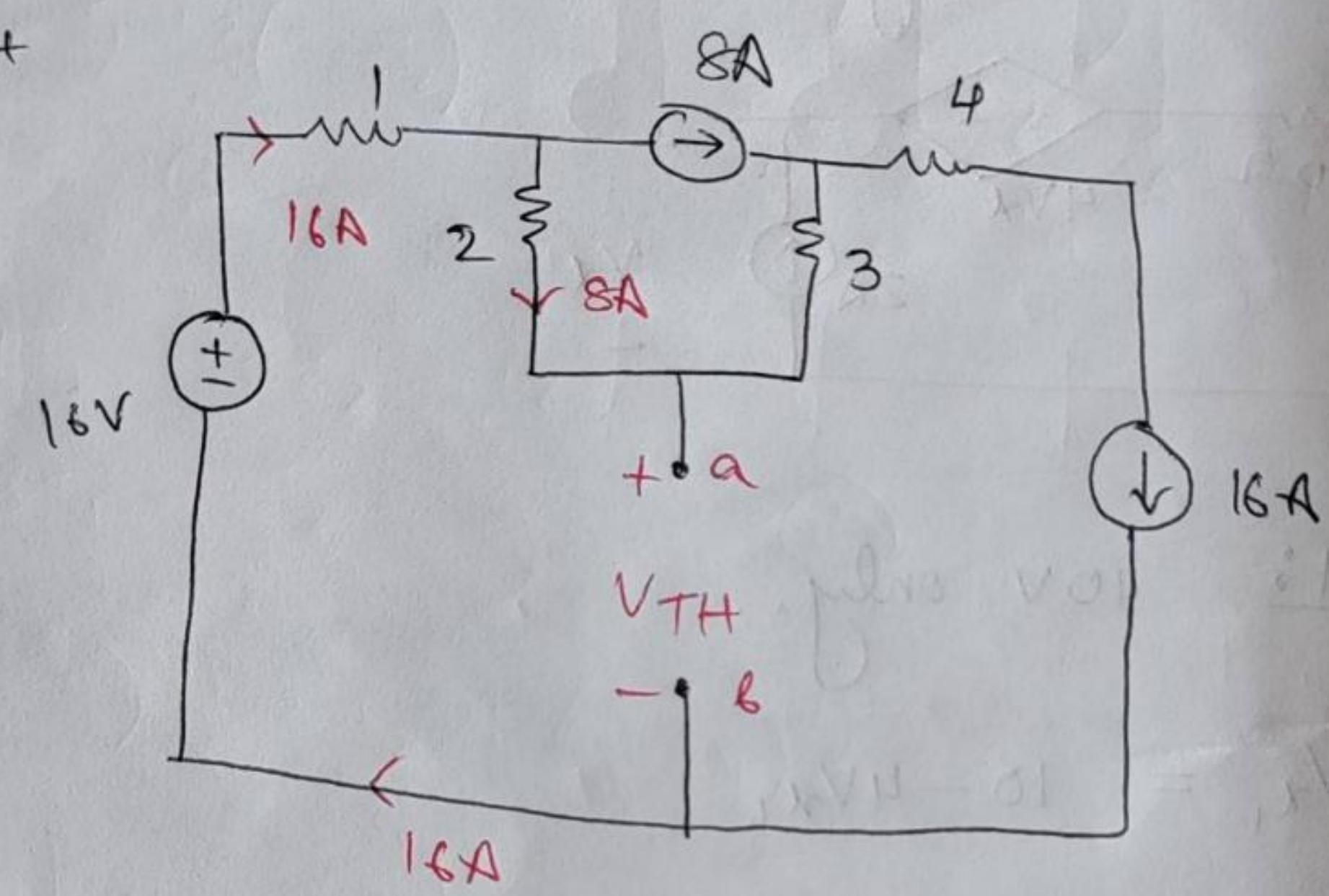

$$-16 + 16 + 16 + V_{TH} = 0$$


$$\Rightarrow V_{TH} = -16V$$

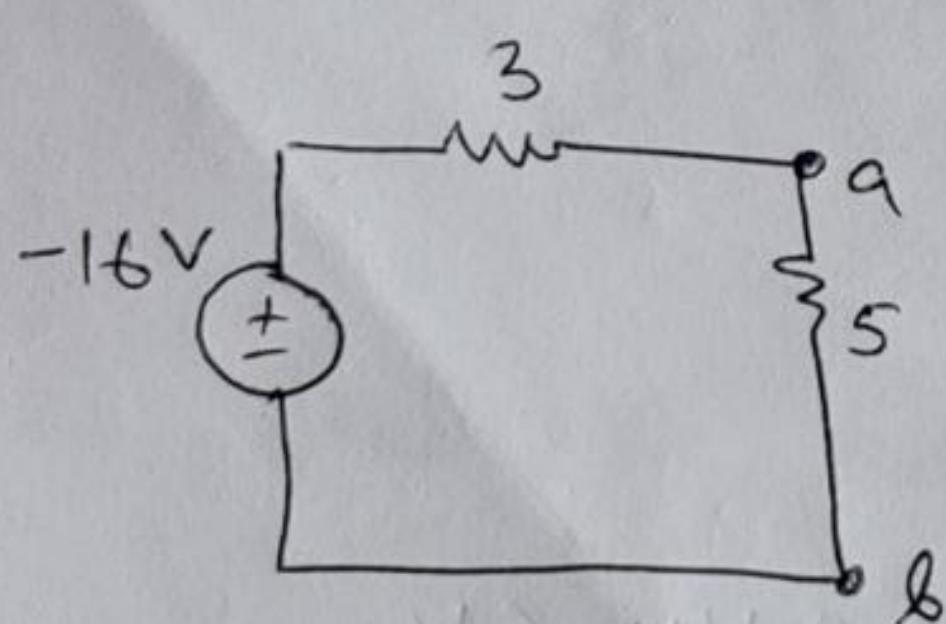

$$I = -\frac{16}{8} = -2A$$

$$P_{lost} = (-2)^2 \times 5 = 20W$$

Norton

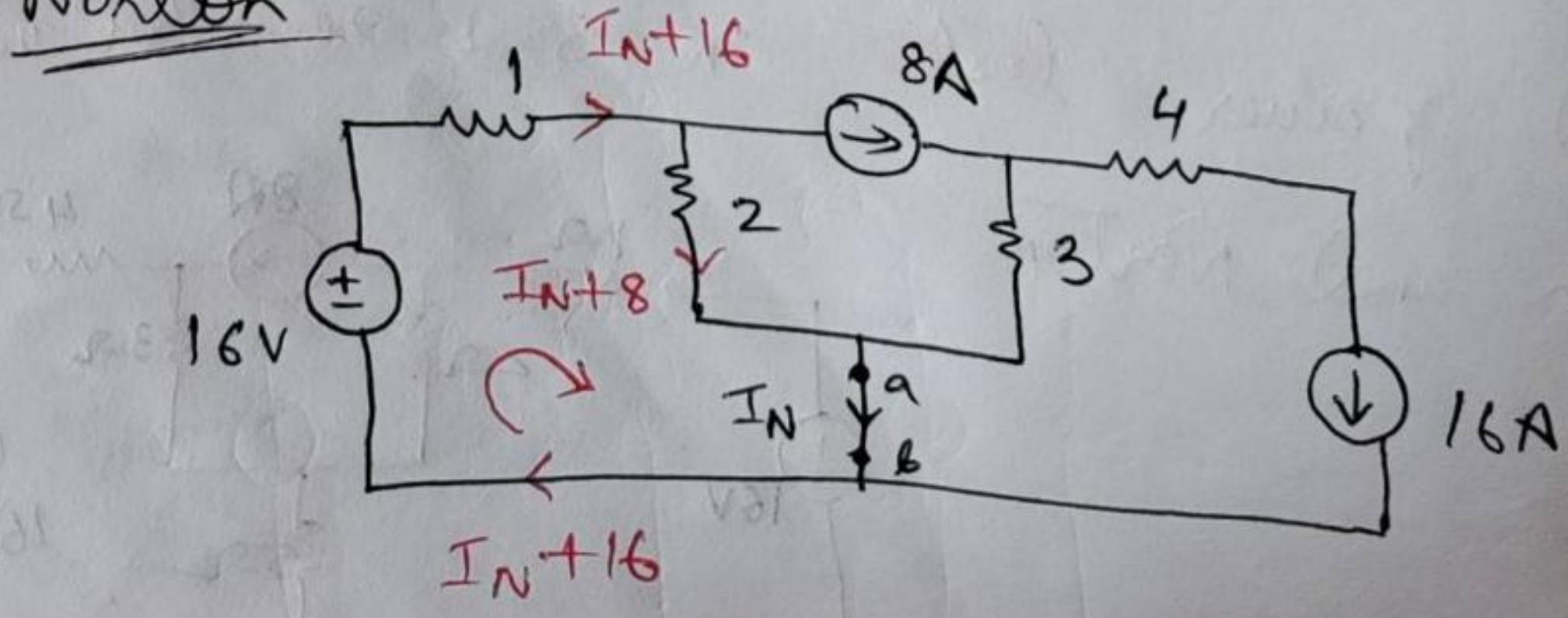


KVL

$$-16 + (I_N + 16) + 2(I_N + 8) = 0$$

$$\Rightarrow 3I_N = -16$$
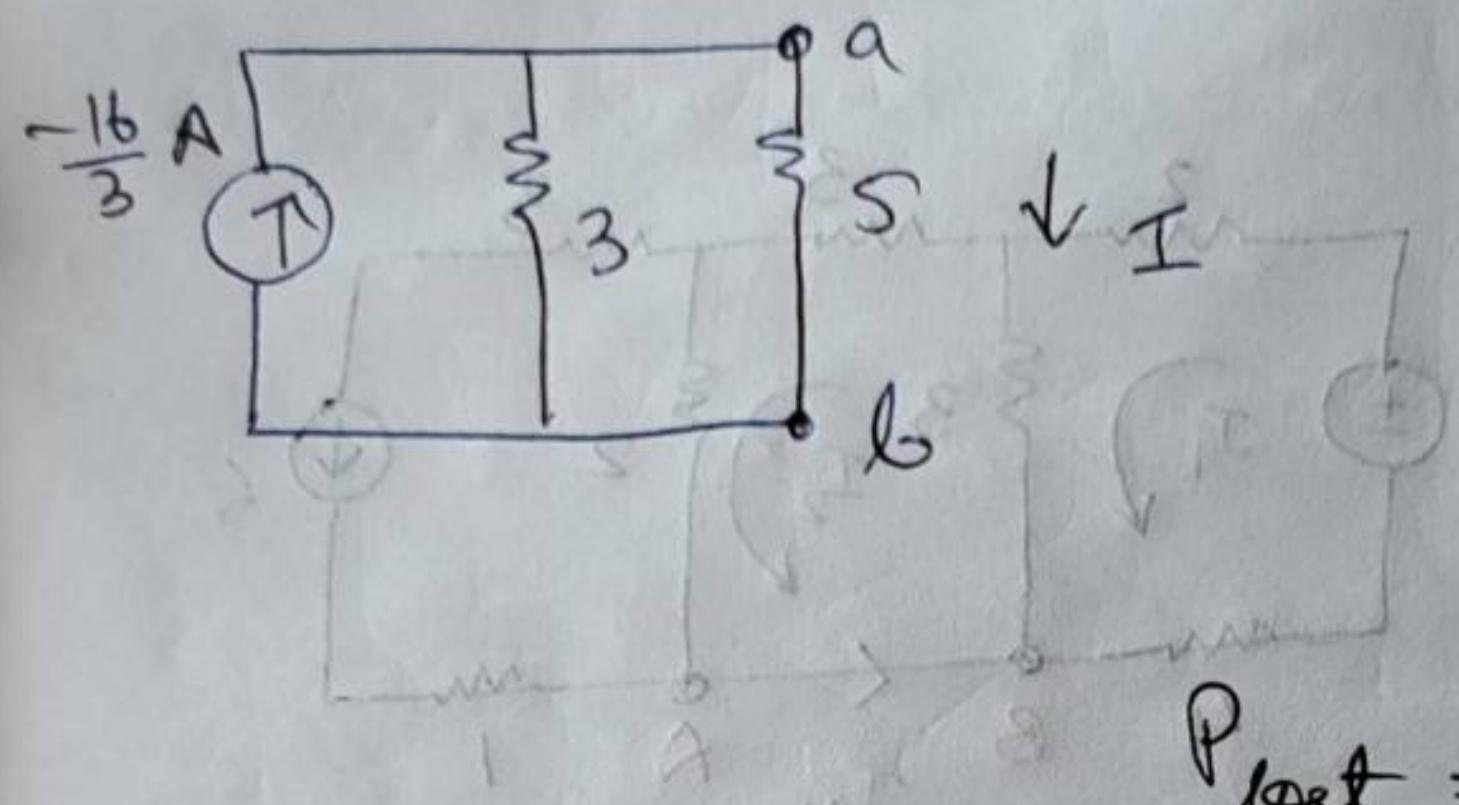
$$\Rightarrow I_N = \frac{-16}{3} \text{ A}$$




$$I = -\frac{16}{3} \left(\frac{3}{3+5} \right)$$

$$= -2 \text{ A}$$


$$P_{lost} = (-2)^2 \times 5 = 20 \text{ W}$$

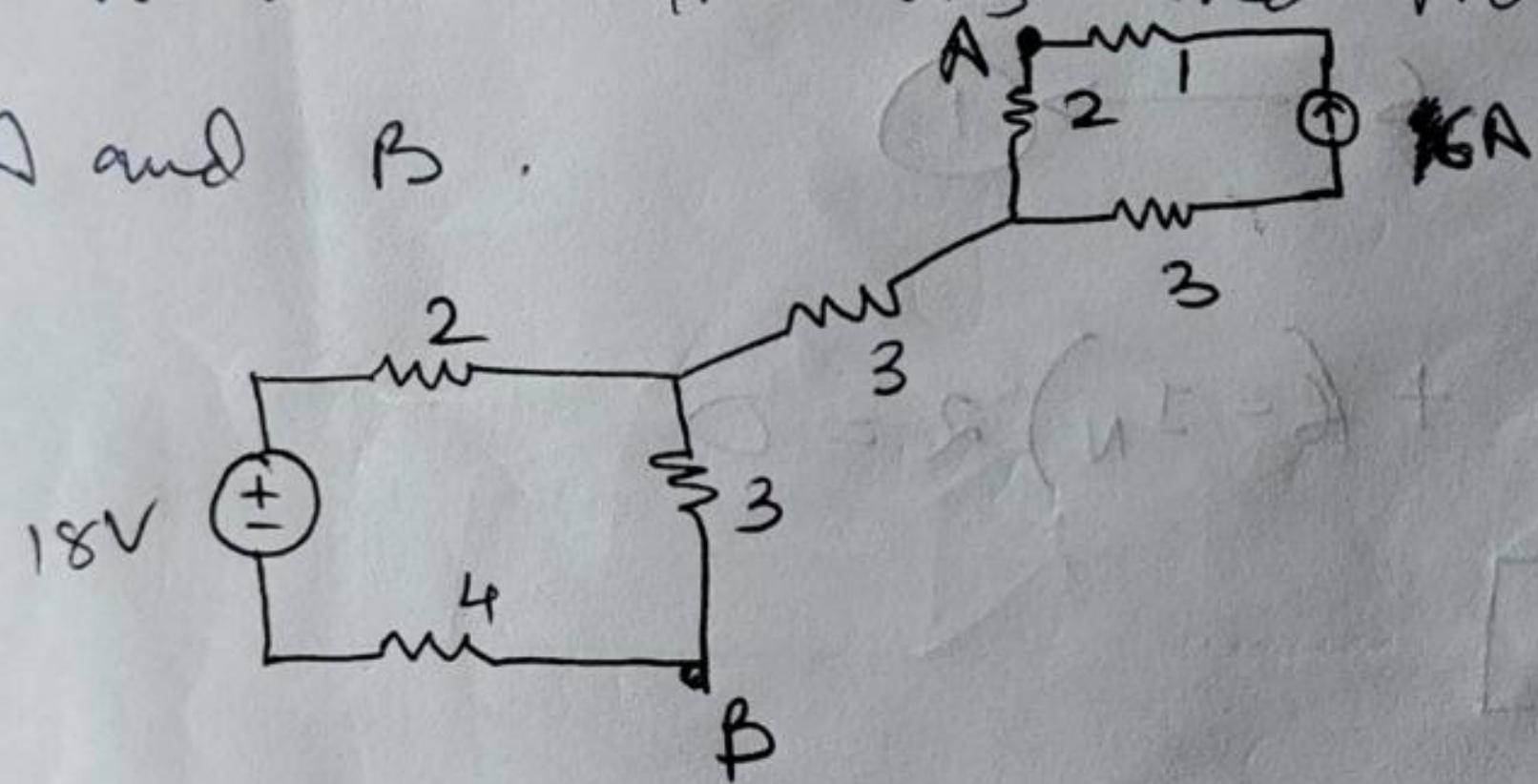5. Determine Thevenin and Norton equivalent b/w A and B.





Soln

R_{TH}


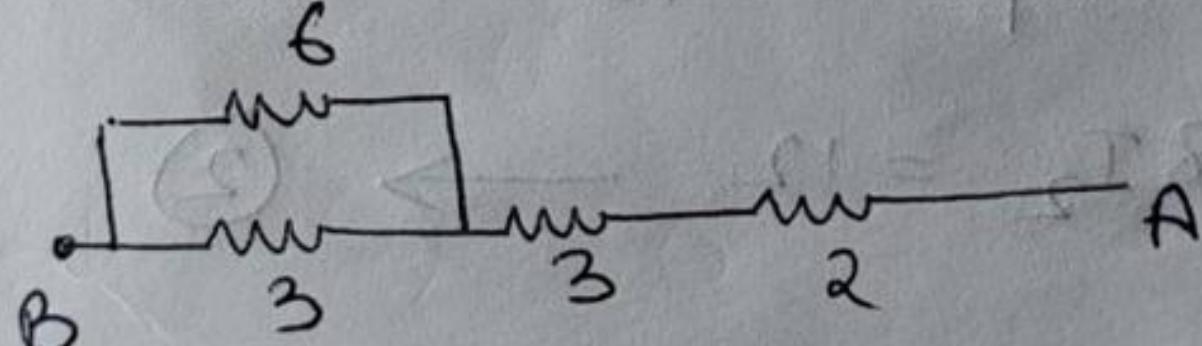


$$R_{TH} = 2 + 3 + \beta(1/6) = 2 + 3 + 2 = 7 \Omega$$

V_{TH}

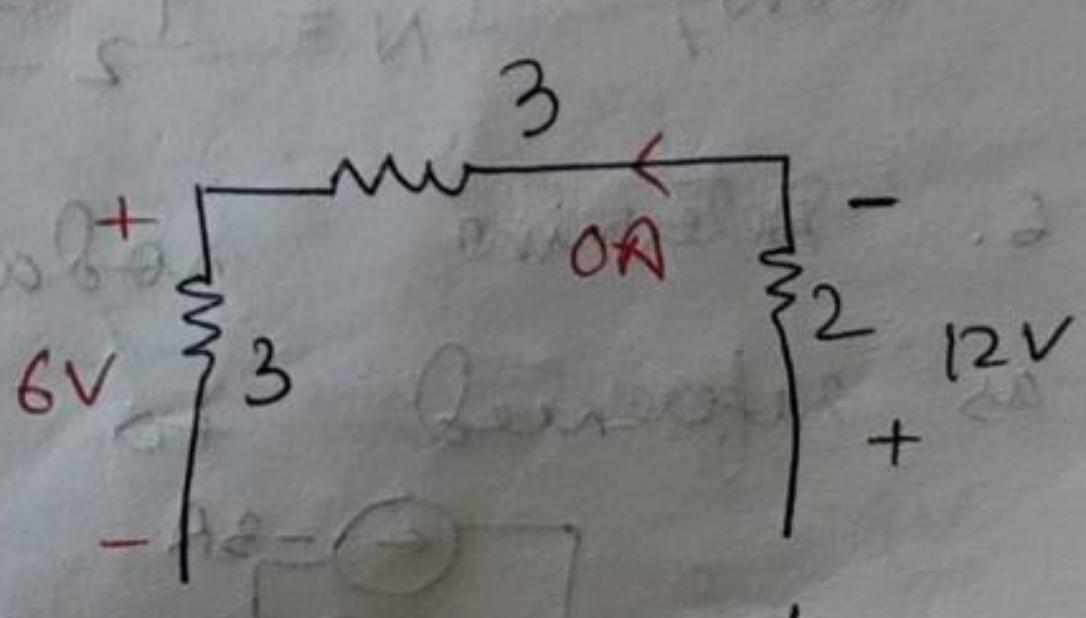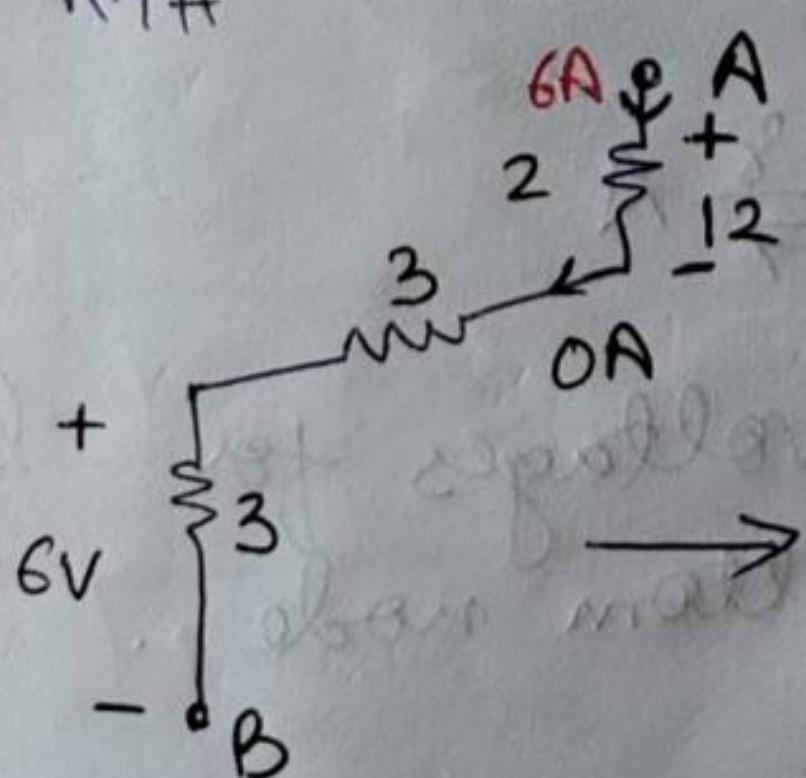

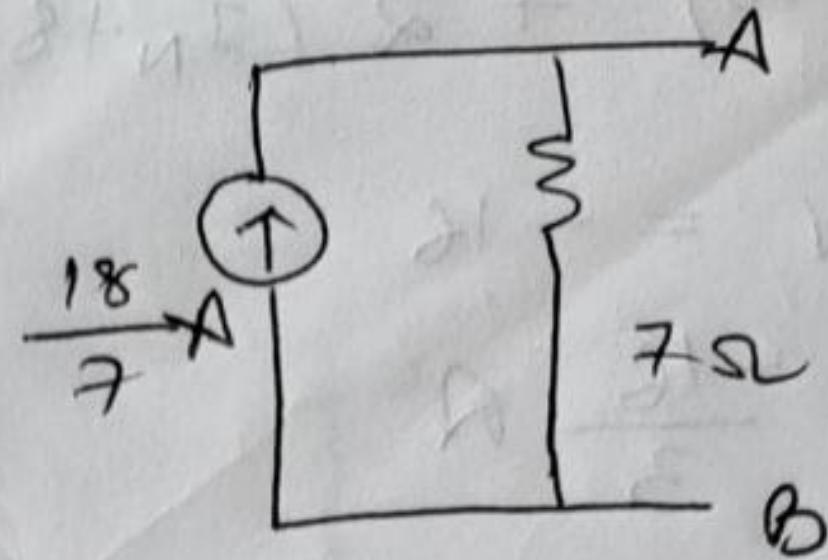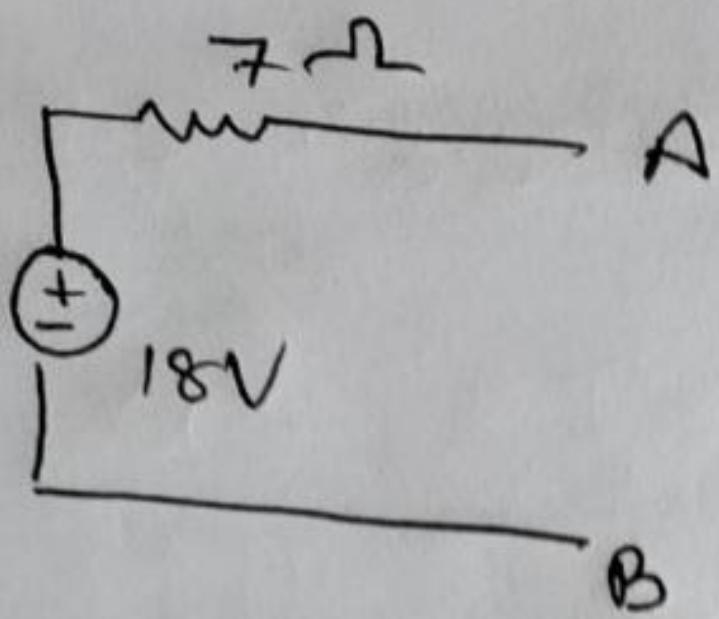
$$V_{TH} - 6 - 12 = 0 \Rightarrow V_{TH} = 18 \text{ V}$$



Nortons

$$R_N = R_{TH} = 7\Omega$$
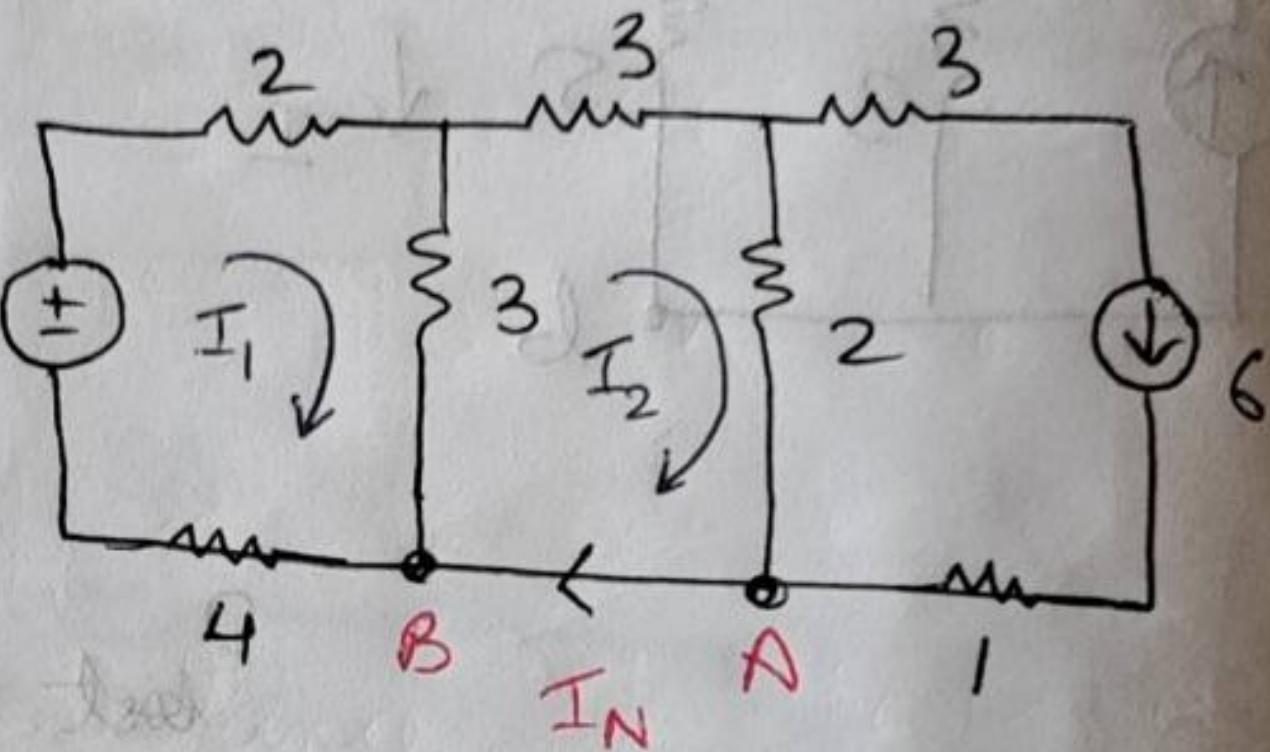
$$\begin{aligned} \text{KVL: } & -18 + 2I_1 + 3(I_1 - I_2) \\ & + 4I_1 = 0 \end{aligned}$$



$$\Rightarrow 9I_1 - 3I_2 = 18$$

$$\Rightarrow 3I_1 - I_2 = 6 \quad \text{--- (1)}$$

$$3(I_2 - I_1) + 3I_2 + (6 - I_N)2 = 0$$

Here

$$\boxed{I_N = I_2}$$


$$\Rightarrow 8I_2 - 3I_1 = -12$$


$$\Rightarrow 3I_1 - 8I_2 = 12 \quad \text{--- (2)}$$

$$\therefore I_2 = \frac{18}{7} \text{ A}$$

$$\text{Now, } I_N = I_2 = \frac{18}{7} \text{ A}$$

6. Determine nodal voltages for the circuit, as referenced to bottom node.

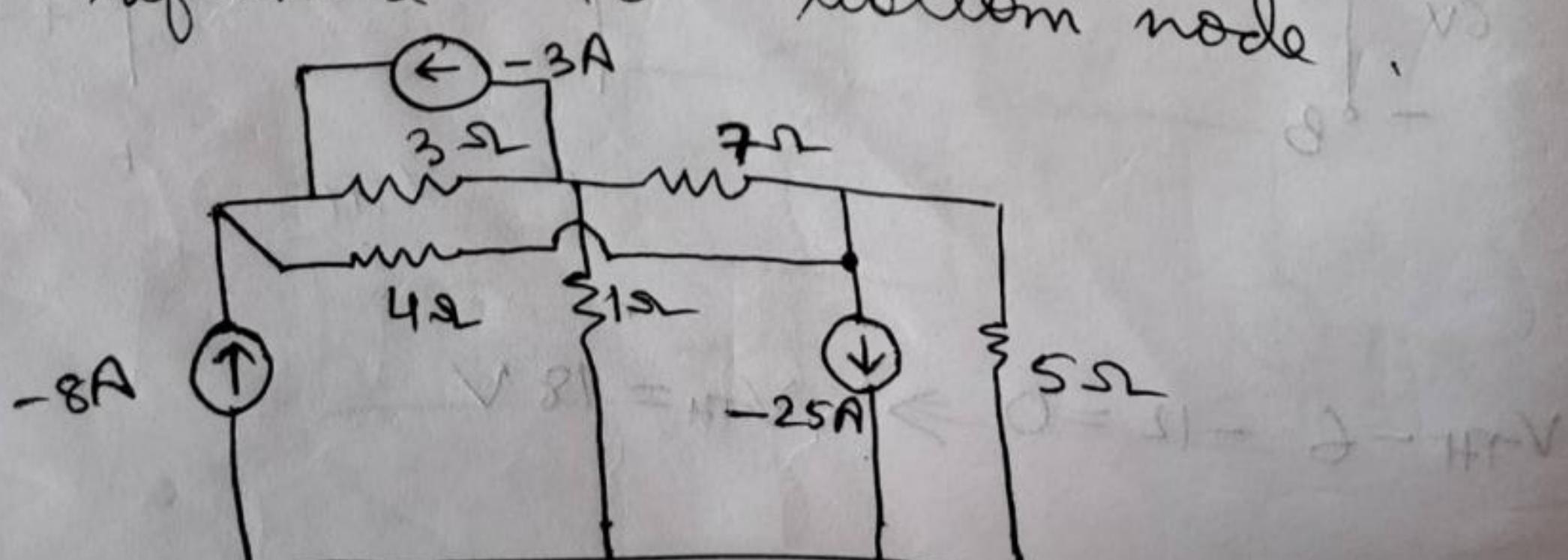

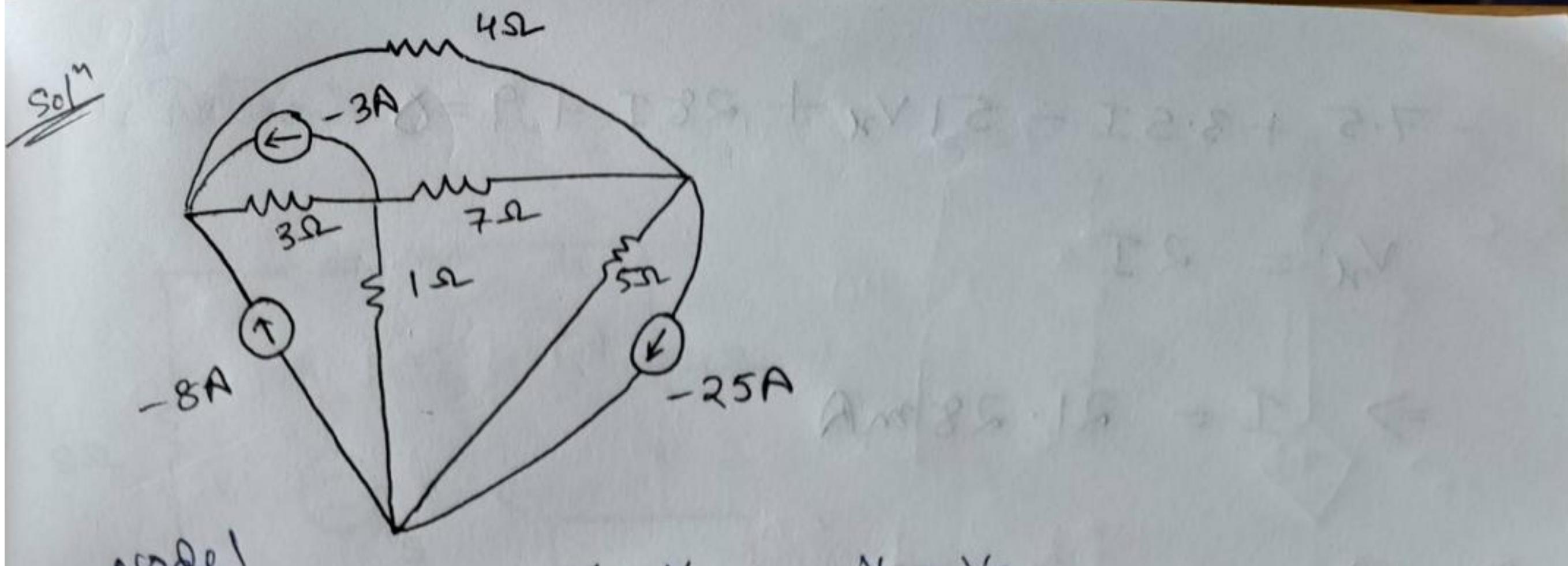

Node 1

$$(-8) - (-3) + \frac{v_1 - v_2}{3} + \frac{v_1 - v_3}{4} = 0 \rightarrow ①$$

Node 2


$$(-3) + \frac{v_2 - v_1}{3} + \frac{v_2}{1} + \frac{v_2 - v_3}{7} = 0 \rightarrow ②$$

Node 3




$$(-25) + \frac{v_3}{5} + \frac{v_3 - v_2}{7} + \frac{v_3 - v_1}{4} = 0 \rightarrow ③$$

$$v_1 = 5.412, \quad v_2 = 7.736, \quad v_3 = 46.32 \text{ V}$$

7. find I.

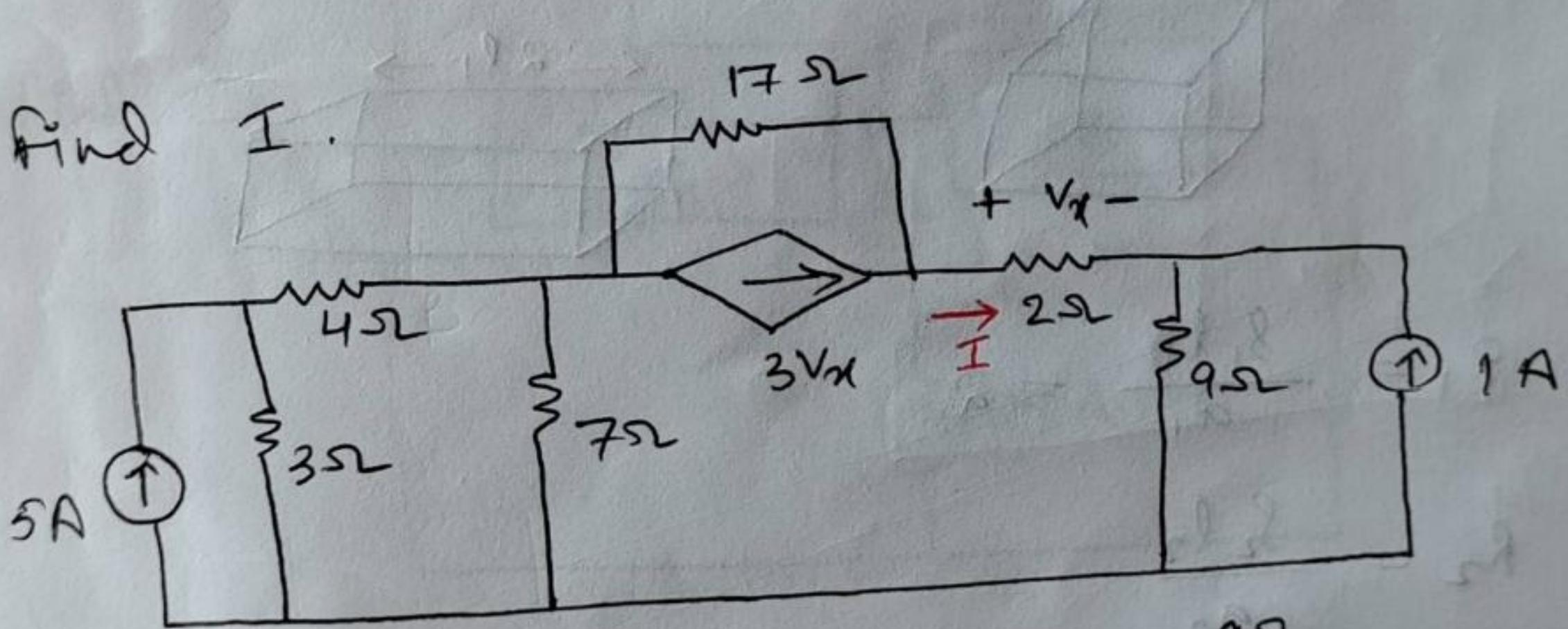

Sol^M
using STT

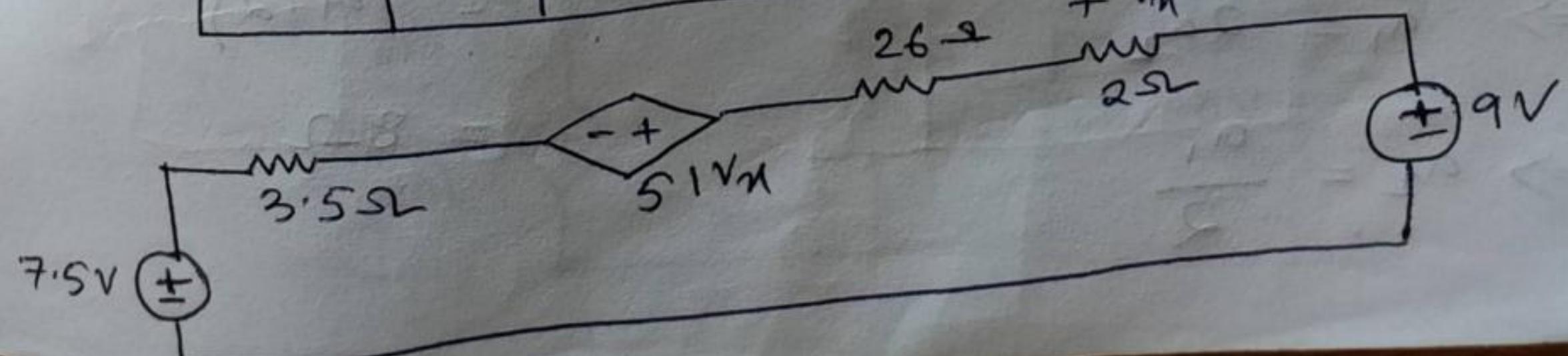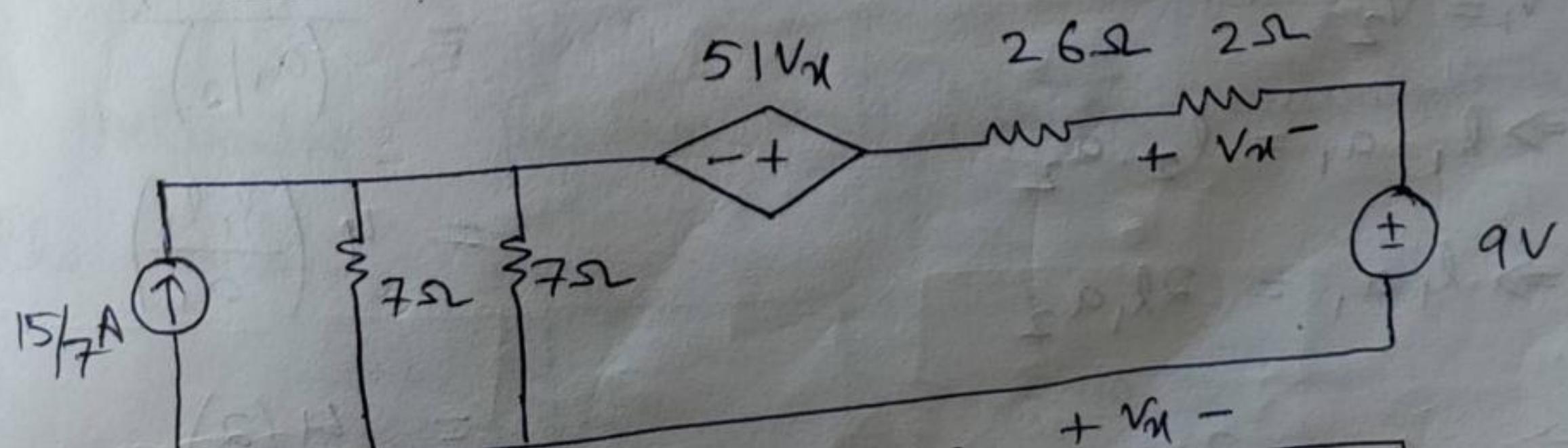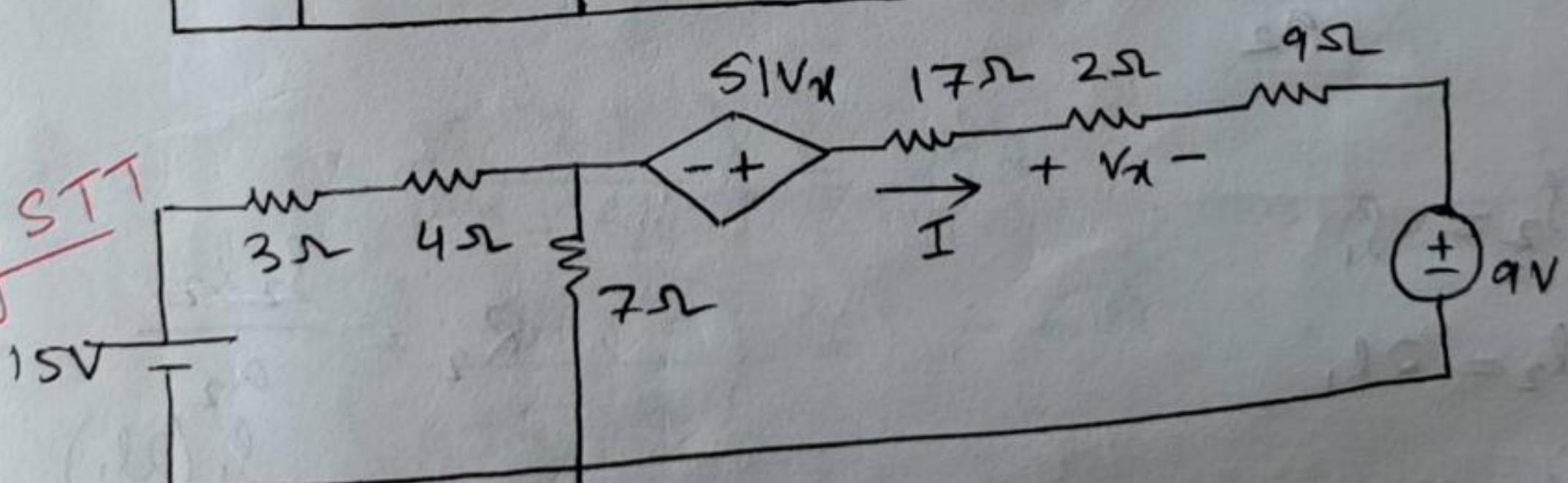



$$-7.5 + 3.5I - 51V_R + 28I + 9 = 0$$

$$V_R = 2I$$

$$\Rightarrow I = 21.28 \text{ mA}$$

8. A cube shaped material has a resistance of 2Ω b/w any of its opposite faces. Now if this material is stretched in one direction by applying linear force to double its original length, then the resistance b/w the opposite stretched face is _____

Soln

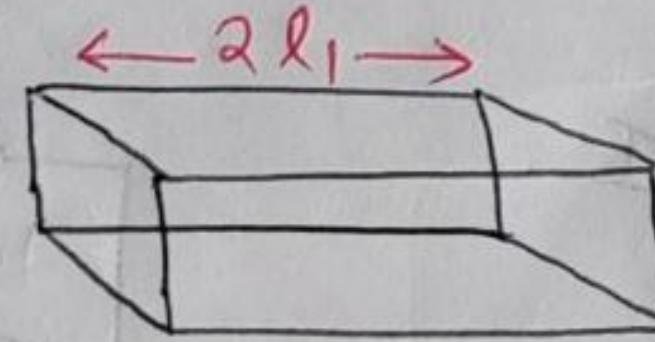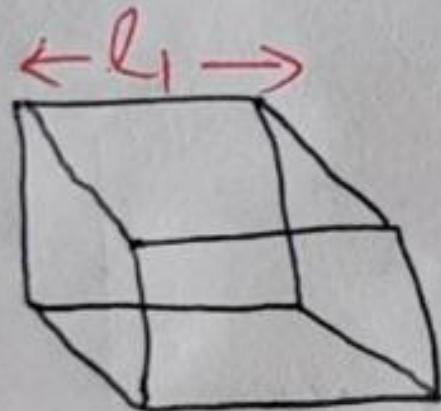

$$R_1 = \frac{\beta_1 l_1}{a_1} = 2$$

$$R_2 = \frac{\beta_2 l_2}{a_2}$$

$$\beta_2 = \beta_1$$

$$l_2 = 2l_1$$

$$V_1 = V_2$$

$$\Rightarrow l_1 \cdot a_1 = l_2 \cdot a_2$$

$$\Rightarrow l_1 a_1 = 2l_1 a_2$$

$$\Rightarrow a_1 = 2a_2$$

$$\Rightarrow a_2 = \frac{a_1}{2}$$


$$R_2 = \frac{\beta_2 l_2}{a_2} = \frac{\beta_1 (2l_1)}{(a_1/2)}$$

$$= 4 \left(\frac{\beta_1 l_1}{a_1} \right)$$

$$= 4(2)$$

$$= 8\Omega$$

9. Determine i .

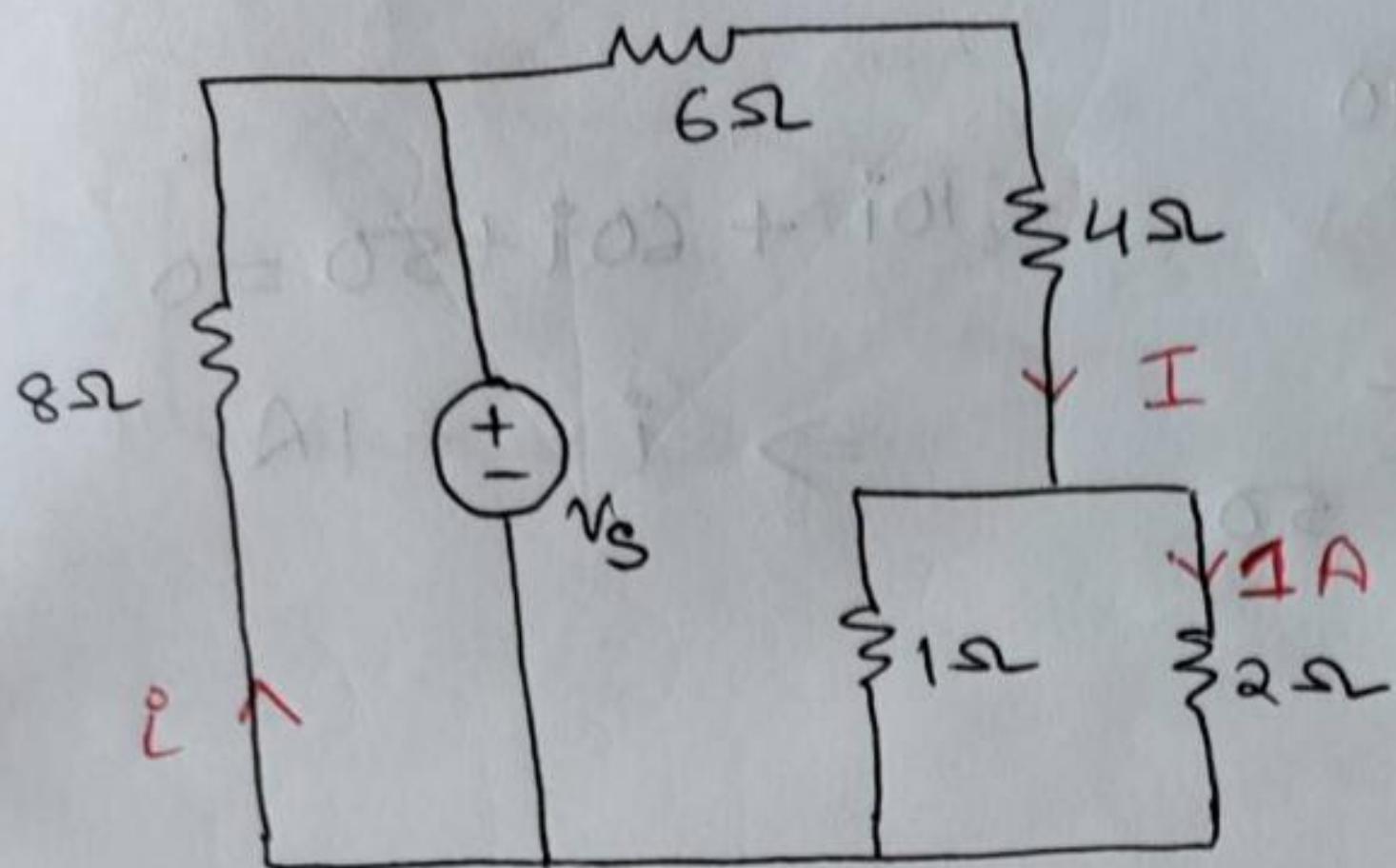


Solⁿ

$$I = i \times \frac{1}{3} \Rightarrow I = 3$$

$$v_s = 3 \left(10 + \frac{2}{3} \right) = 32V$$

$$i = -\frac{32}{8} = -4A$$


10. find I

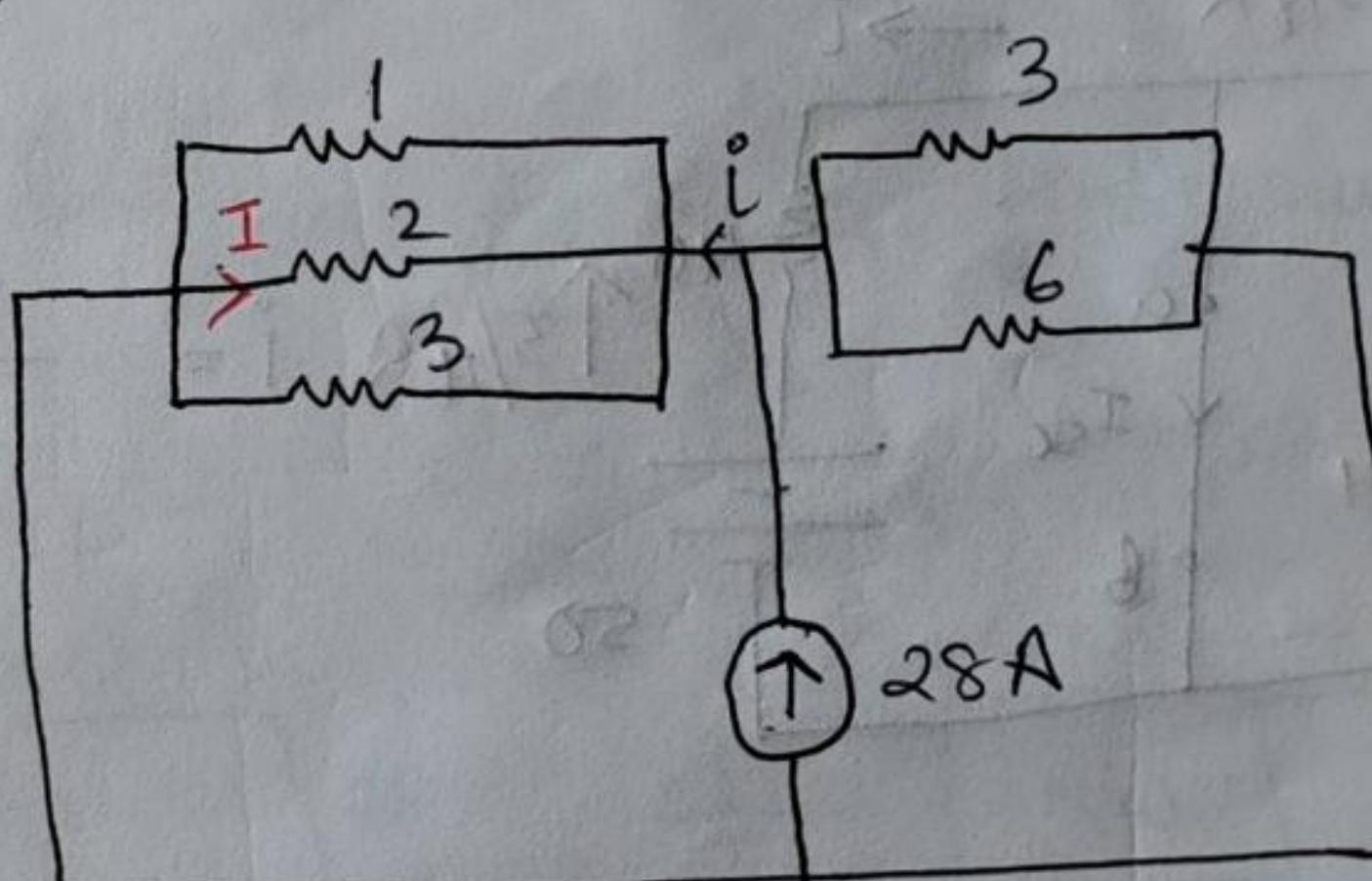


$$i = 28 \left(\frac{2}{2+6/11} \right) = 22A$$

$$I = 22 \left(\frac{3}{6+2+3} \right) = -6A$$

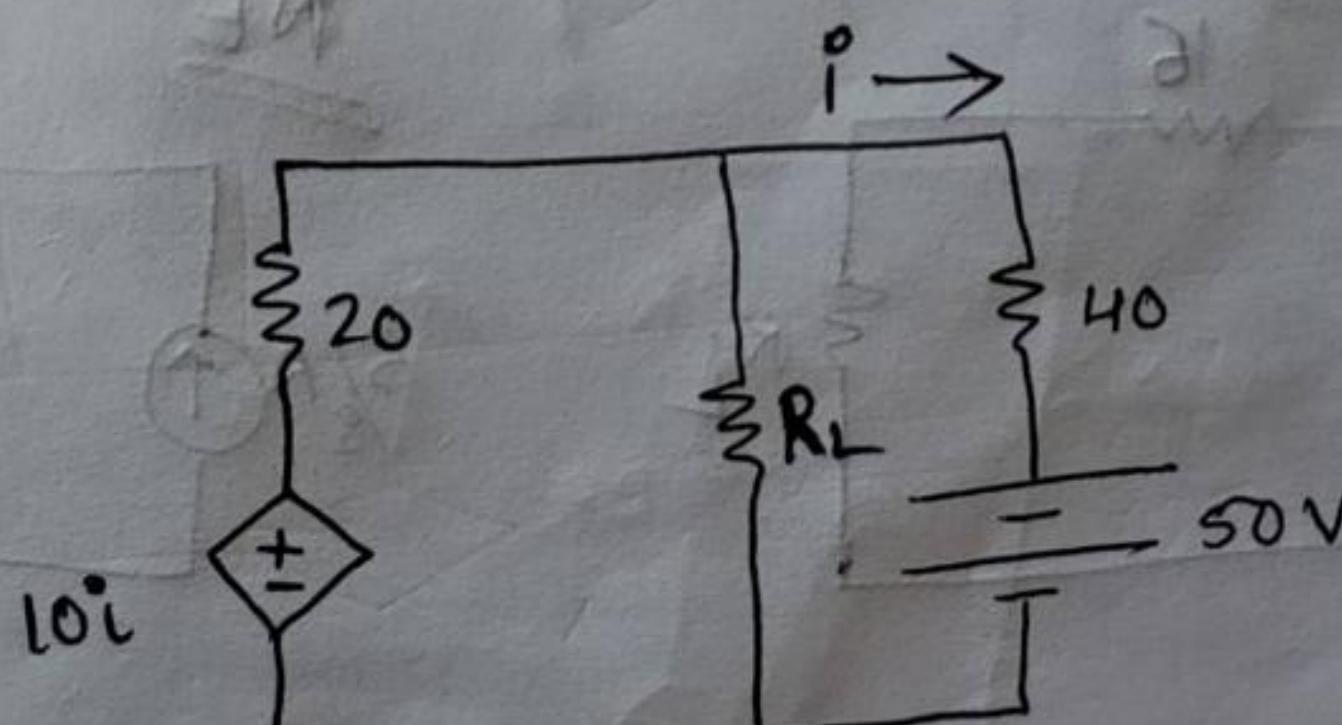11. Determine Thevenin and Norton equivalent across the load.



SOL⁴

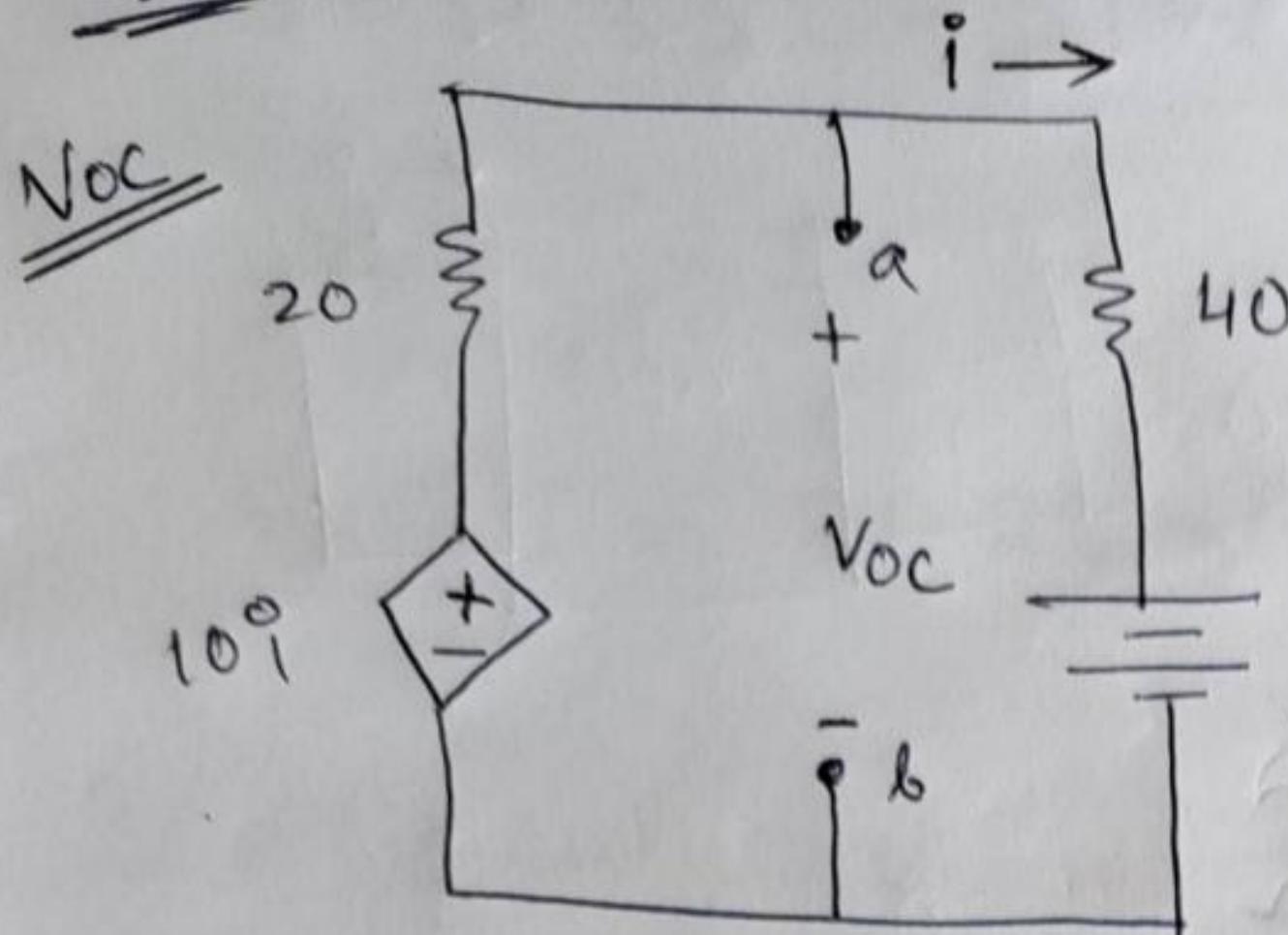

$$-10i + 60i + 50 = 0 \Rightarrow i = -1A$$


KVL

$$-V_{OC} + 40i + 50 = 0$$

$$\Rightarrow -V_{OC} - 40 + 50 = 0$$

$$\Rightarrow V_{OC} = 10V$$

I_{SC}

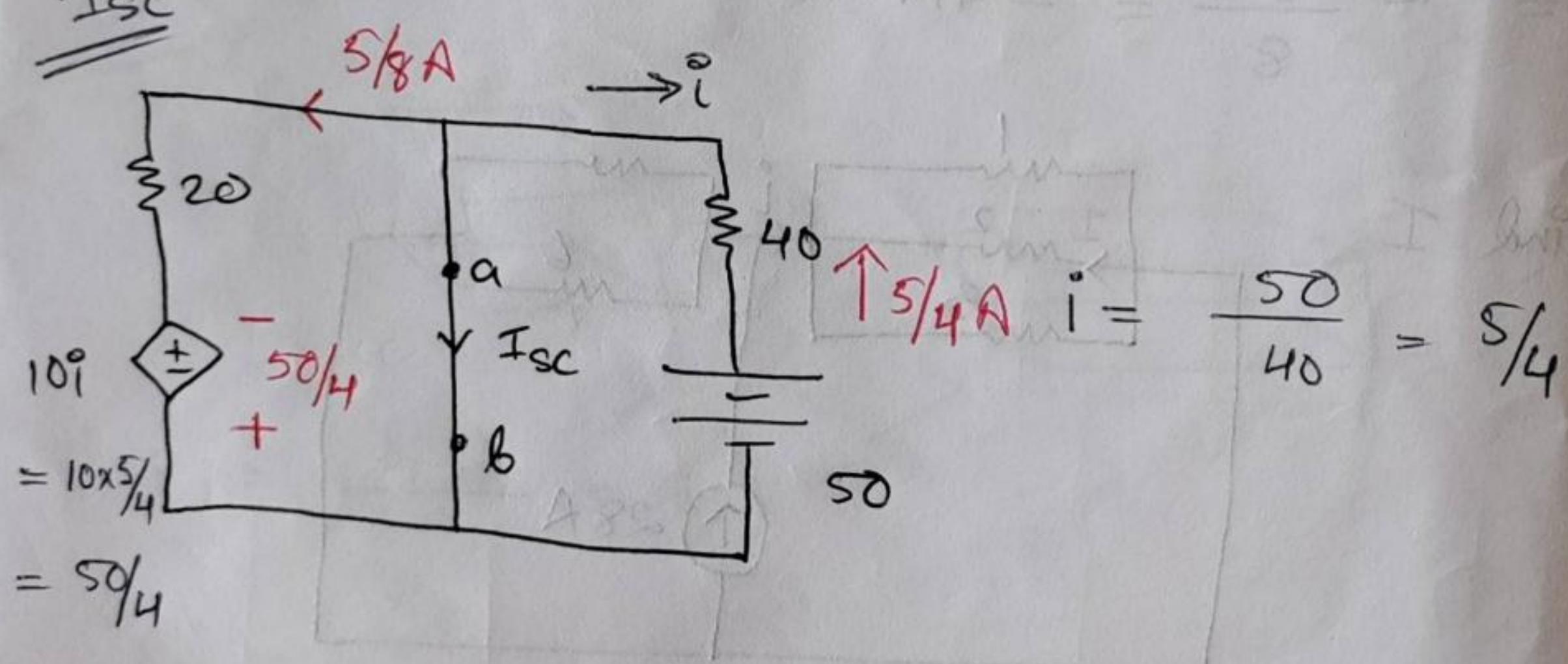


KCL

$$-\frac{5}{4} = \frac{5}{8} + I_{SC}$$


$$\Rightarrow I_{SC} = -\frac{5}{8} A$$


$$R_{TH} = R_N = \frac{V_{OC}}{I_{SC}} = \frac{10 \times 8}{5} = 16\Omega$$

TE

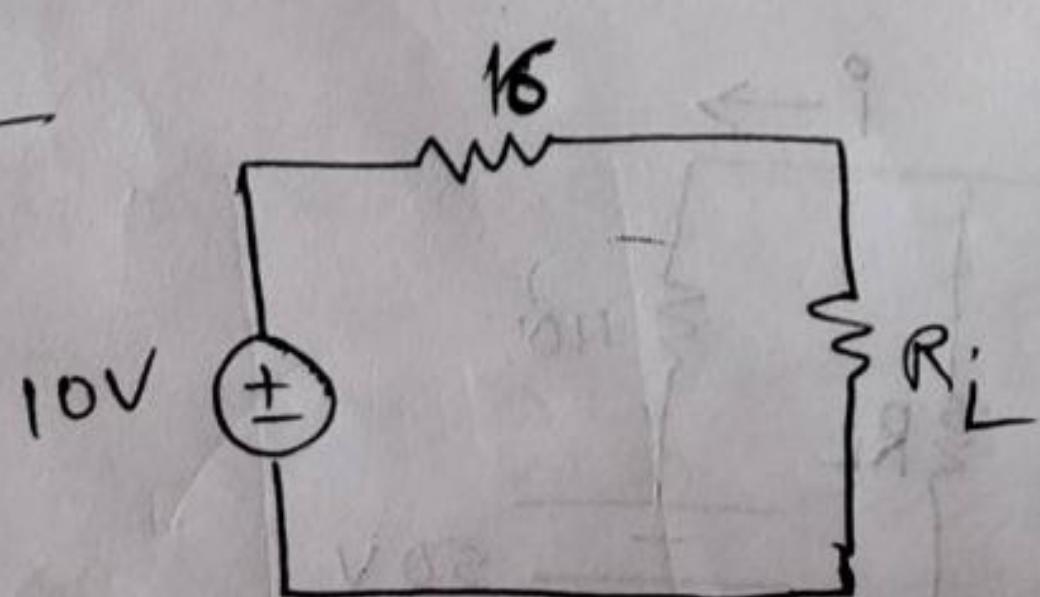


NE

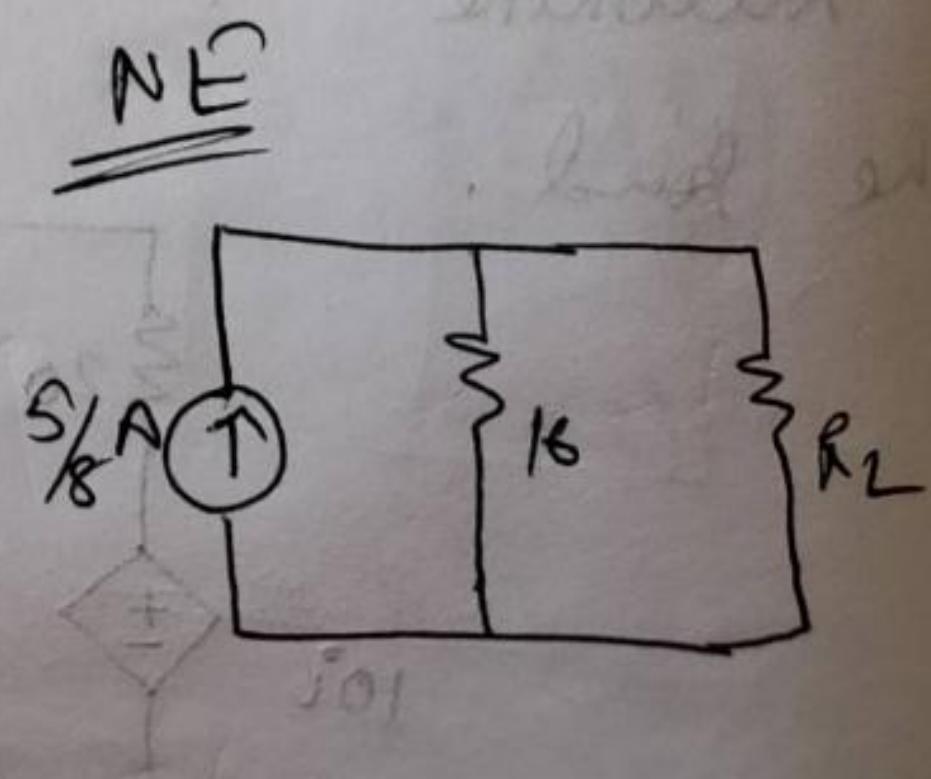

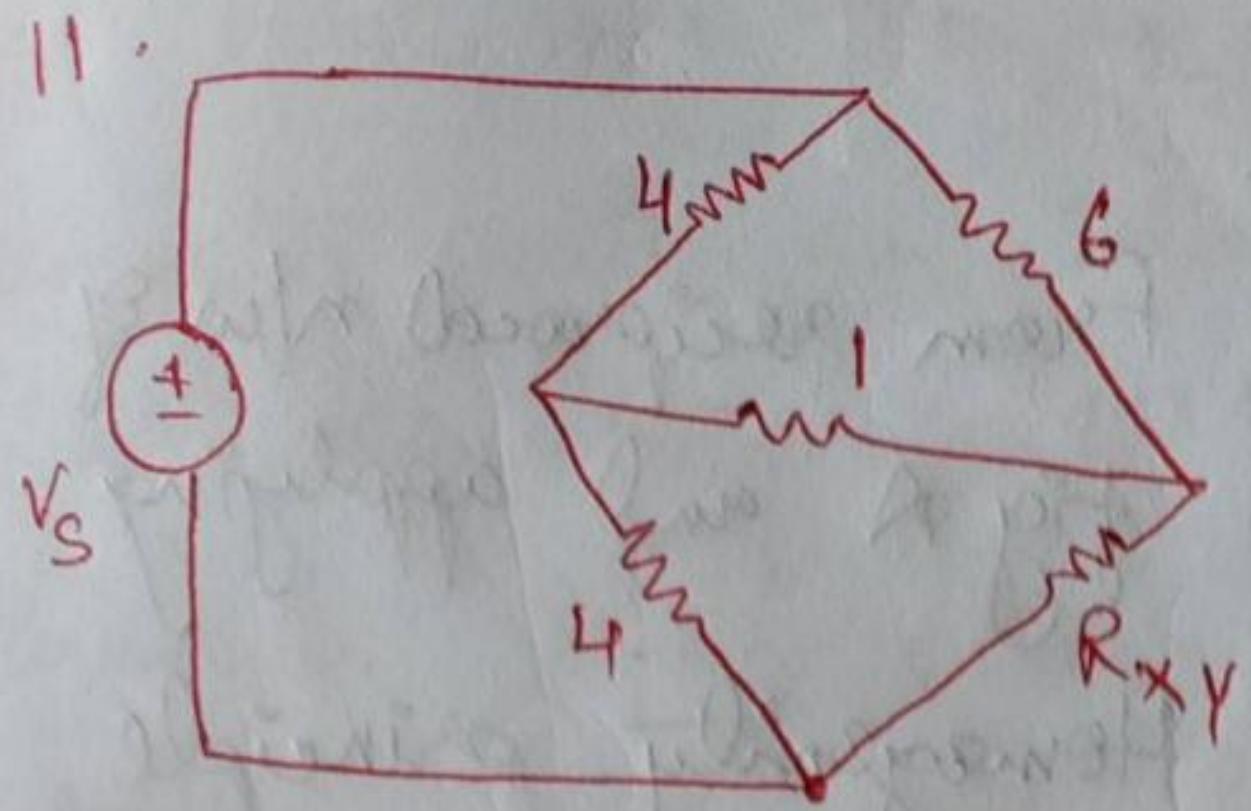

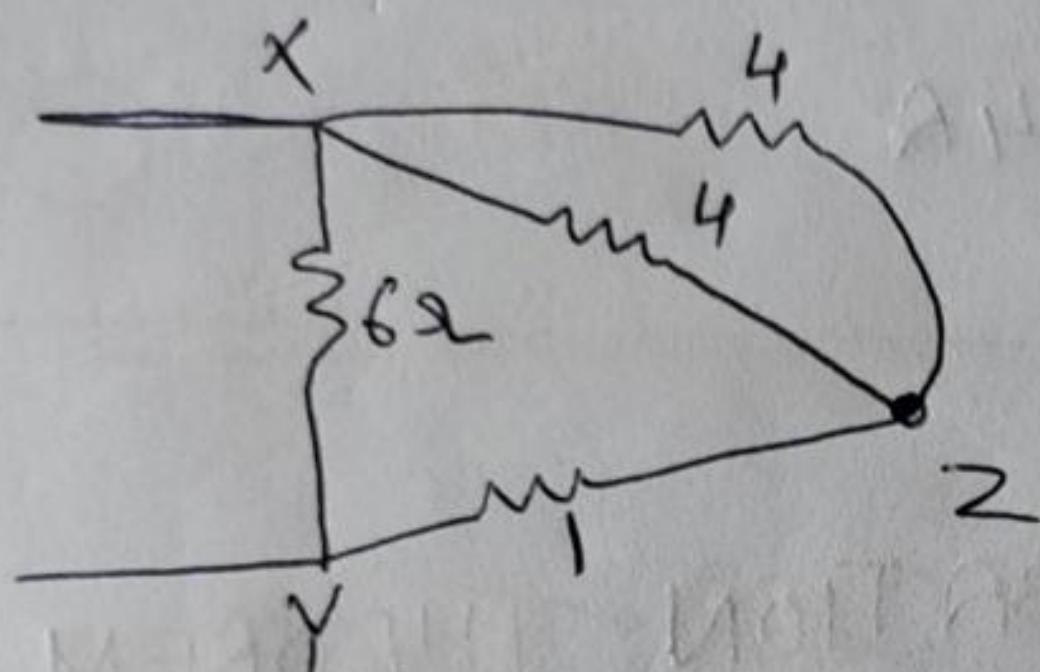what is the value of R_x for which P_{max} occurs.



$$4 \parallel 4 = 2$$

$$\therefore 2 + 1 = 3$$

$$R_{XY} = R_{TH} = 3 \parallel 6 = 2 \Omega$$

12. Use the data in fig A to find current i in fig. B.

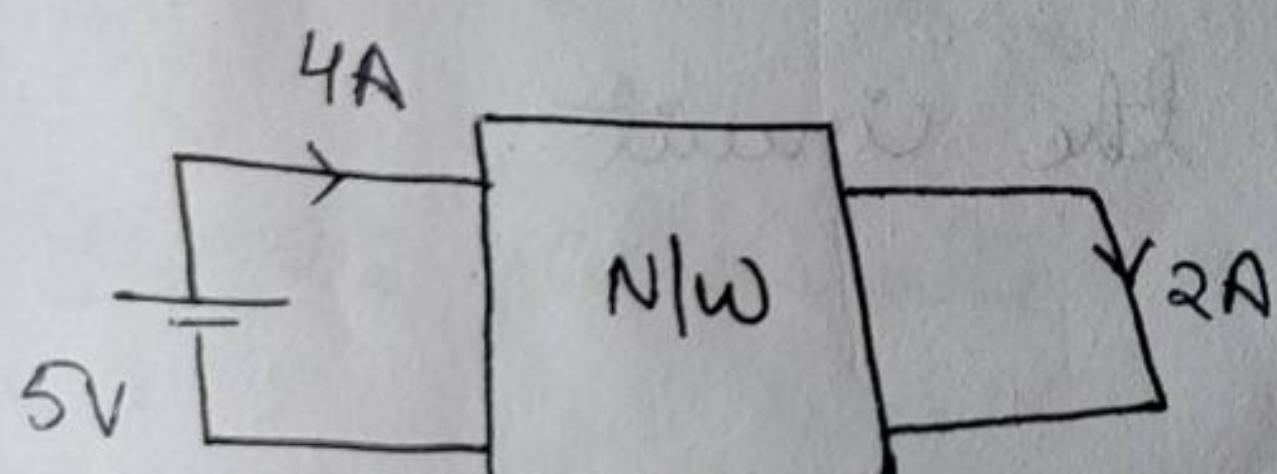


fig A


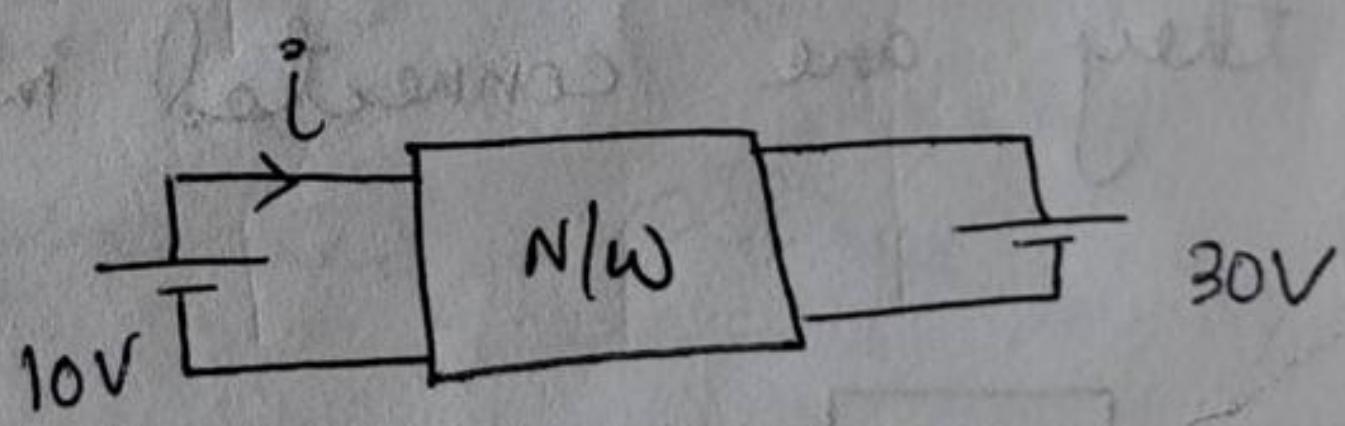


fig B

Solⁿ

Apply Superposition


Step 1

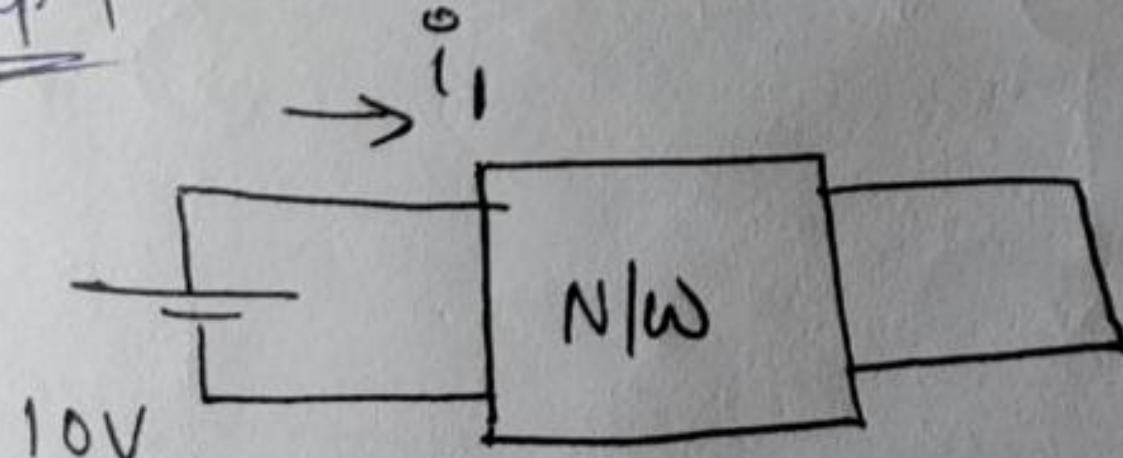

By homogeneity principle from fig A.

$$i_1 = 8A$$

Step 2 :

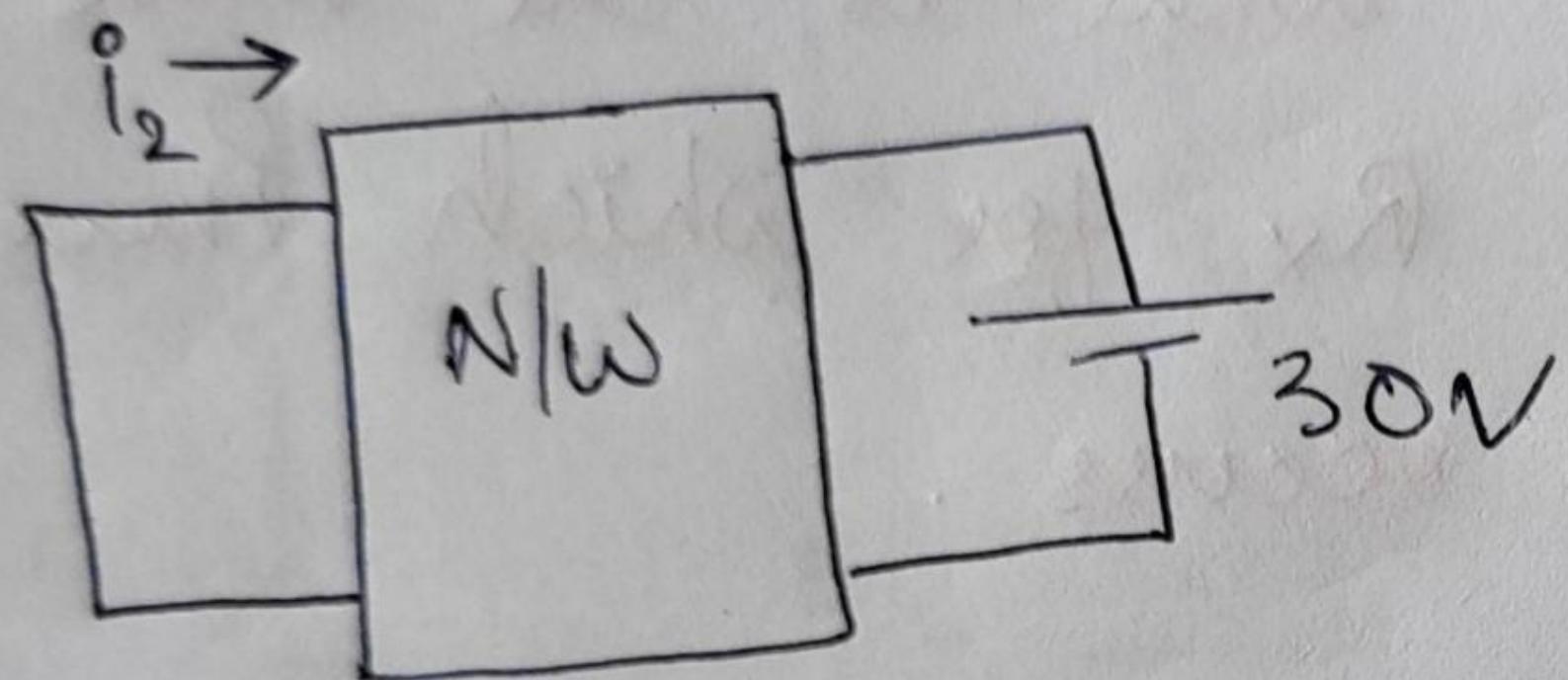


From reciprocal n/w of
fig A and applying
Homogeneity principle

$$\overset{\circ}{i}_2 = -12 \text{ A}$$


$$\overset{\circ}{i} = \overset{\circ}{i}_1 + \overset{\circ}{i}_2 = 8 - 12 = -4 \text{ A}$$

Practice set 5 Answers

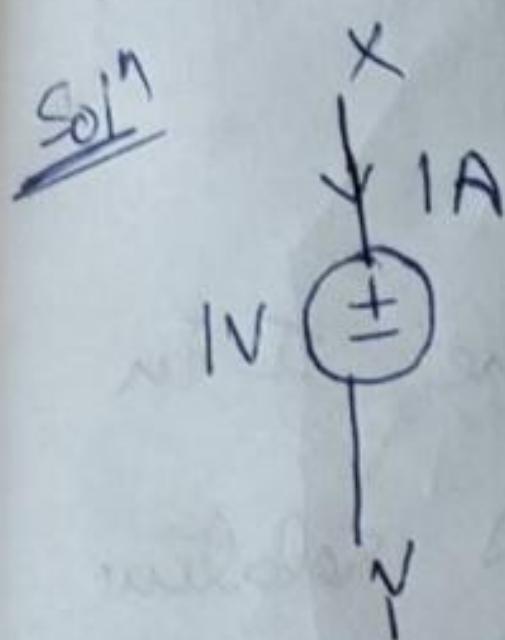
① Use substitution theorem to substitute 1Ω branch in 4 diff. ways.



$$\text{Poles} = 1W$$

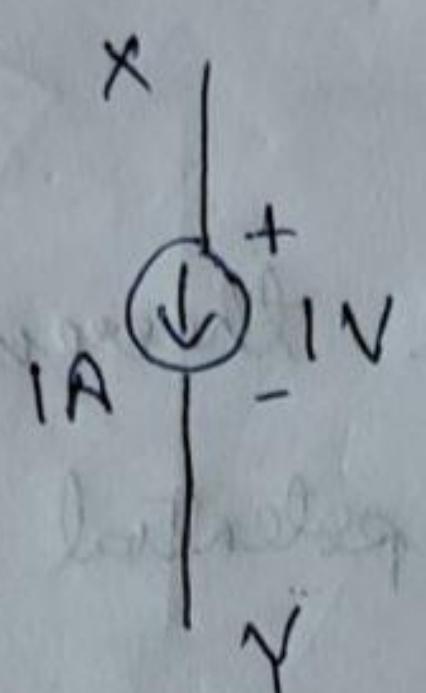


$$\text{Poles} = 1W$$

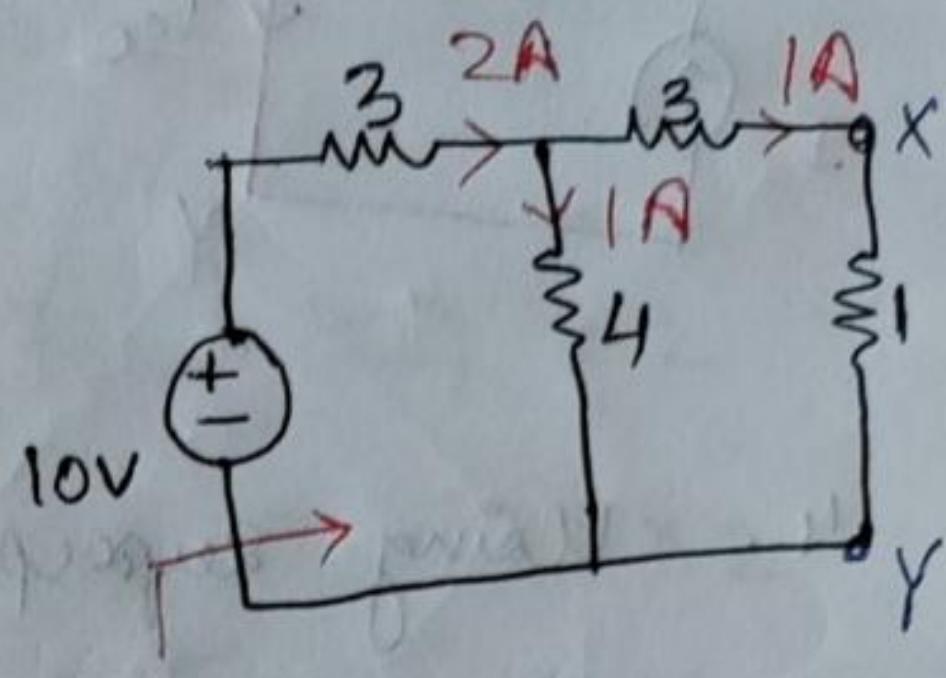

5Ω


5Ω

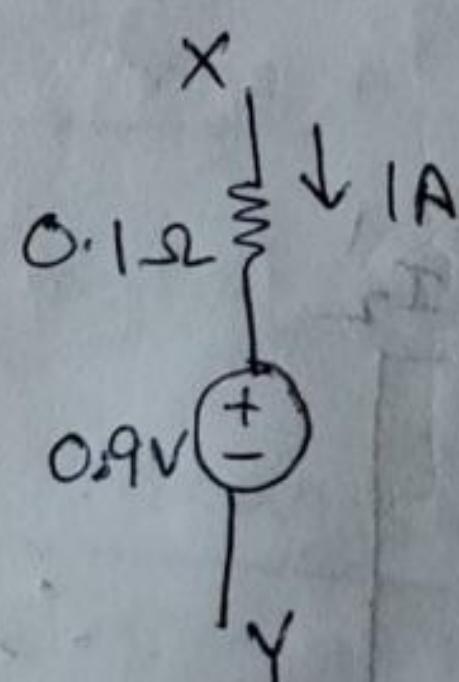


$$\begin{aligned}\text{Poles} &= I^2 \times (0.1) + 0.9 \\ &= 1W\end{aligned}$$

$$\begin{aligned}\text{Poles} &= (1)^2 \times \frac{1}{2} + \frac{1}{2} \times 1 \\ &= 1W\end{aligned}$$

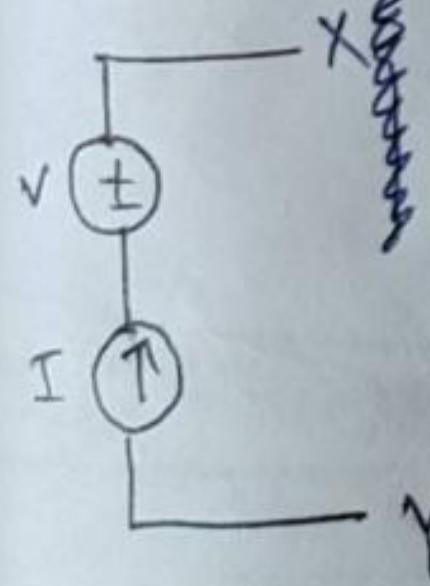
2. Which theorem is applicable (a) Thvenin
 (b) Norton
 (c) Both (d) None




Thvenin

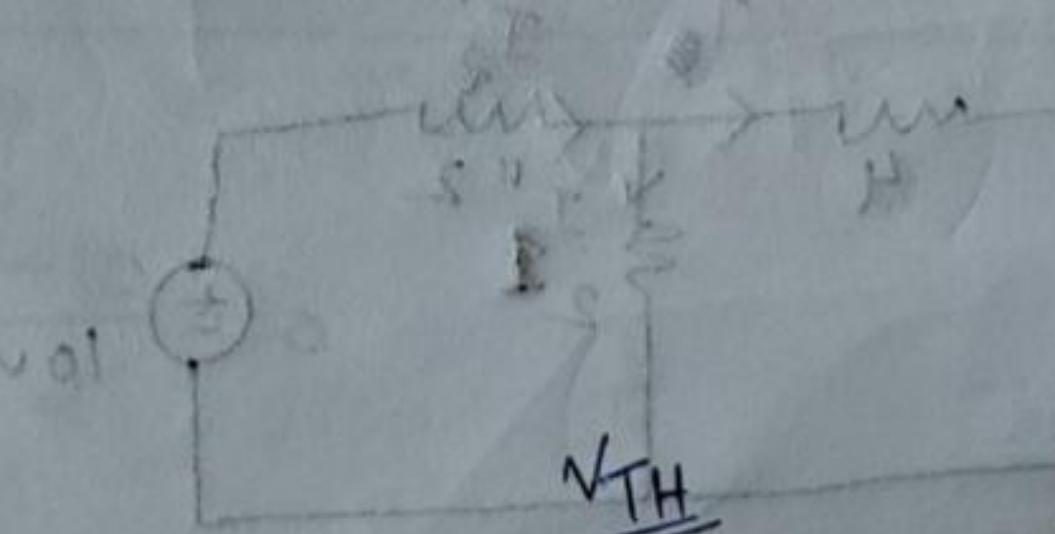

NTH

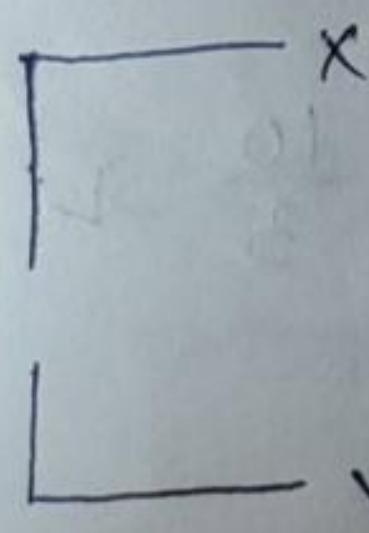

$$R_{TH} = R_N = \infty$$

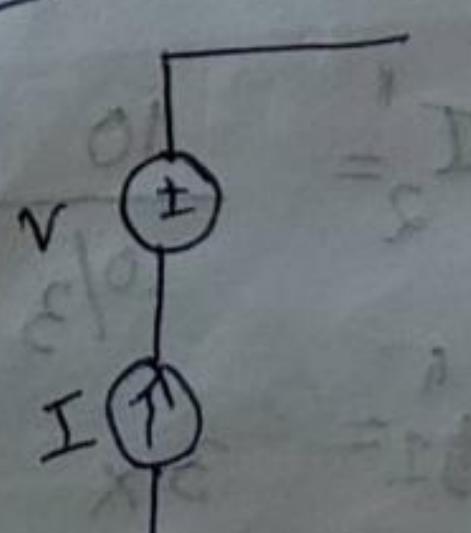


$N_{TH} = \text{can't be determined}$

Norton



$$I_N = I_{sc} = I$$

$$R_N = \infty$$

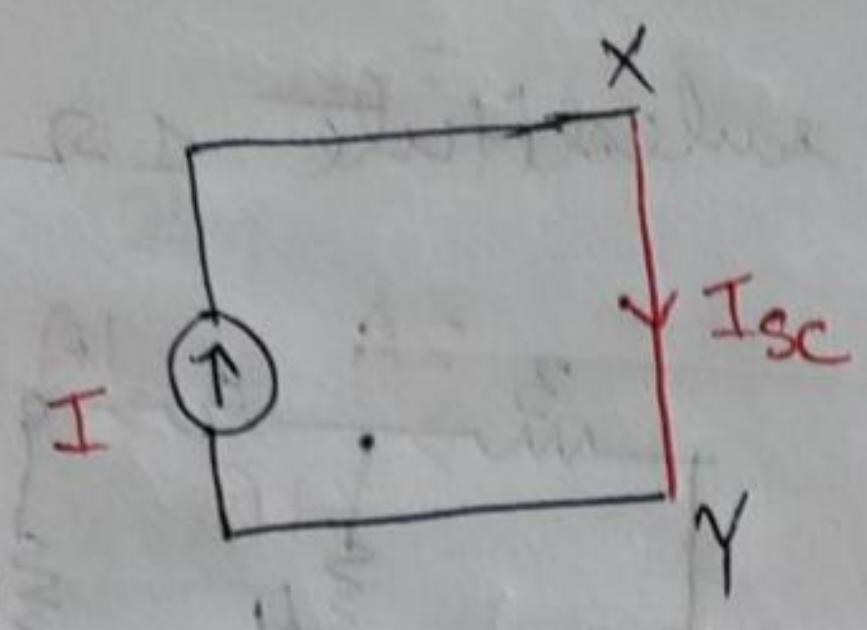

4. Using superpost. theorem determine I in R_1, R_2, R_3 and potential of pt. A relative to point B.

Sol^m

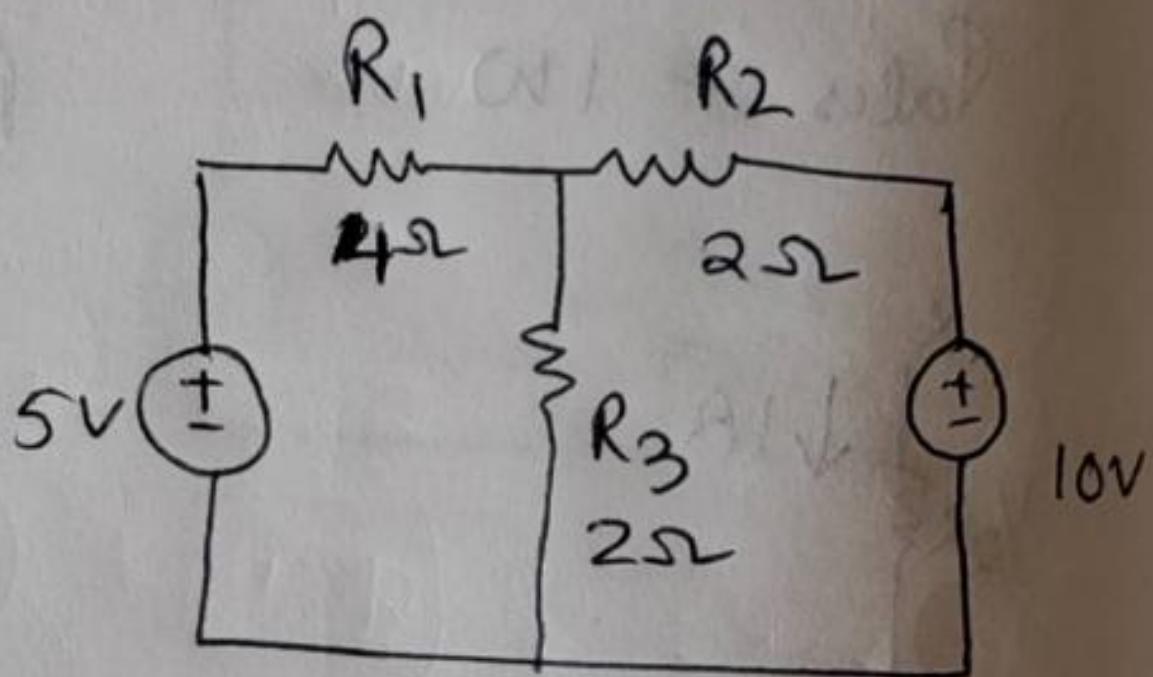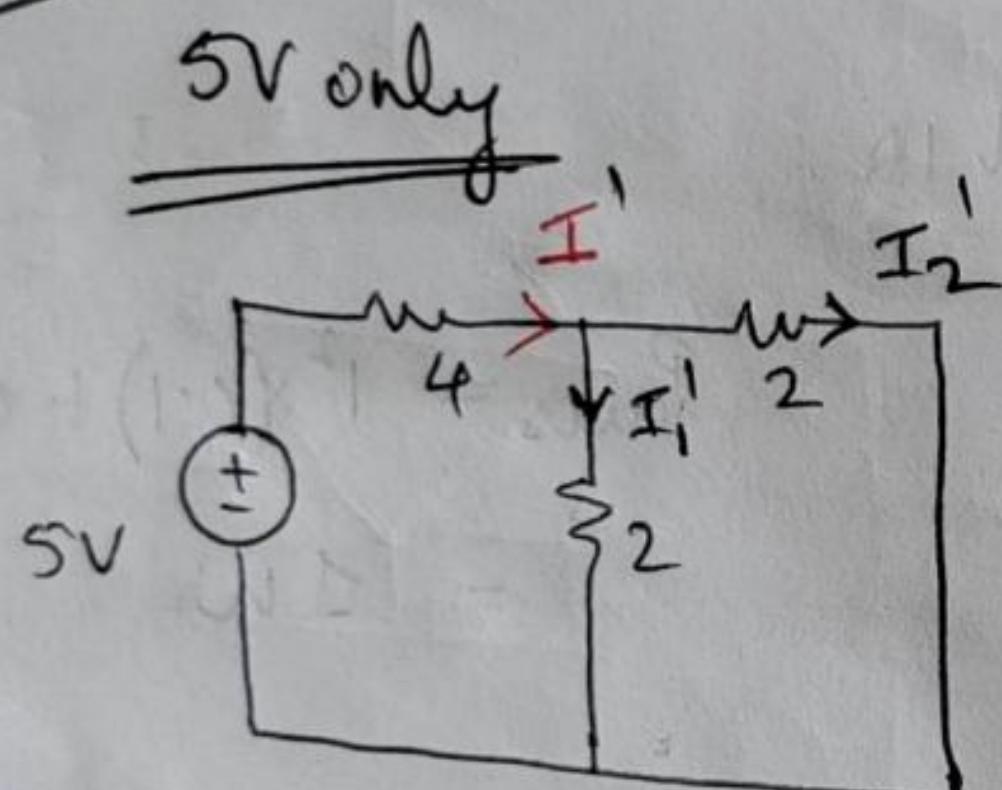


$$\therefore \text{Total Resistance} = 4 + 2 \parallel 2 = 5 \Omega$$

$$\therefore I' = \frac{5V}{5\Omega} = 1A$$

$$I'_1 = 0.5A$$

$$I'_2 = 0.5A$$

10V only

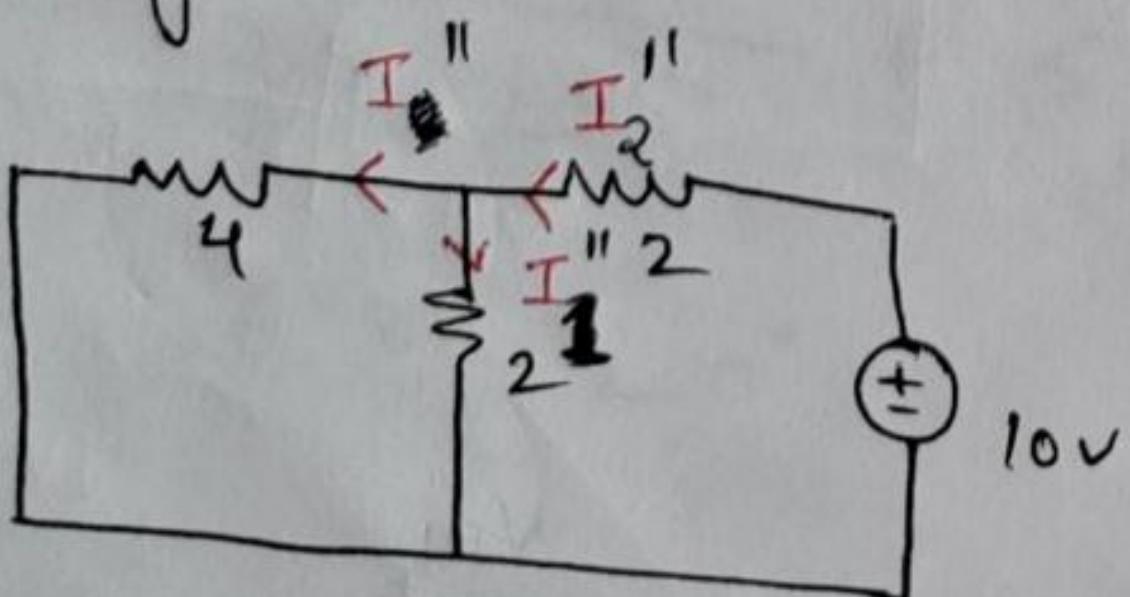

$$I''_2 = \frac{10}{10/3} = 3A$$

$$I''_1 = 3 \times \frac{4}{6} = 2A$$

$$I'' = 3 \times \frac{2}{6} = 1A$$

Total resistance

$$= 2 + (4 \parallel 2)$$

$$= \frac{10}{3} \Omega$$

$$I = I' + I'' = 1 \text{ A} = 2 \text{ OA}$$

$$I_1 = I_1' + I_1'' = 0.5 + 2 = 2.5 \text{ A}$$

$$I_2 = 3 - 0.5 = 2.5 \text{ A}$$

$$\therefore \text{Potential of } A \text{ w.r.t } B = I_1 \times 2 \\ = 2.5 \times 2 \\ = 5 \text{ V}$$


5. Using Millman's, find I in R_3 .

$$V^1 = \frac{V_1 / R_1 + V_2 / R_2 + V_3 / R_3}{1/R_1 + 1/R_2 + 1/R_3} \\ = \frac{(4 \times 0.5) + (0 \times 1) + (10 \times 0.5)}{0.5 + 1 + 0.5}$$

$$V^1 = 3.5 \text{ V}$$

$$R^1 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3} = 0.5$$
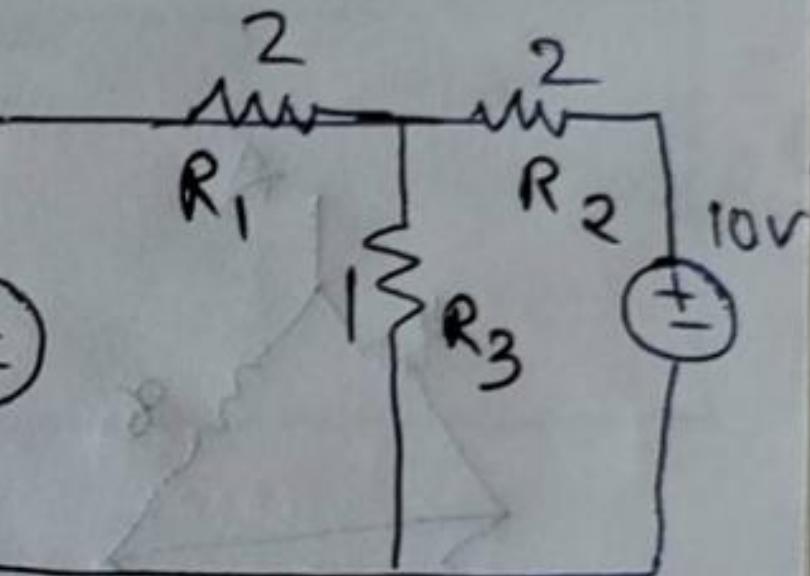
$$\therefore \text{Voltage across } R_3 = \frac{3.5}{1} = 3.5 \text{ A}$$



$$\begin{aligned} & \frac{2}{3} + 2 \\ & \frac{8}{3} \times \frac{2}{3} \\ & = \frac{16}{9} \\ & \frac{16}{9} + \frac{16}{9} \\ & = \frac{32}{9} \end{aligned}$$

Check Nodal

$$\frac{V_1 - 4}{2} + \frac{V_1}{1} + \frac{V_1 - 10}{2} = 0$$

$$\Rightarrow V_1 - 4 + 2V_1 + V_1 - 10 = 0$$

$$\Rightarrow 4V_1 = +14$$



$$\Rightarrow V_1 = \frac{14}{4} = 3.5 \text{ V}$$

$$\Rightarrow V_1 = \frac{14}{4} = 3.5 \text{ V}$$


6. Find I in ammeter A " of $R = 3\Omega$
connected in unbalanced wheatstone bridge

SOL^Y using Thevenin

$$R_{TH} =$$

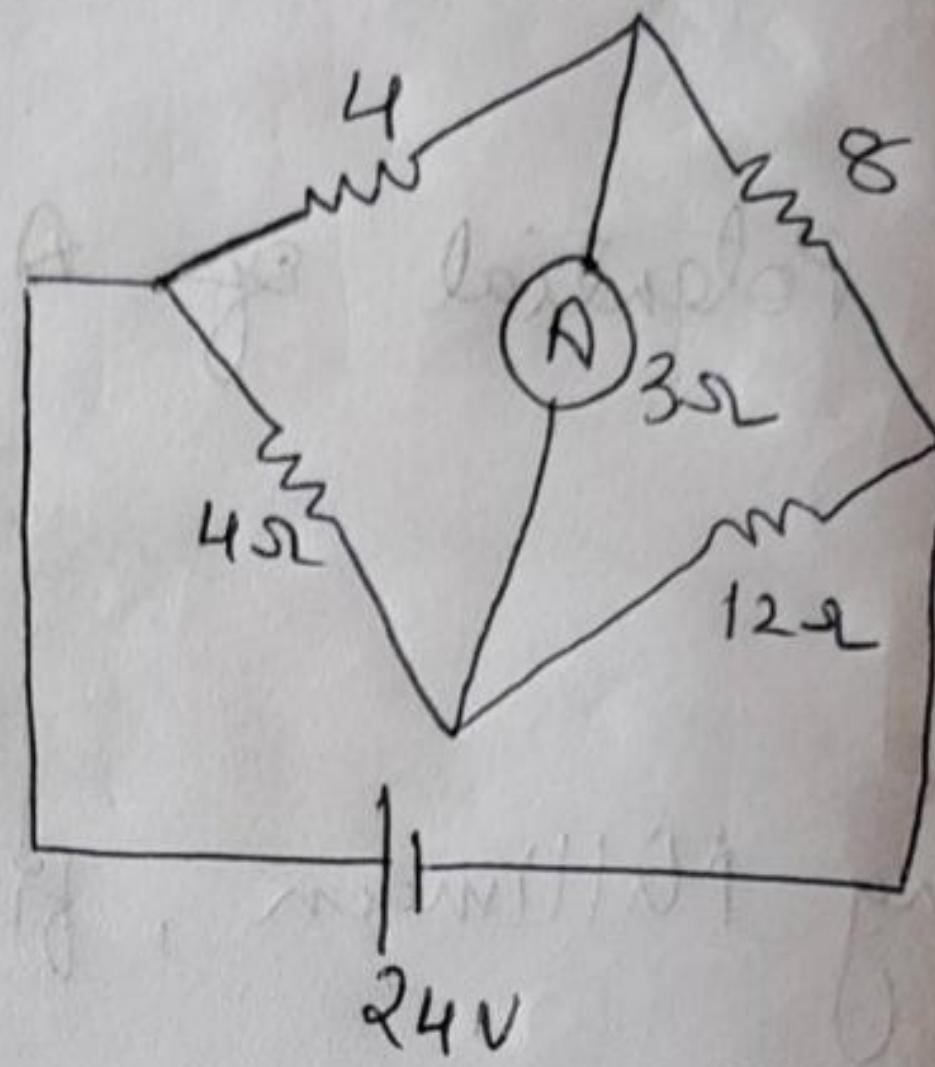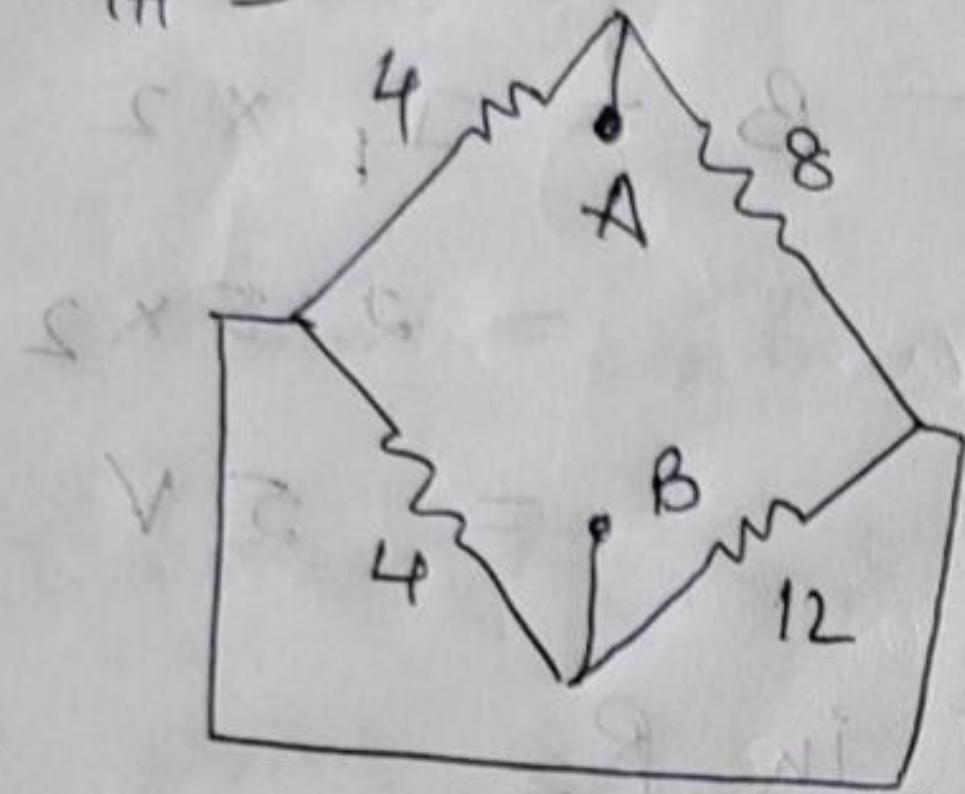
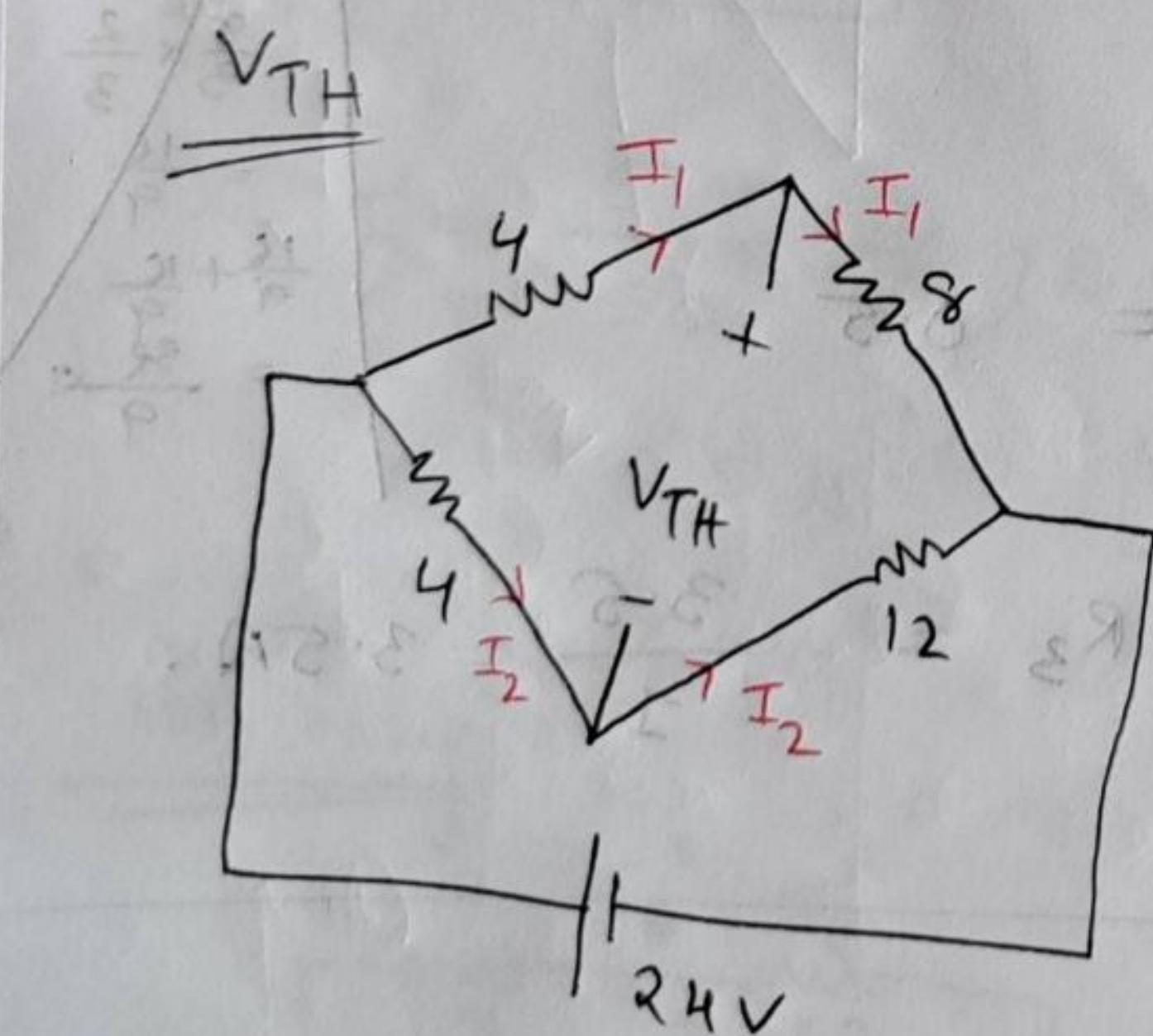
$$R_{TH} = \frac{(8 \parallel 4) + (4 \parallel 12)}{2.0 + 1 + 2.0} = 5.66 \Omega.$$



$$I_1 = \frac{24}{4+8} = 2A$$


$$I_2 = \frac{24}{4+12} = 1.5A$$

KVL

$$4I_1 + V_{TH} - 4I_2 = 0$$

$$\Rightarrow 8 + V_{TH} - 6 = 0$$

$$\Rightarrow V_{TH} = -2V$$

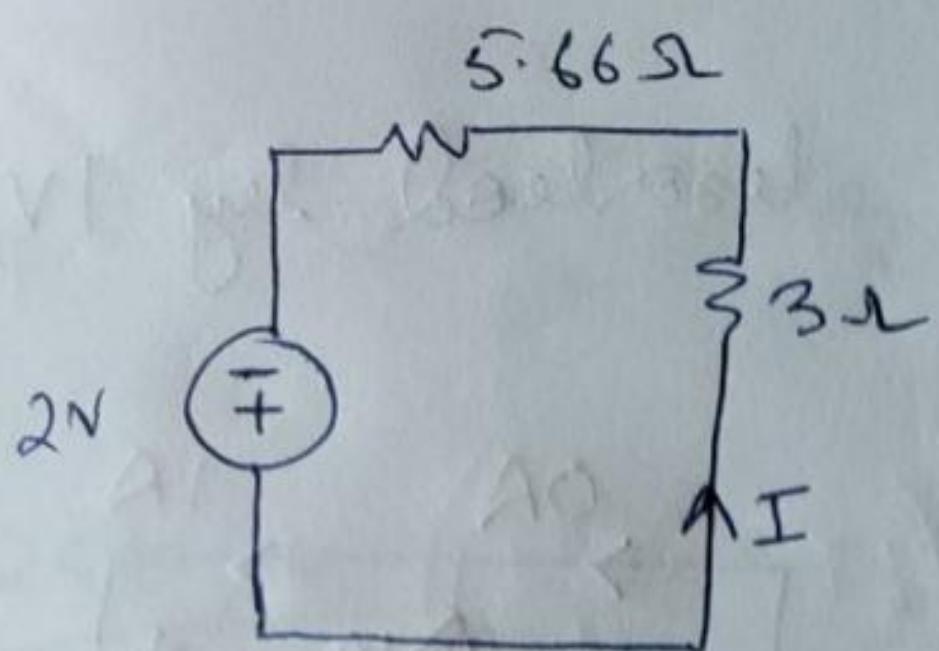


$$I = \frac{2}{5.66 + 3} = 0.23 \text{ A}$$

7. Find current in R_4 if ammeter have internal resistance of 1 ohm is inserted in series with R_4 , what reading will ammeter show?

Sol^m

Compensation theorem

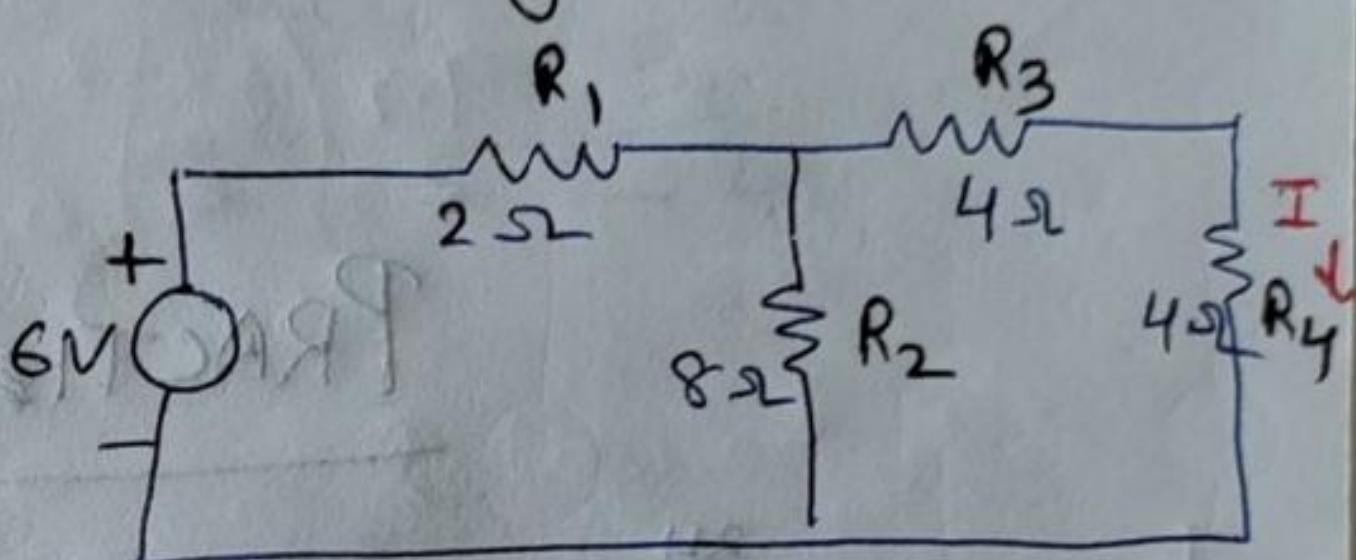


$$\text{Total current} = \frac{6}{2 + (8 + 8)} = 1 \text{ A}$$

$$I = 1 \times \frac{8}{8 + 8} = 0.5 \text{ A}$$

$$\begin{aligned} \text{Compensated voltage, } V_C &= I(\Delta R) \\ &= 0.5 \times 1 = 0.5 \text{ V} \end{aligned}$$

compensated N/W

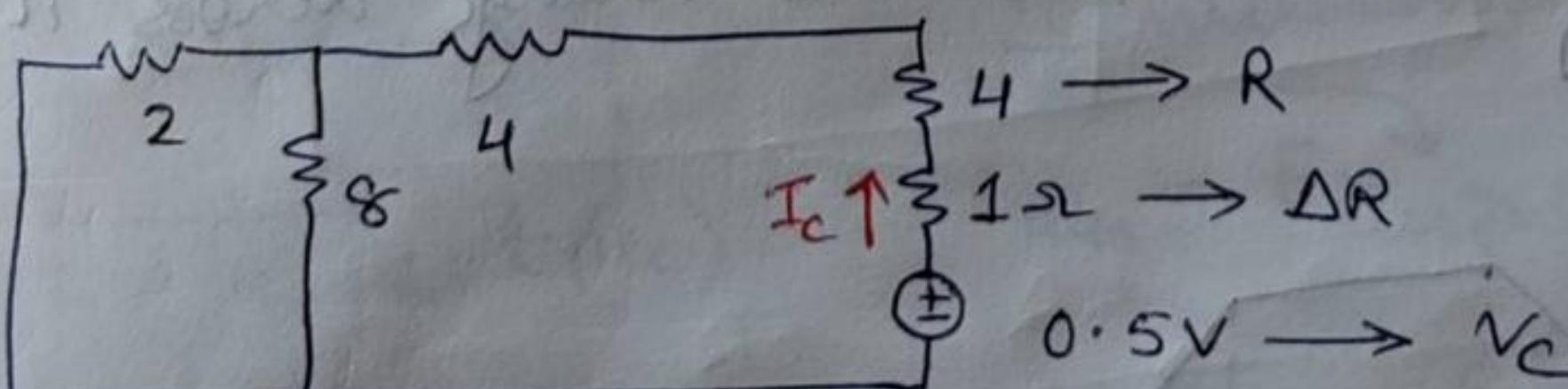

$$I_c = \frac{0.5}{5 + 4 + (8 + 2)} = \frac{0.5}{9 + 1.6} = \frac{0.5}{10.6} = 0.0471 \text{ A}$$

$\therefore I_c$ is opposite to I caused by 6V.


$$\therefore \text{Ammeter reading} = (0.5 - 0.0471) \text{ A} = 0.45 \text{ A}$$

3. Find power delivered or absorbed by $1V$, $1A$, 1Ω .


$$P_{\text{delivered}} \ 1V = 0W$$

$$P_{\text{del}} \ 1A = 1W$$

$$P_{\text{del}} \ 1\Omega = 1W$$

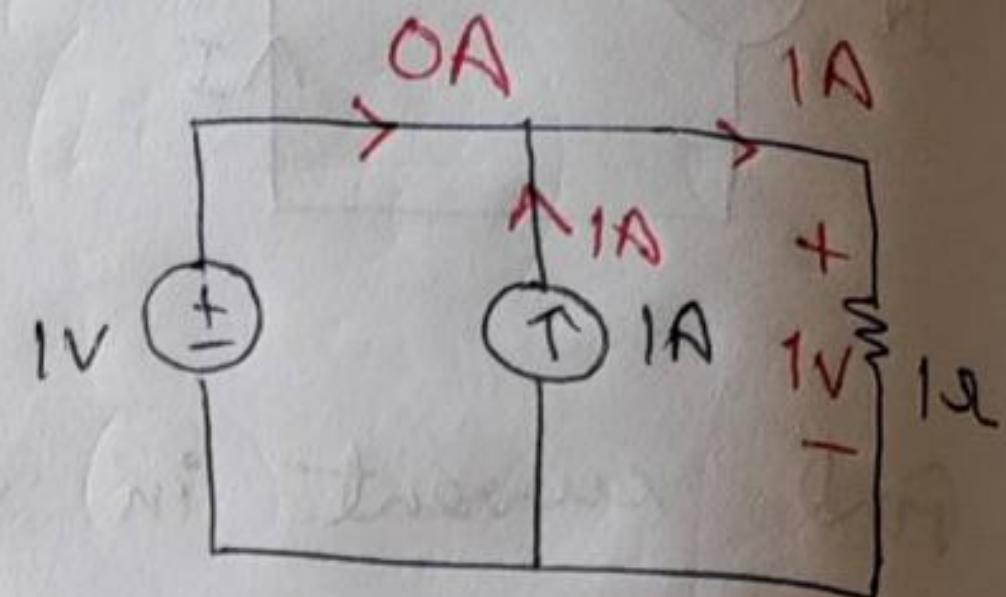

PRACTICE SET 6

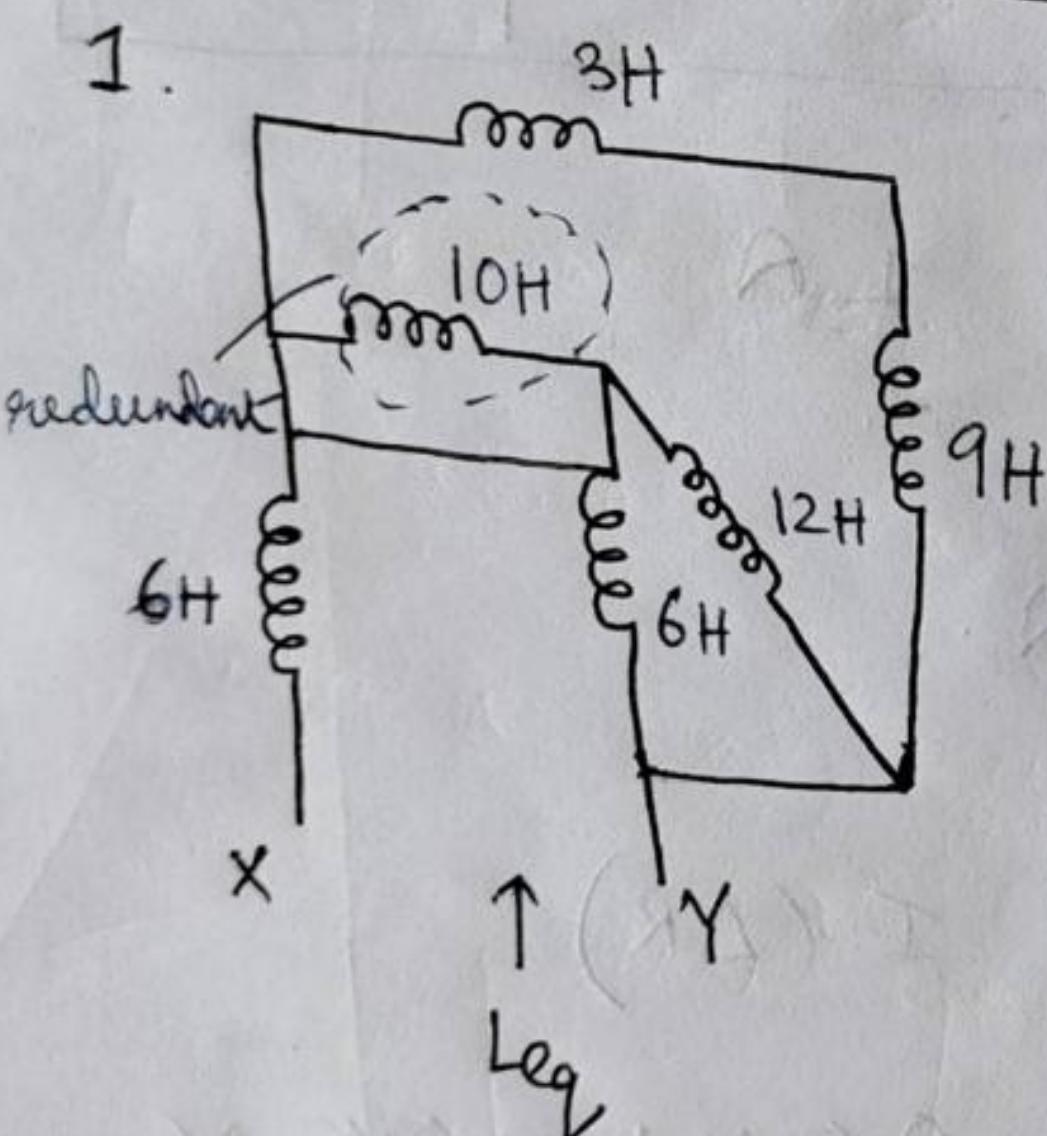


Find L_{eq}

$$L_{\text{eq}} = 6 + (6 \parallel 12 \parallel 11 \parallel 12)$$

$$= 6 + 3 = 9H$$

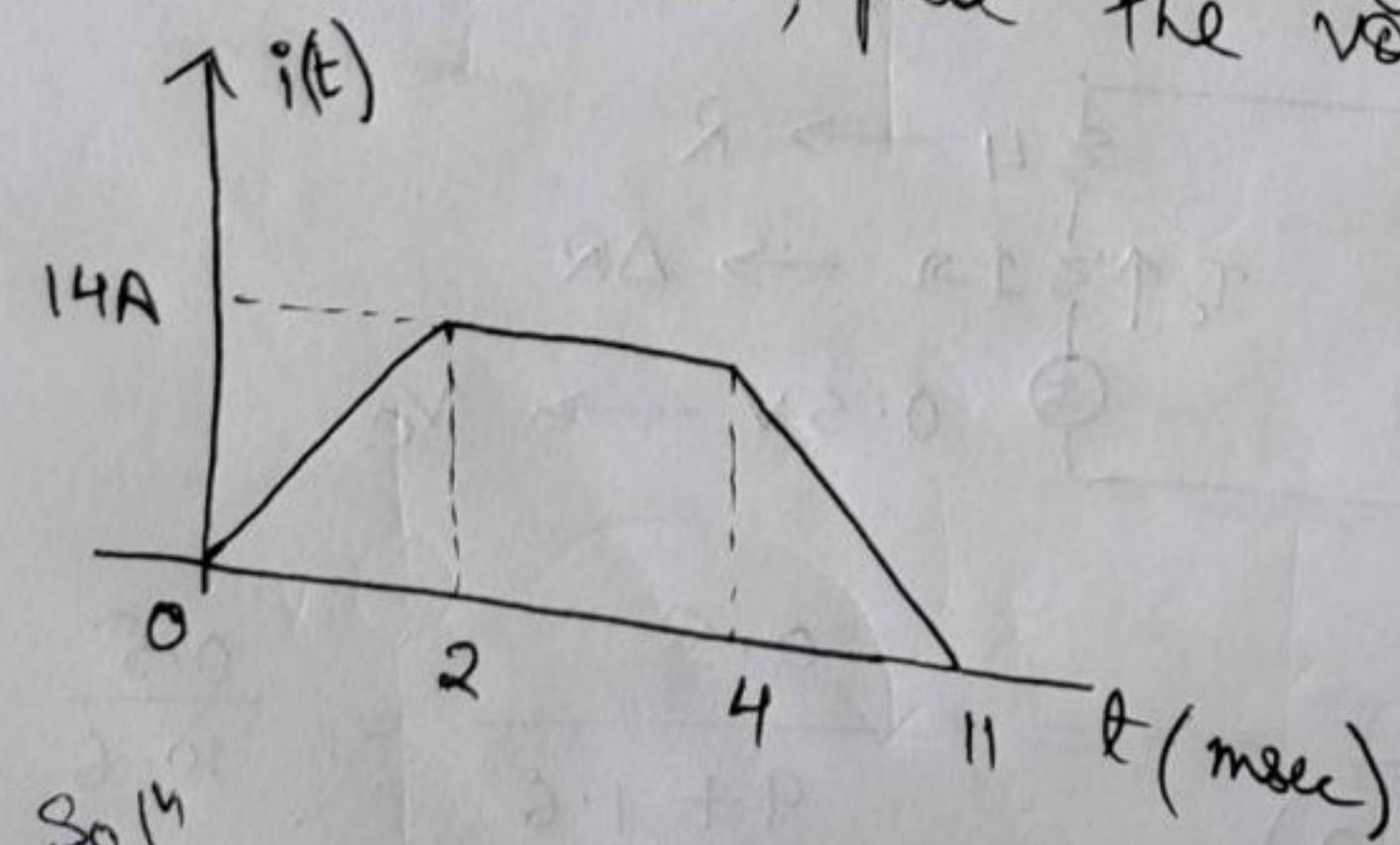2. If the current is as shown, plot the voltage across it.



Soln

$0 < t < 2$

$$i(t) = 7t$$

$$\begin{matrix} 2, 14 \\ 0, 0 \end{matrix}$$

$$\frac{14-0}{2-0} = \frac{14}{2}$$

$$\therefore V = L \frac{di}{dt} = 2 \frac{d}{dt}(7t) = +14V$$


$2 < t < 4$

$$i(t) = 14 \Rightarrow V = L \frac{di}{dt} = 2 \frac{d}{dt}(14) = 0V$$



$4 < t < 11$

$$i(t) = -2t \Rightarrow V = L \frac{di}{dt} = 2 \frac{d}{dt}(-2t)$$

$$= -4V$$

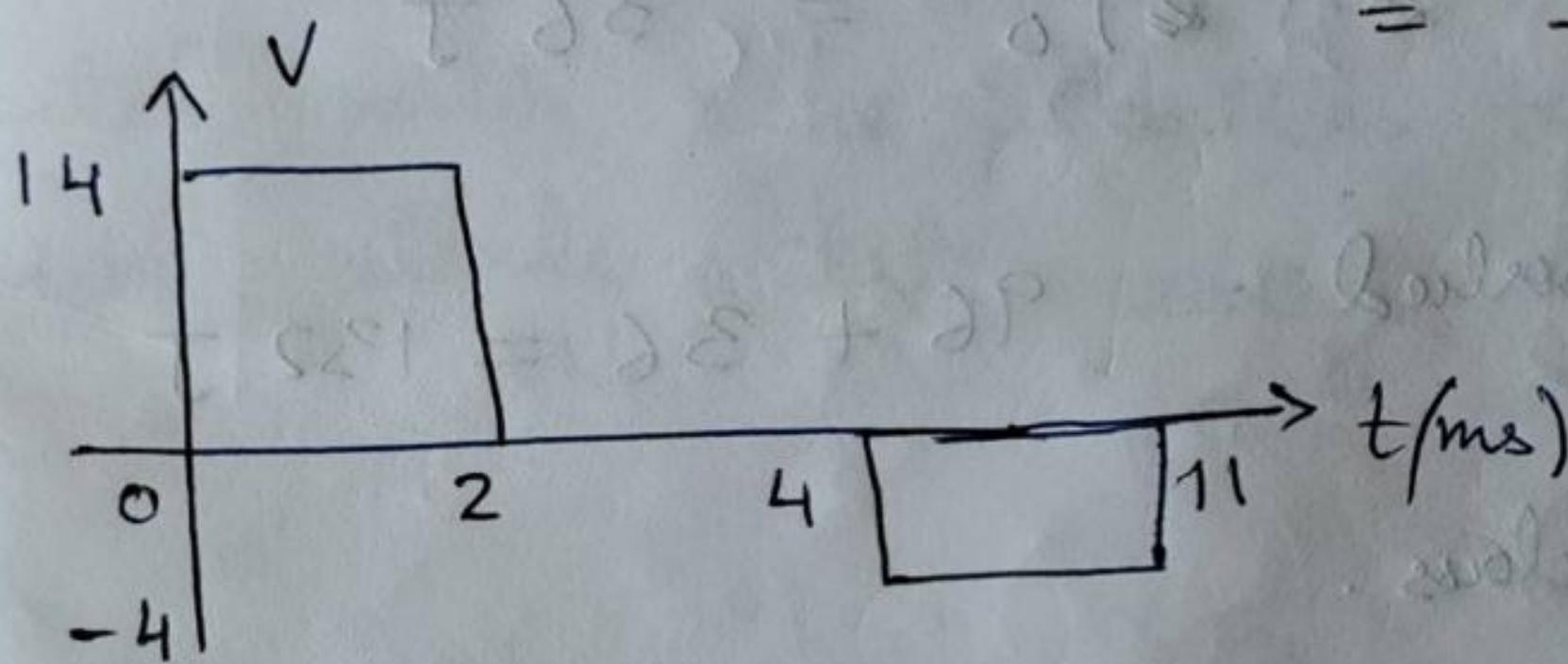

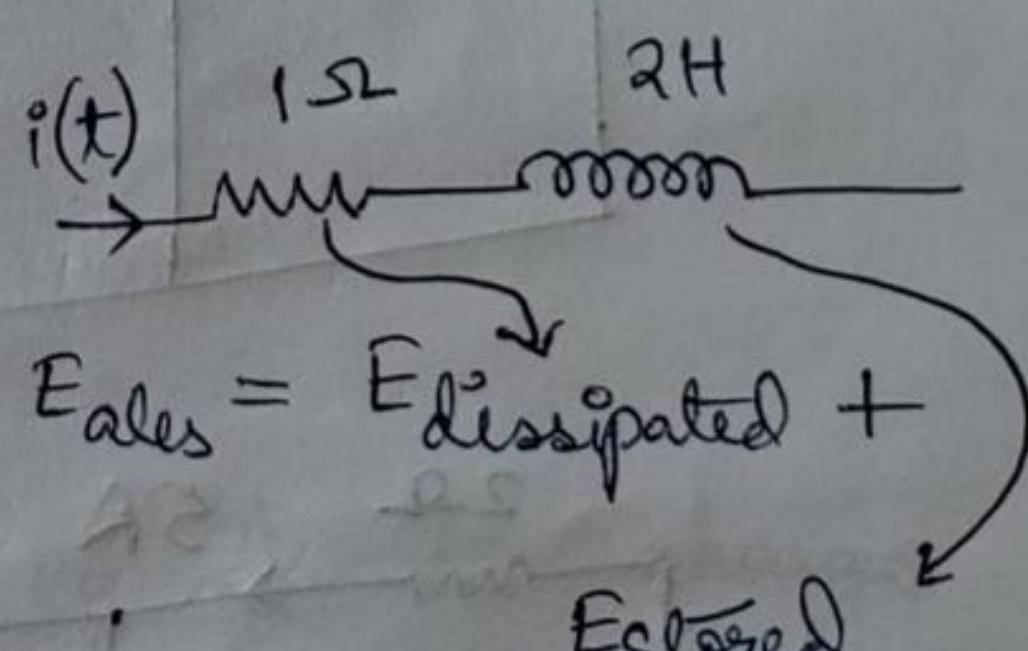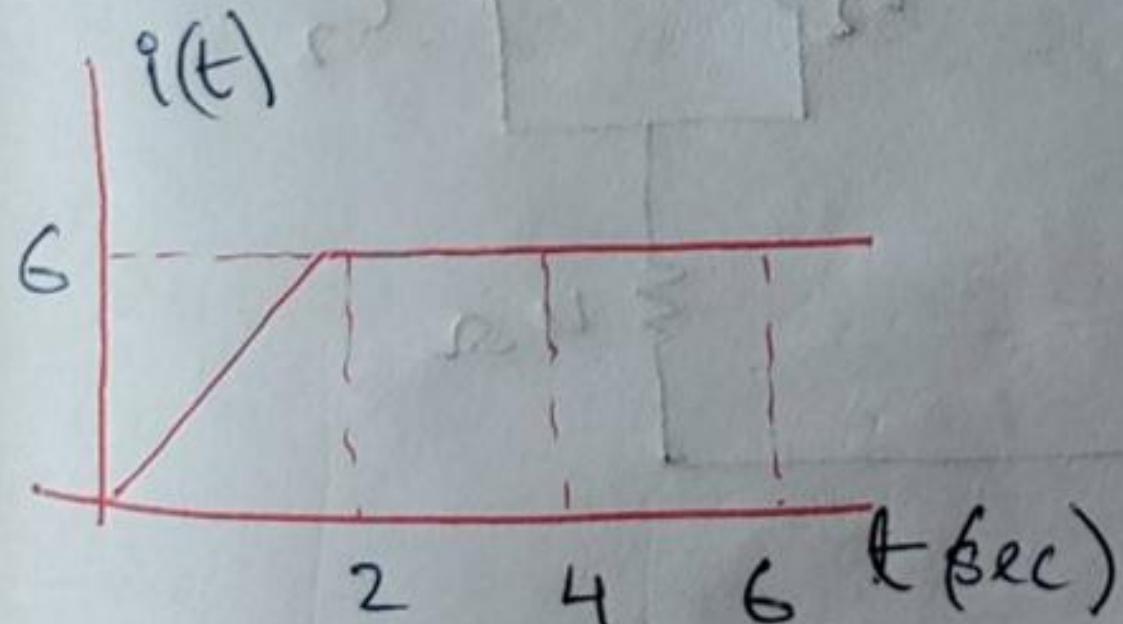3. A practical coil has an inductance of 2H and resistance of 1Ω. If this coil is excited with current as shown below. Find total energy absorbed by the coil upto 1st 4 seconds.



$$E_{\text{abs}} = E_{\text{dissipated}} +$$

E_{stored}

$$E_{\text{dissipated}} = \int P_R dt$$

$$= \int_0^4 [i(t)]^2 R dt$$

$$= \int_0^2 (3t)^2 \times 1 dt + \int_2^4 6^2 dt$$

$$= \frac{9}{3} [t^3]_0 + 36(4-2)$$



$$= 24 + 72 = 96 \text{ J}$$

$$\begin{aligned} E_{\text{stored}} &= \int P_L dt = \int_0^4 \left(L_i \frac{di(t)}{dt} \right) dt \\ &= \int_0^2 \left[2(3t) \frac{d}{dt}(3t) \right] dt + \\ &\quad \int_2^4 \left[2 \cdot 6 \frac{d}{dt}(6) \right] dt \\ &= \frac{9 \times 2}{2} \left(\frac{t^2}{2} \right)_0^2 = 36 \text{ J} \end{aligned}$$

$$\therefore E_{\text{discharged}} = 96 + 36 = 132 \text{ J}$$

4. done in class.

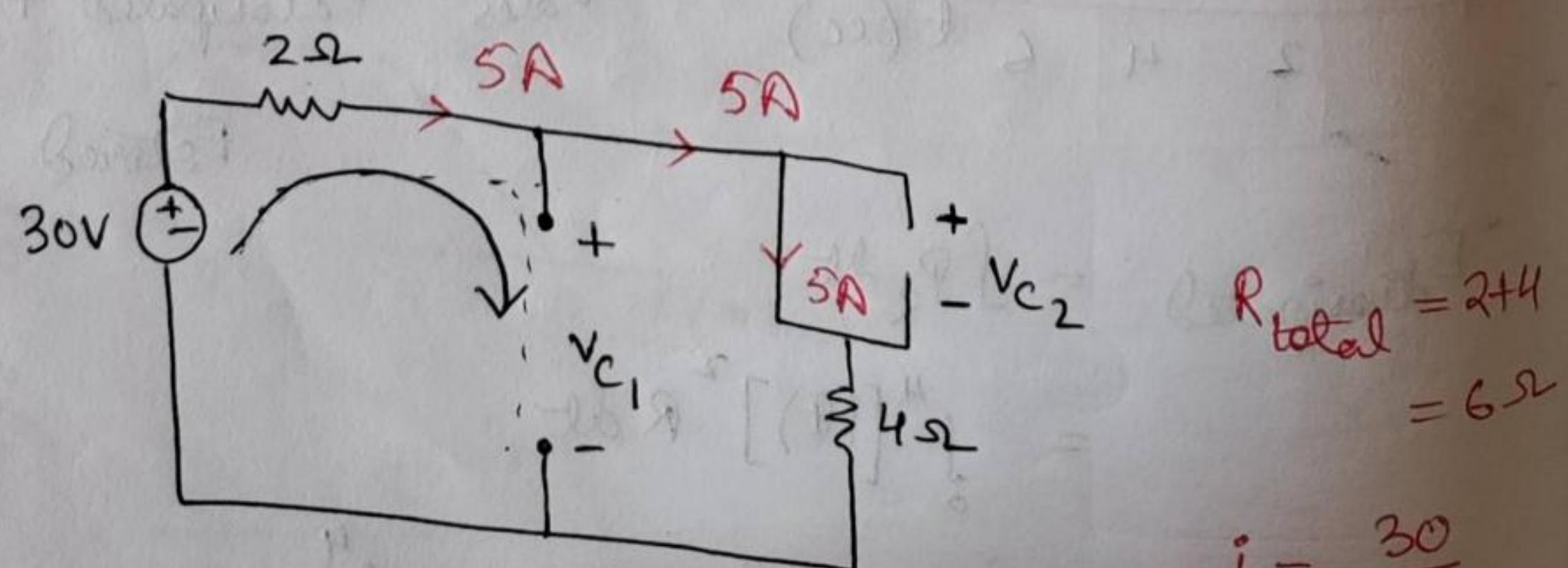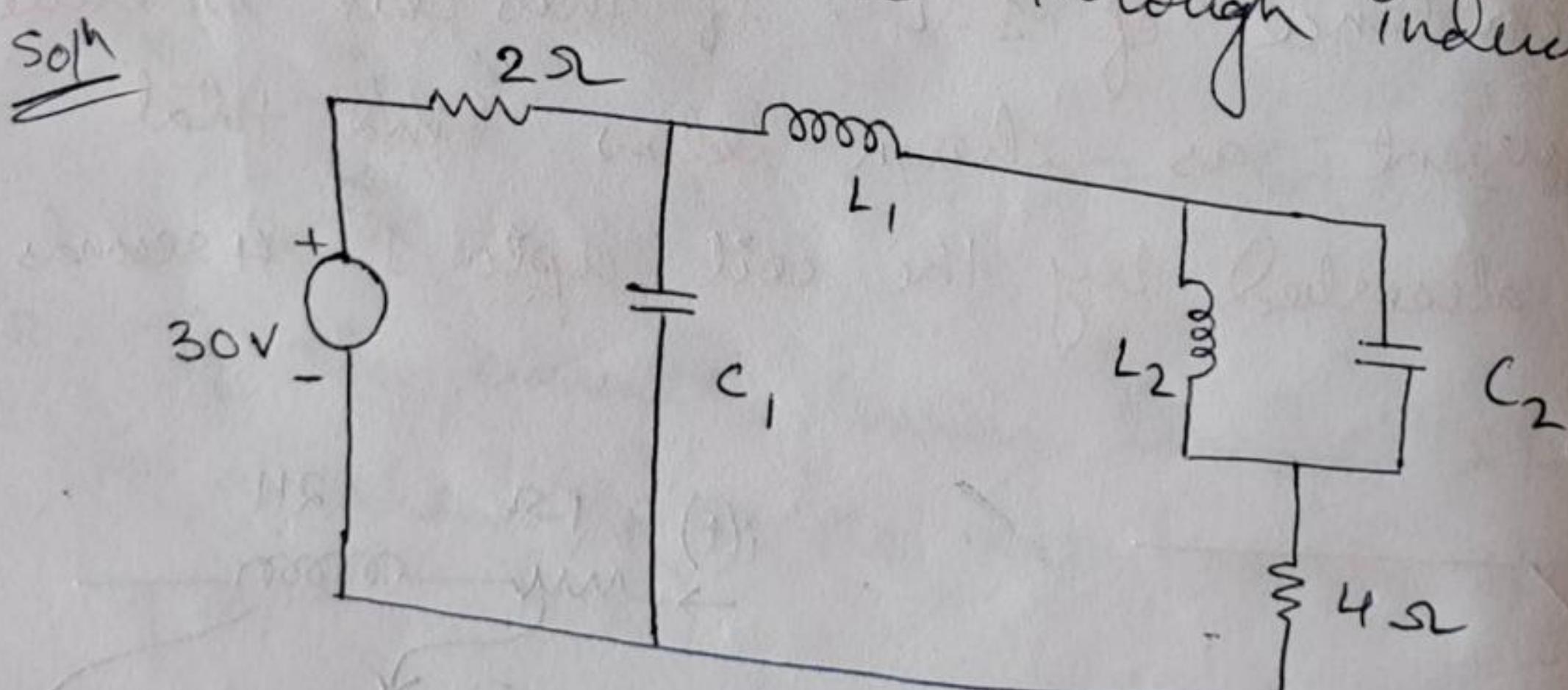5. Determine steady state voltage across capacitor and current through inductor.



$$\therefore I_{L_1} = I_{L_2} = 5 \text{ A}$$

$$\begin{aligned} i &= \frac{30}{6} \\ &= 5 \text{ A} \end{aligned}$$

KVL


$$-30 + 10 + V_{C_1} = 0$$

$$\Rightarrow V_{C_1} = 20V$$

$$V_{C_2} = 0V \quad [\text{across S.C.}]$$

6. Two capacitors of $1\mu F$ and $2\mu F$ are connected in series across a $30V$ DC source. Find their steady voltages and charge on each. Now if these 2 capacitors are disconnected from supply and connected with like polarities together, now determine steady state voltage and charge on them.

Sol

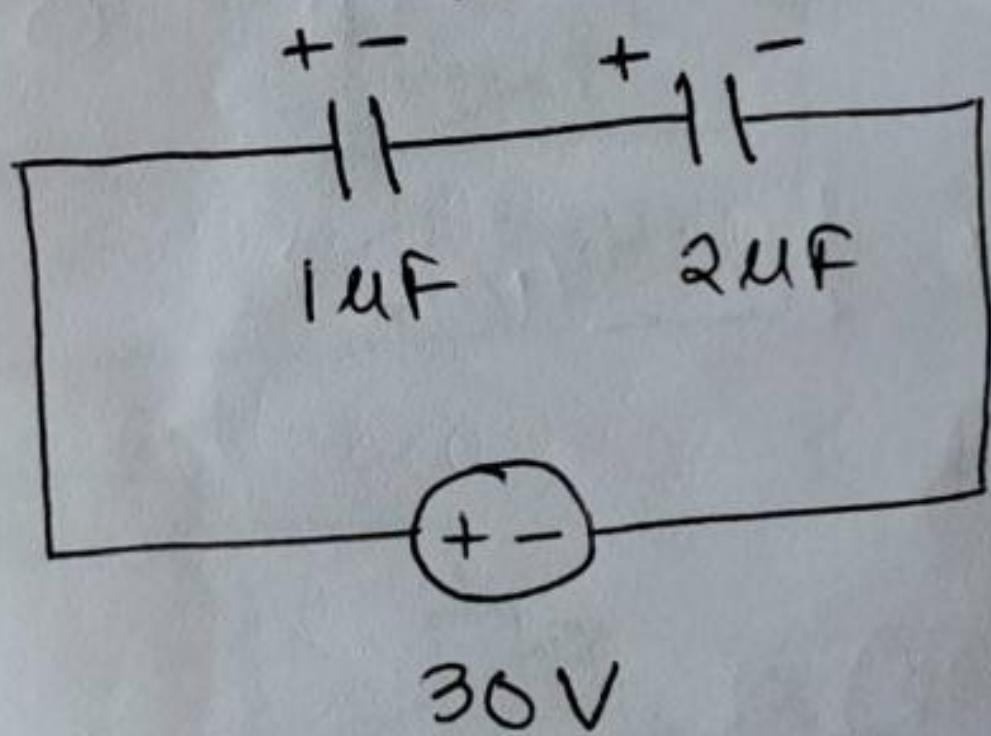

$$V_{1u} = 30 \left(\frac{2}{2+1} \right) \\ = 20V$$

$$V_{2u} = 30 \left(\frac{1}{2+1} \right) = 10V$$


$$q_{1u} = CV = 1 \times 20 = 20\mu C$$

$$q_{2u} = 2 \times 10 = 20\mu C$$

NOTE

In series, current is equal to charge will be same in series connected capacitors

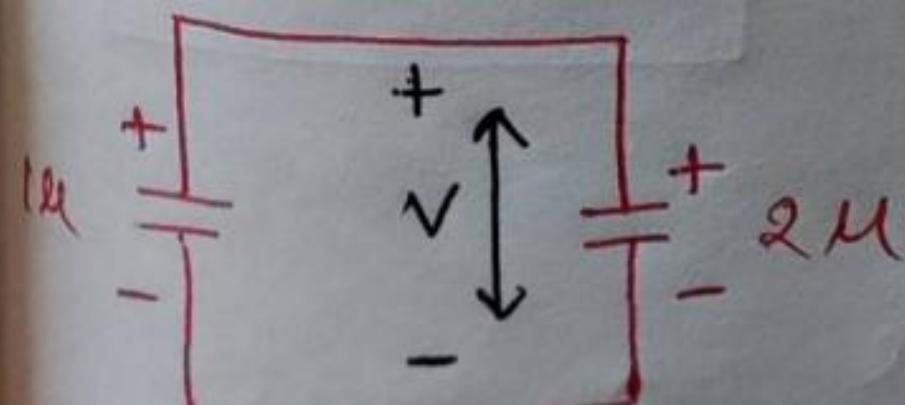Like polarities $\therefore q_{1u} = q_{2u} = 20\mu C$



$$\text{Here } V_{1u} = V_{2u} = V$$

$$\Rightarrow \frac{q_1}{C_1} = \frac{q_2}{C_2} \Rightarrow \frac{q_1}{1} = \frac{q_2}{2}$$

$$\therefore q_2 = 2q_1$$

From law of conservation of charge

$$q_1 + q_2 = 20 + 20 = 40$$

$$\therefore q_1 + 2q_1 = 40$$

$$\Rightarrow q_1 = \frac{40}{3} \text{ uc}$$

$$\therefore q_2 = 2q_1 = \frac{80}{3} \text{ uc}$$

$$\therefore V_1 = V_2 = \frac{q_1}{C_1} = \frac{q_2}{C_2} = \frac{40}{3} \text{ volts}$$

3