

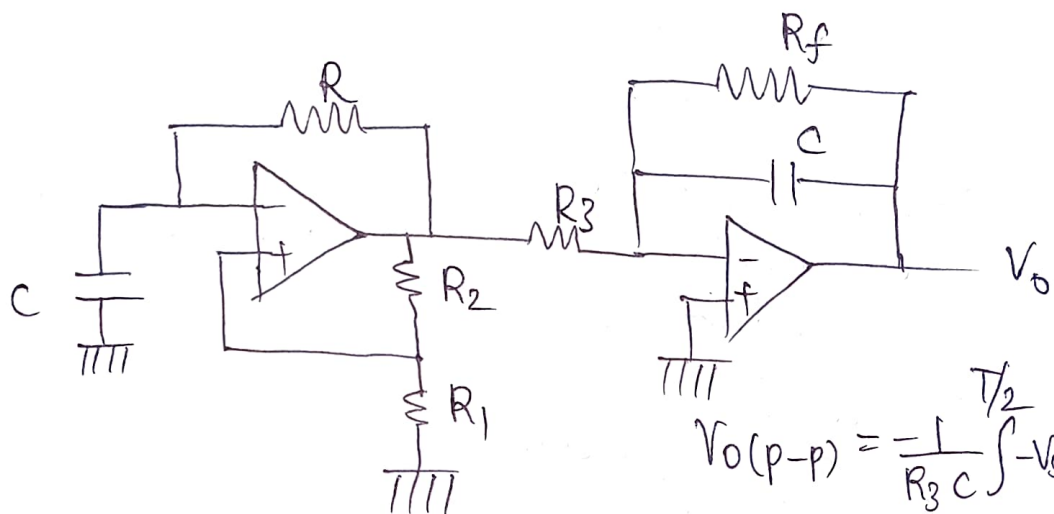


Triangular wave generator using OPAMP:

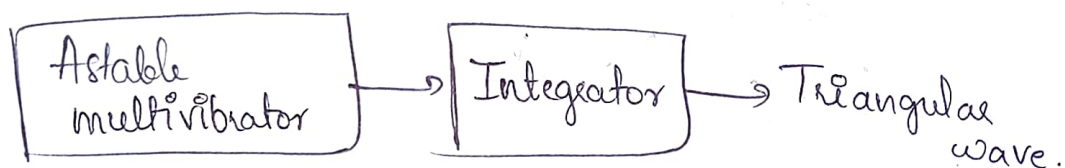
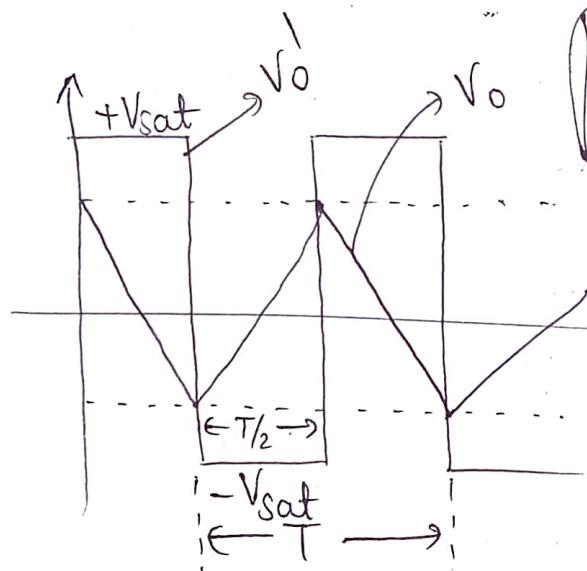
$$V_o(p-p) = \frac{-1}{R_3 C} \int_0^{T/2} -V_{sat} dt$$



$$V_o(p-p) = \frac{+V_{sat} T}{2 R_3 C}$$

Peak to peak output voltage.


$T \rightarrow$ time period of square wave and triangular wave.

$$V_o = \frac{-1}{R_3 C} \int v_o dt$$

$$\frac{V_o(p-p)}{2} = \frac{V_{sat} T}{4 R_3 C} \rightarrow \text{Amplitude of triangular wave.}$$

$$T = 2RC \ln \left(\frac{1+\beta}{1-\beta} \right) \rightarrow \beta = \frac{R_1}{R_1 + R_2}$$

• Analog Multiplier:

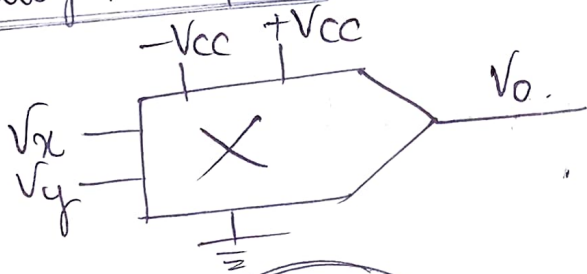


$$V_o = \frac{V_x V_y}{V_{ref}}$$


→ Analog multiplier IC which works only when both inputs V_x & V_y are positive and are called First Quadrant IC's.

→ In Second Quadrant Analog multiplier will produce correct output only when any of the input is '+ve'.

→ In Fourth Quadrant Analog multiplier will produce correct output only when V_x & V_y are either positive or negative.


• Simple Analog Multiplier:

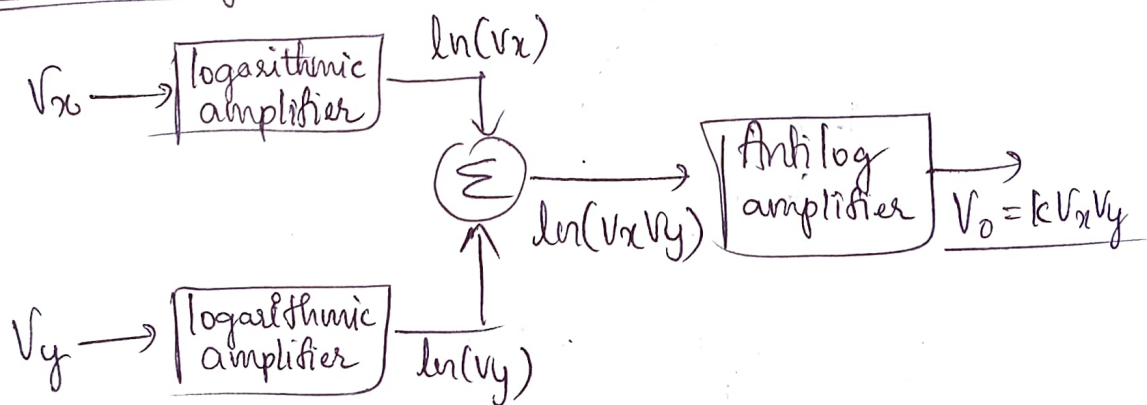

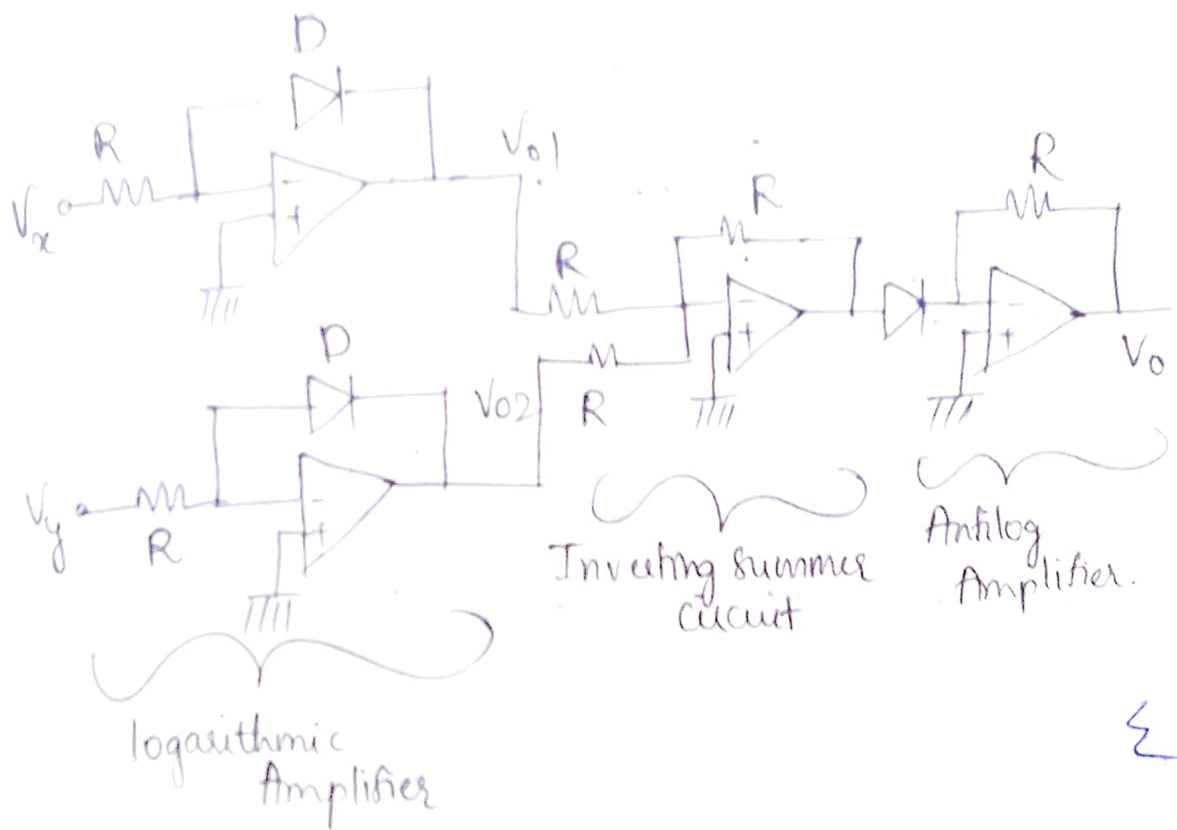

* Applications of Analog Multiplier:

① Divider circuit:

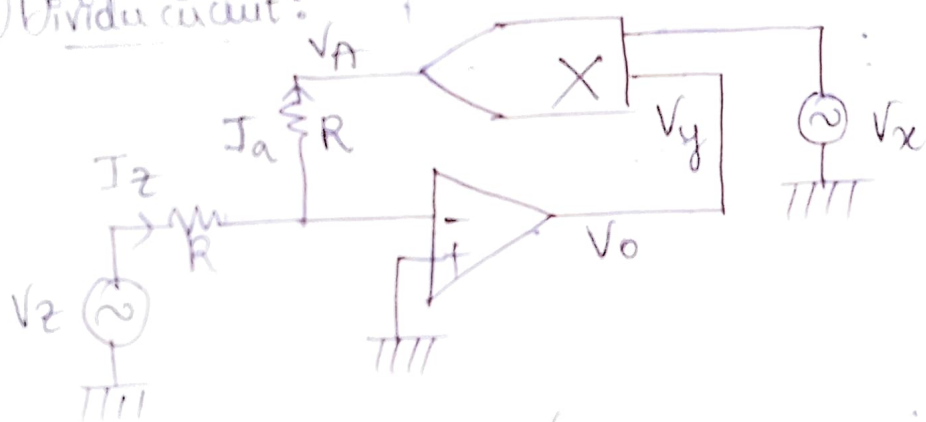

$$I_Z = \frac{V_Z}{R}, I_A = -\frac{V_A}{R} \rightarrow I_Z = I_A$$


$$V_A = \frac{V_Z V_Y}{V_{ref}} = \frac{V_Z V_0}{V_{ref}}$$

$$V_Z = -V_A$$

$$-V_Z = \frac{V_Z V_0}{V_{ref}}$$

$$V_0 = -V_{ref} \cdot \frac{V_Z}{V_Z} \rightarrow \text{divisor}$$


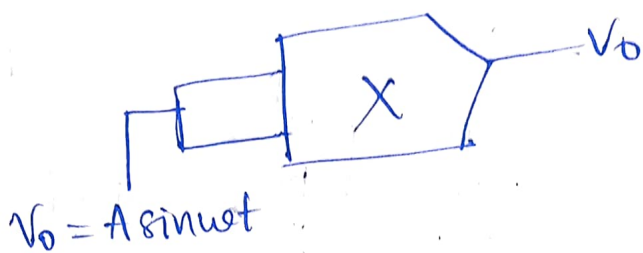
② frequency doubler using Analog Multiplier:



$$V_o = \frac{A^2 \sin^2 \omega t}{V_{ref}} = \frac{A^2}{V_{ref}} \left(\frac{1 - \cos 2\omega t}{2} \right)$$

→ Most of the cases, $V_{ref} = 10$

* Triangular wave generator:

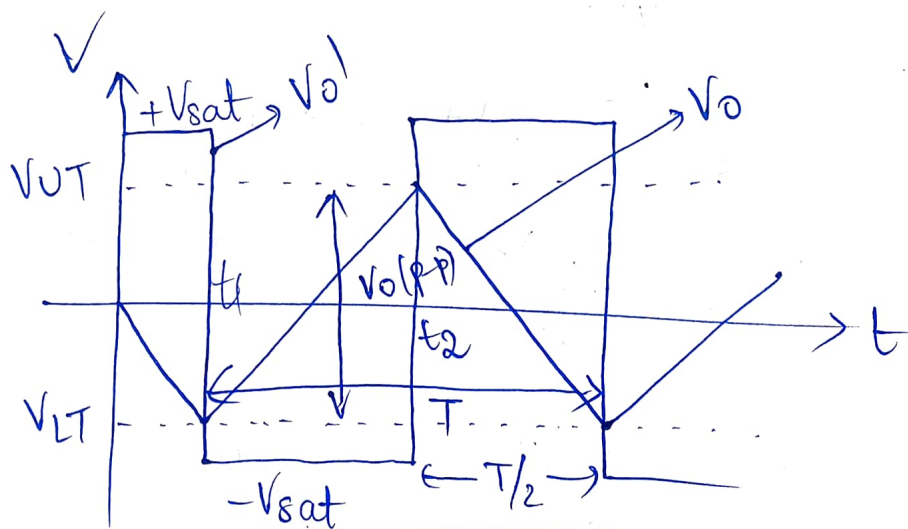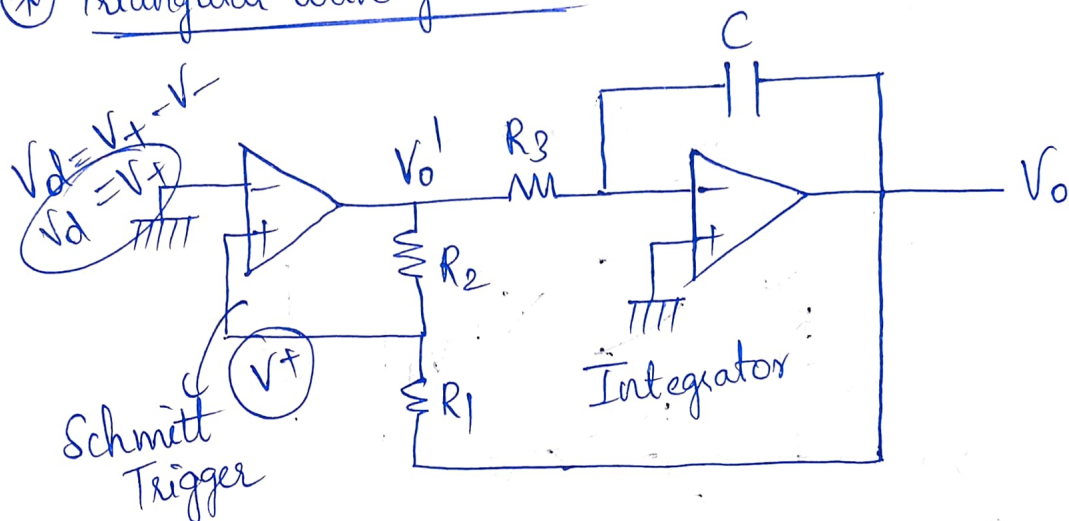

$$V_+ = \frac{V_o' R_1}{R_1 + R_2} + \frac{V_o R_2}{R_1 + R_2}$$

$$V_o = -\frac{1}{R_3 C} \int_0^t V_{sat} dt$$

$$V_o = -\frac{V_{sat} \times t}{R_3 C}$$

→ When $V_o^1 = +V_{sat}$,

$$V_+ = \frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

→ At instant t_1 , $V_+ = 0$

$$0 = \frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

$$V_o = -V_{sat} \times \frac{R_1}{R_2} = V_{LT}$$

→ When $V_o^1 = -V_{sat}$

$$V_+ = -\frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2}$$

At time instant, $t = t_2$;

$$V_+ = 0$$

$$-\frac{V_{sat} \times R_1}{R_1 + R_2} + \frac{V_o \times R_2}{R_1 + R_2} \rightarrow V_o = \frac{V_{sat} \times R_1}{R_2} = V_{UT}$$

$$V_o(p-p) = V_{UT} - V_{LT}$$

$$V_o(p-p) = 2V_{sat} \times \frac{R_1}{R_2}$$

$$V_o(p-p) = -\frac{1}{R_3 C} \int_0^{T/2} -V_{sat} dt$$

$$2V_{sat} \times \frac{R_1}{R_2} = \frac{1}{R_3 C} V_{sat} \times \frac{T}{2} \rightarrow T = \frac{4R_3 C R_1}{R_2}$$

Q: Design a triangular wave generator using OPAMP, with $f = 1\text{kHz}$ & $V_o(\text{P-P}) = 2\text{V}$.

Sol:

$$V_o(\text{P-P}) = 2 \frac{V_{\text{sat}} \times R_1}{R_2}$$

If $V_{\text{CC}} = \pm 15\text{V}$

then assume

$$V_{\text{sat}} \approx 14\text{V}$$

$$2 = 2 \frac{V_{\text{sat}} \times R_1}{R_2}$$

$$\boxed{R_2 = 14R_1}$$

If $R_1 = 10\text{k}\Omega$
then $R_2 = 140\text{k}\Omega$

$$f = \frac{R_2}{4R_3CR_1}$$

$$1 \times 10^3 = \frac{140 \times 10^3}{4 \times R_3 \times C \times 10 \times 10^3}$$


$$R_3C = 3.5 \times 10^{-3}$$

→ Assume $C = 1\mu\text{F}$

$$R_3 \times 10^{-6} = 3.5 \times 10^{-3}$$

$$\boxed{R_3 = 3.5 \times 10^3 \Omega}$$

* Monostable Vibrator using OPAMP:

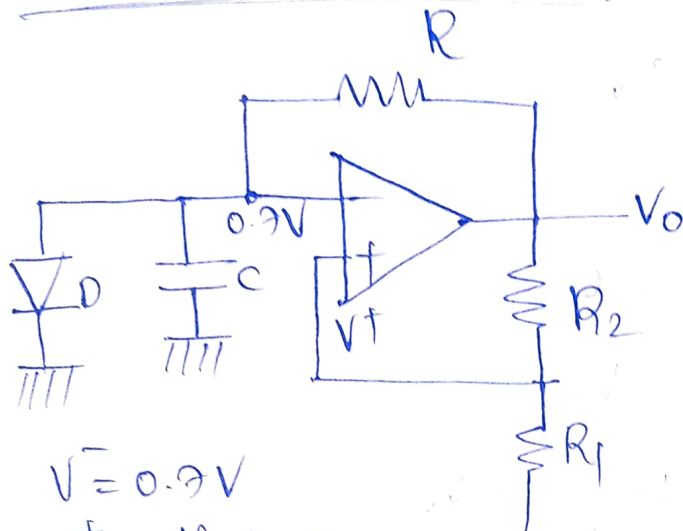

if $V_0 = +V_{sat}$
then it is stable.

$$V^- = 0.7V$$


$$V^+ = \frac{V_{sat} \times R_1}{R_2}$$


$$V_T = 0V$$

(if $V_0 = +V_{sat}$)

$$V_d = V^+ - V^-$$

$$V_d = V^+ - 0.7$$

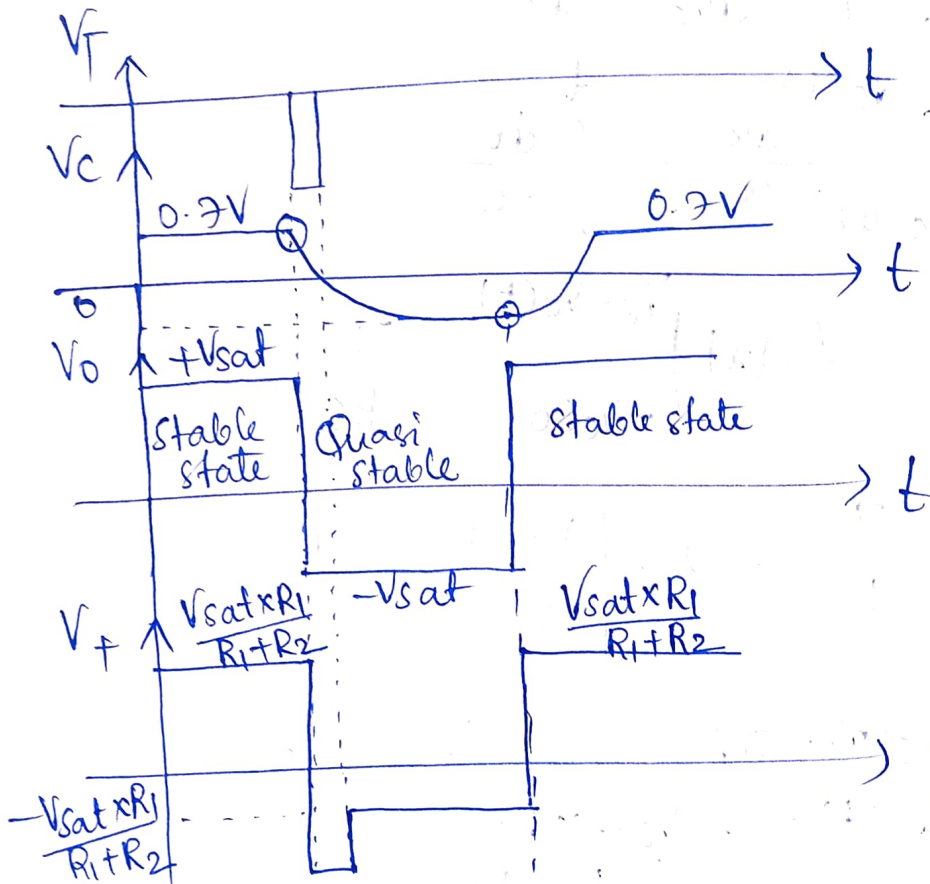

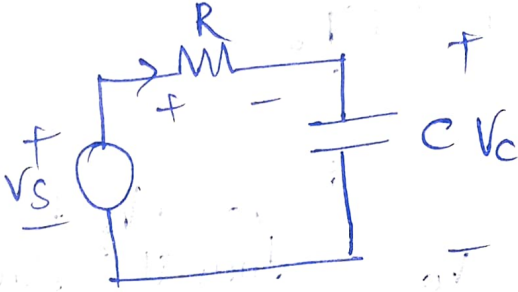

$$V_S - iR - V_C = 0$$

$$V_S = iR + V_C$$

$$V_S = RC \frac{dV_C}{dt} + V_C$$

$$\int_{V_C(0)}^{V_C(t)} \frac{dV_C}{V_S - V_C} = \int_0^t \frac{dt}{RC}$$

$$V_S - V_C = x, \quad dV_C = -dx$$

$$\int_{-V_C(0)}^{V_S - V_C(t)} \frac{dx}{x} = \int_0^t \frac{dt}{RC}$$

$$\ln|x| \Big|_{-V_C(0)}^{V_S - V_C(t)} = \frac{t}{RC}$$

$$\frac{t}{RC} = \ln \left| \frac{V_S - V_C(0)}{V_S - V_C(t)} \right|$$

$$V_C(0) = 0V$$

$$V_S = -V_{sat}$$

$$V_C(t) = -\frac{V_{sat} \times R_1}{R_2 + R_1}$$

$$T = RC \ln \left(1 + \frac{R_1}{R_2} \right)$$

3
4
5
6
7
9

ACTIVE FILTERS

→ A filter is a frequency selective circuit, which allows signals of certain range of frequencies to pass through it and rejecting other frequencies.

→ There are two kinds of filters

① Active filters - {made of passive + active elements}

② Passive filters - {made of only passive elements}

→ Types of Active filters


① Low pass filters

② High pass filters


③ Band pass filters

④ Band reject filter (or) Band stop filter.

→ frequency responses of active filters:

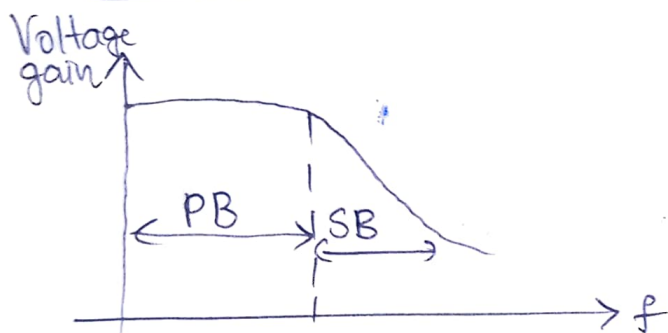


Low pass filter

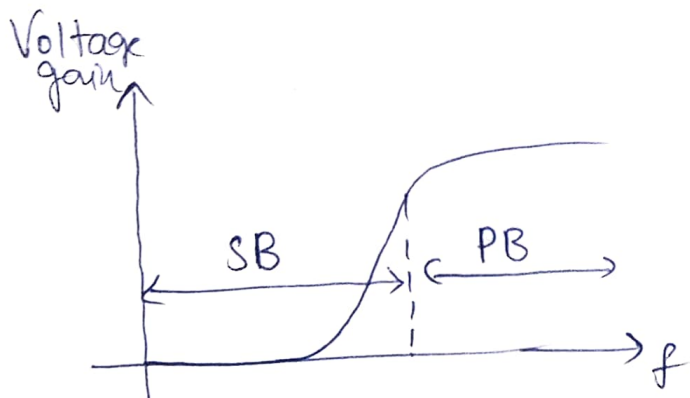

High pass filter


SB - stop Band
PB - pass Band

Voltage gain ↑

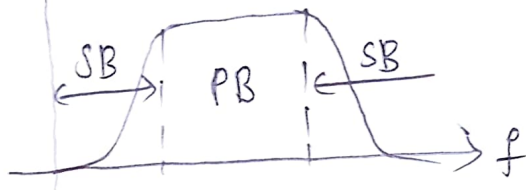

Band Pass filter


Voltage gain ↑

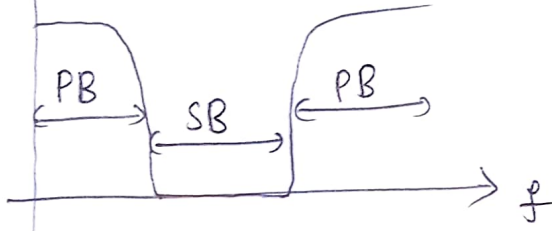

Band Reject filter

① Low pass filter:

(i) first order low pass filter:

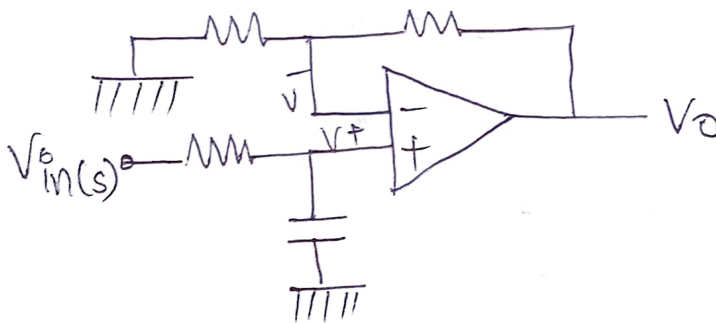

→ It is first order because $A_v(s) = \frac{1 + \frac{R_f}{R_1}}{1 + sRC}$
 $\hookrightarrow s$ has only 1 degree.

$$V^+(s) = \frac{V_{in}(s)}{R + \frac{1}{sC}} \times \frac{1}{sC}$$

$$V^+(s) = \frac{V_{in}(s)}{1 + sRC}$$

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) V_i(s)$$

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) \frac{V_{in}(s)}{1 + sRC}$$

$$A_{vf}(s) = \frac{V_o(s)}{V_{in}(s)} = \left(1 + \frac{R_f}{R_i}\right) \times \frac{1}{1 + sRC}$$

$$s = j\omega$$

$$A_{vf}(j\omega) = \left(1 + \frac{R_f}{R_i}\right) \times \frac{1}{1 + j\omega RC}$$

$$|A_{vf}(j\omega)| = \frac{\left(1 + \frac{R_f}{R_i}\right)}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$|A_{vf}(j\omega)|_{\max} \text{ when } \omega = 0$$

$$|A_{vf}(j\omega)|_{\max} = 1 + \frac{R_f}{R_i}$$

$$|A_{vf}(j\omega)| = \frac{|A_{vf}(j\omega)|_{\max}}{\sqrt{1 + \omega^2 R^2 C^2}}$$


ω_0 $f_0 \rightarrow$ frequency at which gain is $\frac{1}{\sqrt{2}}$ times maximum gain.

$$\frac{|A_{vf}|_{\max}}{\sqrt{2}} = \frac{|A_{vf}|_{\max}}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Cutoff frequency.


$$\omega_0 = \frac{1}{RC} \rightarrow \boxed{f_0 = \frac{1}{2\pi RC}}$$

→ When ω_0 is very large, then $|A_{vfb}|_{\max} = 0$

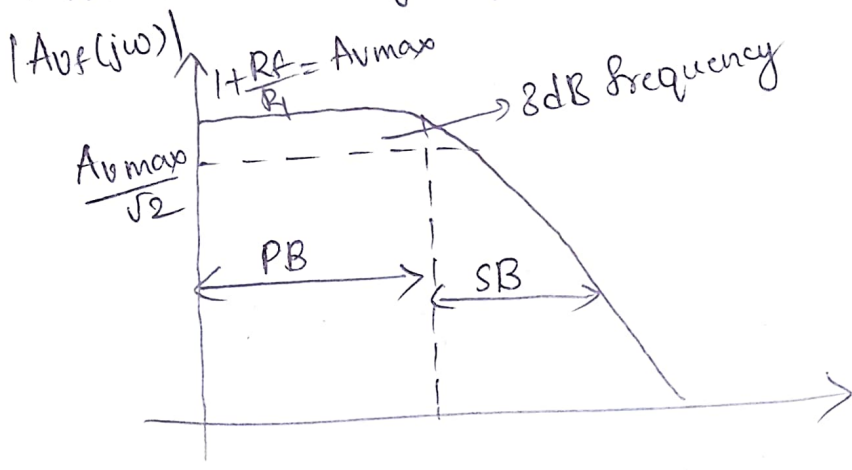

→ This is also called as Butterworth 1st order LPF.

⑤ High pass filter:

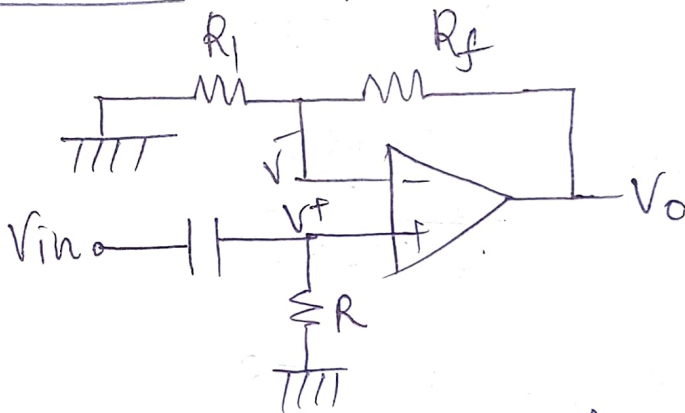

→ This is first order HPF, also called as Butterworth 1st order HPF.

$$V^+(s) = \frac{V_{in}(s) \times R}{\frac{1}{sC} + R}$$

$$V^+(s) = \frac{V_{in}(s) \times sCR}{1 + sCR}$$

For non-inverting OP-AMP,

$$V_o(s) = V^+(s) \left(1 + \frac{R_f}{R_1} \right)$$

$$V_o(s) = \frac{V_{in}(s) \times sCR}{1 + sCR} \left(1 + \frac{R_f}{R_1} \right)$$

$$A_{vf}(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{SRC \left(1 + \frac{R_f}{R_i}\right)}{1 + SRC}$$

$$s = j\omega$$

$$A_{vf}(j\omega) = \frac{j\omega RC \left(1 + \frac{R_f}{R_i}\right)}{1 + j\omega RC}$$

$$|A_{vf}(j\omega)| = \frac{\omega RC \left(1 + \frac{R_f}{R_i}\right)}{\sqrt{1 + \omega^2 R^2 C^2}}$$


$$|A_{vf}(j\omega)| = \frac{\left(1 + \frac{R_f}{R_i}\right)}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}}$$

→ Maximum voltage gain occurs at $\omega = \infty$

$$|A_{vf}|_{\max} = \left(1 + \frac{R_f}{R_i}\right)$$

→ Minimum voltage gain occurs at $\omega = 0$

$$|A_{vf}|_{\min} = 0$$

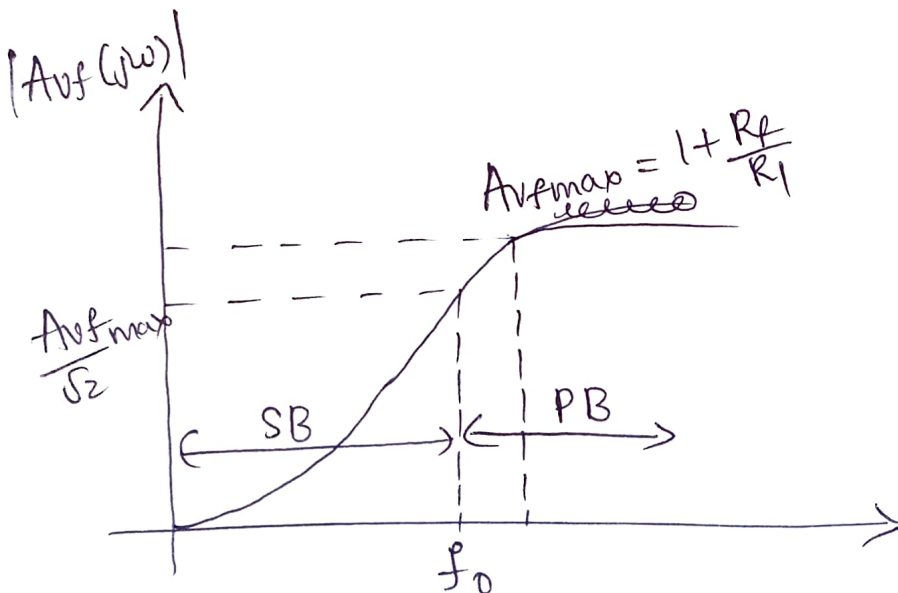

At $f = f_0$ (cut off frequency),
gain is $\frac{1}{\sqrt{2}}$ times the maximum gain.

$$|A_{vf}(2\pi f_0)| = \frac{A_{vf \max}}{\sqrt{2}}$$

$$\frac{A_{vf \max}}{\sqrt{2}} = \frac{A_{vf \max}}{\sqrt{1 + \frac{1}{\omega_0^2 R^2 C^2}}}$$


$$\frac{1}{\omega_0^2 R^2 C^2} = 2 - 1$$

$$\omega_0^2 R^2 C^2 = 1$$

$$\boxed{\omega_0 = \frac{1}{RC}}$$

$$\boxed{f_0 = \frac{1}{2\pi RC}}$$

Practical Differentiator using OPAMP:

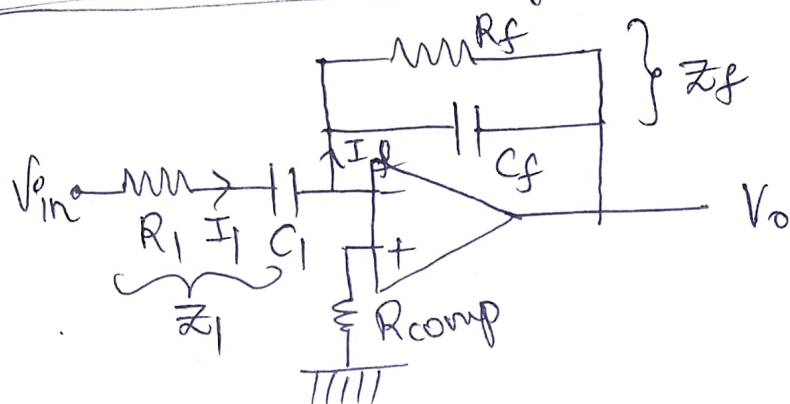

$$Z_1(s) = R_1 + \frac{1}{sC_1} = \frac{sC_1R_1 + 1}{sC_1}$$

$$Z_f(s) = R_f \parallel C_f = \frac{R_f \times \frac{1}{sC_f}}{R_f + \frac{1}{sC_f}} = \frac{R_f}{1 + sC_fR_f}$$

$$I_1(s) = \frac{V_{in}(s) - 0}{Z_1(s)} \quad I_2(s) = \frac{0 - V_o(s)}{Z_2(s)}$$


$$I_1(s) = I_2(s) \quad (\text{Virtual ground})$$

$$\frac{V_{in}(s)}{Z_1(s)} = \frac{-V_o(s)}{Z_2(s)}$$

$$\frac{V_{in}(s)}{\frac{1 + sC_1R_1}{sC_1}} = \frac{-V_o(s)}{\frac{R_f}{1 + sC_fR_f}}$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-R_f}{(1 + sC_fR_f)} \times \frac{sC_1}{(1 + sC_1R_1)}$$

$$|A_v(s)| = \frac{sR_fC_1}{(1 + sC_fR_f)(1 + sC_1R_1)}$$

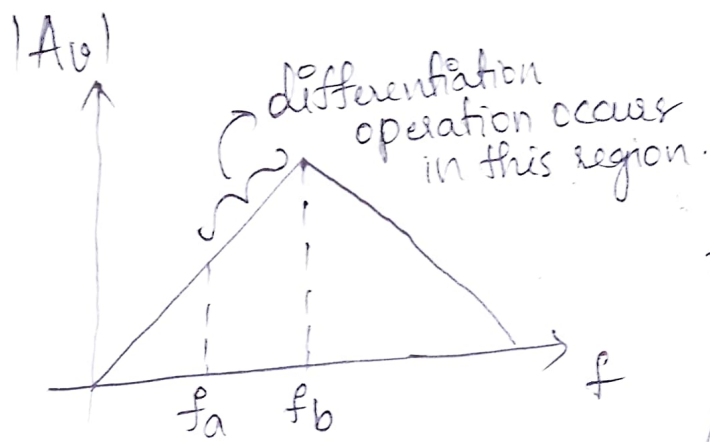

$f_a \rightarrow$ frequency at which gain = 1.

For proper differentiation,

If $R_f C_1 \gg R_f C_f$
 $R_f C_1 \gg R_1 C_1$ then

$$\left(\begin{aligned} f_a &= \frac{1}{2\pi R_f C_1} \\ f_b &= \frac{1}{2\pi R_1 C_1} \end{aligned} \right)$$

$$A_v(s) = -s R_f C_1$$

$$\frac{V_o(s)}{V_{in}(s)} = -s R_f C_1$$

$$V_o(s) = -s V_{in}(s) R_f C_1$$

$$V_o(t) = -R_f C_1 \frac{d V_{in}(t)}{dt}$$

If $R_1 C_1 = R_f C_f$

$$|A_v(s)| = \frac{s R_f C_1}{(1 + s^2 R_1^2 C_1^2)}$$

$$|A_v(s)| = \frac{j\omega R_f C_1}{(1 + j\omega C_1 R_1)^2}$$

$$|A_v(s)| = \frac{f/f_a}{1 + (f/f_b)^2}$$

Q: Design a differentiator using op-amp to differentiate an input signal with $f_{\max}^{\min} = 200 \text{ Hz}$. Draw output waveform for sine wave with 1V peak at 200 Hz.

Sol: $f_{\max}^{\min} = f_a = 200 \text{ Hz}$
 $\frac{1}{2\pi R_f C_f} = 200$
 $\rightarrow (\text{let } C_f = 0.1 \mu\text{F})$

$$R_f = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 200} = 7.962 \text{ k}\Omega$$


$$f_b = 10 f_a$$

$$\frac{1}{2\pi R_i C_f} = 10 \times 200$$

$$R_i = \frac{1}{2\pi \times 2000 \times 0.1 \times 10^{-6}} = 0.796 \text{ k}\Omega$$

$$R_i C_f = R_f C_f$$

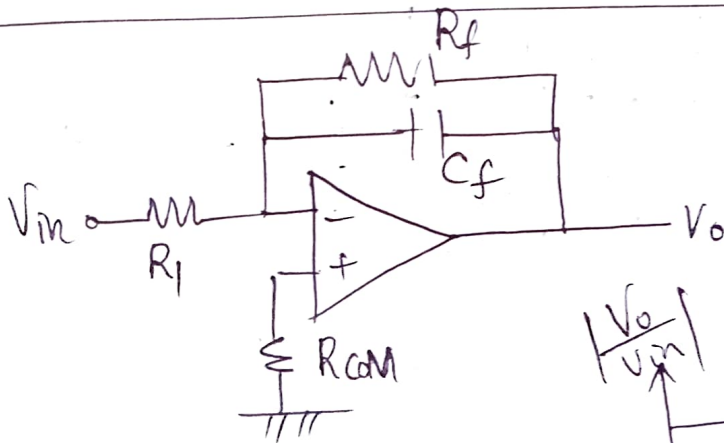
$$C_f = \frac{R_i C_f}{R_f} = 0.01 \mu\text{F}$$



$$f_b = 10 f_a$$

$$f_a = \frac{1}{2\pi R_f C_f}$$

$$f_b = \frac{1}{2\pi R_i C_f}$$

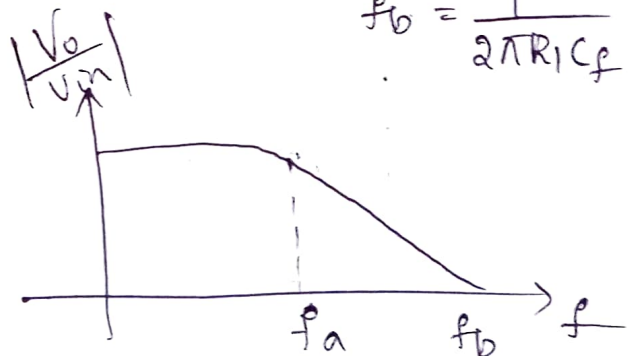

Q: Design a practical integrator with lower limit of frequency is 160 Hz.

Sol: $f_a = 160 \text{ Hz}$

$$\frac{1}{2\pi R_f C_f} = 160$$

Assume, $C_f = 0.01 \text{ nF}$


$$R_f = \frac{1}{2\pi \times 160 \times 0.01 \times 10^{-9}}$$

$$f_b = 10 f_a = 1600 \text{ Hz}$$

$$\frac{1}{2\pi R_1 C_f} = 1600 \rightarrow R_1 = \frac{1}{2\pi \times 1600 \times 0.01 \times 10^{-9}}$$

Q: Design a circuit using OPAMP, which gives output $V_o = 5V_2 - 8V_1$ where V_2 & V_1 are inputs.

Sol:

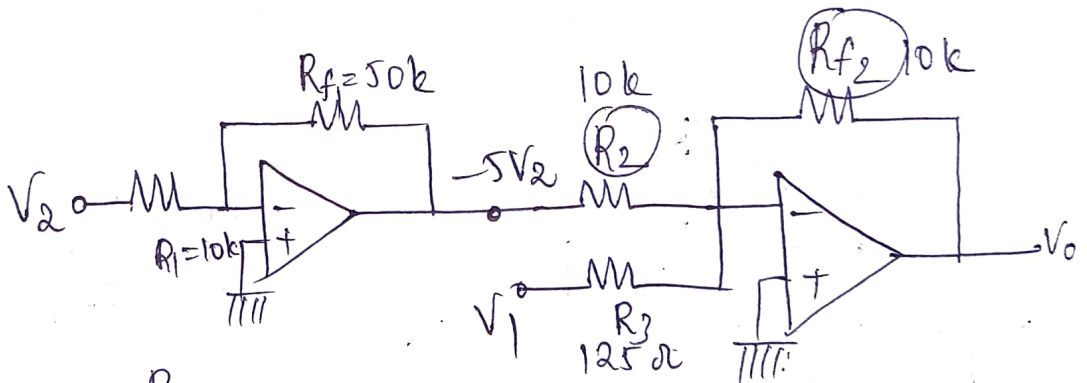

$$\frac{R_{f1}}{R_1} = 5$$

$$R_{f1} = 50k$$


$$\frac{R_{f2}}{R_2} = 1 \rightarrow R_{f2} = R_2 = 10k$$

$$\frac{R_{f2}}{R_3} = 8 \rightarrow R_3 = \frac{10k}{8} = 125\Omega$$

Q: Design an OPAMP circuit which performs following operation

$$V_0 = -V_1 - 2V_2 - 3V_3$$

Sol:

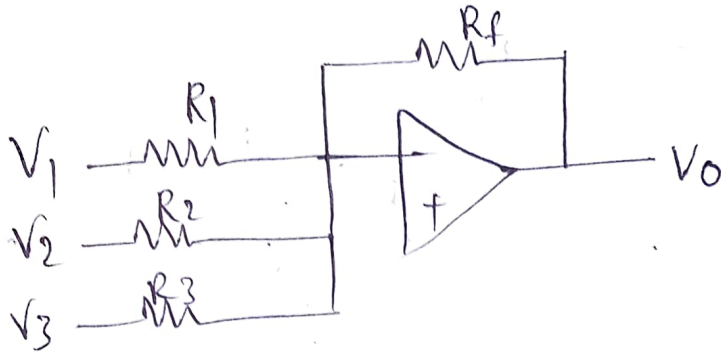

$$-\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 - \frac{R_f}{R_3} \times V_3 = V_0$$

$$\frac{R_f}{R_1} = 1$$

$$\frac{R_f}{R_2} = 2$$


$$\frac{R_f}{R_3} = 3$$

Let $R_f = 100\text{ k}$,

$$\begin{aligned} R_1 &= 100\text{ k} \\ R_2 &= 50\text{ k} \\ R_3 &= \frac{100\text{ k}}{3} \end{aligned}$$

Q: Design a practical integrator with a signal having max freq 200Hz.

Q: Find the output

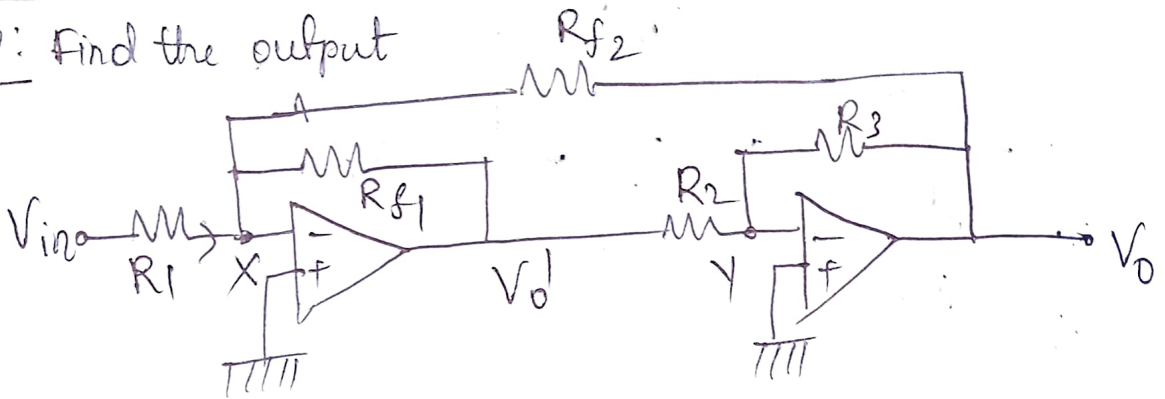

Sol:

Apply KCL at Node X,

$$\frac{V_{in}}{R_1} = -\frac{V_{01}}{R_{f1}} - \frac{V_0}{R_{f2}}$$

Apply KCL at Node Y,

$$\frac{V_{01}}{R_2} = -\frac{V_0}{R_3}$$

$$\boxed{V_{01} = -\frac{R_2}{R_3} \times V_0}$$

$$\frac{V_{in}}{R_1} = +\frac{R_2}{R_3 R_{f1}} V_0 - \frac{V_0}{R_{f2}}$$

$$= -V_0 \left(\frac{-R_2 R_{f2} + R_3 R_{f1}}{R_3 R_{f1} R_{f2}} \right)$$

$$\boxed{\frac{V_0}{V_{in}} = \frac{-R_3 R_{f1} R_{f2}}{R_1 (-R_2 R_{f2} + R_3 R_{f1})}}$$